

Intro

Monday, August 22, 2016 9:00 AM


Norm Galassi
Office: SKSU 105 10-10:50 MW Mon also 11-11:50
<http://nrgalassi.org> EECE 211
must be caps

use gmail

$$\text{charge } q_f = 1.602 \times 10^{-19} \text{ Coul}$$



$$\textcircled{X} \text{ Current } = \frac{dq}{dt} \quad \frac{1 \text{ coul}}{1 \text{ sec}} = \text{lamp} \quad \begin{matrix} + \\ \rightarrow \\ - \end{matrix}$$

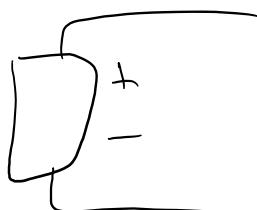
$$\textcircled{X} \text{ Voltage} = \frac{dw}{dq}$$




$$\textcircled{X} \text{ Power} = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{q}{dt} = V \cdot i$$

Passive sign convention

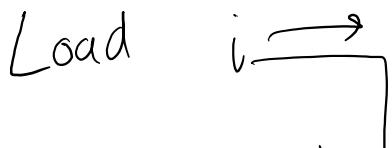
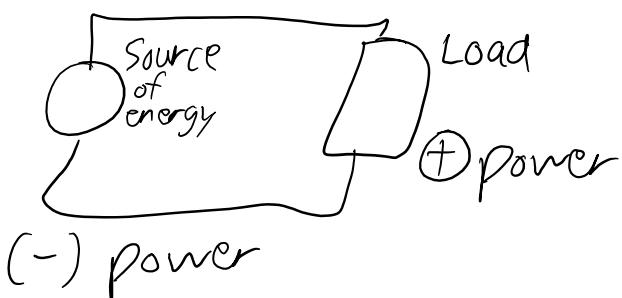


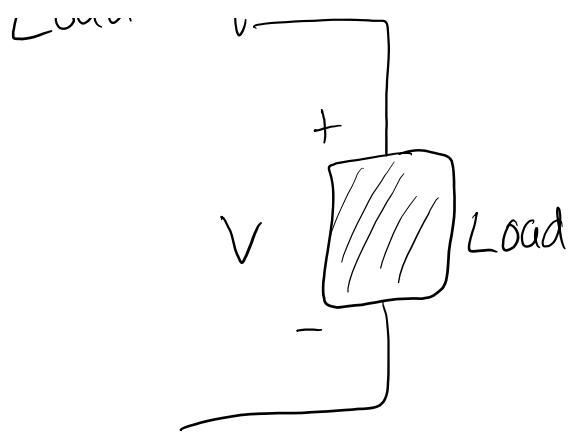

$$P = (+) V_i$$



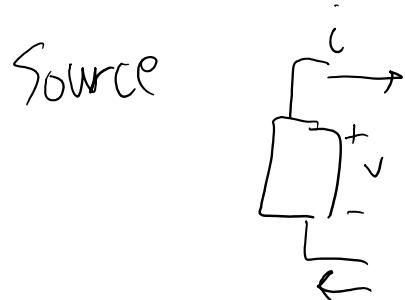

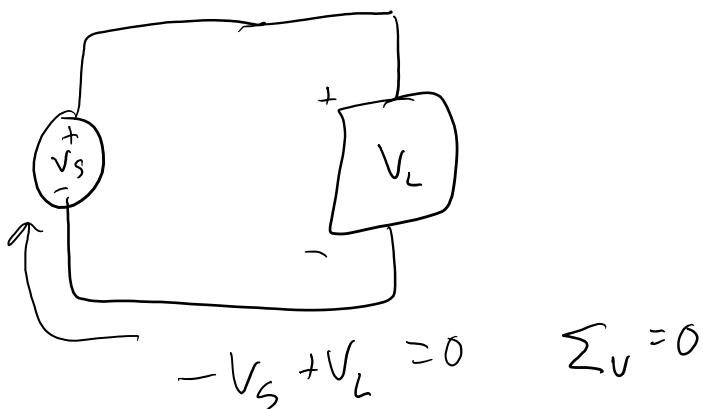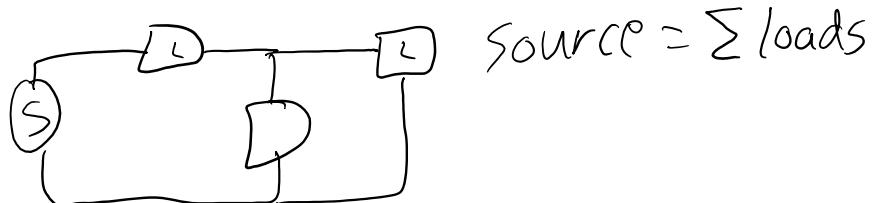
$$\sum i = 0 \quad \text{in} = \text{out}$$




Passive Sign Convention

Wednesday, August 24, 2016 9:00 AM

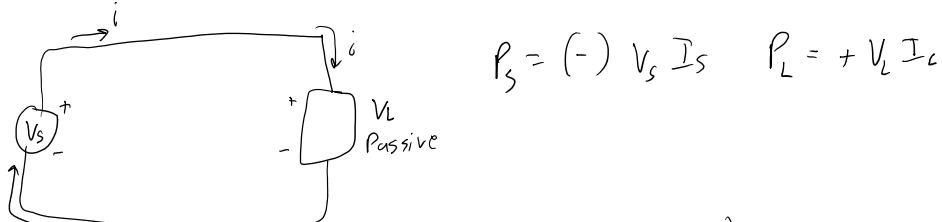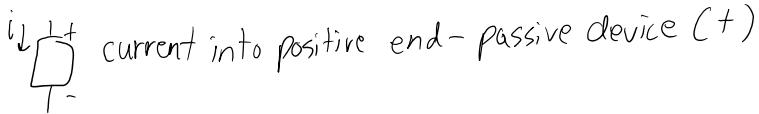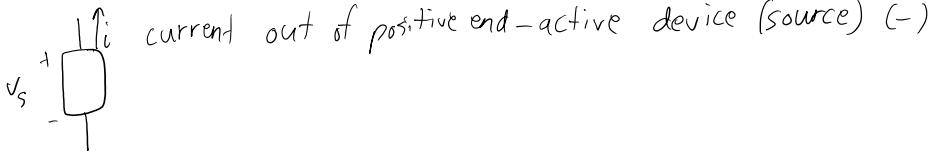

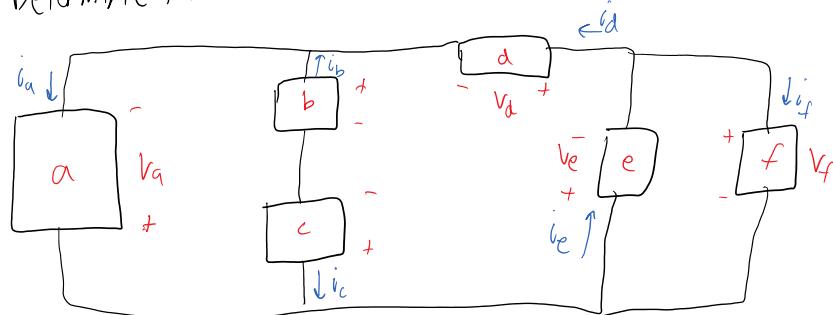
Ex: Determine if circuit is valid (Power in = Power out)





element	V	I	Type of Filament	Calculation	what it really is → element
a	-3 kV	-250 μA	a	(-) (-3 × 10 ³) · (250 × 10 ⁻⁶) = -0.75 W	active
b	4 kV	-400 μA	b	(-) (4 × 10 ³) · (-400 × 10 ⁻⁶) = +1.6 W	passive
c	1 kV	400 μA	c	(-) (1 × 10 ³) · (400 × 10 ⁻⁶) = -0.4 W	active
d	1 kV	150 μA	d	(+) (1 × 10 ³) · (150 × 10 ⁻⁶) = +0.15 W	passive
e	-4 kV	200 μA	e	(+) (-4 × 10 ³) · (200 × 10 ⁻⁶) = -0.8 W	active
f	4 kV	50 μA	f	(+) (4 × 10 ³) · (50 × 10 ⁻⁶) = +0.2 W	passive

$$-0.75 - 0.4 - 0.8 + 1.6 + 0.15 + 0.2 = 0$$

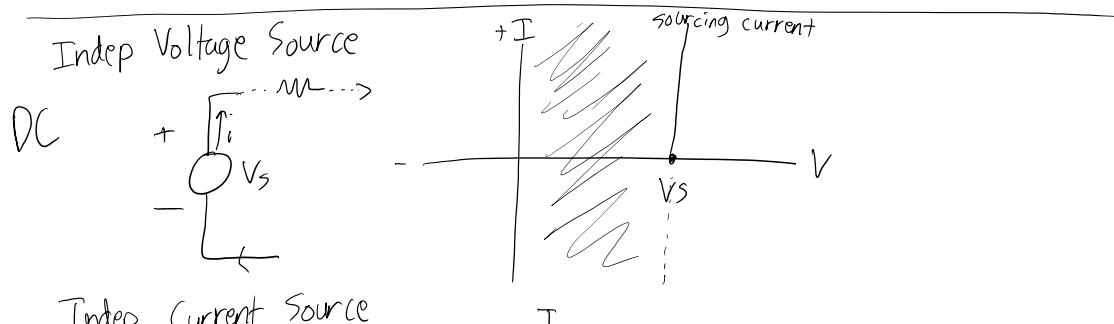
$\underbrace{-1.95}_{\text{Valid circuit } \checkmark}$ $\underbrace{+ 1.95}_{\text{(If not } = 0, \text{ invalid circuit)}}$



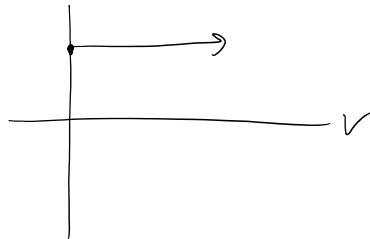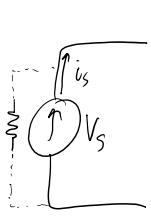


dependent Source Probably not on exam


Voltage Controlled Voltage Source (VCVS)

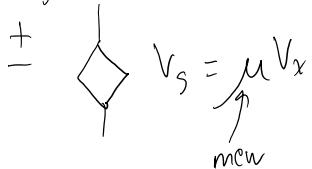


Current Controlled Voltage Source (CCVS)

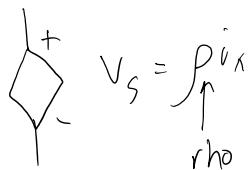

Voltage Controlled Current Source (VCCS)

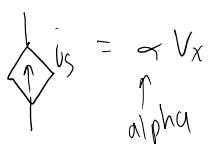

Current Controlled Current Source (CCCS)

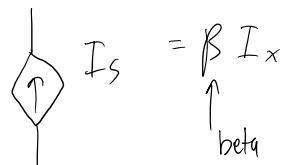


All of these are usually in semiconductors/solid state

Kirchoff's Laws

Friday, August 26, 2016 9:00 AM


$$G = \text{conductance} = \frac{1}{R}$$

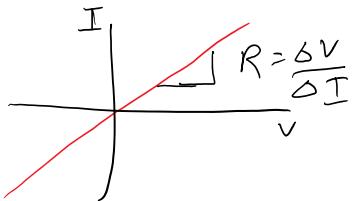


$$G_T = \frac{1}{G_1} + \frac{1}{G_2} + \frac{1}{G_3}$$

$$R_T = \frac{1}{G_T}$$

$$P_R = (+) VI = I^2 R = \frac{V^2}{R}$$

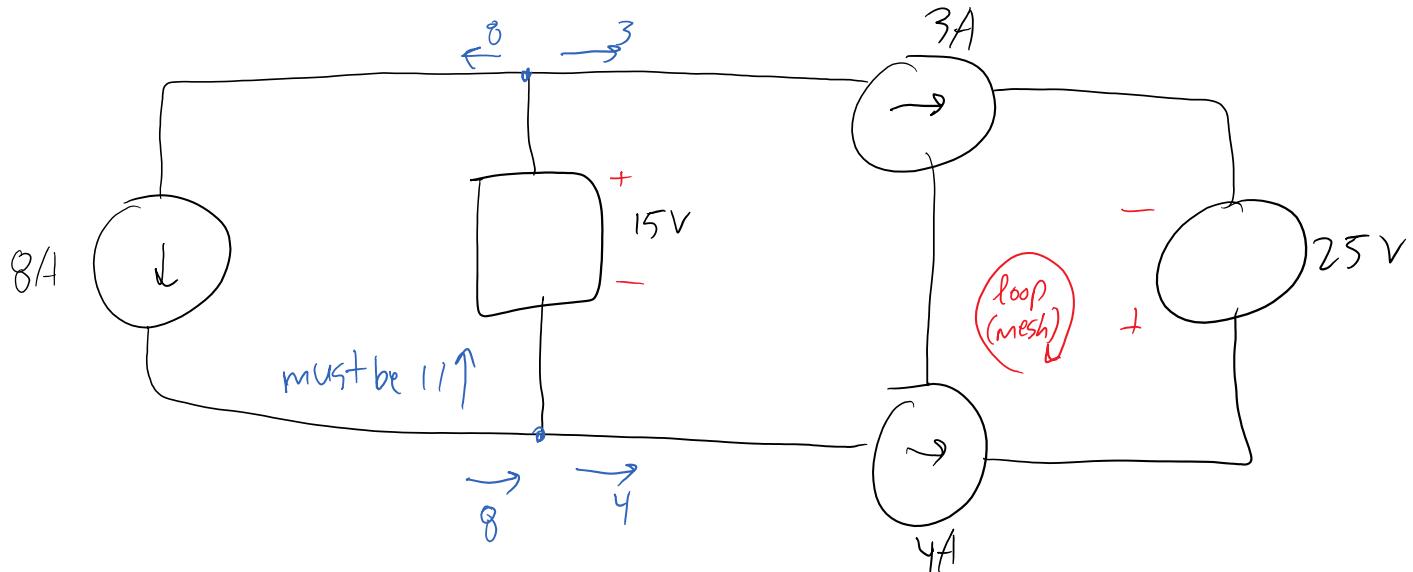

$15 \neq 8$ invalid circuit

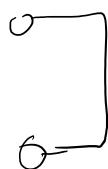



Short circuit
 $R=0$

— open circuit
 $R=\infty$

Kirchoff's Voltage Law (loops)
 $\sum \text{Voltage around a loop} = \emptyset$

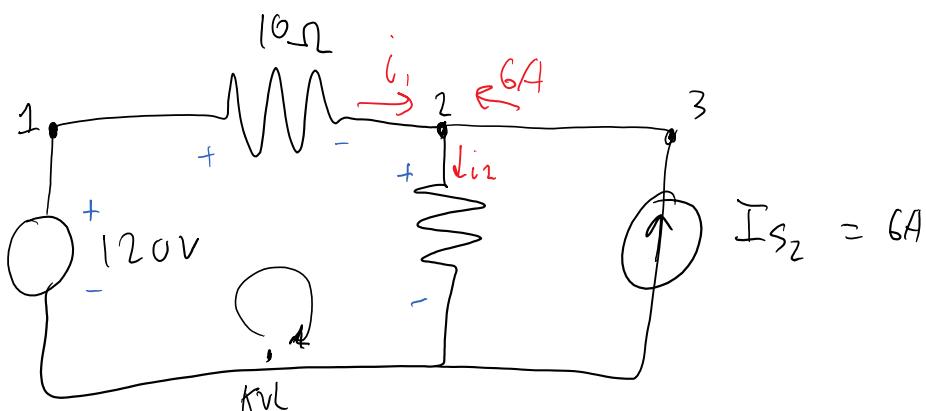Kirchoff's Current Law (nodes)
 $\sum \text{current entering node} = \emptyset$



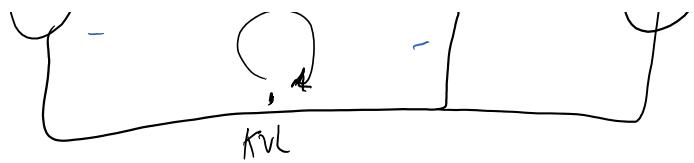

$$\text{Node } 3 = 6A$$

KCL \rightarrow Node 2

$$I_1 - I_2 + I_3 = 0$$

$$I_1 - I_2 = -6$$


$$10I_1 + 50I_2 = 120$$

KVL - loops

$$-120V + i_1 \cdot 10\Omega + i_2 \cdot 5\Omega = 0$$

$$\left| \begin{array}{cc|c} 1 & -1 & I_1 \\ 10 & 50 & I_2 \end{array} \right| \left| \begin{array}{c} -6 \\ 120 \end{array} \right| \quad \begin{array}{l} I_1 = -3 \\ I_2 = 3 \end{array}$$
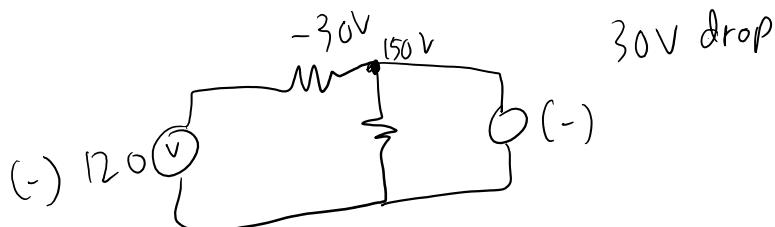
$$\text{So } i_1 = -3 \quad \leftarrow i_1$$




$$-(120V)(-3A) + (-3A)(-30V) + (3A)(150V) = 150(6)$$

$$+360W + 90W + 450W - 900W = 0 \checkmark$$

Sources

Monday, August 29, 2016 9:03 AM

Dependent Source Examples

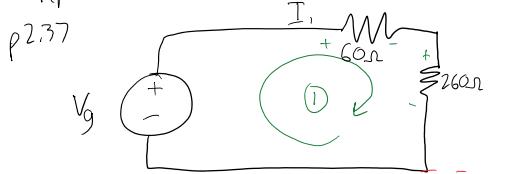

Indep Source


Find V_1 and V_g when $V_o = +5V$

$$-V_g + 60I_1 + 260I_1 = 0$$

$$-V_g + 320I_1 = 0$$

$$-V_g = -320I_1$$

$$V_g = 320I_1 = 1V$$

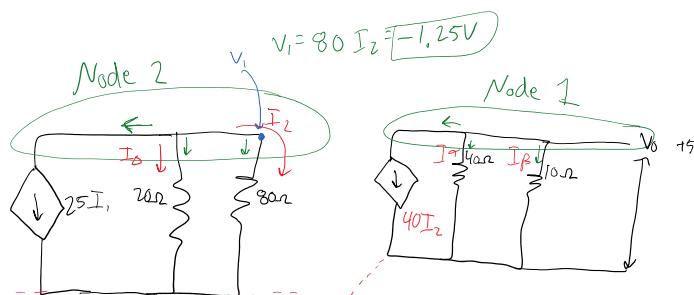

$$I_\alpha = \frac{5}{40} = 0.125$$

$$I_\beta = \frac{5}{10} = 0.5$$

Hint: Begin at right hand side (i.e. V_o)

Node 1:

$$-40I_2 - I_\alpha - I_\beta = 0$$

$$-40I_2 - 0.125 - 0.5 = 0$$

$$-40I_2 = +0.625A$$

$$\boxed{I_2 = -0.015625A}$$

$$-25I_1 - I_\alpha - I_2 = 0$$

$$-25I_1 - I_\alpha + 0.015625 = 0$$


$$I_\alpha = -\frac{1.25}{20} = -0.0625$$

$$-25I_1 + 0.0625 + 0.015625 = 0$$

$$-25I_1 + 0.07825 = 0$$

$$-25I_1 = -0.02825$$

$$\boxed{I_1 = 0.003125}$$

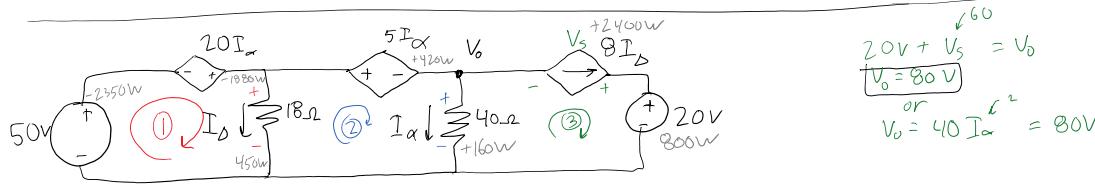

Calculate I_α and V_o

Loop 1

$$-50V - 20I_\alpha + 18I_\alpha = 0$$

$$-20I_\alpha + 18I_\alpha = 50$$

Loop 2

$$-18I_\alpha + 5I_\alpha + 40I_\alpha = 0$$

$$45I_\alpha - 18I_\alpha = 0$$

Loop 3

$$-40I_\alpha - V_s + 20 = 0$$

$$-40I_\alpha - V_s = -20$$

$$\begin{aligned} 20V + V_s &= V_o \\ V_o &= 80V \end{aligned}$$

$$\left| \begin{array}{ccc} I_\alpha & I_\alpha & V_s \\ -20 & 18 & 0 \\ 45 & -18 & 0 \\ -40 & 0 & -1 \end{array} \right| \left| \begin{array}{c} I_\alpha \\ I_\alpha \\ V_s \end{array} \right| \left| \begin{array}{c} 50 \\ 0 \\ -20 \end{array} \right|$$


$$I_\alpha = 2$$

$$\boxed{I_\alpha = 5}$$

$$V_s = -60$$


Series and Parallel Circuit

Wednesday, August 31, 2016 9:00 AM

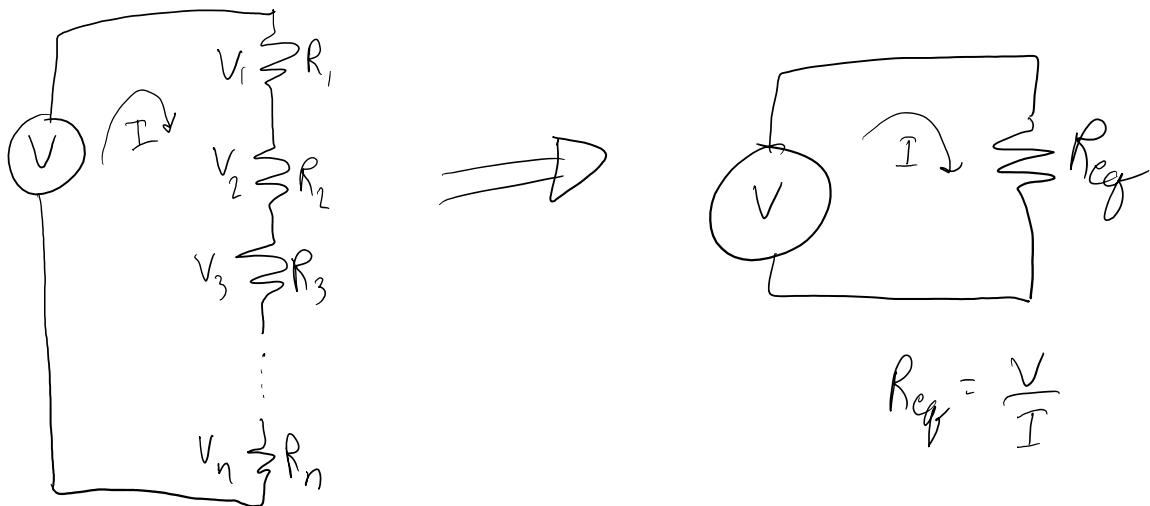

$$R_{eq} = \frac{V}{I} \quad [R_{eq} = R_1 + R_2 + \dots + R_n]$$

Voltage Divider

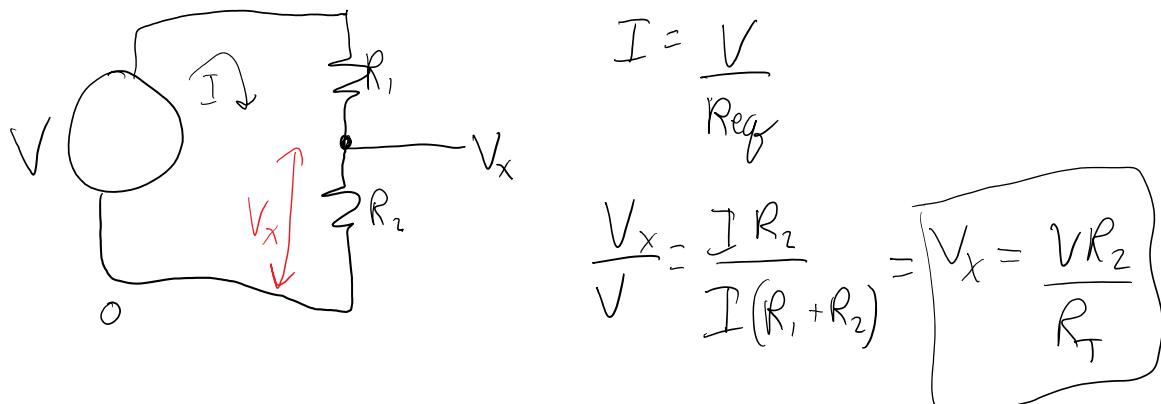


Parallel Resistors

T

$$I = I_1 + I_2 + I_3 + \dots + I_n$$

Currents in parallel

$$I = I_1 + I_2 + I_3 + \dots + I_n$$

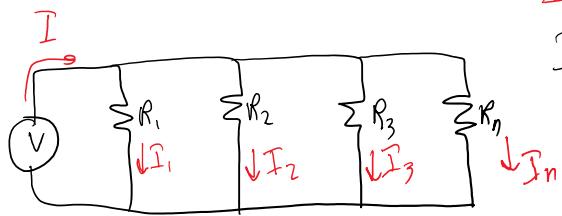

$$I = \frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} + \dots + \frac{V}{R_n}$$




$$R_{eq} = \frac{V}{I} = \underbrace{\frac{V}{\frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} + \dots + \frac{V}{R_n}}}_{\text{symbol}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}}$$

For 2 Resistors in Parallel (II): $R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{1}{\frac{R_1 + R_2}{R_1 R_2}} = \frac{R_1 R_2}{R_1 + R_2}$


Resistance of each resistor $\frac{R}{N}$

$$R_{eq} = \frac{R}{N} = \frac{1000}{20} = 50$$


of resistors

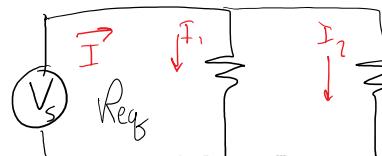
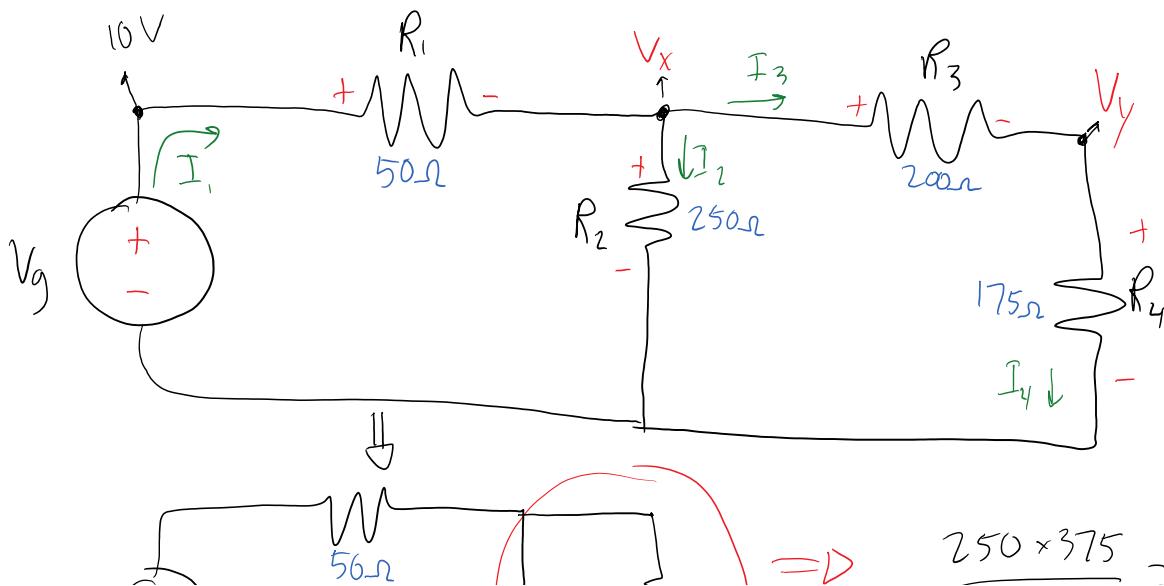
$$\frac{I_1}{I_2} = \frac{\frac{V_s}{R_1}}{\frac{V_s}{R_1 + R_2}} = \frac{1}{R_1} \times \frac{R_1 R_2}{R_1 + R_2} = \frac{I_1}{I} = \frac{R_2}{R_1 + R_2}$$


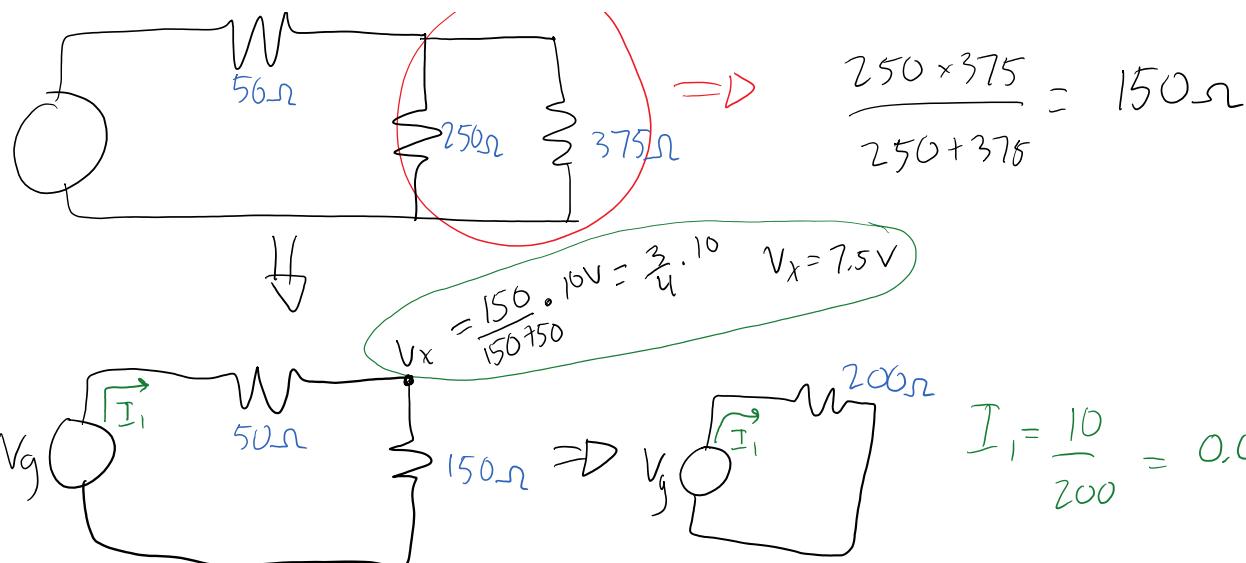
$$\frac{250 \times 375}{250 + 375} = 150 \Omega$$



$$I_1 = 0.05A$$

$$I_2 = 0.03A$$

$$I_3 = 0.02A$$

$$I_4 = 0.02A$$

voltage divider $\rightarrow V_x = 7.5V$

$$V_y = 3.5V$$

$$I_2 = \frac{7.5V}{250\Omega} = 0.03A$$

I_2

$$I_1 = I_2 + I_3$$

$$0.05 = 0.03 + I_3 \quad I_3 = 0.02A$$


$I_3 = I_4 \rightarrow$ resistors R_3 and R_4 are in series

$$V_y = \frac{R_4}{R_3 + R_4} (V_x)$$

$$V_y = \frac{175 \cdot (7.5V)}{200 + 175} = 3.5V$$

$\overbrace{0.05A}$


$$I_2 = 0.05 \times \frac{375}{625}$$

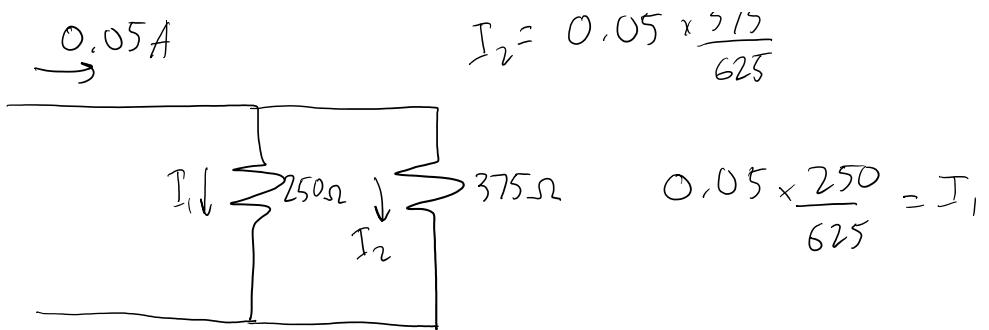

Delta and Wye Conversions

Friday, September 2, 2016 8:59 AM

Wheatstone Bridge *not on exam*

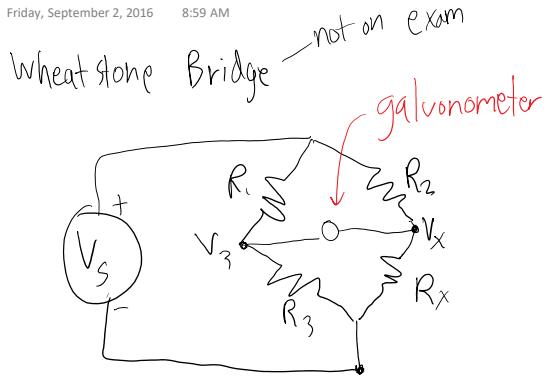

R_3 is a variable resistor

no current thru galvanometer when no Voltage on galvanometer \Rightarrow balanced

$$V_3 = \frac{V_s (R_3)}{R_1 + R_3}$$


$$V_x = \frac{V_s (R_x)}{R_2 + R_x}$$

$$V_3 = V_x \quad \text{so} \quad \frac{V_s (R_3)}{R_1 + R_3} = \frac{V_s (R_x)}{R_2 + R_x}$$





$$\cancel{R_3 R_2 + R_3 R_x} = R_1 R_x + \cancel{R_3 R_x}$$

$$R_3 R_2 = R_1 R_x$$

$$R_x = \frac{R_3 R_2}{R_1}$$

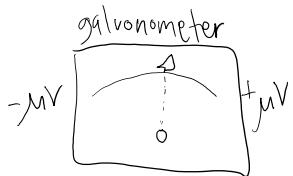

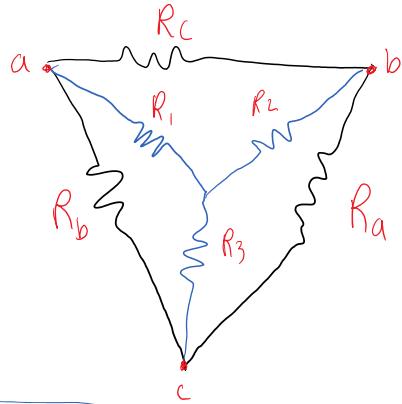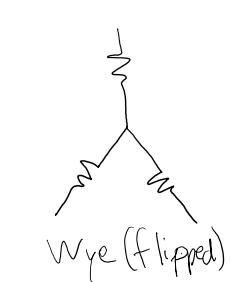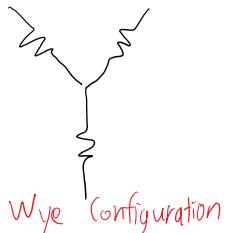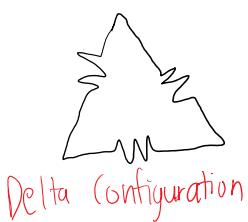Delta to Wye & Wye to Delta Transformations - In HW, probably not on exam



Delta to Wye

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$


$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

Wye to Delta

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

Delta seen as P_i Network (usually)



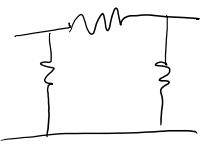

Wye seen as T Network (usually)





$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$


Ex:

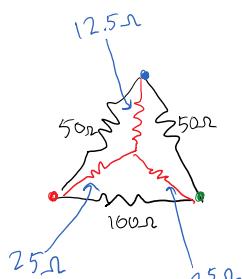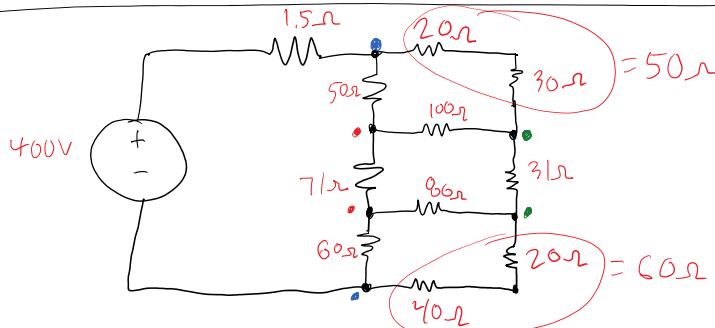

$$\frac{50 \cdot 50}{200} = 12.5 \Omega$$

$$\frac{50 \cdot 100}{200} = 25 \Omega$$


$$\frac{50 \cdot 100}{200} = 25 \Omega$$

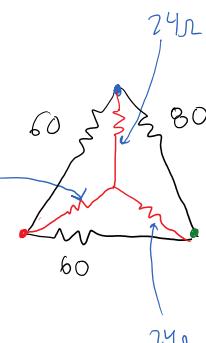

$$\frac{60 \cdot 80}{200} = 24 \Omega$$


$$\frac{60 \cdot 80}{200} = 24 \Omega$$

$$\frac{60 \cdot 60}{200} = 18 \Omega$$

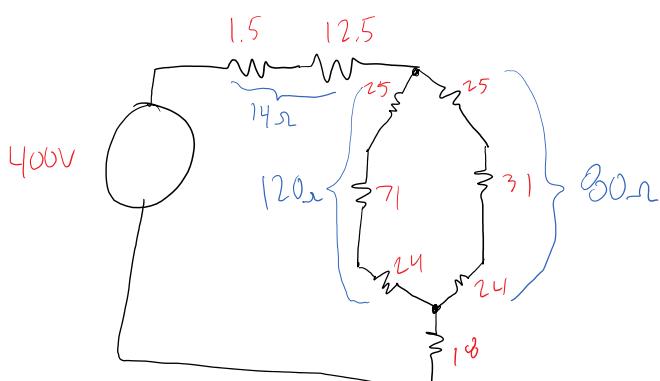


$$\frac{120 \cdot 80}{200} = 48 \Omega$$

Find Power in 31Ω resistor, Find Load

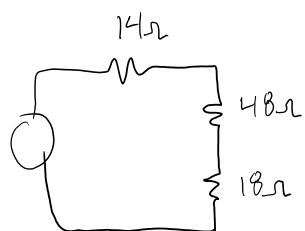


\Rightarrow

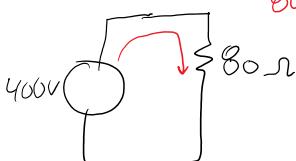

$$I = \frac{400V}{80\Omega} = 5A$$

$$\text{Load} = 80\Omega$$

(Load = 80Ω)

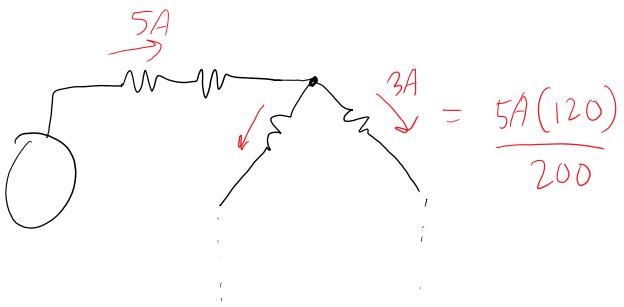


$$I_R = \frac{R_{\text{Not Path}}}{R_{\text{Sum of Path}}} \cdot I_T$$

$$P = I^2 R$$


$$P = 3^2 (31)$$

$$P = 9(31) = 279\text{W}$$

Wye to Delta

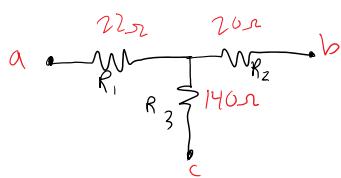
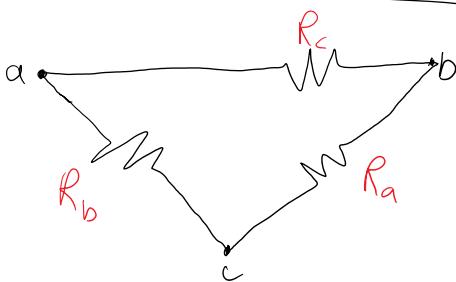
$$R_1 R_2 + R_2 R_3 + R_3 R_1 \\ (22)(20) + 20(140) + 140(22) = 6320$$



$$R_a = \frac{6320}{R_1} = \frac{6320}{22} = 287\Omega$$

$$R_b = \frac{6320}{R_2} = \frac{6320}{20} = 316\Omega$$


$$R_c = \frac{6320}{R_3} = \frac{6320}{140} = 45\Omega$$

Node Voltage Method

Wednesday, September 7, 2016 8:57 AM

$$i_a = \frac{128 - V_x}{5\Omega} \quad i_b = \frac{V_x - 0}{60\Omega} \quad i_c = \frac{V_x - V_y}{4\Omega} \quad i_d = \frac{V_y - 0}{8\Omega} \quad i_e = \frac{V_y - 320}{10\Omega}$$

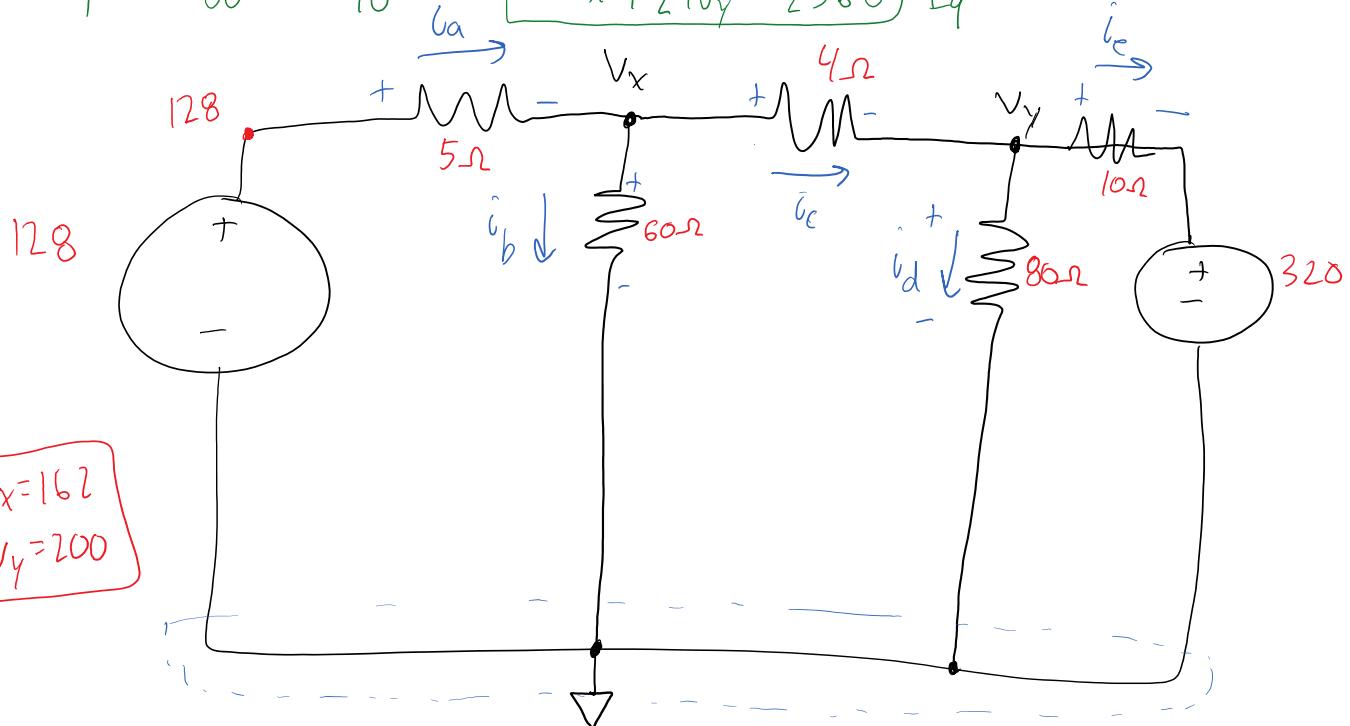
$$\frac{V_x - V_y}{4} = \frac{V_y}{80} + \frac{V_y - 320}{10} \quad \boxed{\begin{aligned} 20V_x - 20V_y &= V_y + 8V_y - 2560 \\ -20V_x + 29V_y &= 2560 \end{aligned}} \quad \text{Eq \#2}$$



$$i_a = i_b + i_c \quad \frac{128 - V_x}{5} = \frac{V_x}{60} + \frac{V_x - V_y}{4} \quad 1536 - 12V_x = V_x + 15V_x - 15V_y$$

$$\text{Eq \#1: } \boxed{28V_x - 15V_y = 1536}$$

- ① Identify a reference node in the circuit and assign a value of zero to that point in the circuit.
- ② Identify independent nodes \leftarrow any node where the voltage is unknown
- ③ Assign current directions to all "branches" in the circuit, Write KCL for all independent nodes using Ohm's law to express the currents in terms of the voltages or voltage differences
- ④ Solve the system of equations
- ⑤ Use the node voltages to find the desired electrical quantities

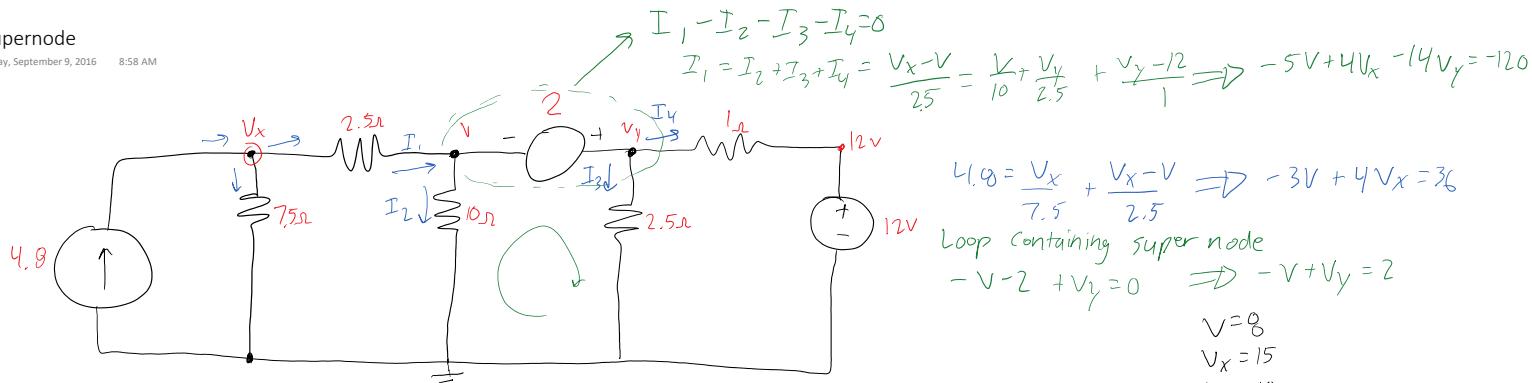


Whenever two non-reference nodes are directly connected by an independent or dependent voltage source, it is convenient to apply the supernode concept.

A supernode is a closed surface and Kirchoff's current law applies to closed surfaces as well.

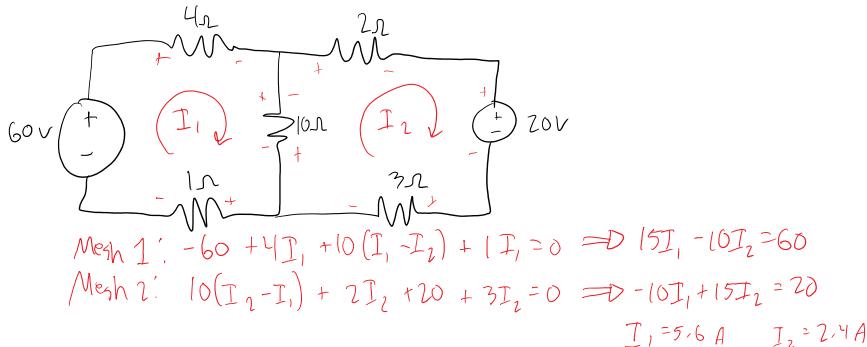
- 1) Define supernode
- 2) Write KCL for supernode
- 3) write KCL for all other nodes
- 4) Write KVL for supernode

Mesh Current Method

A generalized technique only valid for Planar Circuits that can be drawn on a flat piece of paper.



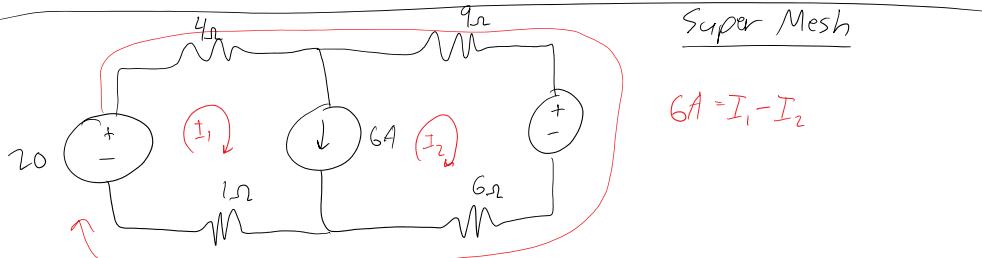
- 1) Define currents flowing in meshes of a planar circuit
- 2) write the KVL around the meshes using Ohm's law to express the voltages across the resistors in terms of the mesh currents.
- 3) Solve the system of equations
- 4) Use the mesh currents to find desired electrical quantities.



- 1) Pick a closed path that does not include the current source
- 2) write mesh KVL for meshes not including current source
- 3) write equation for currents shared with current source
- 4) solve equations
- 5) use the currents to find all other electrical quantities

Node Voltage vs Mesh Current

Monday, September 12, 2016 9:00 AM

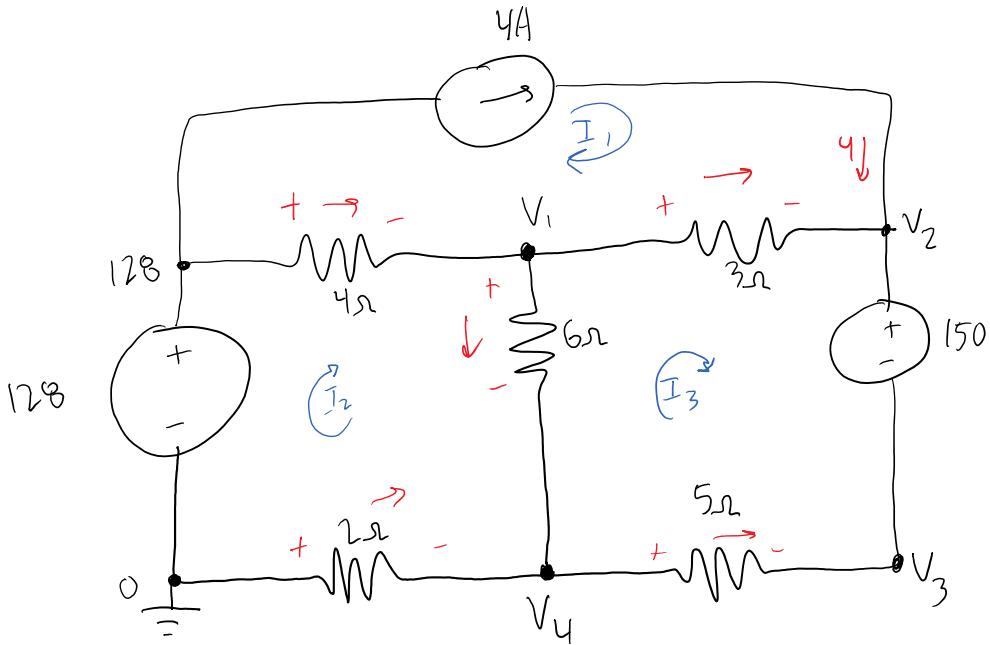

Node Voltage

$$\frac{128 - V_1}{4} = \frac{V_1 - V_4}{6} + \frac{V_1 - V_2}{3}$$

$$384 - 3V_1 = 2V_1 - 2V_4 + 4V_1 - 4V_2$$

$$\textcircled{1} \quad [9V_1 - 4V_2 - 2V_4 = 384]$$

Supernode

$$4 + \frac{V_1 - V_2}{3} + \frac{V_4 - V_3}{5} = 0$$

$$60 + 5V_1 - 3V_2 + 3V_4 - 3V_3 = 0$$

$$\textcircled{2} \quad [5V_1 - 5V_2 + 3V_4 - 3V_3 = -60]$$

$$\textcircled{3} \quad [V_2 - V_3 = 150]$$

Node \$V_4\$

$$\frac{0 - V_4}{2} + \frac{V_1 - V_4}{6} = \frac{V_4 - V_3}{5}$$

$$-15V_4 + 5V_1 - 5V_4 - 6V_4 + 6V_3 = 0$$

$$\textcircled{4} \quad [5V_1 + 6V_3 - 26V_4 = 0]$$

Mesh

$$\textcircled{2} \quad -128 + 4(I_2 - I_1) + 6(I_2 - I_3) + 2I_2 = 0$$

$$12I_2 - 6I_3 - 16 - 128 = 0$$

$$\boxed{12I_2 - 6I_3 = 144}$$

$$\textcircled{3} \quad 6(I_3 - I_2) + 3(I_1 - I_3) + 150 + 5I_3 = 0$$

$$-6I_2 + 14I_3 - 12 + 150 = 0$$

$$\boxed{-6I_2 + 14I_3 = -138}$$

$$I_1 = 4A$$

$$I_2 = 9A$$

$$I_3 = -6A$$

$$-15V_4 + 5V_1 - 3V_4 - 6V_4 + 6V_3 = 0$$

$$(4) \quad \boxed{5V_1 + 6V_3 - 26V_4 = 0}$$

$$V_1 = 108 \text{ V}$$


$$V_2 = 138 \text{ V}$$

$$V_3 = -12 \text{ V}$$




$$V_4 = 18 \text{ V}$$

Source Transformations

Wednesday, September 14, 2016 9:00 AM

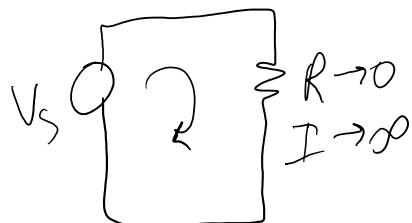


Ideal

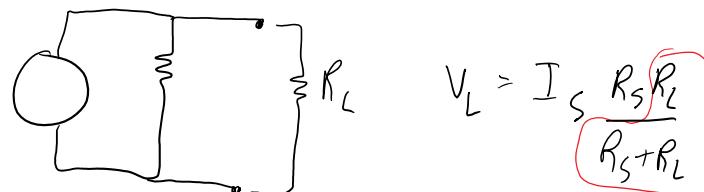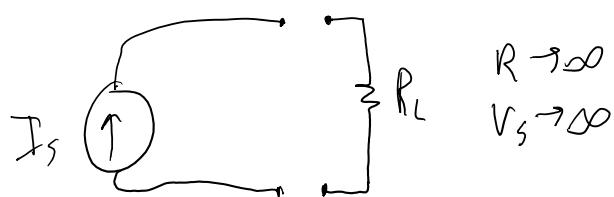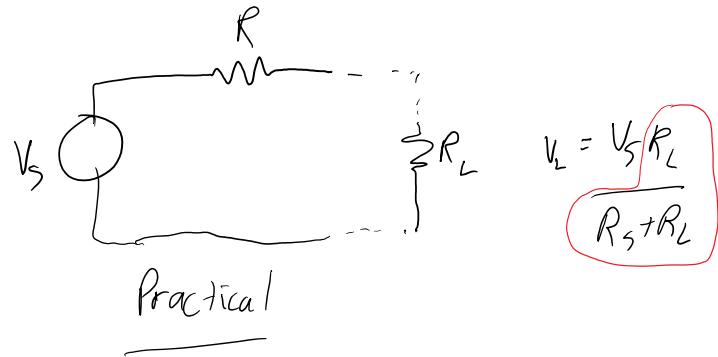


$$\text{If } V_L = V_L$$

$$V_s = I_s R_s$$

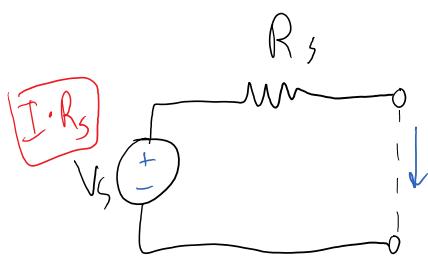

\equiv

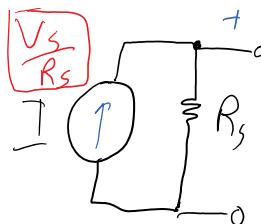

$$V_{\text{open circuit}} = V_s$$


$$V_{oc} = I(R_s)$$

$$I_{\text{short circuit}} = \frac{V_s}{R_s}$$

$$I_{sc} = I$$

Method of Source Transformation

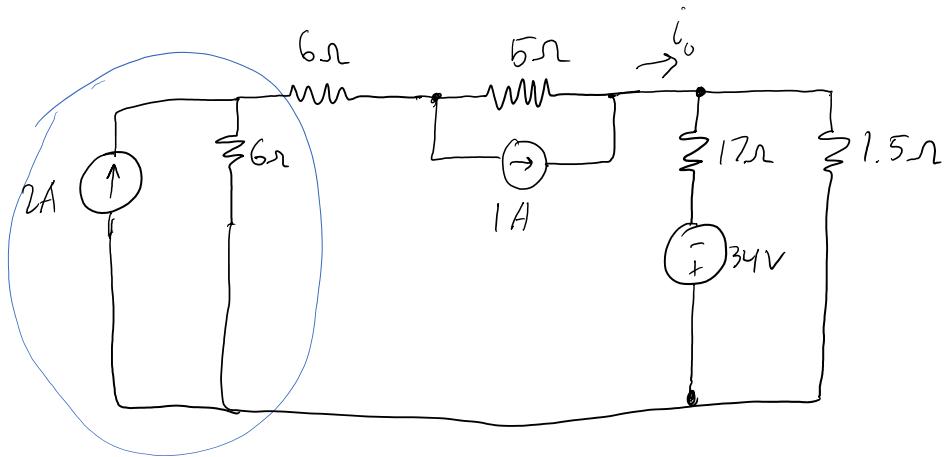
A practical voltage source can be replaced by a practical current source and a practical current source can be replaced by a practical voltage source as long as $V_s = I_s(R_s)$ and $I_s = \frac{V_s}{R_s}$





$$I_{SC} = 2A$$

$$V_{OC} = 12V \Rightarrow$$

$$R_S = 6\Omega$$


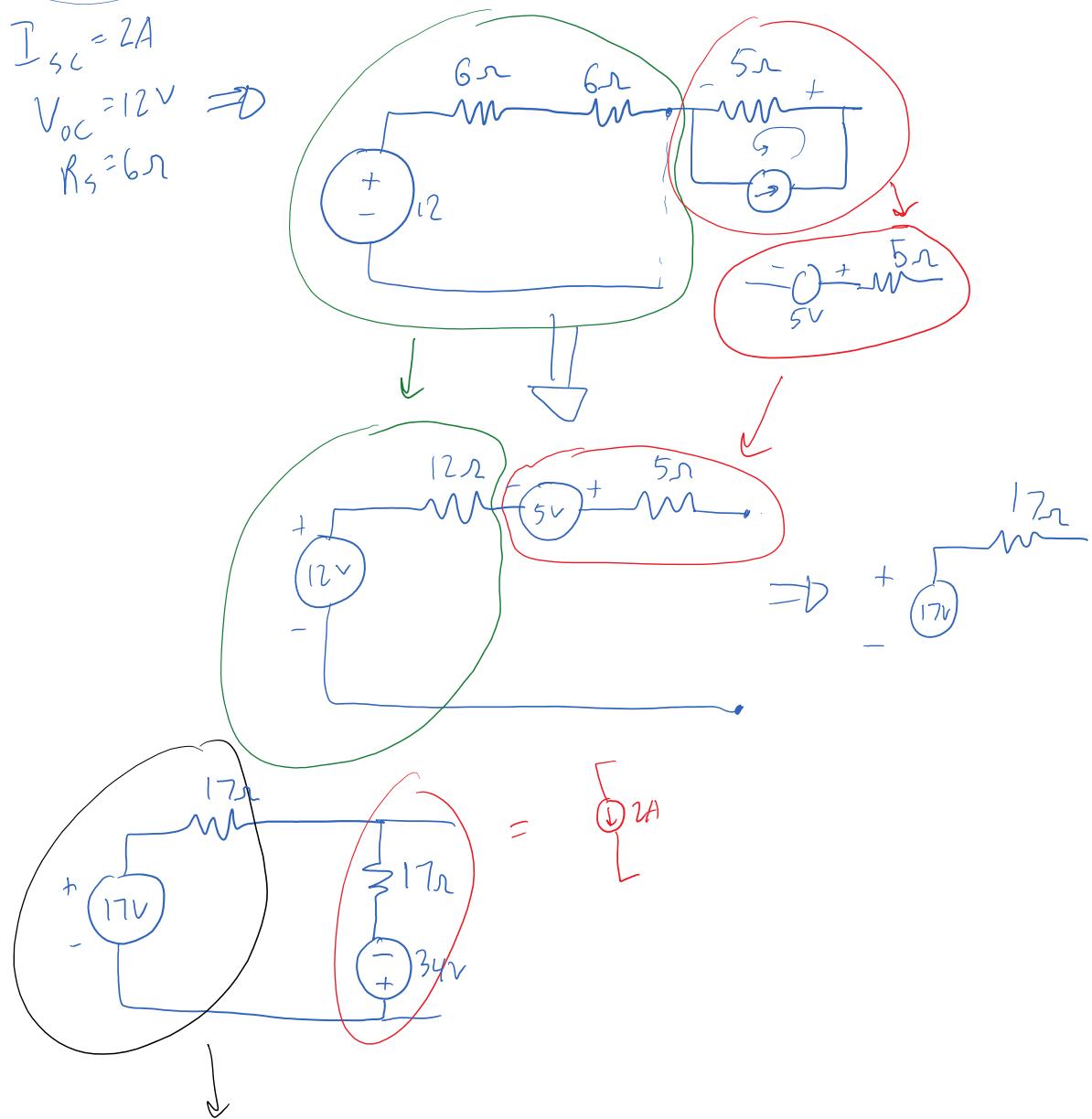


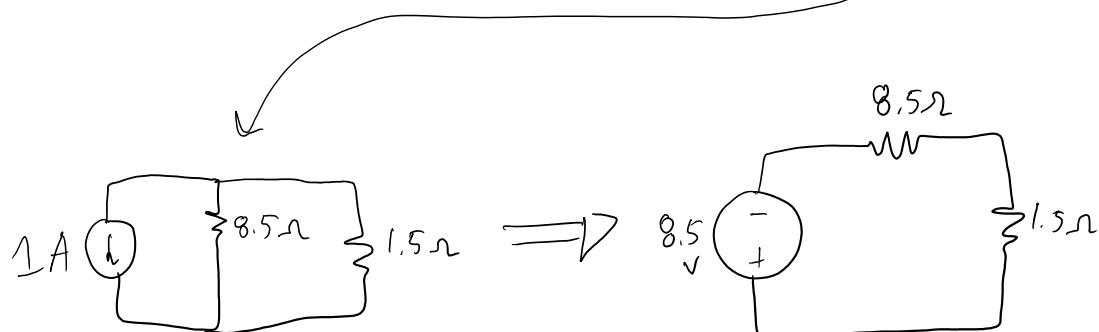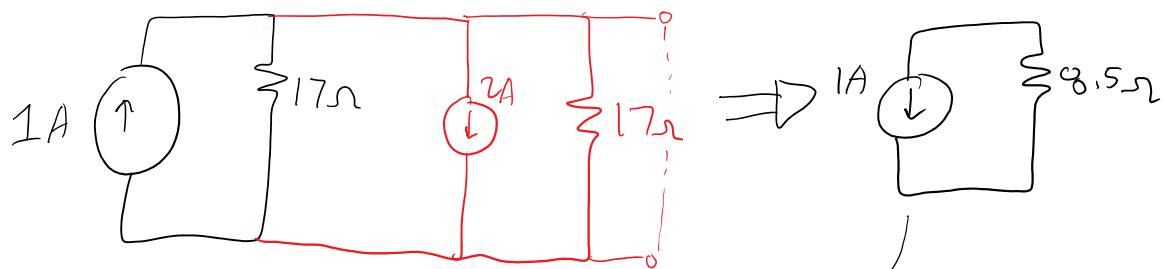


$$I_o = \frac{8.5V}{10\Omega} = 0.85A$$






$$V_o = \frac{8.5(1.5)}{10} = 1.275 V$$

$$V_o = \frac{R_1(R_2)}{R_1+R_2}$$

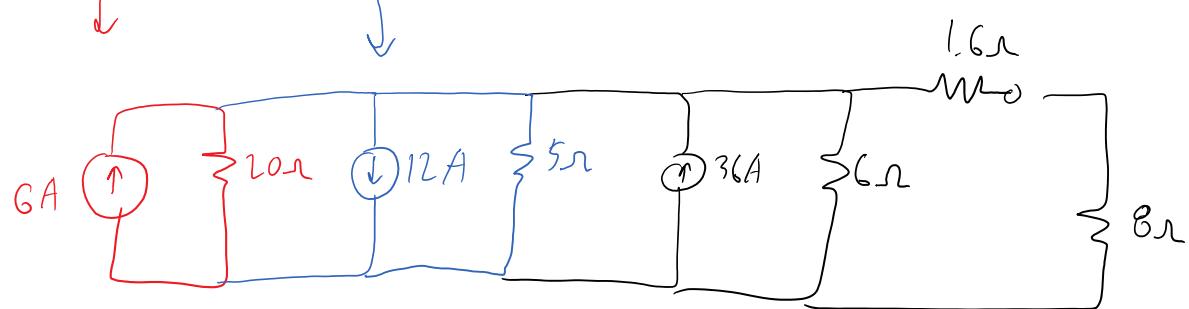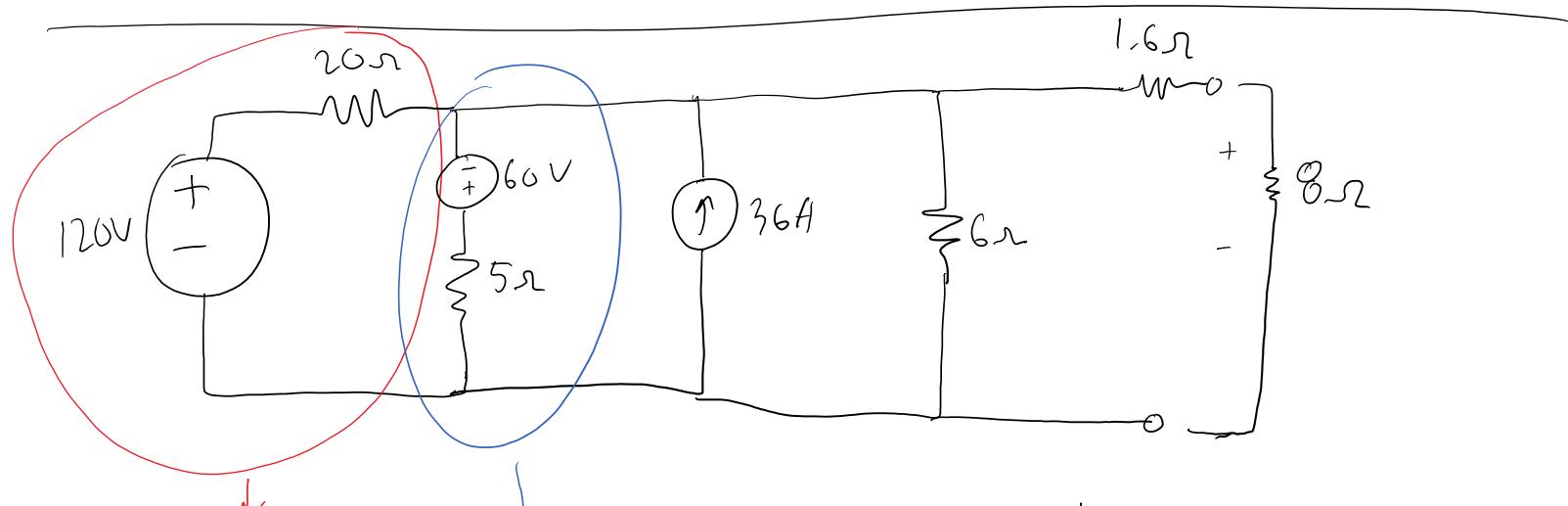

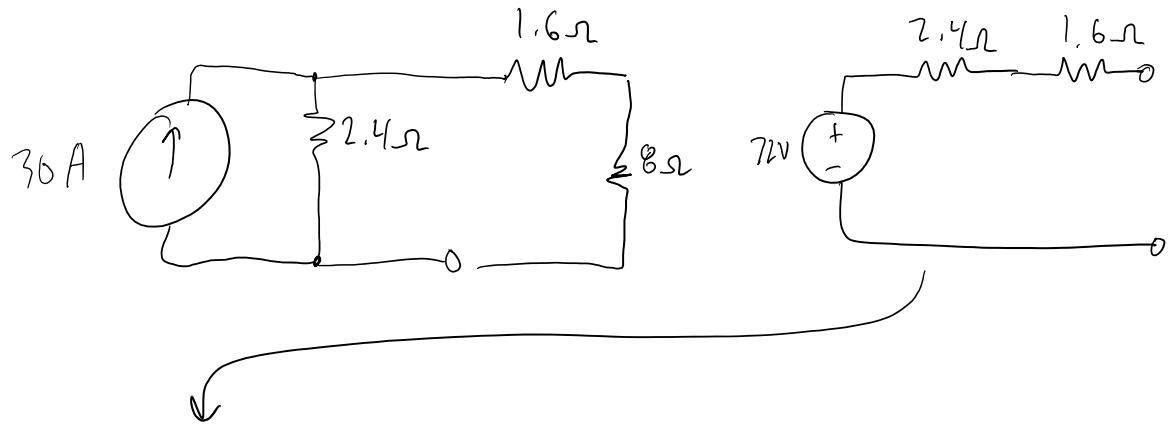


$$V_o = \frac{72(8)}{12} = 48$$

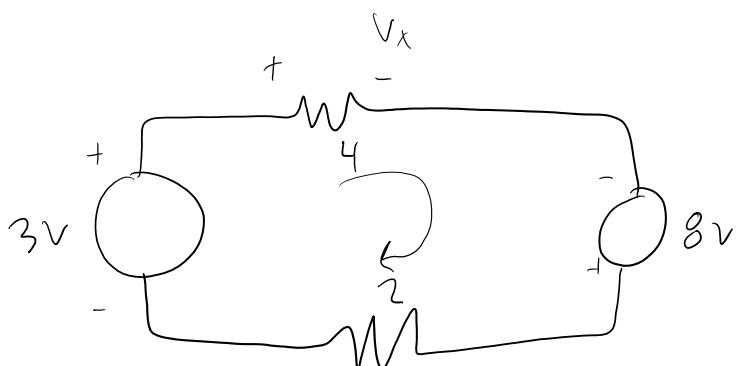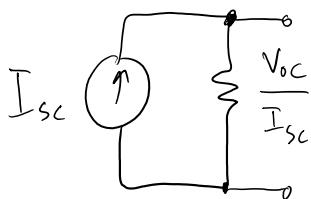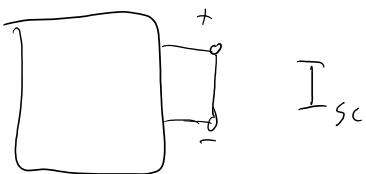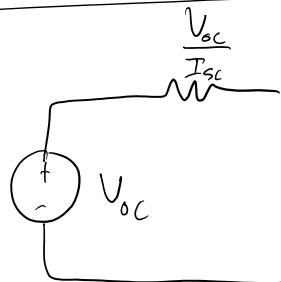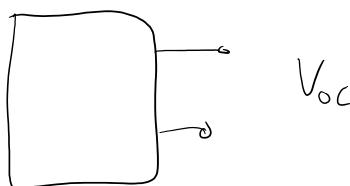

$$V_y = -V_x$$

$$-3 + 4I - 8 + 2I$$

For passive

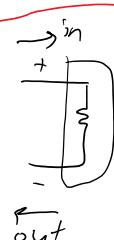

in on +, out of -

For active




$$v_y = -v_x$$

$-$ m $+$


For active

in on -, out of +

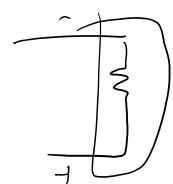


Thevenin and Norton

Friday, September 16, 2016 9:02 AM

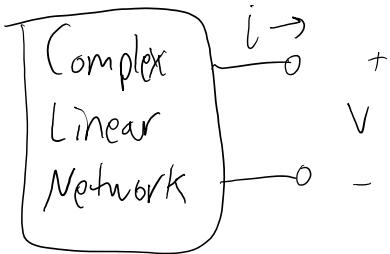

Thevenin Form

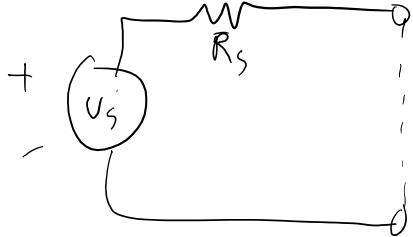


$$V_{OC} = V_S$$

$$I_{SC} = \frac{V_S}{R_S}$$

Equivalent if I_{SC} are equal and V_{OC} are equal $R_n = R_S$ and $V_{OC} = V_n$ or $I_{SC} = I_n$


Norton Form

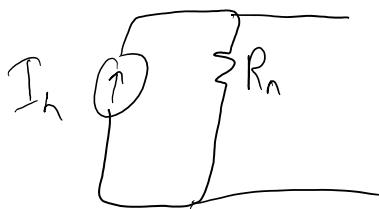



$$V_{OC} = I_n R_n$$


$$I_{SC} = I_n$$

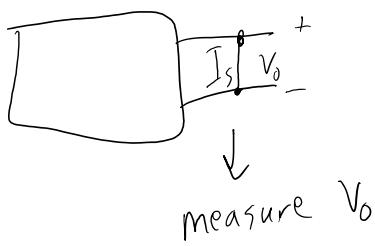Any complex, linear, one port, network can be replaced with an equivalent circuit consisting of a source and a resistor such that the characteristics at the terminal are the same.





Thevenin Form =

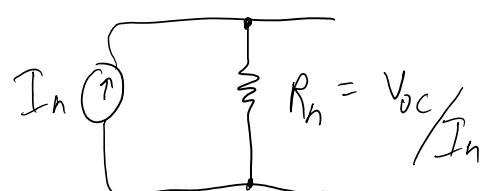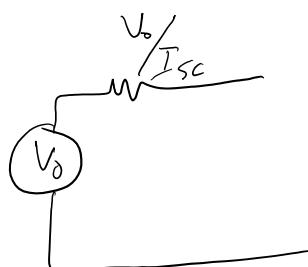

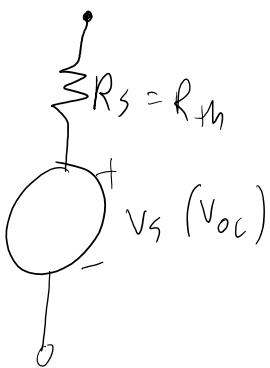

$$V_{OC} / I_n$$

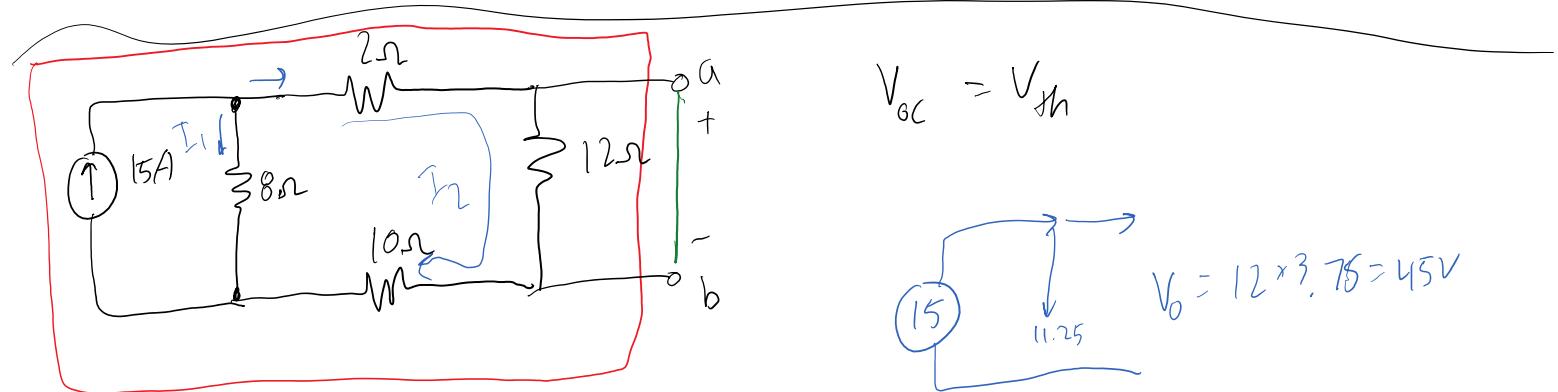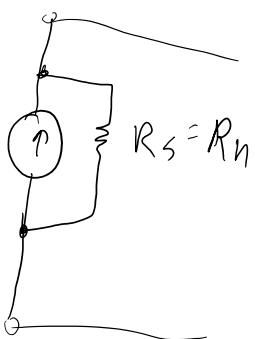


$$V_0 = 12 \times 3.75 = 45V$$

$$I_1 = \frac{15 \times 24}{32} = 11.25A$$

$$I_2 = \frac{15 \times 8}{32} = 3.75A$$

$$I_{SC} = \frac{15 \times 8}{20} = 6A \quad R_N = \frac{45V}{6A} \quad R_N = 7.5\Omega$$

Norton

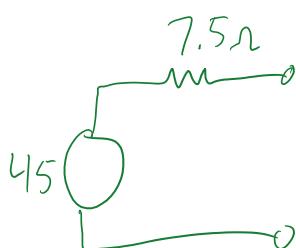


$$V_{OC} = 45V$$

$$I_S = 6A$$

$$V_{OC} = 45V$$

$$I_{SC} = 6A$$

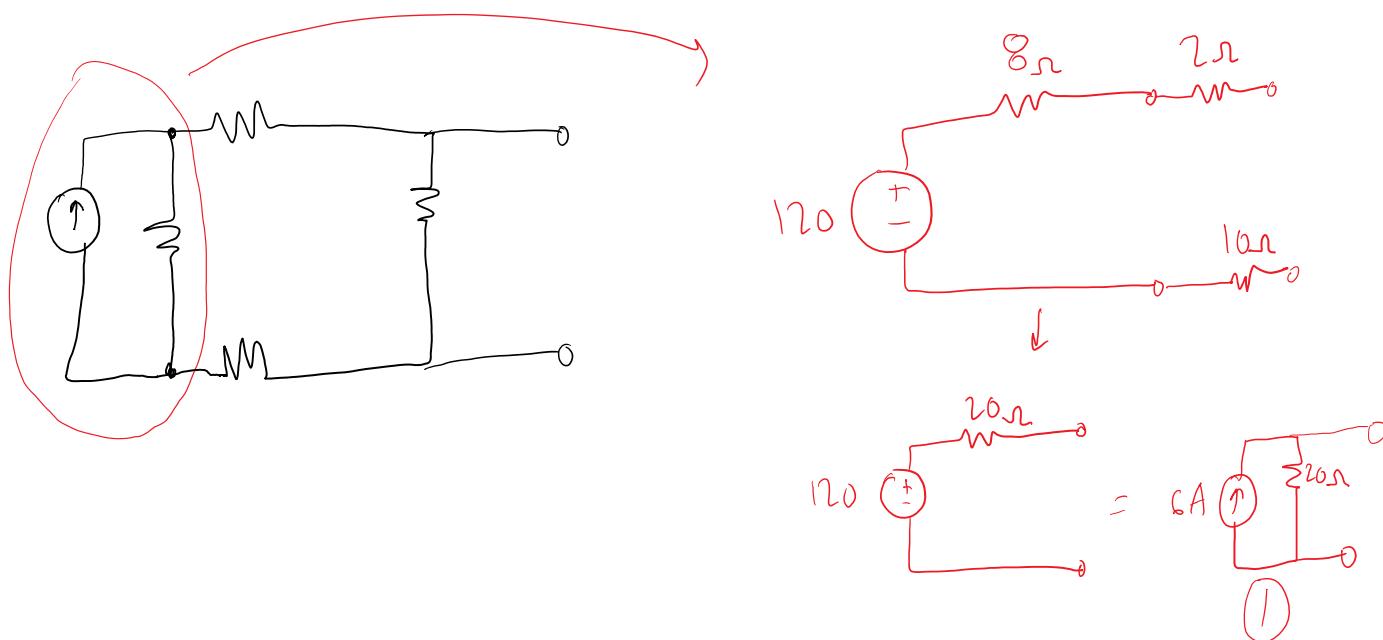


$$(1) \quad \text{6A} \quad \left(\begin{array}{c} \uparrow \\ \downarrow \end{array} \right) \quad \left\{ \begin{array}{l} 20\Omega \\ 12\Omega \end{array} \right\}$$

$$\frac{12 \times 20}{12 + 20} = \frac{240}{32} = 7.5\Omega$$

$$\text{V}_{oc} = 6 \cdot 7.5 = 45V$$


$$I_n = I_{sc} = 6A$$

$$R_N = \frac{45}{6} = 7.5\Omega$$

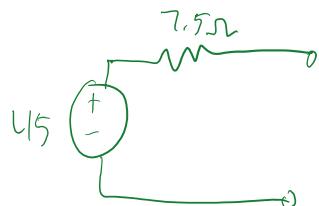

$$\text{V}_{oc} = 45V$$

$$I_{sc} = 6A$$

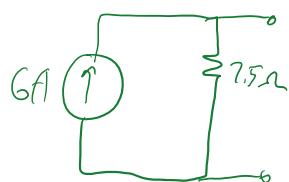

$$\text{V}_{oc} = 45V$$

$$I_{sc} = 6A$$

"Easy Way"


- 1) short all voltage sources or/and open all current sources
- 2) compare the equivalent resistance from the point of the output "port"

$$\frac{12+8}{2} = 20$$
$$\Rightarrow \frac{20 \times 12}{12+20} = 7.5 \Omega$$


Superposition

Monday, September 19, 2016 9:02 AM

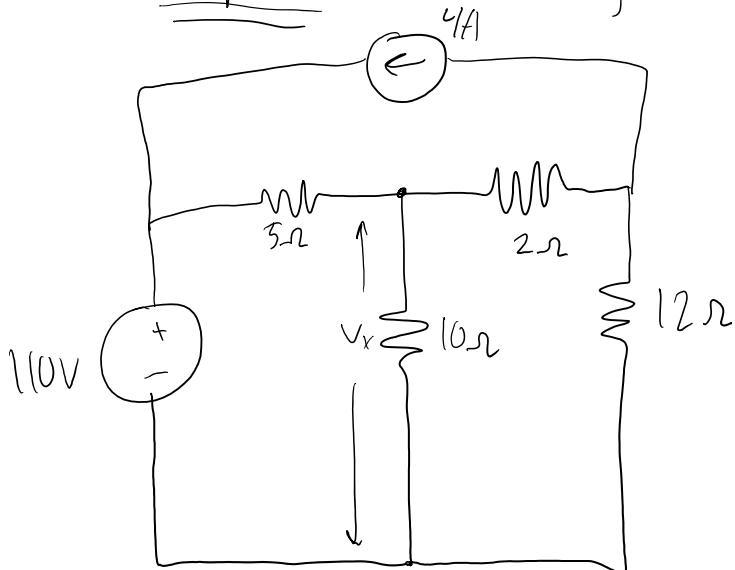Given a linear network, any circuit voltage or current may be calculated as the algebraic sum of the individual voltages or currents caused by two or more independent sources acting alone.



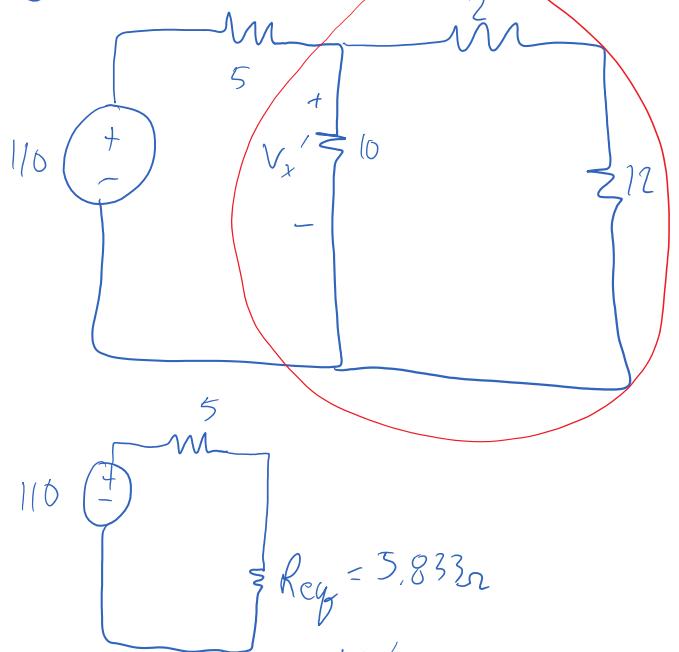① Zero out current source $\frac{14}{110}$







$$R_{eq} = 5.833\Omega$$

$$Vx' = \frac{5.833}{5+5.833} \cdot 110$$

$$Vx' = 59.231V$$

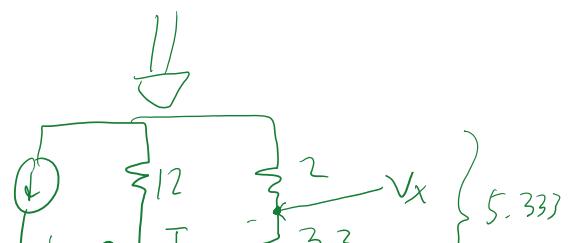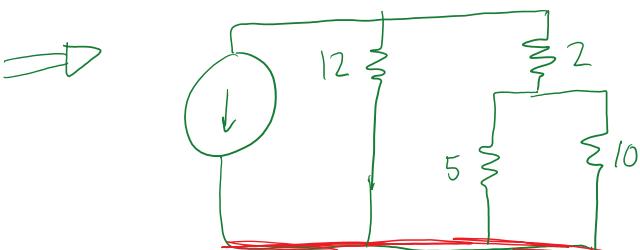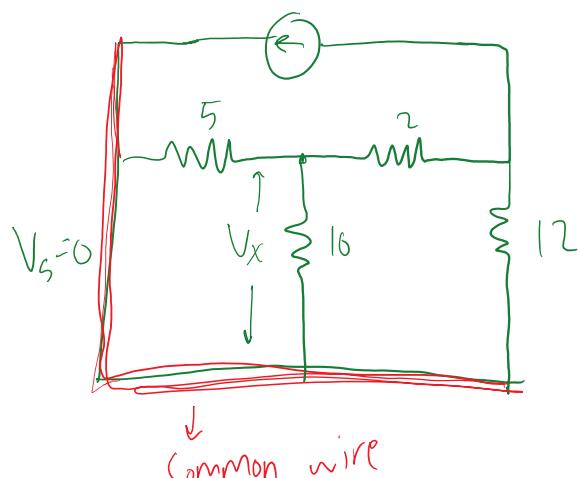② Zero out Voltage source, Activate current source



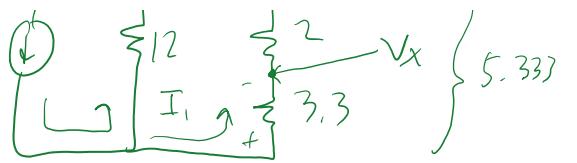

$$V_X = V_X' + V_X''$$

$$\boxed{V_X = 50 \text{ V}}$$

$$I_1 = \frac{4(12)}{12+5.33}$$

$$I_1 = 2.769 \text{ A}$$

$$V_X = I_1 (3.3 \Omega)$$


$$(\text{Direction of resistor flipped}) V_X'' = -9.231 \text{ V}$$

Max Power

If $R_m = R_{\text{load}}$, max power has been transferred

Test Prep

Wednesday, September 21, 2016 9:10 AM

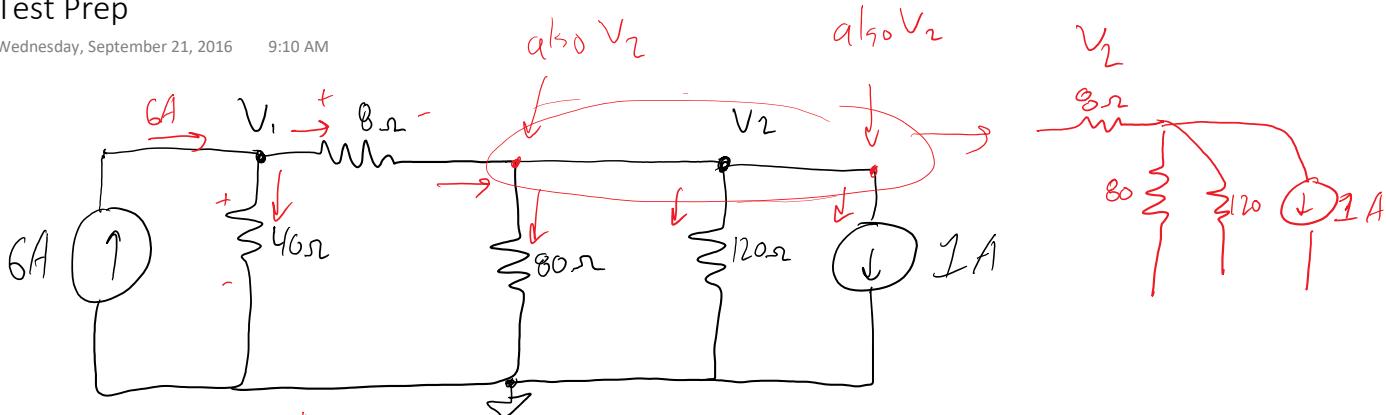

Node Voltage Analysis

$$\underline{V_1}: \quad 6 = \frac{V_1 - 0}{40} + \frac{V_1 - V_2}{8} \quad \textcircled{1} \quad 240 = V_1 + 5V_1 - 5V_2$$

$$6V_1 - 5V_2 = 240$$


$$\underline{V_2}: \quad \frac{V_1 - V_2}{8} = \frac{V_2 - 0}{80} + \frac{V_2 - 0}{120} + 1$$

$$15V_1 - 15V_2 = 1.5V_2 + V_2 + 120$$

$$\textcircled{2} \quad 15V_1 - 17.5V_2 = 120$$

$$\boxed{\begin{aligned} V_1 &= 120 \text{ V} \\ V_2 &= 96 \text{ V} \end{aligned}}$$

Mesh Method

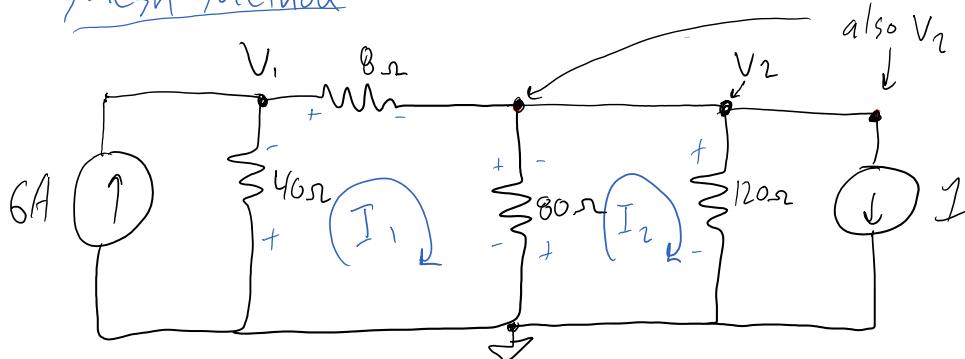

Mesh 1:

$$40(I_1 - 6) + 8I_1 + 80(I_1 - I_2) = 0$$

$$40I_1 - 240 + 8I_1 + 80I_1 - 80I_2 = 0$$

$$\textcircled{1} \quad 128I_1 - 80I_2 = 240$$

Mesh 2:

$$80(I_2 - I_1) + 120(I_2 - 1) = 0$$

$$80I_2 - 80I_1 + 120I_2 - 120 = 0$$

$$\textcircled{2} \quad -80I_1 + 200I_2 = 120$$

$$I_1 = 3A$$


$$I_2 = 1.8A$$

$$V_1 = 40(6 - I_1) \quad V_1 = 40(3) \quad \boxed{V_1 = 120 \text{ V}} \quad \checkmark$$


$$V_2 = V_1 - 8(I_1) \quad V_2 = 120 - 24 \quad \boxed{V_2 = 96} \quad \checkmark$$

Test Prep (cont)

Friday, September 23, 2016 9:01 AM

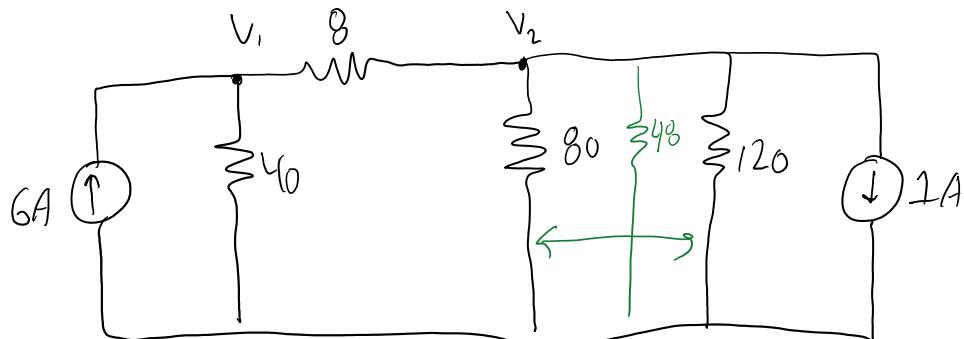



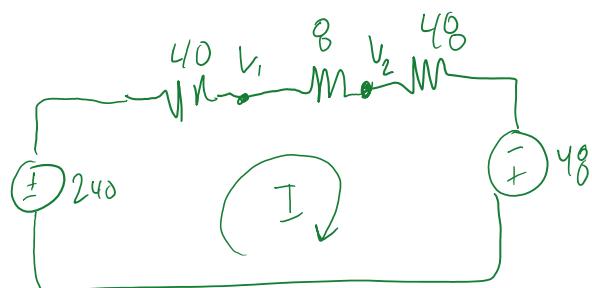
$$R_N = \frac{80 \cdot 120}{80 + 120} = 48$$



$$-240 + 40I + 8I + 48I - 48 = 0$$


$$a_6 I = 238 \quad I = 3A$$
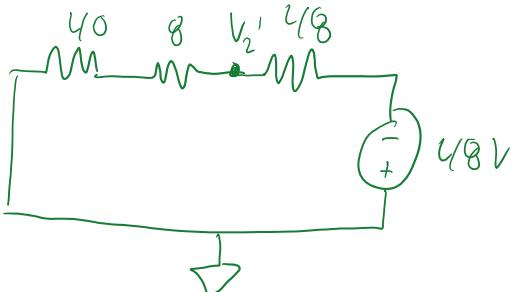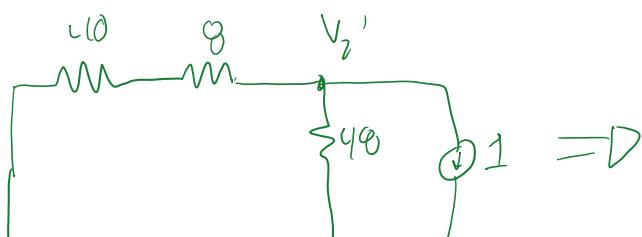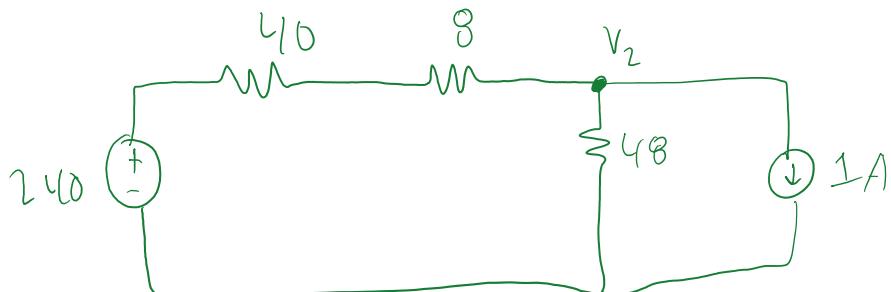
$$\begin{aligned} 240 - 3(40) &= 120 = V_1 \\ 120 - 8(3) &= 96 = V_2 \end{aligned}$$






$$V_2' = -48 \left(\frac{40+8}{96} \right) = -24$$

Voltage divider

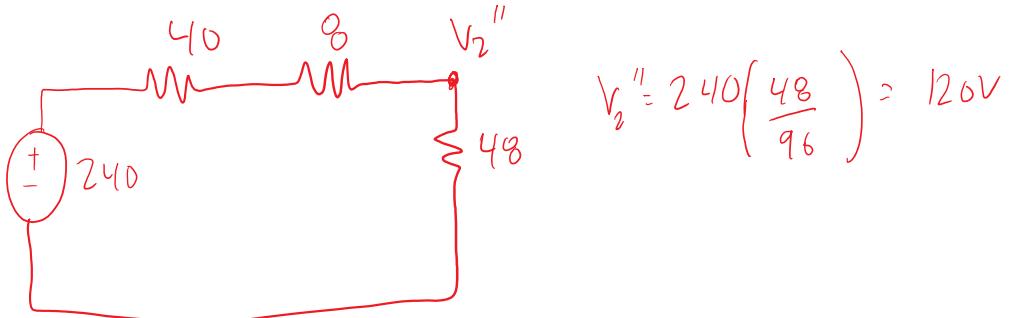


$$V_2 = V_2' + V_2'' = -24 + 120 = 96$$

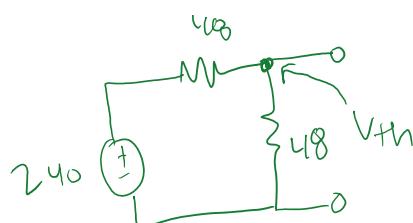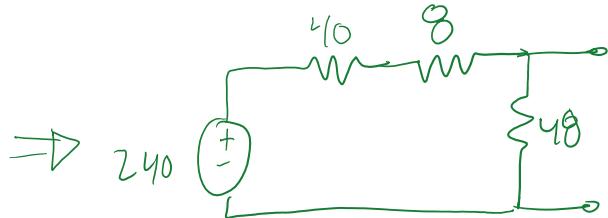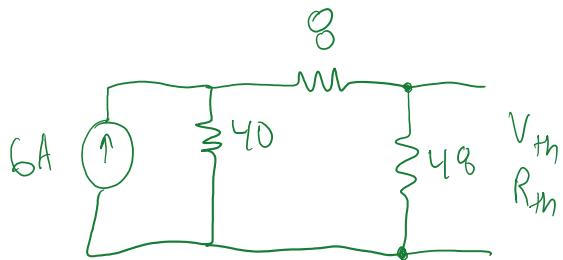


$$V_{th} = 240 \left(\frac{48}{96} \right) = 120V$$

$$R_{th} = \frac{V_{th}}{I_{sc}}$$

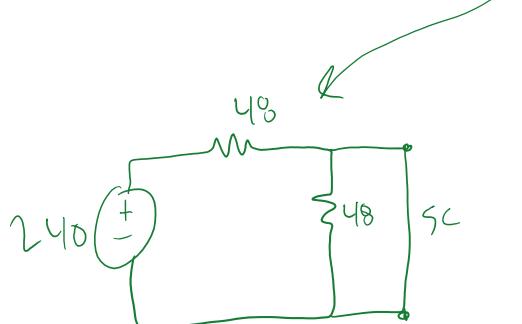


$$I_{sc} = \frac{V}{R} = \frac{240}{48} = 5A$$

$$R_{th} = \frac{120V}{5A} = 24\Omega$$

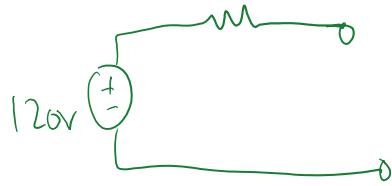


Voltage Divider

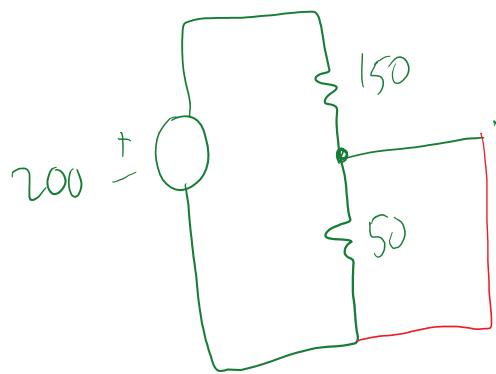

$$V = 200 \left(\frac{50}{200} \right) \quad V_{th} = 50V$$
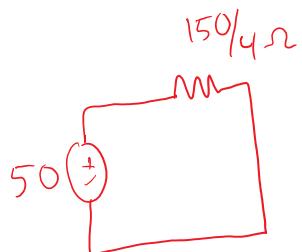
$$I_{sc} = \frac{200}{150} = \frac{4}{3} A$$




$$R_{th} = \frac{V}{I} \quad R_{th} = \frac{50}{\frac{4}{3}} = \frac{150}{4}$$

Operational Amplifiers

Wednesday, September 28, 2016 8:59 AM


Role of an amplifier

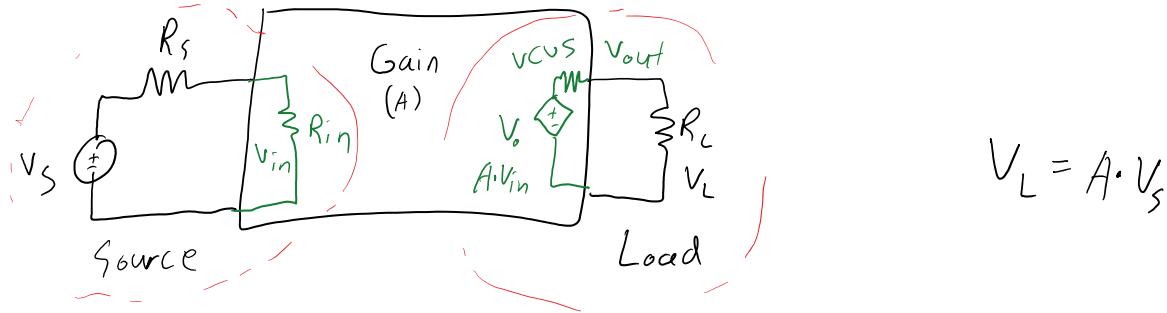- A circuit designed to boost the power of the source voltage V_s



$$V_{in} = \frac{R_{in}}{R_s + R_{in}} \quad R_{in} \rightarrow \text{large}$$

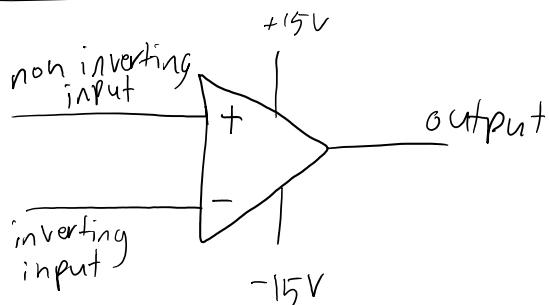- Input Resistance Large (10^6 to 10^9)
- High Gain (A) (10^5 to 10^6)
- $V_L = \frac{A \cdot V_{in} \cdot R_L}{R_L + R_s}$, so want very low output resistance ($< 1 \Omega$)




$$R_{in} \rightarrow \infty$$

$$R_{out} \sim 0$$

$$A \rightarrow \infty$$

Classic opamp circuit

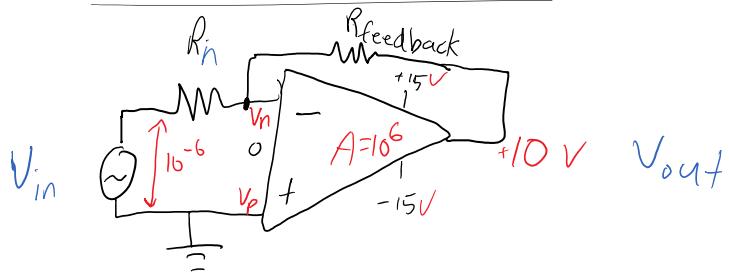

$$V_p - V_n = 0$$




$$V_p - V_n = 0$$

$$V_{in} = \frac{V_s \cdot R_n}{R}$$

virtual Ground

$$i_1 = \frac{V_s}{R_s}$$

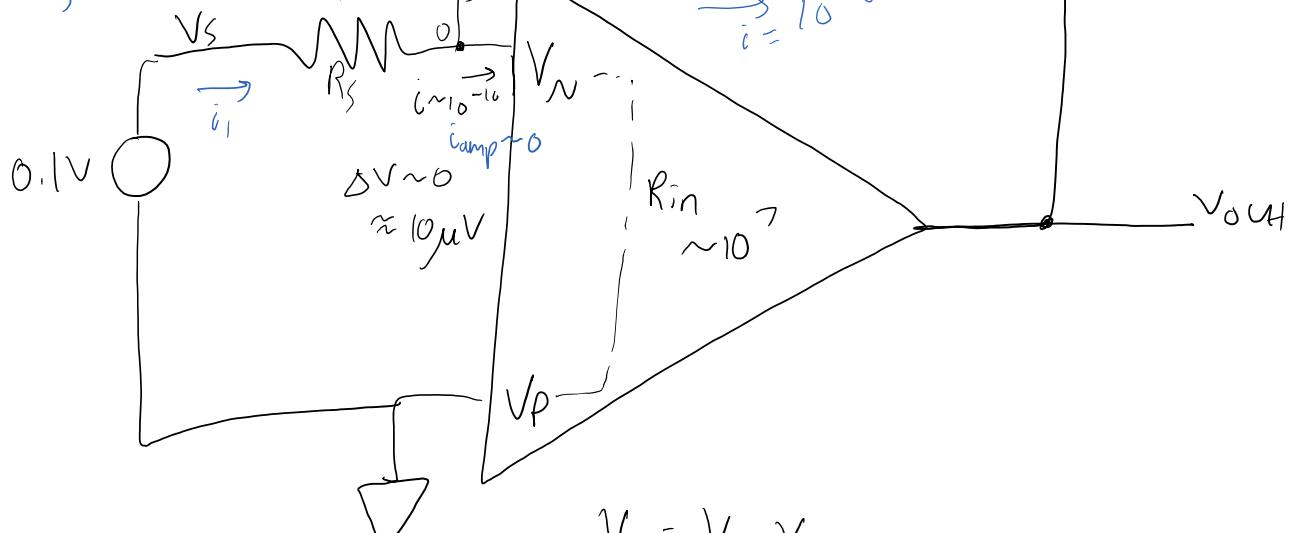


$$V_b = V_n - V_p$$

$$V_{out} = -10^6 \times 10^{-5} = -10V$$

Negative Feedback

Friday, September 30, 2016 9:03 AM

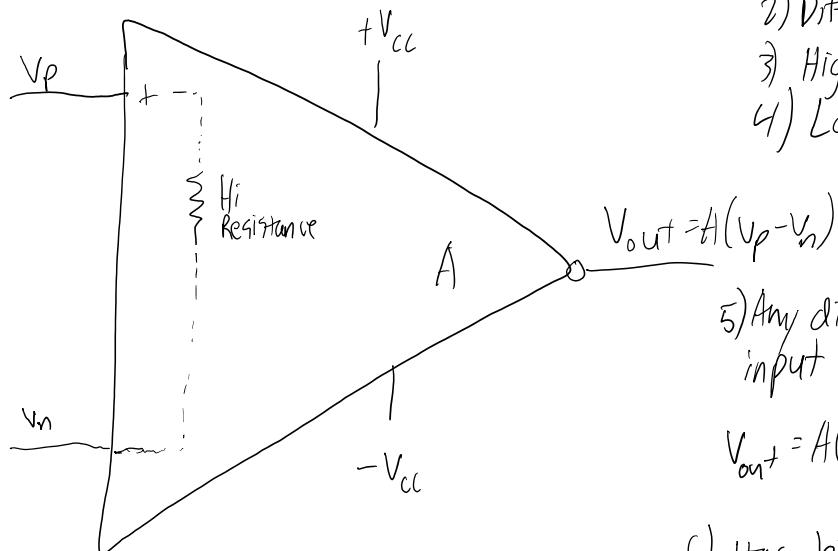


- 1) High Gain ($10^5, 10^6$)
- 2) Differential Input
- 3) High Input Resistance
- 4) Low Output Resistance

5) Any differential signal in the input is multiplied by A


$$V_{out} = A(V_p - V_n) = V(V_n - V_p)$$

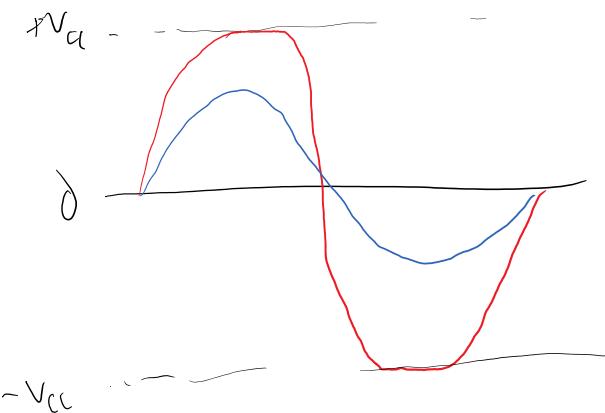
6) Has bipolar power supplies to support a bipolar output





Feedback

Positive F.B.

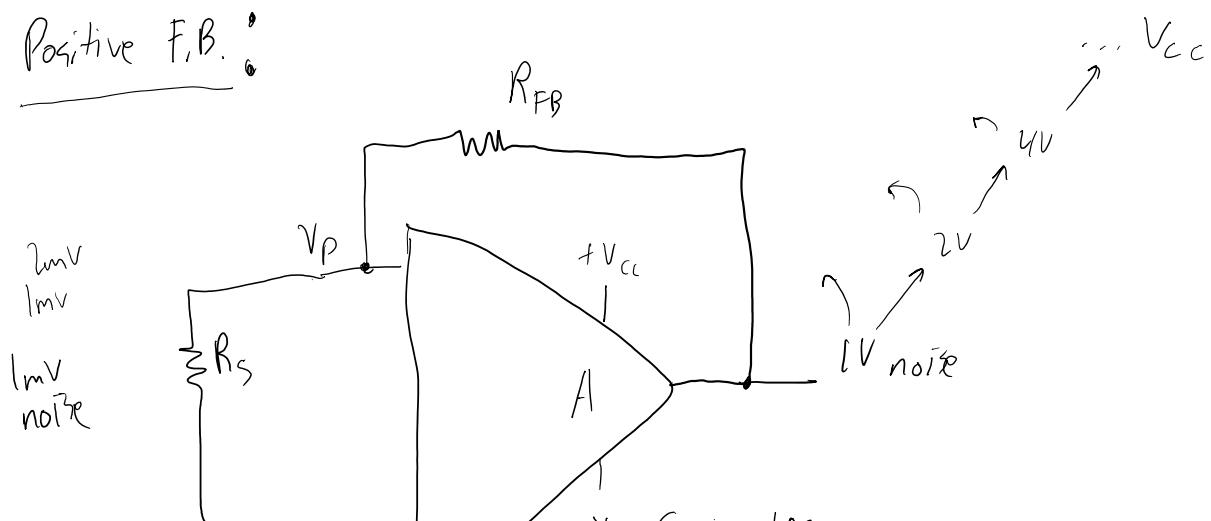

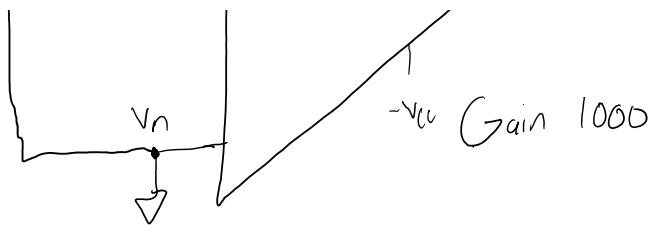

Negative F.B.:

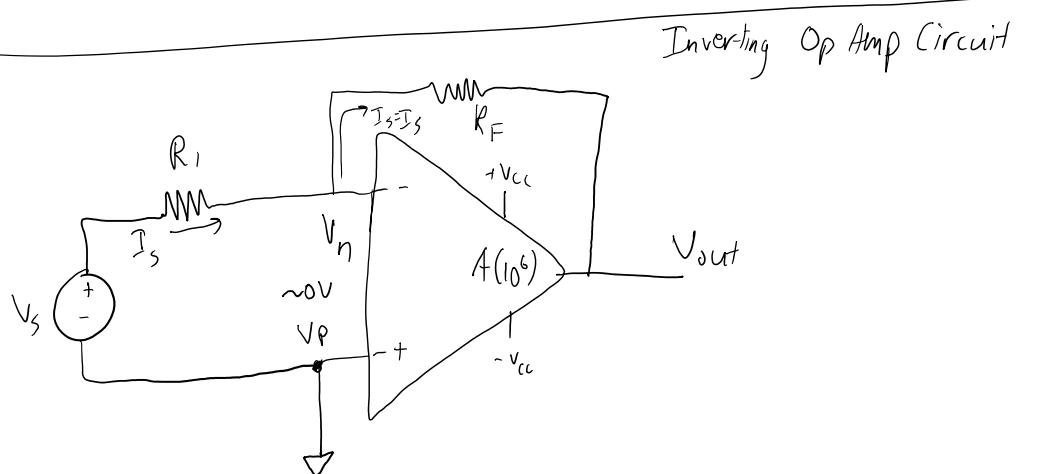
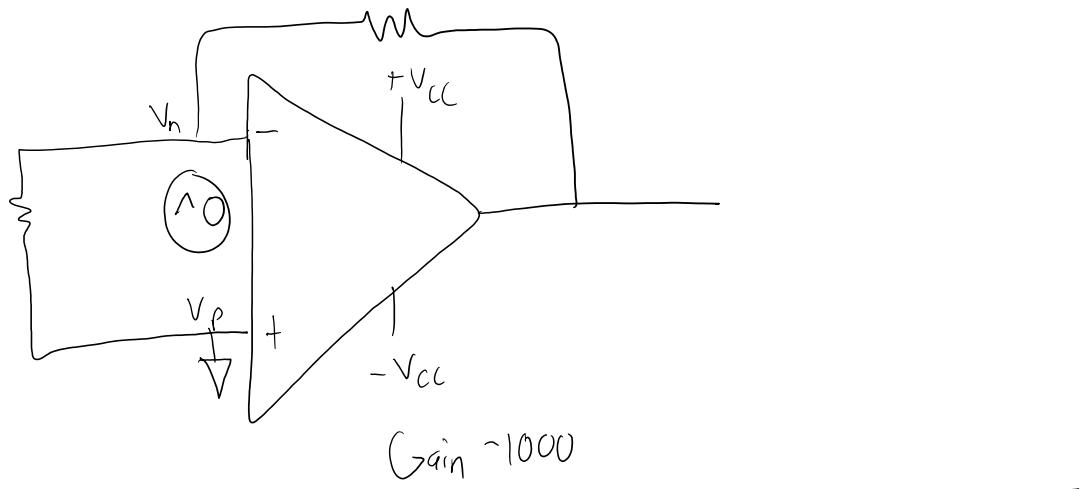


$$I_s = \frac{V_s - 0}{R_s} = \frac{V_s}{R_s}$$


$$V_{out} = 0 - I_s R_F = - \frac{V_s}{R_s} R_F$$

$$\text{Gain of Circuit} = G = - \frac{V_{out}}{V_s} = - \frac{V_s R_F}{R_s} \cdot \frac{1}{V_s}$$

$$\text{Gain} = - \frac{R_F}{R_s}$$

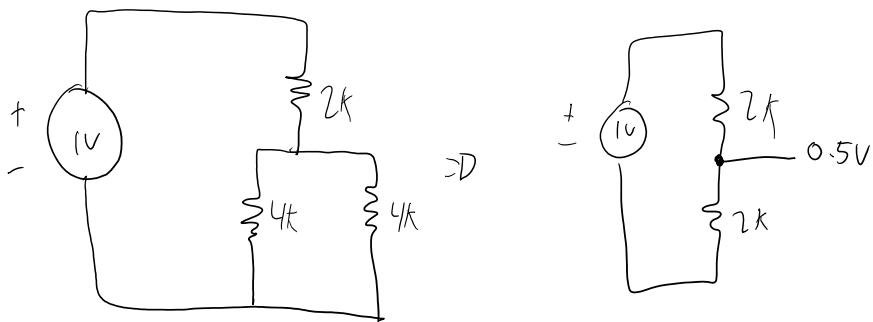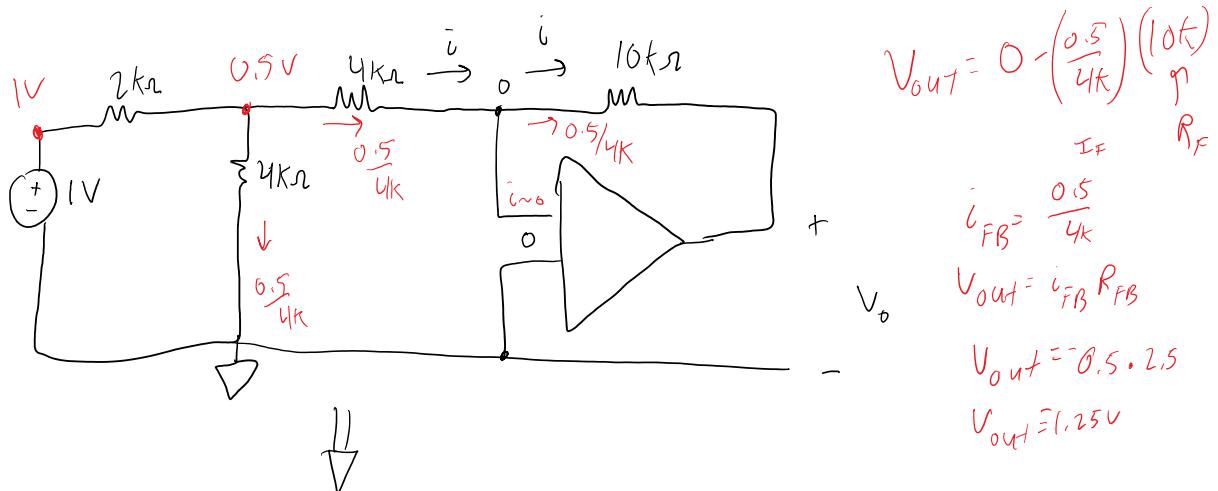

$$1) a) A_v = \frac{V_o}{V_s}$$

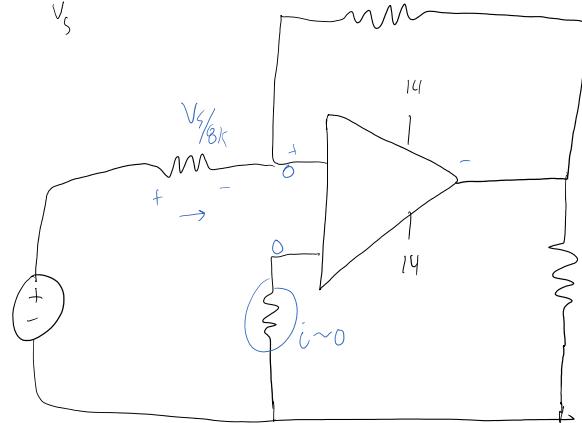

$$V_{out} = 40k \left(\frac{V_s}{8k} \right) = -6V_s$$

b) For $-3V$


$$V_{out} = -6(-3) = 18V \text{ theor}$$

$14V$ actual

$$V_{out} = -6(1.5) = -9V \text{ theor}$$


actual

2)

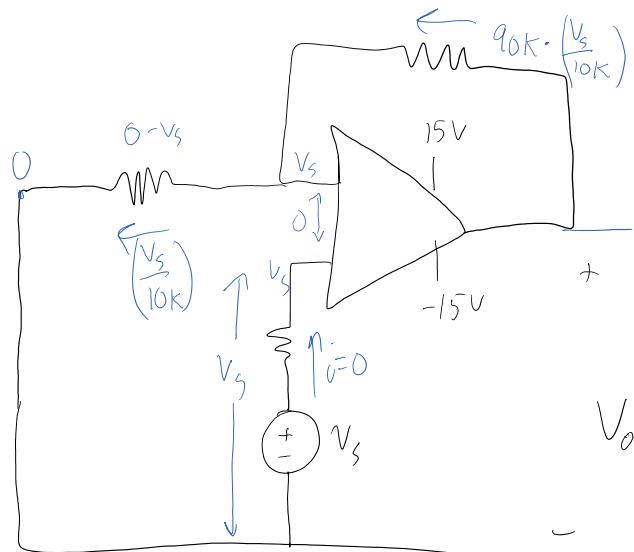

$$V_s \left(\frac{R_F}{R_I} + 1 \right) = V_s \left(\frac{90k}{10k} + 1 \right) = 10V_s$$

V_o

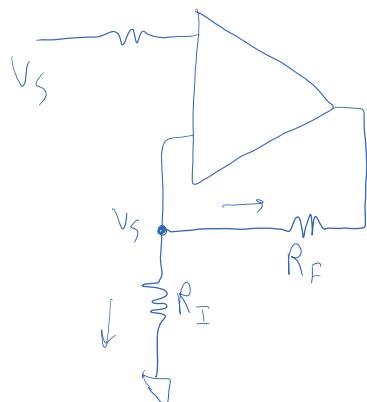



$$\frac{V_s}{R_I}$$

$$V_{RF} = R_F \cdot \frac{V_s}{R_I}$$


$$V_{out} = V_{RF} + V_{RI}$$


$$V_{out} = V_s \left(\frac{R_F}{R_I} \right) + V_s$$
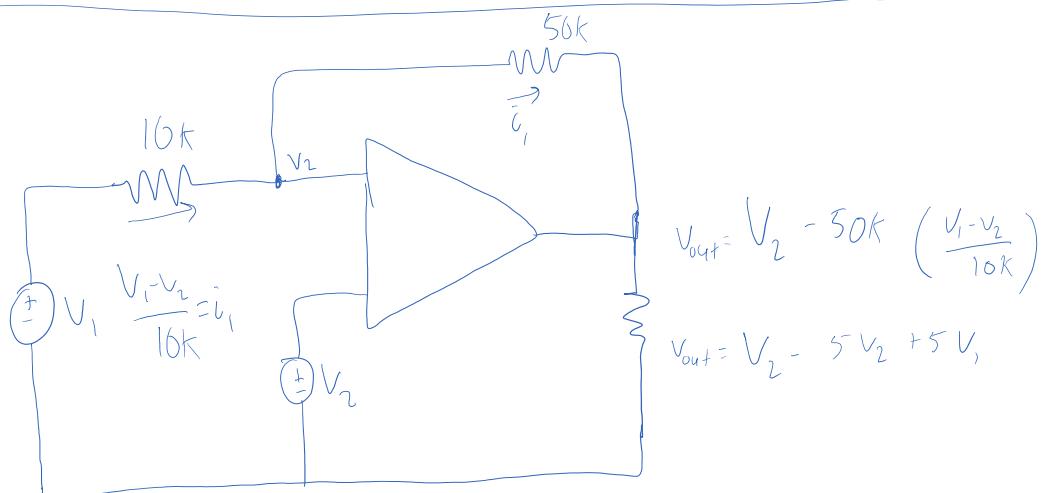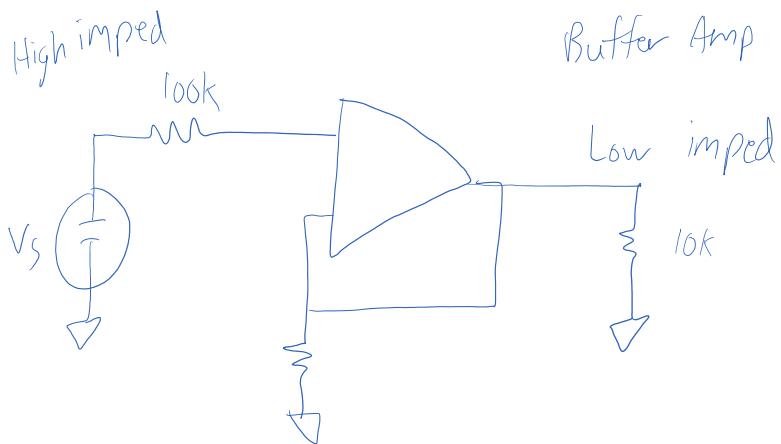
$$= V_s \left(\frac{R_F}{R_I} + 1 \right)$$



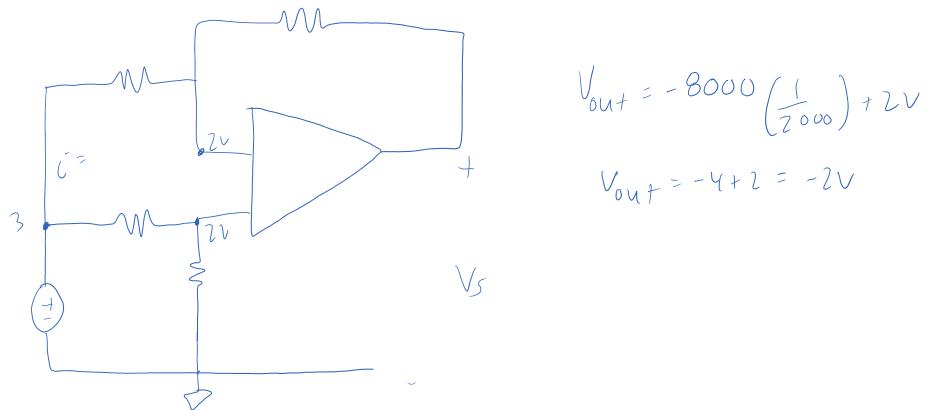4) $V = \frac{3(10)}{15} = \frac{30}{15} = 2V$



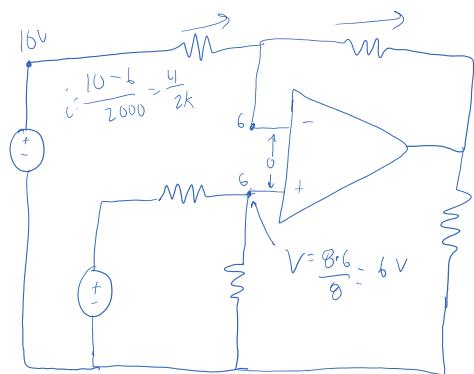


$$6 - 4k \left(\frac{y}{2k} \right)$$

$$6 - 8 = -2V$$

Inductors and Capacitors

Friday, October 7, 2016 9:02 AM

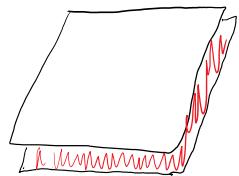

$$\text{Constant } \epsilon_r$$

$$\epsilon_0 = 8.85 \times 10^{-12} \frac{F}{m}$$

$$C = \frac{\epsilon_r \epsilon_0 A}{d}$$

$$V = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int v dt$$

$$U = \frac{1}{2} L I^2$$

$$V = \frac{1}{C} \int i dt$$

$$i = C \frac{dv}{dt}$$


$$U = \frac{1}{2} CV^2$$

$$\frac{1}{C} \text{ cap (passive)}$$

$$q = CV$$

$$\frac{\text{Coul}}{\text{Volt}} = \text{Farrad} = \frac{\text{Amp - Sec}}{\text{Volt}}$$

{ inductor
(passive)
conductor

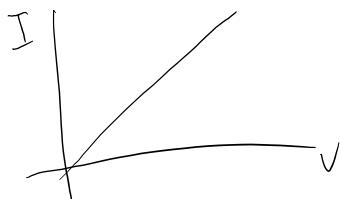


$$i = \frac{dq}{dt} = C \frac{dv}{dt}$$

$$i = C \frac{dv}{dt}$$

$$V = \frac{1}{C} \int i dt$$

$$U = \int P dt = \int V \cdot I dt = V C \frac{dv}{dt} C \int v \frac{dv}{dt} = \frac{CV^2}{2} = U$$

Caps in parallel

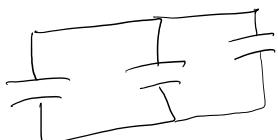


$$C_T = C_1 + C_2 + C_3$$

Caps in Series




$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$
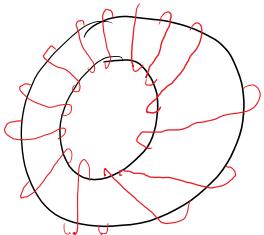
$$\text{Inductance } L = \text{Henry} = \frac{\text{Volts - Sec}}{\text{Amp}}$$



$$\lambda = LI = N \Phi$$


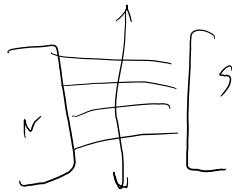
$$V = \frac{d\lambda}{dt} = \frac{d}{dt} LI$$




inductor

$$V = \frac{d}{dt} LI$$

$$= L \frac{dI}{dt}$$

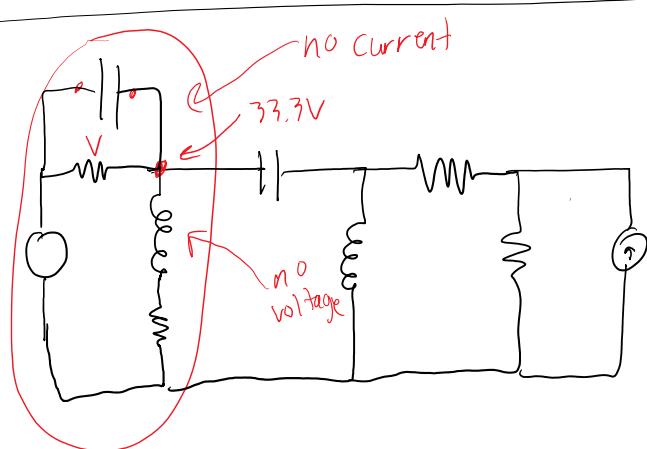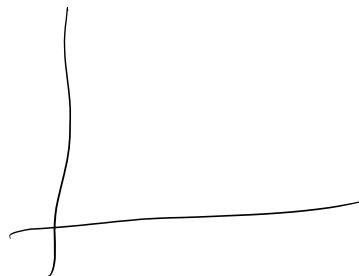


$$V = 100 \cdot \frac{100}{150}$$

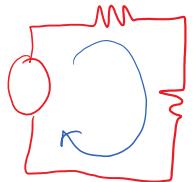

$$U = \frac{1}{2} L I^2$$

$$I = \frac{100V}{150\Omega} = \frac{2}{3} A$$

$$U = \frac{1}{2} L I^2$$

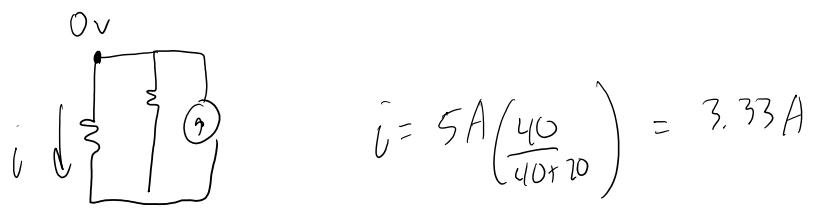



$$i = 5A \left(\frac{40}{40+20} \right) = 3.33A$$

$$U = i_2 L I^2$$

Transient Response of 1st Order Circuits

Monday, October 10, 2016 9:01 AM

Natural Response

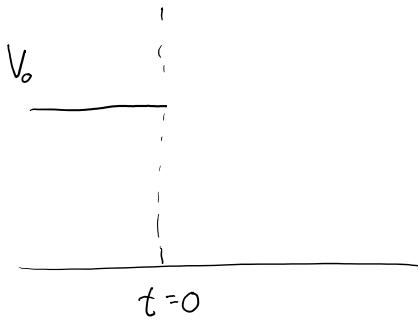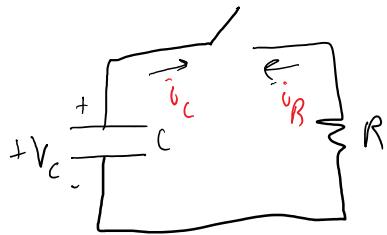


$$\dot{V}_R = \frac{V_c}{R}$$

$$i_c = C \frac{dV_c}{dt}$$

$$\frac{V_c}{R} + C \frac{dV_c}{dt} = 0$$
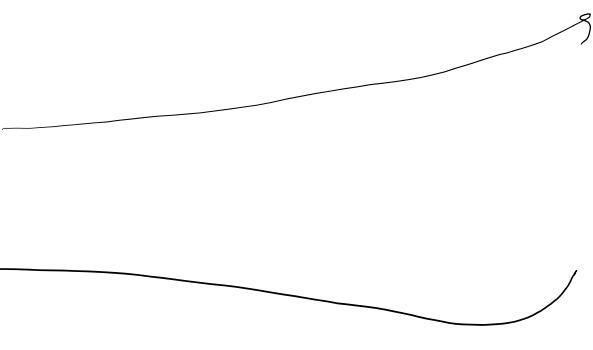
$$\left. \begin{aligned} V_c &= ke^{st} \\ V'_c &= ske^{st} \end{aligned} \right\}$$



$$V_c + R_C \frac{dV}{dt} = 0$$

$$ke^{st} + sR_C ke^{st} = 0$$

$$(1 + sR_C) ke^{st} = 0$$

$$1 + sR_C = 0$$


$$s = \frac{-1}{RC}$$


$$V_{o-} = V_{o+} = V_c = ke^{-t/RC}$$

$$V_c(0) = K$$


$$V_c = V_o e^{-t/\tau} \quad \tau = RC$$

$$V_c = V_o e^{-t/\tau}$$

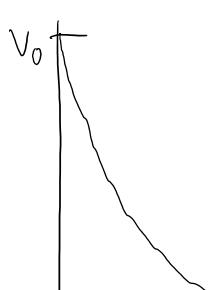

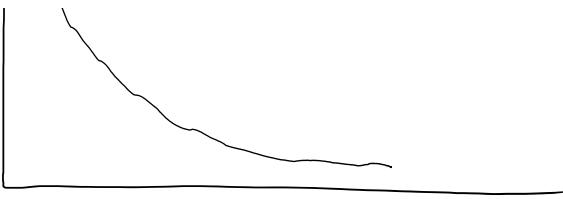

RL - Natural Response

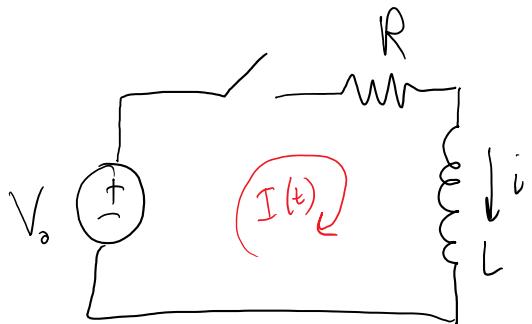

$$-V + i_t R + L \frac{di_t}{dt} = 0$$

$$i_t R + L \frac{di_t}{dt} = V$$

$$i_t = K_1 + K_2 e^{st}$$

$$R(K_1 + K_2 e^{st}) + K_2 L s e^{st} = V$$

$$R(K_1) + (R + sL)K_2 e^{st} = V$$

$$R + sL = 0$$

$$sL = -R \quad s = -\frac{R}{L}$$

$$RK_1 = V$$

$$K_1 = \frac{V}{R}$$

$$i_t = \frac{V_s}{R} + K_2 e^{-\frac{R}{L}t} \quad \frac{L}{R} = \gamma$$


$$i_t = \frac{V_s}{R} + K_2 e^{-t/\gamma}$$

$$i_{o+} = i_{o-} = 0 = \frac{V_s}{R} + K_2 e^{\frac{R}{L}(0)}$$

$$0 = \frac{V_o}{R} + K_2 \quad K_2 = -\frac{V_o}{R} \quad V_s = V_o$$

$$i(t) = \frac{V_o}{R} - \frac{V_o}{R} e^{-t/\gamma}$$

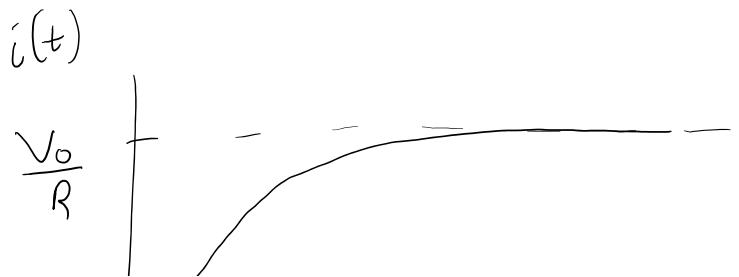
$$i(t) = \frac{V_o}{R} (1 - e^{-t/\gamma})$$



$$i(t) = \frac{V_0}{R} \left(1 - e^{-t/\tau} \right)$$



$$V_i = V_0 - i_t R$$

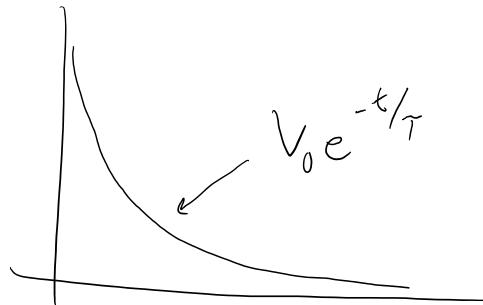

Process for Switched LR & RC Circuits

Step 1) Find the time constant for RC: $\tau = R_{eq} \cdot C$
for LR: $\tau = L/R_{eq}$

Step 2) Evaluate the initial value

for L: i_0 is often 0 at $t=0$

for C: V_0 is the voltage on the capacitor at $t=0$

Step 3) Evaluate the final value at t very large

Capacitors are open circuits at t large

Inductors are short circuits at t large

Step 4) $x(t) = x_f + (x_0 - x_f) e^{-t/\tau}$

for cap: $V(t) = 0 + (V_0 - 0) e^{-t/\tau_{RC}} \rightarrow V_0 e^{-t/\tau_{RC}}$

for ind: $I(t) = \frac{V}{R} + \left(0 - \frac{V}{R} \right) e^{-\frac{Rt}{L}} \rightarrow \frac{V}{R} - \frac{V}{R} e^{-\frac{Rt}{L}}$

Transient Analysis, Step by Step Procedure

Step 1: Find the time constant

$$\text{Cap: } T = R_{\text{eq}} \cdot C$$

$$\text{Ind: } T = L/R_{\text{eq}}$$

Step 2: Find Initial Value X_0

$$\text{Cap: } V_{s0-} = V_{s0+}$$

$$\text{Ind: } I_{s0-} = I_{s0+}$$

Step 3: Find the Final Value $\boxed{X_F}$ (>5 time constants later)


$$\text{Step 4: } X_t = X_F + (X_0 - X_F) e^{-t/T}$$

$$V_t$$

$$I_t$$

$$X_t = X_F + (X_0 - X_F) e^{-t/T}$$

HW #2

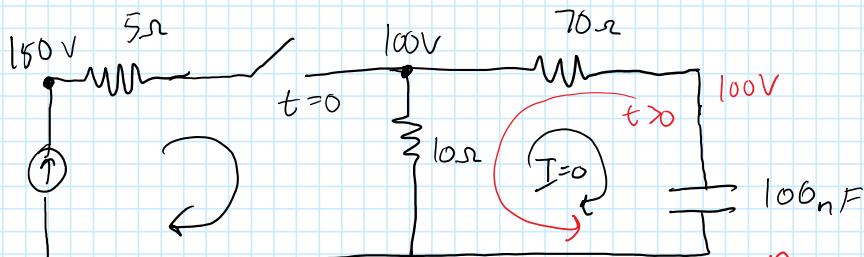

$$100V = V_{co-} = V_{co+}$$


$$R_{\text{eq}} = 70 + 10 \quad T = 100nF \times 80\Omega$$

$$V_{cf} = 0V$$

$$V_c(t) = 0 + (100 - 0) e^{-t/T}$$

$$V_c(t) = 100 e^{-t/T}$$

HW #3

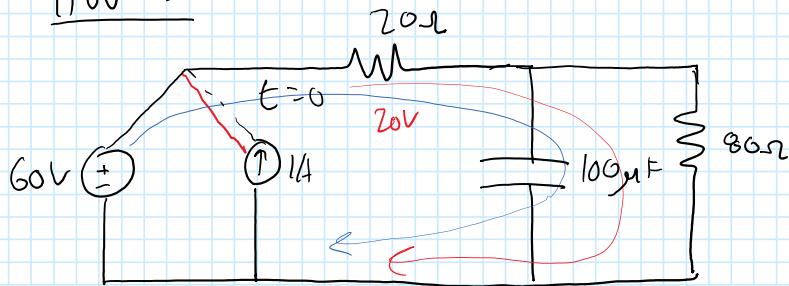


$$V_{co} = \frac{60(80)}{80+20} = 48V$$

$$V_{co+} = 48V$$

$$V_{cf} = 80V$$

$$x(t) = 80 + (-32)e^{-t/\tau}$$

$$\tau = 100 \mu F \cdot (80 \Omega)$$

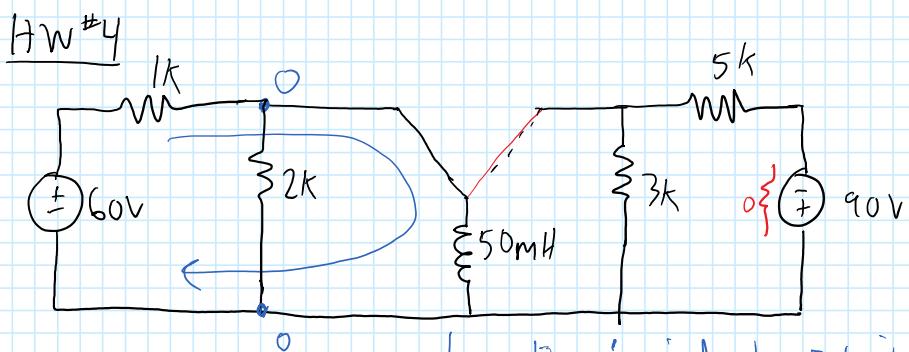


$$I_L(t_0) = I_L(t_0+) = \frac{60V}{1k} \text{ long time: inductor = wire} \\ 0.06A = X_0$$

$$R_{eq} = \frac{3+5}{3+5} = 1.875k$$

$$\tau = \frac{0.05H}{1.875k}$$

$$\text{If 'final' inductor = wire, so } i = \frac{90V}{5k} = -0.018A$$

HW #5:

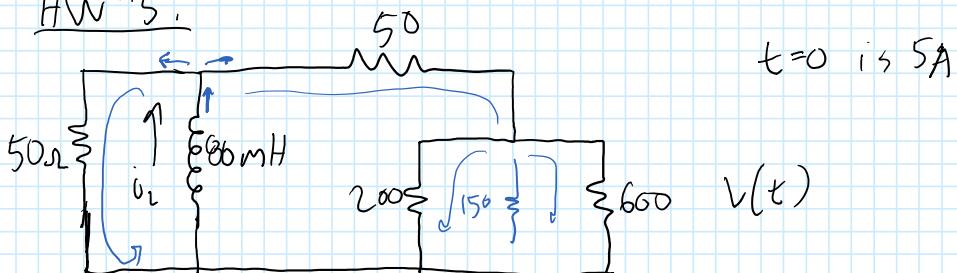

$$I_{0+}(t) = 5A$$

$$R_{eq} = 150 + 50 \parallel 50$$

$$R_{eq} = \frac{200(50)}{250} \quad R_{eq} = 40\Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{0.08H}{40\Omega}$$

$$I_F = 0A \quad I(t) = 0 + (5-0)e^{-t/\tau}$$


$$V_{tF} = 0V$$

$$V_{tu} =$$

HW #6:



$$R_{eq} = 10(40) - 8\Omega$$

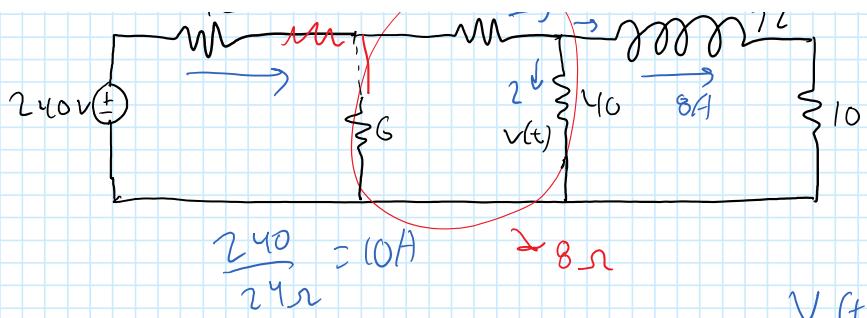

$$R_{eq} = \frac{10(40)}{50} = 8\Omega$$

$$I_o = \frac{10(40)}{50} = 8A$$

$$V_o(t) = 40(z) = 80V$$



$$X_F = 0$$

$$X(t) = 0 + (80 - 0)e^{-t/\tau}$$

Sequential Switching






Friday, October 14, 2016 9:02 AM

General solution

$$x(t) = x_{\text{Final}} + [x_{\text{initial}} - x_{\text{Final}}] e^{-t/\tau}$$

Find $i_1(t)$

Find $V(t)$

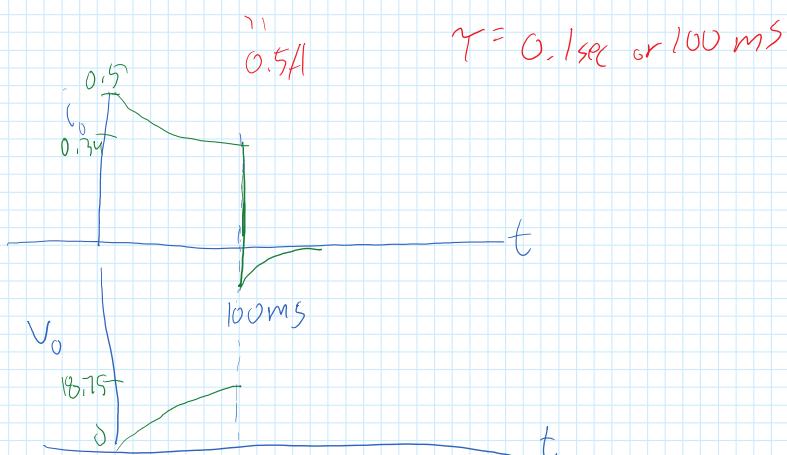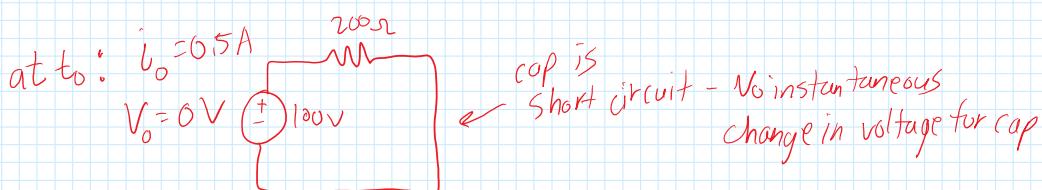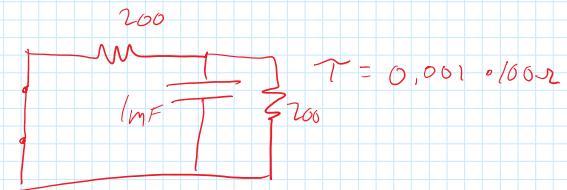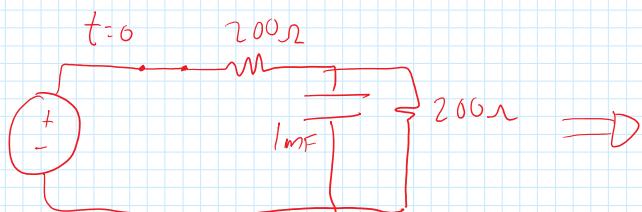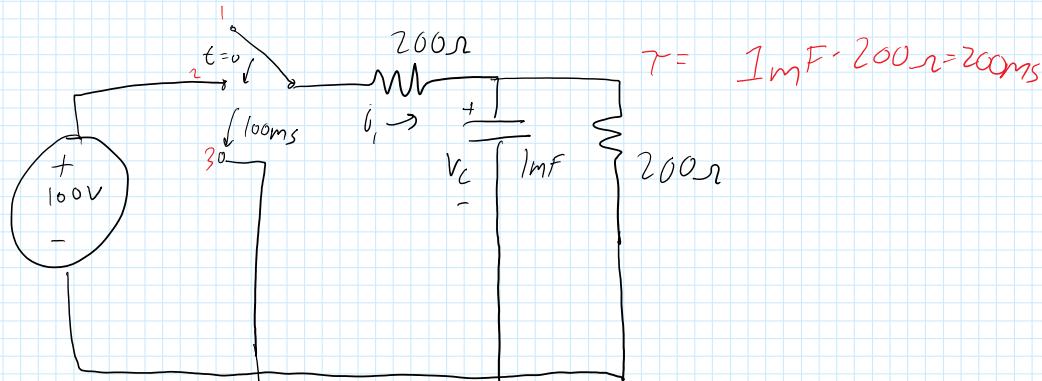

$$V_{\text{Final}} = 50\text{V}$$


$$i_{\text{final}} = 0.25\text{A}$$



cap charged - no current

Circuit

$$V_{final} = 0.25A$$

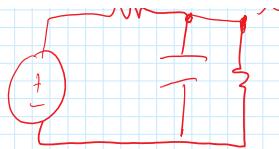

$$i(t) = 0.25 + [0.5 - 0.25] e^{-t/\tau}$$

$$i(t) = 0.25 + 0.25e^{-t/\tau}$$

$$i(0.1) = 0.25 + 0.25e^{-0.1/0.1}$$

$$i(0.1) = 0.3425 A$$

$$V_C(t) = 50 + [0 - 50] e^{-t/\tau} \quad V_C(0.1) = 50 - 50e^{-0.1/0.1}$$


$$V_C(0.1) = 18.5 V$$

$$i_{new,0+} = -0.0925A \quad i_{f(new)} = 0$$

$$V_{C,new,0+} = 18.5 V$$

$$V_{f(new)} = 0$$
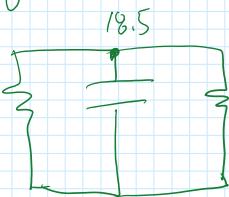
$$\begin{aligned} & \frac{18.5}{200} \\ &= 0.0925A \end{aligned}$$



$$\tau = 0.1 \text{ sec}$$

$$i_{new}(t) = 0 + [-0.0925 - 0] e^{-t/0.1} \quad i_{new}(0) = -0.0925 e^{-t/0.1}$$


$$V_{new}(t) = 0 + [18.5 - 0] e^{-t/0.1}$$

$$V_{new}(t) = 18.5 e^{-t/0.1}$$

Polar Math

Monday, October 17, 2016 9:05 AM
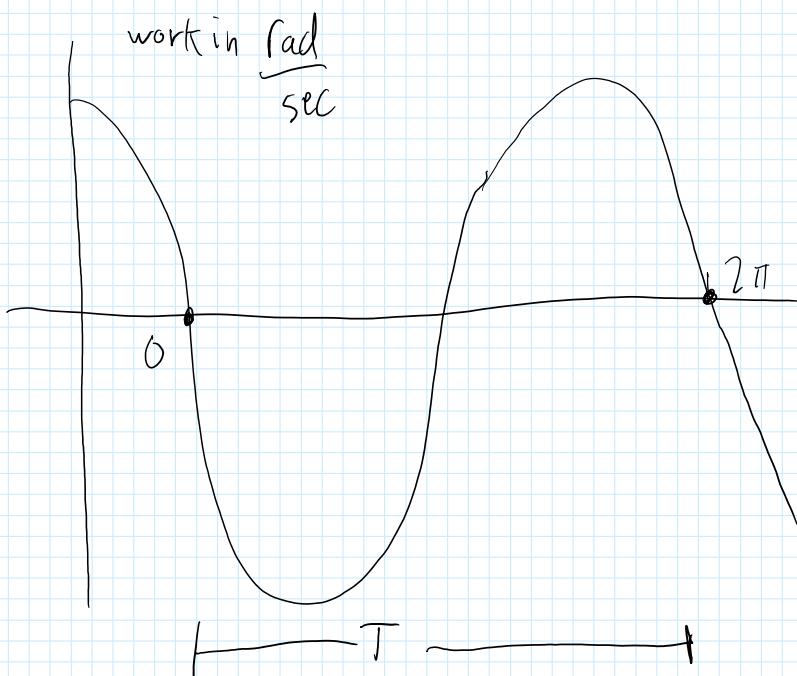
$$f = \text{frequency} = \frac{1}{T} = \frac{\text{cycles}}{\text{sec}} = \text{Hz}$$



$$V(t) = \text{Amplitude} - \text{VA}$$

$T = \text{period of sine wave} = \text{sec}$

$\omega = \text{radian Frequency; } 1/\text{sec}$


$$\omega = 2\pi f$$

$$v(t) = \cos(\omega t + \phi)$$

$$\text{Note: } \sin \theta = \cos \theta + 90^\circ$$

Euler's Identity $e^{j\phi} = \cos \phi + j \sin \phi$ $j = \sqrt{-1}$ $j^2 = -1$
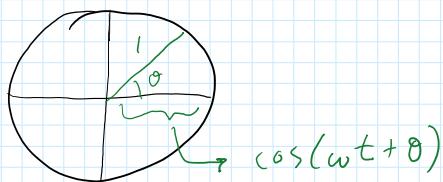
$$V(t) = \text{Re} \left\{ V_m e^{j(\omega t + \phi)} \right\}$$





$$V(t) = \text{Re} \left\{ V_m \cos(\omega t + \phi) + j \sin \omega t + \phi \right\}$$

Phasor

$$\bar{V} = V_m \angle \phi = V \angle$$

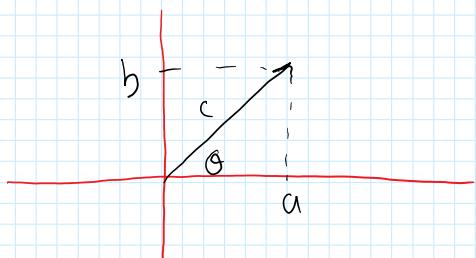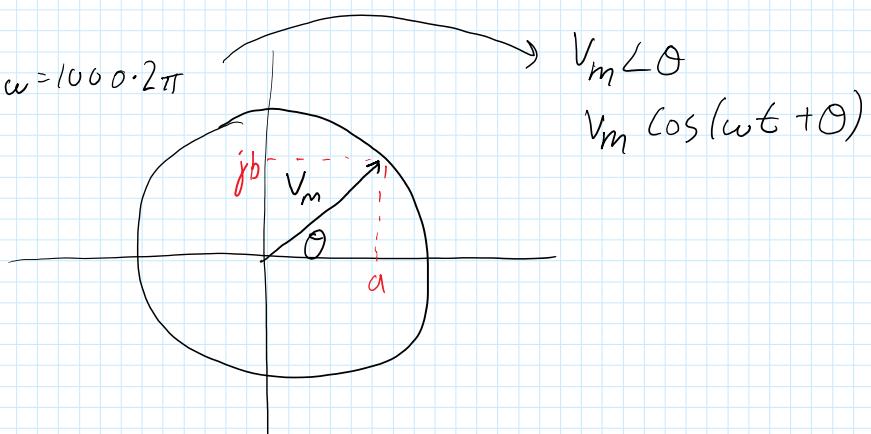
$$f = 1000 \text{ Hz} \quad \omega = 1000 \cdot 2\pi$$



Rectangular: $a + jb$

Polar: $(c \angle \phi)$

Rect \rightarrow Polar

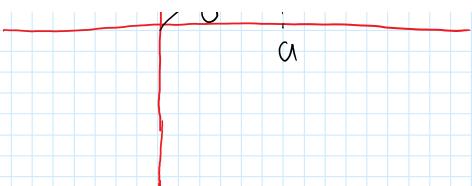

Rect \rightarrow Polar

$$c = \sqrt{a^2 + b^2}$$

$$\theta = \tan^{-1}\left(\frac{b}{a}\right)$$

Polar \rightarrow Rect

$$a = c \cos \theta$$

$$b = c \sin \theta$$

Basic Arithmetic:


Add + Sub \rightarrow use Rectangular

Mult + Div + Exponential \rightarrow use Polar

Complex Conjugate : $n = a + jb$

$$n^* = a - jb \rightarrow \text{complex conjugate}$$
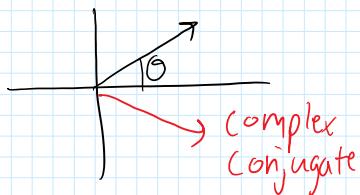
$$n^k = (a + jb)^k = (ce^{j\theta})^k = c^k e^{jk\theta} = (\sqrt{c} e^{j\theta})^k = \sqrt{c}^k \angle k\theta$$



$$n_1 = 4 + j3 = 5 \angle 36^\circ$$

$$n_2 = 13 \angle 67.4^\circ = 5 + j12$$

$$n_1 + n_2 = 4 + j3 + 5 + j12 = 9 + j15 = 17.5 \angle 59^\circ$$

$$\frac{n_1}{n_2} = \frac{4 + j3}{5 + j12} = \frac{5 \angle 36^\circ}{13 \angle 67.4^\circ} = \frac{5}{13} \angle -30.51^\circ$$

$$(5 \angle 36.9) ^4 = 5^4 \angle 147.48^\circ = 625 \angle 147.48^\circ$$

$$(n_1^*)(n_2) = (5 \angle -36^\circ)(13 \angle 67.4^\circ) = 65 \angle 31.4^\circ$$


Circuit Elements in the Frequency Domain

Wednesday, October 19, 2016 9:02 AM

$$V(t) = V_m \cos(\omega t + \phi) \quad \text{Re} \{ V_m e^{j\omega t + \phi} \}$$

$$i(t) = I_m \cos(\omega t + \phi) \quad \text{Re} \{ I_m e^{j\omega t + \phi} \}$$

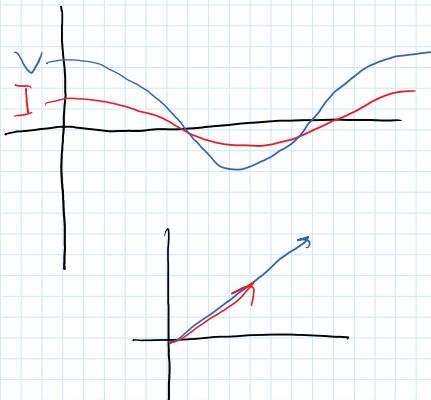
$$\frac{V_m e^{j\omega t + \phi_v}}{e^{j\omega t}} = \frac{RI e^{j\omega t + \phi_i}}{e^{j\omega t}}$$



$$V_m e^{j\phi_v} = RI e^{j\phi_i}$$

$$V_L = RI_L$$

$$\phi_v = \phi_i$$

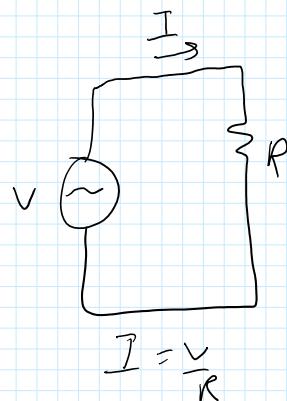

$$I_L = \frac{V_L}{R}$$

Inductor: $V_L = L \frac{di}{dt}$



$$L \frac{d}{dt} I_m e^{j(\omega t + \phi)}$$

$$\frac{V e^{j(\omega t + \phi_v)}}{e^{j\omega t}} = L j\omega I e^{j(\omega t + \phi_i)}$$

$$V e^{j\phi_v} = j\omega L I e^{j\phi_i}$$


$$V_L = j\omega L I$$

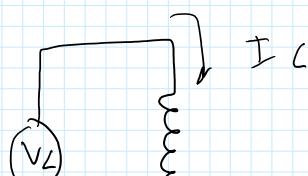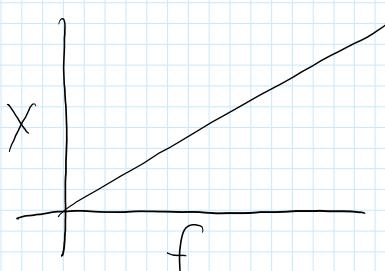$X_L \rightarrow$ inductive reactance, frequency dependent in ohms


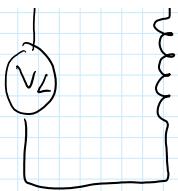
$$I_L = \frac{V_L}{j\omega L} \cdot \frac{j}{j}$$






$$V = j\omega L I$$

$$I = \frac{V}{j\omega L}$$

$$V = j\omega L I$$

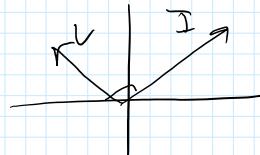

Capacitor: $i(t) = C \frac{dV(t)}{dt}$



$$I_m e^{j(\omega t + \theta_v)} = C \frac{dV_m e^{j(\omega t + \theta_i)}}{dt}$$

$$\frac{I_m e^{j(\omega t + \theta_i)}}{e^{j\omega t}} = \frac{j\omega C V e^{j(\omega t + \theta_i)}}{e^{j\omega t}}$$

$$I_m e^{j\theta_v} = C j\omega V e^{j\theta_i}$$

$$\frac{1}{j\omega t} = \frac{V}{I} = jX$$
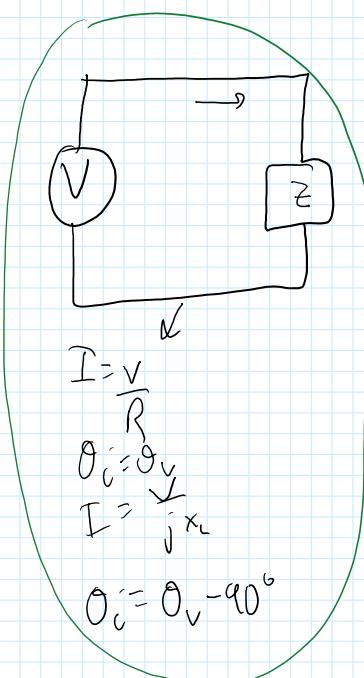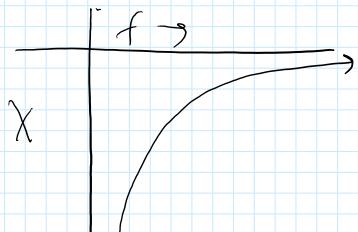
$$X = \frac{1}{j\omega C} \quad X_C = -\frac{j}{\omega C}$$



Resistor

$$V = I R$$

$$V_{\theta_v} = I_{\theta_v} R$$

$$\theta_v = \theta_i \quad \text{for resistors}$$

Capacitor

$$V = I (-jX_C)$$

$$V_{\theta_v} = I_{\theta_v} (X_C - 90^\circ)$$

$$\theta_v = \theta_i - 90^\circ$$


Inductor

$$V = I j X_L$$


$$V_{\theta_v} = I_{\theta_v} (X_L + 90^\circ)$$

$$\theta_v = \theta_i + 90^\circ$$
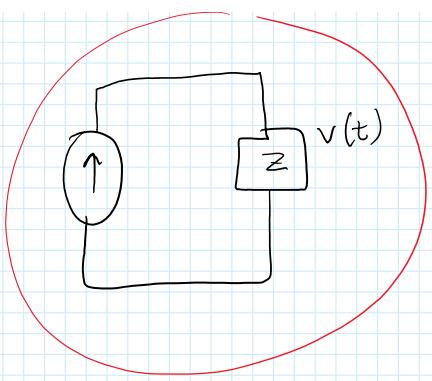
$$T = \frac{V}{j\omega C} = \frac{jV}{X_C} \quad \theta_i = \theta_v + 90^\circ$$


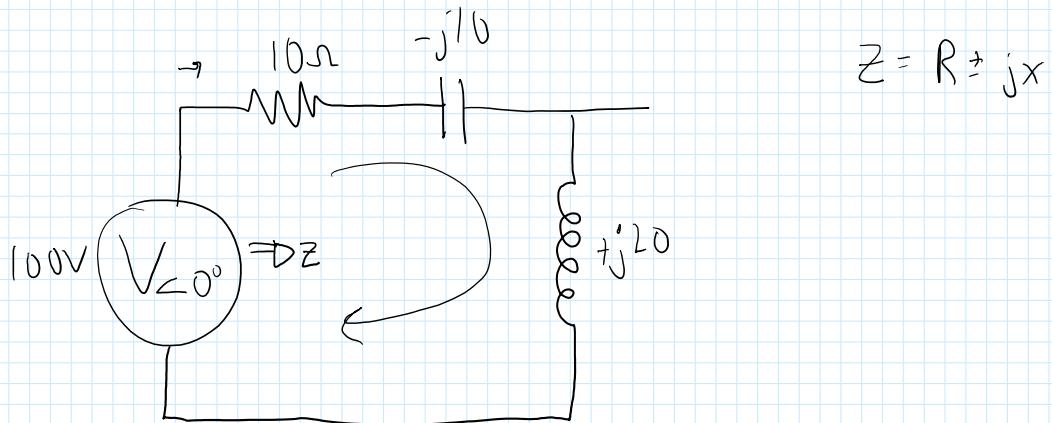
$$I = \frac{V}{-jX_L + j} = \frac{jV}{X_C} \quad V_i = 0 \text{ V}$$



$$Z = R \pm jX$$

$$Z = 10 - j10 - j20 = 10 + j10$$

$$i = \frac{100V}{10 + j10} \quad V_{out} = \frac{j20(100V)}{10 + j10}$$

- Reactance of Elements is frequency dependent

- Impedance: Resistor Inductor Capacitor

$$R$$

$$j\omega L$$

$$\frac{-j}{\omega C}$$

Element	Impedance	Reactance	Conductance Susceptance	Admittance
Resistor	$R + j0$	$j0$	$\frac{1}{R} = G$	$\frac{1}{R} + j0$
Inductor	$0 + j\omega L$	$j\omega L$	$\frac{1}{j\omega L} = -\frac{j}{\omega L}$	$0 - \frac{j}{\omega L}$
Capacitor	$0 - \frac{j}{\omega C}$	$-\frac{j}{\omega C}$	$-\frac{1}{j\omega C} = j\omega C$	$0 + j\omega C$

Sinusoidal Steady State Analysis


- 1) Identify the frequency
- 2) Convert from the time domain to the frequency domain
- 3) Solve the linear system:

$$\underline{V} = \underline{I} \underline{Z}$$

$$\underline{I} = \frac{\underline{V}}{\underline{Z}} = \underline{Y} \cdot \underline{V} \rightarrow (\text{admittance})$$

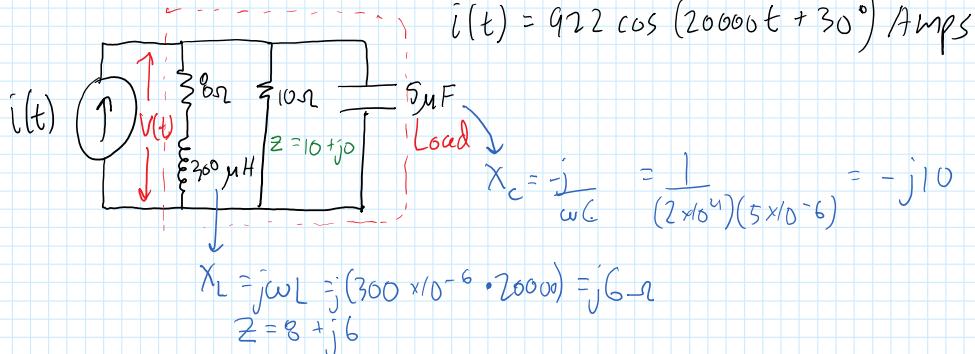- 4) When requested, convert back to the time domain

$$V_L \Rightarrow V_m \cos(\omega t + \theta)$$



$$Z = \underline{Z}$$

$$V(t) = V_m \cos(\omega t + \theta) \quad \text{frequency } \omega = 2\pi f$$

$$I(t) = I_m \cos(\omega t + \theta) \quad \text{Angle } \theta$$


magnitude phase

$$f = 1000 \text{ Hz}$$

$$\omega = 2\pi f = 6280 \text{ rad/sec}$$

$$\text{Phasor } V = V_m \angle \theta$$

$$I = I_m \angle \theta$$

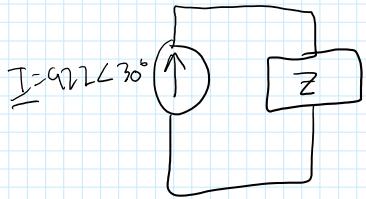

$$Z = \frac{1}{\frac{1}{8+j6} + \frac{1}{j6} + \frac{1}{j10}}$$

$$Y = (0.08 - j0.06) + 0.1 + 0.1j = 0.18 + 0.04j$$

$$Z = \frac{1}{Y} = \frac{1}{0.18 + 0.04j} = 5.294 - j1.176$$

$$Z = \frac{1}{0.184 \angle 12.52^\circ} \quad \boxed{Z = 5.423 \angle -12.52^\circ}$$


$$V = (922 \angle 30^\circ) \cdot (5.423 \angle -12.52^\circ)$$

$$\boxed{V = 5000.24 \angle 17.47^\circ}$$

time domain \rightarrow equivalent

$$\boxed{V(t) = 5000.24 \cos(2000t + 17.47^\circ)}$$

$$\frac{1}{0.18 + j0.04}$$

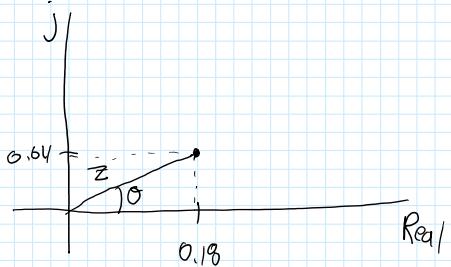


$$|Z| = \sqrt{0.18^2 + 0.04^2} = 0.184$$

$$\theta = \tan^{-1}\left(\frac{0.04}{0.18}\right) = 12.528^\circ$$

Examples for Impedance

Monday, October 24, 2016 9:01 AM

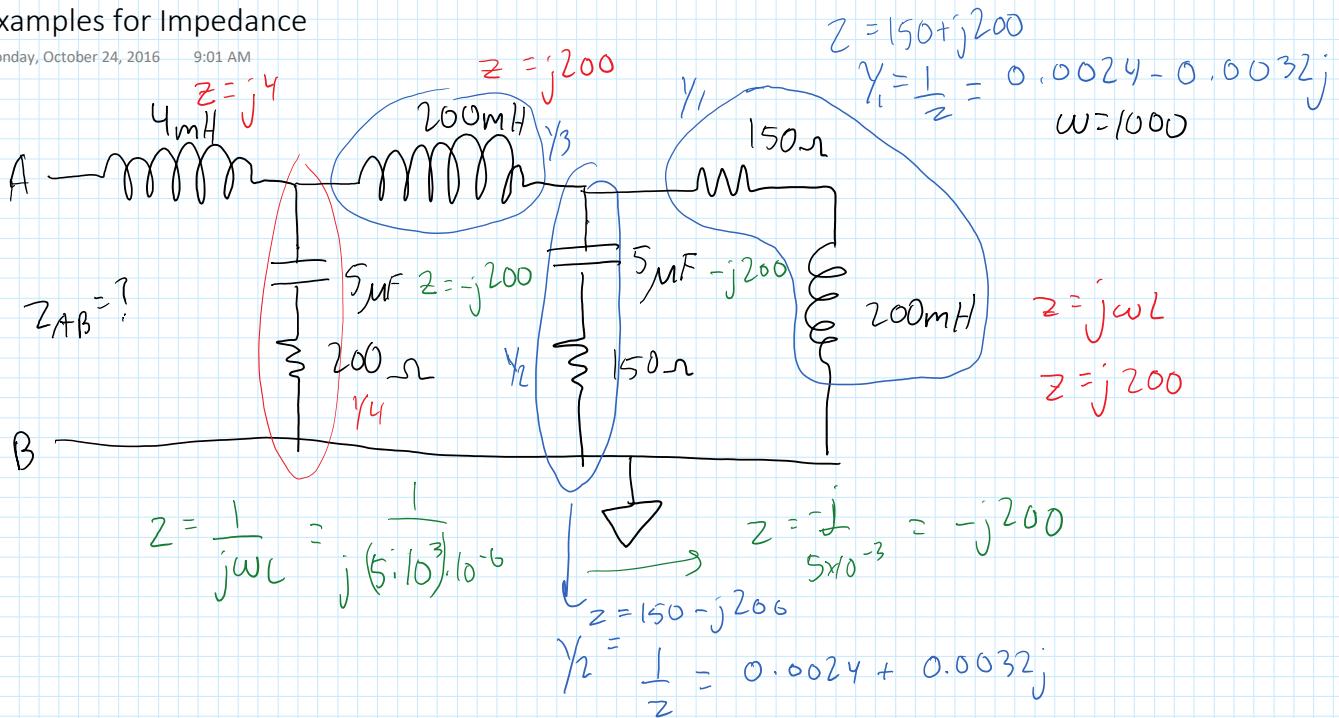

$$Y_T = Y_1 + Y_2 = 0.0048$$

$$Z_T = \frac{1}{Y_T} = 208.3 \Omega$$

$$Y_3 = Y_1 + Y_2 = (208.3 + j200)^{-1} = 6.002498 - 0.002398j$$


$$Y_4 = (200 - j200)^{-1} = 0.0025 + 0.0025j$$

$$Y_T = Y_3 + Y_4 = 0.004998 + 0.000102j \quad Z_T = 200 - 4.08163j$$


$$Z_{AB} = 200 - 4.08163j + j4$$


$$\boxed{Z_{AB} = 200 - 0.08163j} = 200 \angle -0.02j$$

$$Z_{AB} = 200 \angle -1.169$$

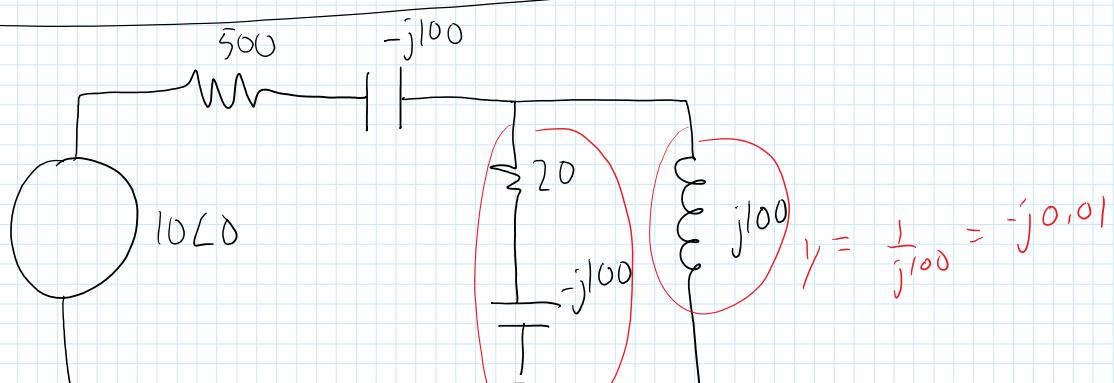

$$\downarrow 500 - j100$$

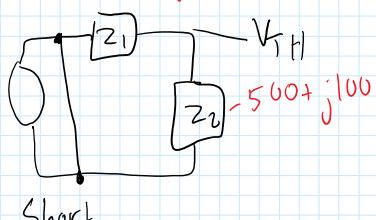

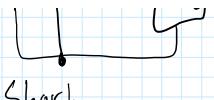

Short
out source
for Z_{th}

11 12

$$Z_2 = 500 + j100$$

$$V_{TH} = \frac{10(Z_2)}{Z_1 + Z_2} = \frac{10(500 + j100)}{500 - j100 + 500 + j100} = \frac{10(500 + j100)}{1000}$$


$$\boxed{V_{TH} = 5 + j1} = 5.099 \angle 11.31^\circ = \overline{V_{TH}}$$

$$Z_{th} = Z_1 \parallel Z_2 \quad Z_{th} = 500 - j100 \parallel 500 + j100$$

$$\boxed{Z_{th} = 260 \Omega}$$

More Transient Circuits

Wednesday, October 26, 2016 9:04 AM

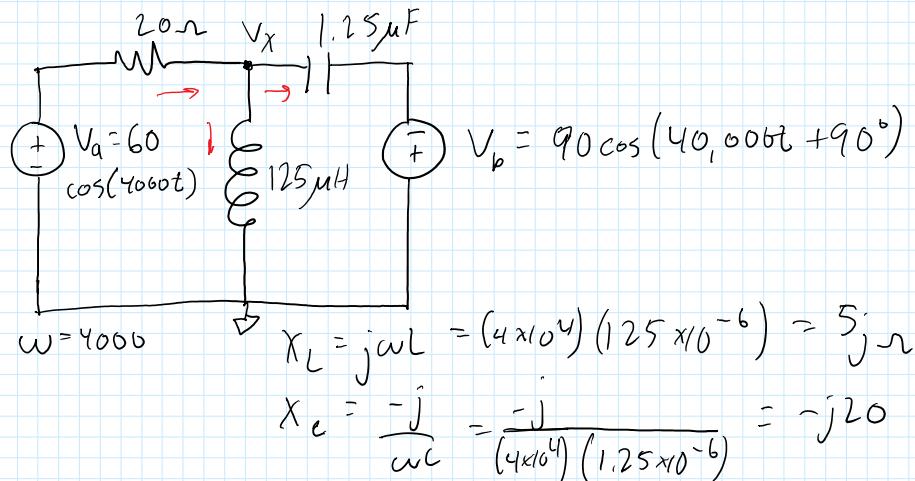

$$V_a = 60 \angle 0^\circ$$

$$V_b = 90 \angle 90^\circ$$

$$\frac{V_a - V_x}{20 \Omega} = \frac{V_x - V_b}{j20 \Omega} + \frac{V_x}{5 \Omega}$$

$$\frac{(60 \angle 0^\circ) - V_x}{20} = \frac{V_x - (90 \angle 90^\circ)}{-j20} + \frac{V_x}{j5}$$

$$3 - 0.05 V_x = 0.05j V_x + j4.5 \angle 90^\circ - j0.2 V_x$$

$$7.5 - 0.05 V_x = 0.05j V_x - j0.2 V_x$$


$$7.5 = 0.05 V_x - 0.15j V_x$$

$$V_x = \frac{7.5}{0.05 - j0.15}$$

$$V_x = 47 \angle 71.56^\circ$$

$4.5 \angle 90^\circ$

-4.5

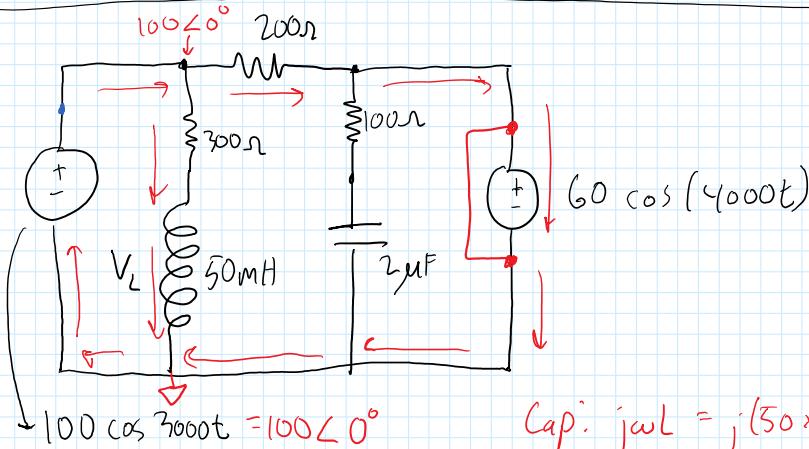

Superposition

$$\omega = 3000$$


$$V_L = \frac{(100 \angle 0^\circ)(j150)}{300 + j150}$$

} voltage divider

$$V'_L = 44 \angle 63.4^\circ$$

$$V'_L(t) = 44 \cos(3000t + 63.4^\circ)$$

short

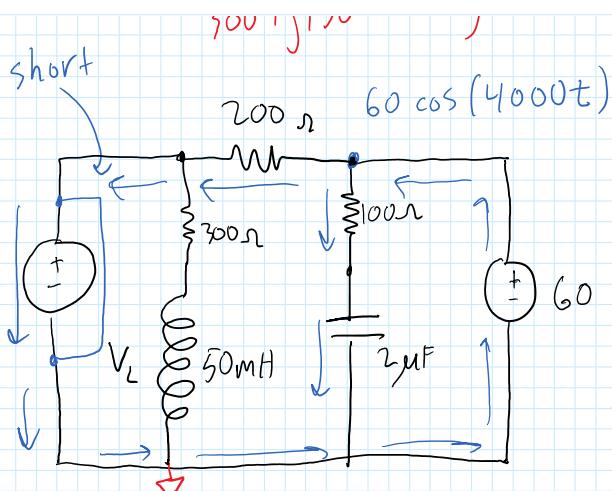

$$V_L(t) = 44 \cos(3000t + 63.4^\circ)$$


$$V_L'' = 0$$

$$V_L = V_L'' + V_L'$$

$$V_L(t) = 44 \cos(3000t + 63.4^\circ)$$

Exam 2 Review

Friday, October 28, 2016 9:00 AM

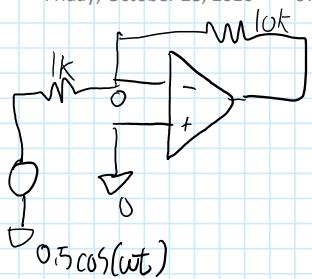


inverting (negative feedback)

1) OP AMPS


$$Gain = \left(-\frac{R_f}{R_i} \right)$$

$$Gain = -10$$
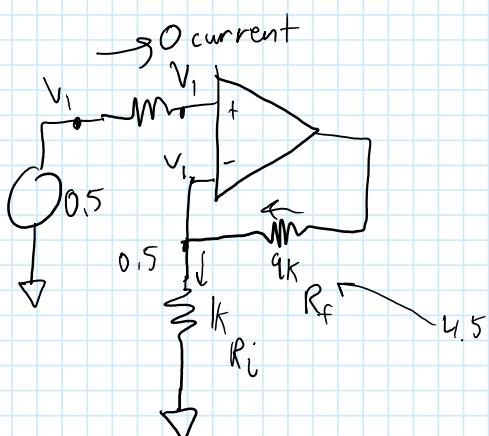
$$Output = 5 \cos(\omega t + 180^\circ) \text{ or } -5 \cos(\omega t)$$


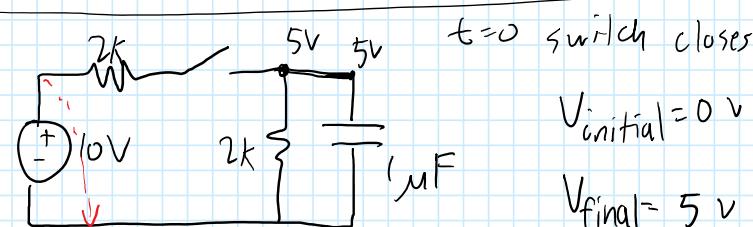
$$Gain = +\left(\frac{R_f}{R_i} + 1 \right)$$



$$2k \boxed{2k} = 1k$$

$$V_{initial} = 0 \text{ V}$$

$$\tau = R_C C$$

$$V_{final} = 5 \text{ V}$$

$$\tau = (1k)(10^{-6}) = 10^{-3}$$

$$V(t) = V_f + (V_i - V_f) e^{-t/\tau}$$

$$V(t) = 5 + (0 - 5) e^{-t/10^{-3}}$$

2) Transient Response

$$V(t) = 5 - 5 e^{-t/0.001}$$

$$\bar{V} = V_m \angle 0 \rightarrow \text{frequency domain}$$

$$\omega = 2\pi f = \frac{\text{rad}}{\text{sec}}$$


$$V(t) = V_m (\cos \omega t + j \sin \omega t) \rightarrow \text{time domain}$$

Impedance: $Z = R + jX$

$$X_C = \frac{-j}{\omega C} \quad X_L = j\omega L$$


Admittance: $Y = \frac{1}{Z}$

Ex:

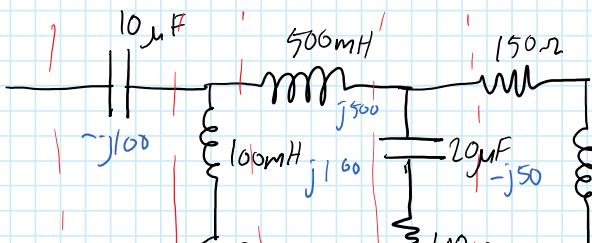

$$Y = \frac{1}{Z} = \frac{1}{1000} (200 \times 10^{-3})$$

$$Y = 1.2 \text{ S}$$

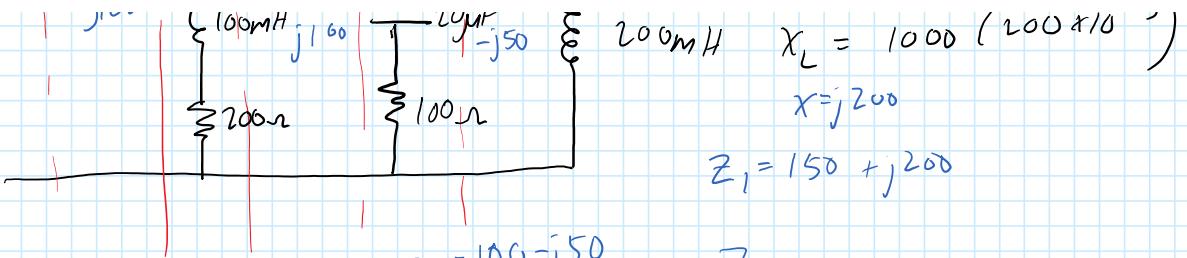


$$Z_4 = Z_3 + j500$$

$$Z_5 = ((Z_4)^{-1} + (200 + j100)^{-1})^{-1}$$

$$Z_{AB} = Z_5 - j100$$
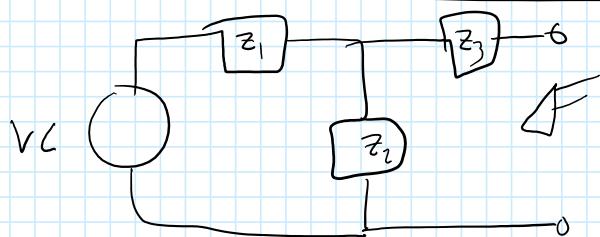
$$Z_3 = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2}}$$



$$V_{TH} = \frac{V_c(z_2)}{z_1 + z_2}$$








$$Z_{TH} = z_3 + (z_2 || z_1)$$

Power: 50/60 Hz + harmonics

Communications/Control

Frequency Spectrum

Steady State Analysis

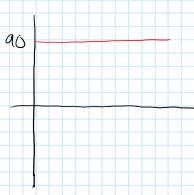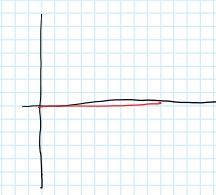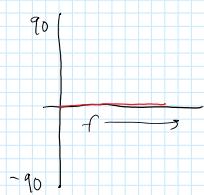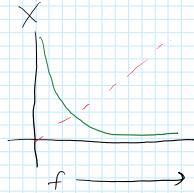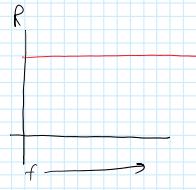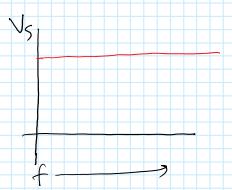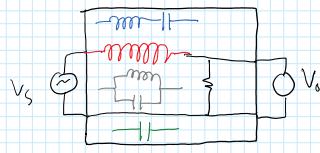

Transfer Functions

$$V_o = \frac{V_s(R)}{(R + jX_c)}$$

$$V_o = \frac{V_s(R)}{R + jX_c}$$

$$V_o = \frac{V_s(R)}{R + \left(\frac{1}{Y_c}\right) \rightarrow X_0}$$

at res, $\frac{1}{Y_{res}} \rightarrow 0$, so $X_{res} = \infty$

$$P = \frac{V^2}{R} = \left| \frac{V_s}{\sqrt{2}} \right|^2 \cdot \frac{1}{R}$$


$\frac{1}{2}$ power point $\rightarrow 0.707 |V_{max}|$
 $-(3dB)$ voltage point $\rightarrow 0.707 |V_{max}|$
 $-(6dB)$ power point $\rightarrow \frac{1}{2}$ power

Lowpass filter
High pass filter
Band pass filter
Band reject filter


$$Q = \frac{F}{\Delta F} = \frac{X}{R}$$

Reactive Power

Friday, November 4, 2016 9:04 AM

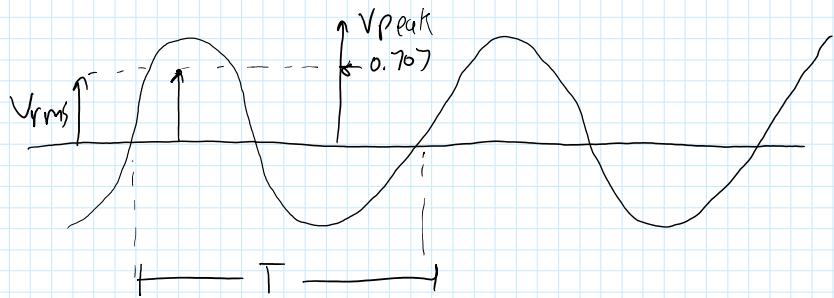

$$P = \frac{V^2}{R}$$




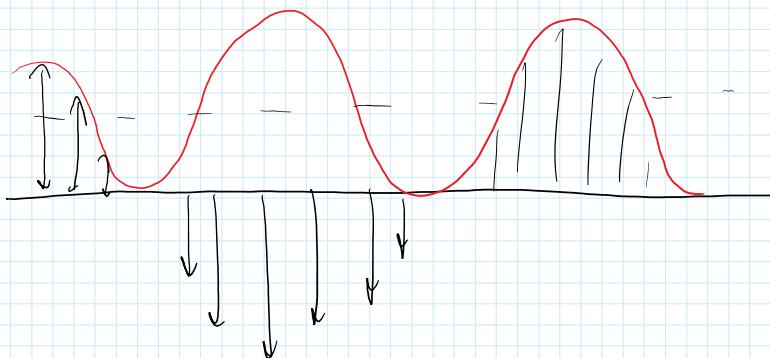


$$V_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V^2 \cos(\omega t + \theta) dt}$$

Appendix G:


$$\int \cos^2 \alpha x dx = \frac{x}{2} + \frac{\sin^2 \alpha x}{4\alpha}$$
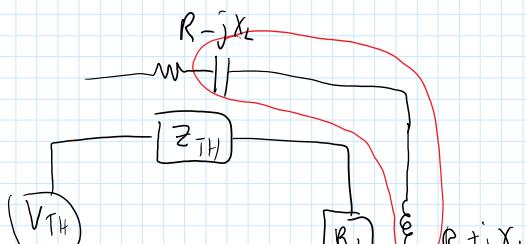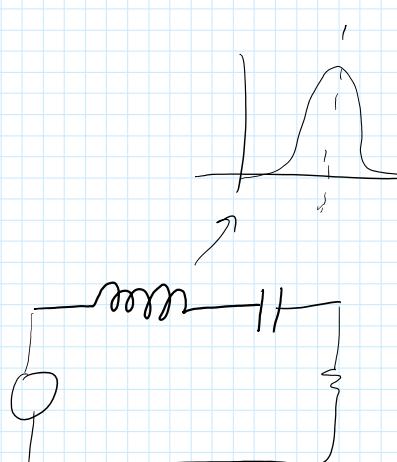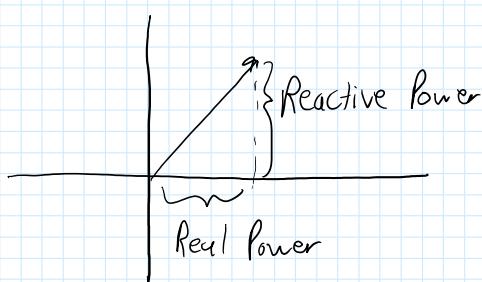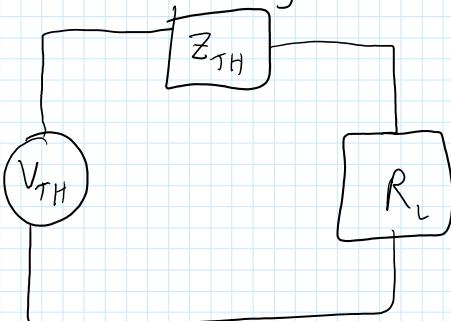
$$V_{rms} = \left[\frac{V_m^2}{T} \left(\frac{1}{2} \right) \right]^{1/2} = \frac{V_m}{\sqrt{2}} = \frac{V_m}{1.414} \approx 0.707 V_m$$



$$(R - j X_L)^* = (R + j X_L)$$



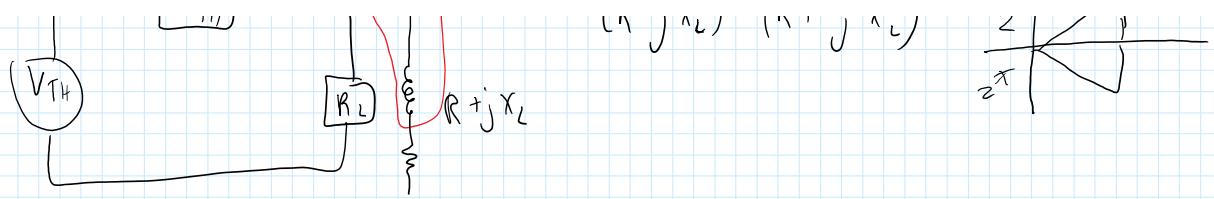

Sinusoidal Steady State Power

Monday, November 7, 2016 9:02 AM

$$P(t) = V_i$$

$$V(t) = V_{\max} \cos(\omega t + \theta_v)$$

$$i(t) = I_{\max} \cos(\omega t + \theta_i)$$

$$\vec{V} \angle (\theta_v - \theta_i) = V_m \cos(\omega t + \theta_v - \theta_i)$$

$$\vec{I} \angle 0 = I_m \cos(\omega t)$$

$$P(t) = V_m I_m \left[\cos(\omega t + \theta_v - \theta_i) \cdot \cos(\omega t) \right]$$

$$\cos \alpha \cos \beta = \frac{1}{2} \cos(\alpha - \beta) + \frac{1}{2} \cos(\alpha + \beta)$$

$$P(t) = V_m I_m \left[\frac{1}{2} \cos(\omega t + \theta_v - \theta_i - \omega t) + \frac{1}{2} \cos(\omega t + \theta_v - \theta_i + \omega t) \right]$$

$$= V_m I_m \left[\frac{1}{2} \cos(\theta_v - \theta_i) + \frac{1}{2} \underbrace{\cos(2\omega t + \theta_v - \theta_i)} \right]$$

$$\cos \alpha + \cos \beta = \cos \alpha \cos \beta - \sin \alpha \sin \beta$$


$$\alpha = 2\omega t \quad \beta = \theta_v - \theta_i$$

$$= \cos(\theta_v - \theta_i) \cos(2\omega t) - \sin(\theta_v - \theta_i) \sin(2\omega t)$$

$$P(t) = \frac{V_m I_m}{2} \left[\cos(\theta_v - \theta_i) \right] + \frac{V_m I_m}{2} \left[\cos(\theta_v - \theta_i) \cos(2\omega t) - \sin(\theta_v - \theta_i) \sin(2\omega t) \right]$$

For a resistor (R), $\theta_v - \theta_i = 0$

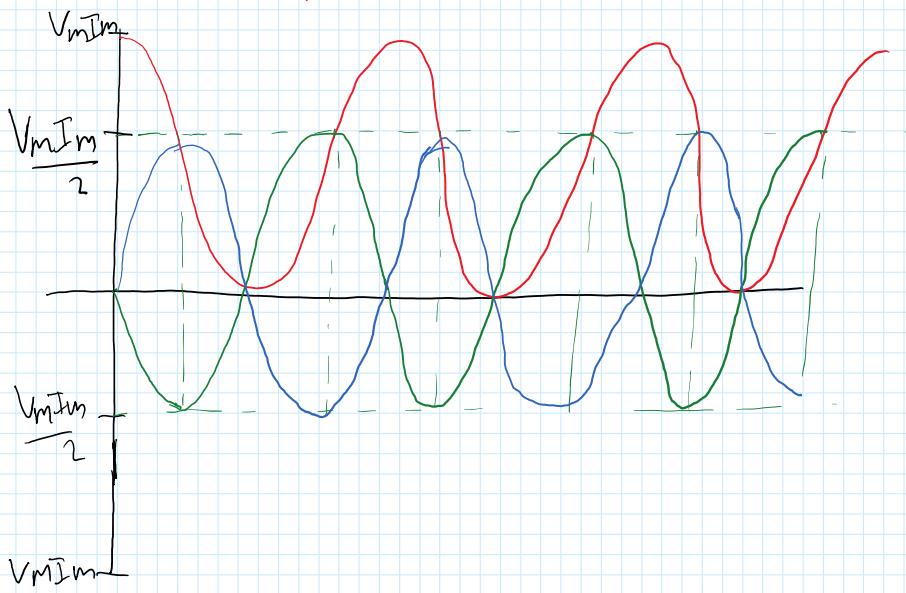$2\omega = 2 \cdot \text{line frequency}$ [rad/sec]



For an inductor, $\theta_v - \theta_i = 90^\circ$

For a capacitor, $\theta_v - \theta_i = -90^\circ$

$$S = P + jQ$$

$$S = \frac{V_m I_m}{2} \left[\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i) \right] = V_m I_m e^{j(\theta_v - \theta_i)} = \frac{1}{2} V_m I_m \angle (\theta_v - \theta_i)$$

$$S = \underline{V_m I_m} \angle \theta_v - \theta_i = V_{rms} I_{rms} \angle \theta_v - \theta_i$$

$$I_{rms}^2 e^{-j\theta_i} = I_{rms}^2 (\cos \theta_i + j \sin(-\theta_i)) = I_{rms}^2 (\cos \theta_i - j \sin \theta_i)$$

$$S = V_{rms} I_{rms}^*$$


Note Also: $V_{rms} = I_{rms} Z$ $A \cdot A^* = |A|^2$

$$S = (I_{rms})(I_{rms})^* Z = |I_{rms}|^2 Z - \frac{V_{rms}^2}{Z}$$


$$S = P + jQ ; \quad S = |I_{rms}|^2 Z = \frac{|V_{rms}|^2}{Z}$$

Power Factor

Wednesday, November 9, 2016 9:05 AM

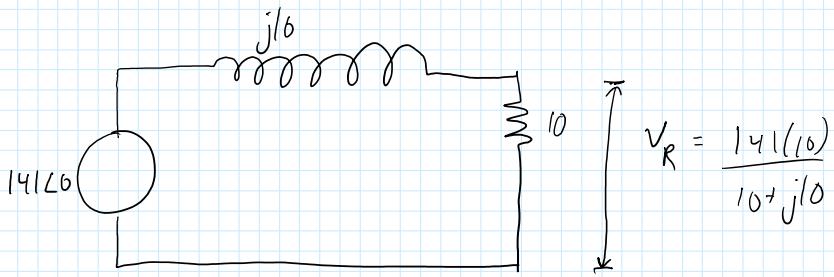

$$V_{RMS} = 0.707 V_m$$

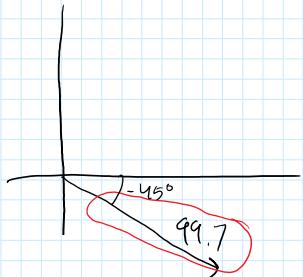

$$S = P + jQ$$

$$S = V_{rms} + I_{rms}^*$$

$$V_{rms} = I_{rms} Z$$


$$\boxed{I_{rms} Z \neq I_{rms}^*}$$

$$\boxed{|I_{rms}|^2}$$

$$S = P + jQ$$


$$S = |I_{rms}|^2 R + |I_{rms}|^2 X$$

$$S = \left| \frac{V_{rms}}{R} \right|^2 + \left| \frac{V_{rms}}{X} \right|^2$$

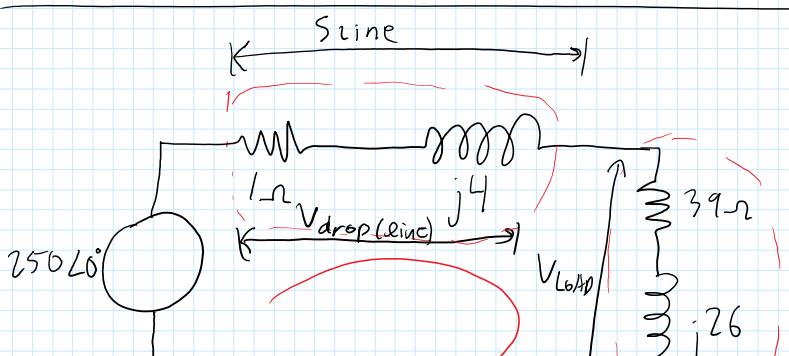

$$I = \frac{250 \angle 0^\circ}{40 + j30} = 4 - j3 \quad \underline{\underline{OR}}$$

current

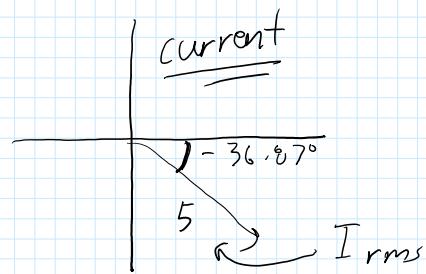


$$V_{\text{Load}} = (39 + j26)(4 - j3) = 234 - j13 \quad \text{watts} \quad \text{VAR} = \text{Volt Amperes Reactive}$$

$$S_{\text{Load}} = V_L I^+ = (234 - j13)(4 + j3) = 975 + j650$$


$\vdash V_{\text{line}} \longrightarrow$

$$S_{\text{Line}} = I_{\text{line}} Z_{\text{line}} I_{\text{line}}^* = (4 - j3)(1 + j4)(4 + j3) = 25 \text{ watts} + j160 \text{ VAR}$$
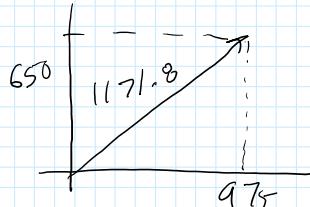
$$S_{\text{Total}} \longrightarrow 1000 + j750$$


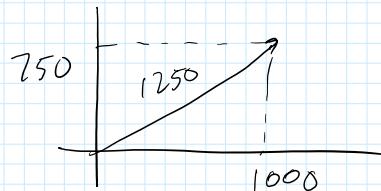
$$S = 1250 \angle 36.87^\circ = 1000 + j750$$



OR


$$S_{\text{Line}} = I_{\text{rms}}^2 R + I_{\text{rms}}^2 X = (5)^2 1 + (5)^2 (j4) = 25 + j100 \checkmark$$

$$S_{\text{Load}} = I_{\text{rms}}^2 R + I_{\text{rms}}^2 X = (5)^2 39 + (5)^2 j26 = 975 + j650 \checkmark$$

$1000 + j750 \checkmark$


Leading Implies Current Leads Voltage (Inductive)

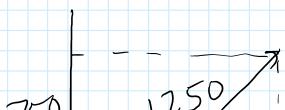Lagging Implies Current Lags Voltage (Capacitive)



P.F. (Power Factor)
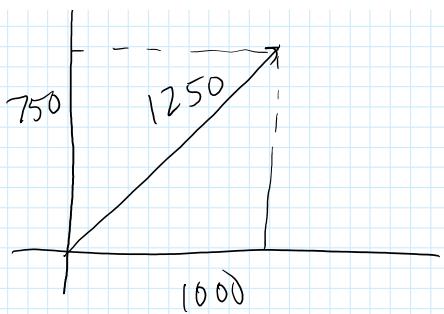
$$\frac{1000 \text{ watts}}{1171.8 \text{ watts}} = 0.8$$




P.F. (Power Factor)

Leading

$$\frac{1000 \text{ watts}}{1250 \text{ watts}} = 0.8$$

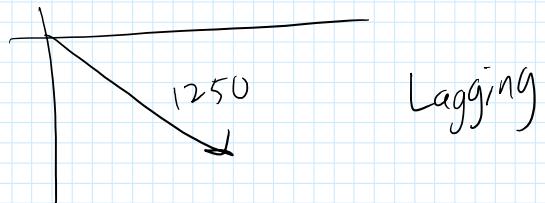
$$36.87^\circ = \cos^{-1}\left(\frac{1000}{1250}\right)$$




Lagging

Mutual Inductance

Monday, November 14, 2016 9:06 AM

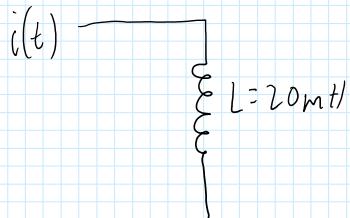

$$V(t) = L \frac{di(t)}{dt}$$

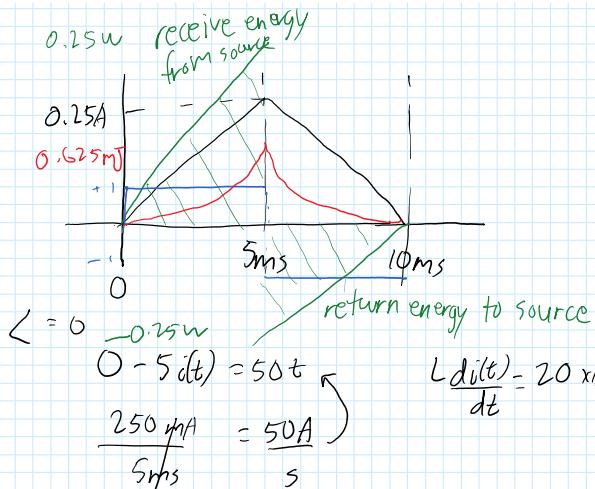

$$\text{Energy} = \text{Power} \cdot \text{Time} = \frac{1}{2} L I^2$$



$$\begin{aligned} & \angle = 0 \\ & 0.25 \text{ W} \\ & (0 - 5 \frac{dt}{dt}) = 50t \\ & \frac{250 \mu\text{A}}{5 \text{ ms}} = 50 \text{ A} \end{aligned}$$

$$L \frac{di(t)}{dt} = 20 \times 10^{-3} \times 50 = +1 \text{ volt}$$

$$> 10 \text{ ms} = 0$$

$$5 - 10 i(t) = 0.25 - 50t \quad L \frac{di(t)}{dt} = 20 \times 10^{-3} \times (-50) = -1 \text{ volt}$$

$$\text{Power} = V(t) I(t)$$

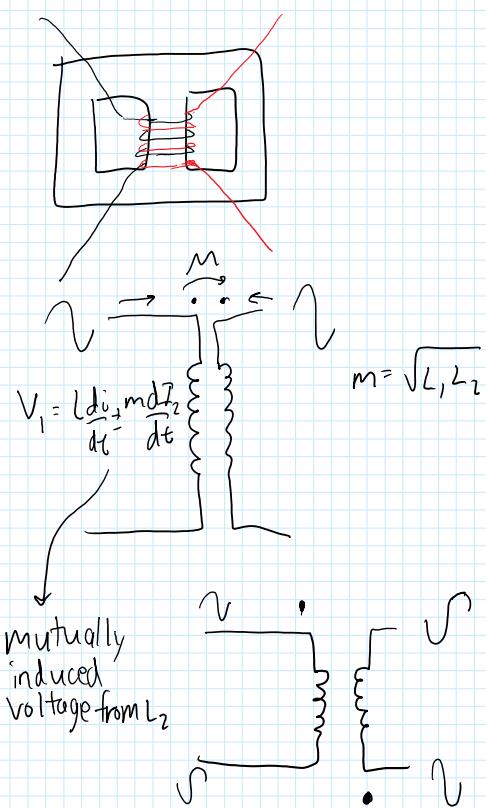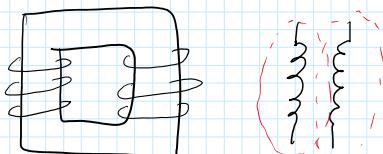

$$V_1 = L \frac{dI_1(t)}{dt} + m \frac{dI_2(t)}{dt}$$



Mesh 1

$$-V_s + 3i_1 + 2 \times 10^{-3} \frac{dI_1(t)}{dt} - 3 \times 10^{-3} \frac{dI_2}{dt} = 0$$

$$V_2 = L \frac{dI_2(t)}{dt} + m \frac{dI_1(t)}{dt}$$

Mesh 2

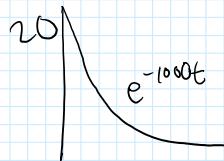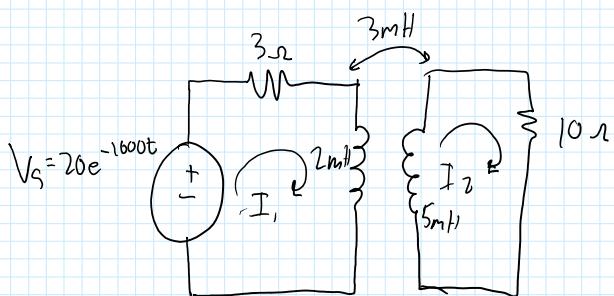
$$10i_2 + 5 \times 10^{-3} \frac{dI_2}{dt} - 3 \times 10^{-3} \frac{dI_1}{dt} = 0$$



HW 8 Examples

Wednesday, November 16, 2016

9:05 AM

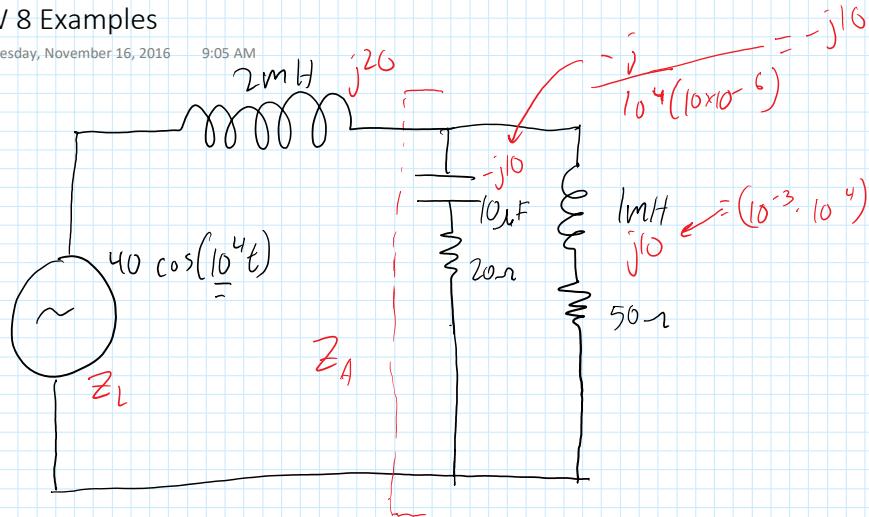

$$Z_L = Z_mH + Z_a$$

$$Z_L = 15.7 + j15.7$$

$$S = \frac{V^2}{Z_L} = \frac{40^2}{15.7 + j15.7}$$

$$S = \underline{50.9} - j\underline{50.9}$$


$$S = 72 \angle -45^\circ$$

$$Z_a = \left((50 + j10)^{-1} + (20 - j10)^{-1} \right)^{-1}$$

$$= 15.7 - j4.28$$


a) Real and Reactive Power

b) Apparent power $\rightarrow 72$

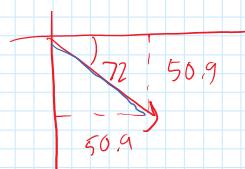

c) Power Factor

$$\cos(45) = 0.707 = 70.7\%$$

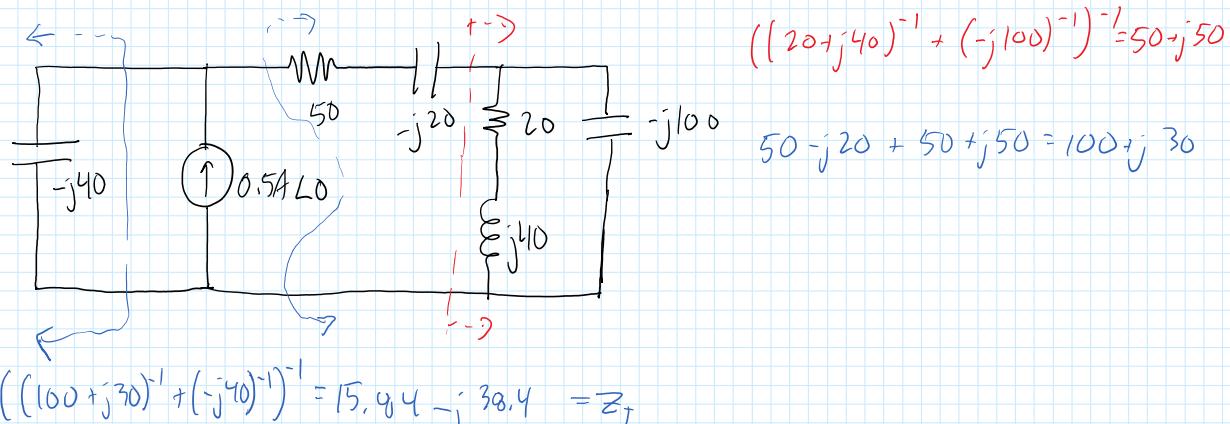

$$((20 + j40)^{-1} + (-j100)^{-1})^{-1} = 50 - j50$$

$$50 - j20 + 50 + j50 = 100 + j30$$

$$((100 + j30)^{-1} + (-j40)^{-1})^{-1} = 15.84 - j38.4 = Z_T$$

$$S = (0.5)^2 (Z_T) \quad S = (0.5)^2 (15.84 - j38.4) = 3.96 - j9.6$$




$$= 10.38 \angle -67.59^\circ$$

$$VA = 10.388 = \sqrt{3.96^2 + 9.6^2}$$

$$\text{WATTS} = 596$$

$$\text{VAR} = 96$$
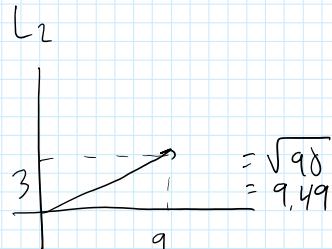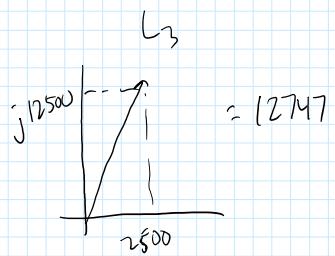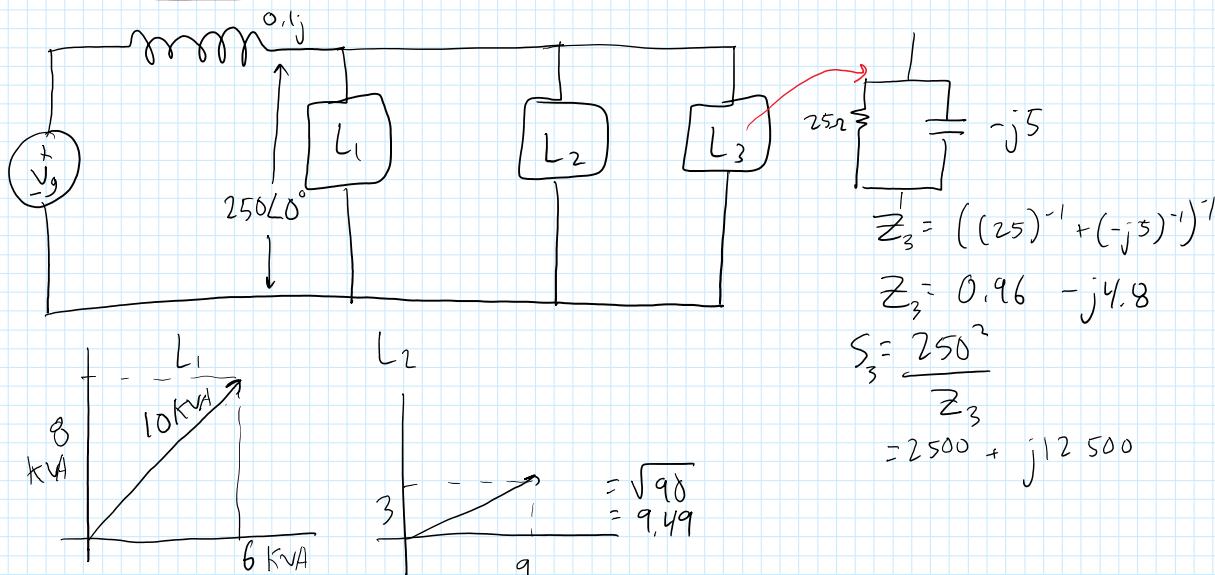
$$\text{PF} = \cos(67.5^\circ) = 0.38 = 38\%$$




$$V_g = 250 + j0.1 (I_T) \quad I = \frac{S}{V}$$

$$I = \frac{9490}{250} + \frac{10000}{250} + \frac{12747}{250}$$

$$I = 128.95$$


$$V_g = 250 + j0.1 (129A)$$

$$V_g = 250 + 12.9j$$

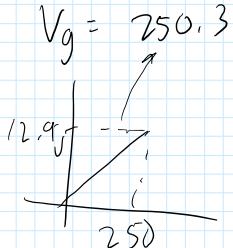

Transformers

Friday, November 18, 2016 9:06 AM

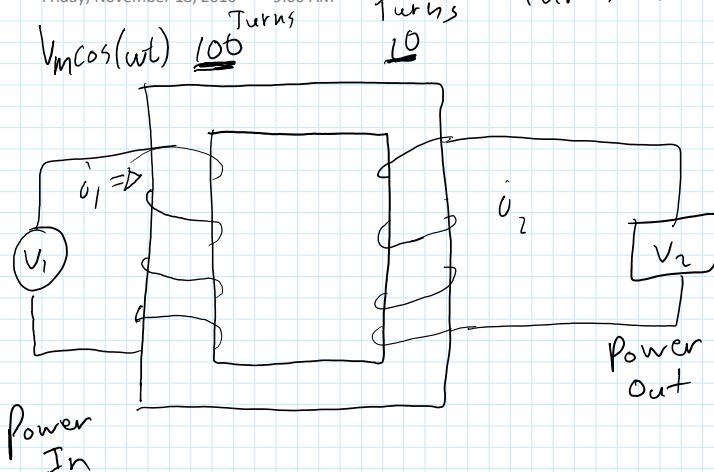

N_1 turns

N_2 Turns

Primary

Secondary

(Source Side)

(Load Side)

$$V_1 = N_1 \frac{d\Phi}{dt}$$

$$V_2 = N_2 \frac{d\Phi}{dt}$$

$$\frac{V_1}{N_1} = \frac{d\Phi}{dt}$$

$$\frac{V_2}{N_2} = \frac{d\Phi}{dt}$$

$$V = N \frac{d\Phi}{dt}$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$V_2 = V_1 \left(\frac{N_2}{N_1} \right)^{10}$$

$$V_2 = 0.1 V_1$$

Turns Ratio


100 : 10

$$P_{in} = P_{out}$$

$$V_1 I_1 = V_2 I_2$$

100W
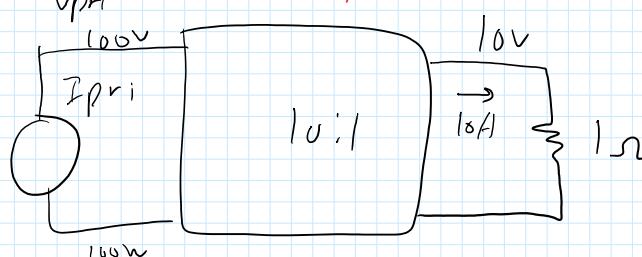
$$100V \cdot 1A \quad 10V \cdot 10A \quad V \downarrow, I \uparrow$$



$$V = 10V$$

$$I = 10A$$

$$P = 100W$$

100W

$$V = 100V$$

$$I = 1A$$

$$P = 100W$$

$$\xrightarrow{\text{Voltage Ratio}} \text{Voltage Ratio} = \text{Turns Ratio}$$

$$\text{Current Ratio} = \frac{1}{\text{Turns Ratio}}$$

$$S = S$$

$$Z_{pri} = \frac{V_{pri}}{I_{pri}}$$


$$Z_2 = 1 \cdot \underline{z}_{sec}$$

$$Z_{\text{pri}} = \frac{V_{\text{pri}}}{I_{\text{pri}}} \quad Z_2 = 1 \Omega$$

$$\frac{V_{\text{pri}}}{I_{\text{pri}}} = \frac{V_s \times 10}{I_s \times 0.1} = \frac{N \frac{V_{\text{sec}}}{I_{\text{sec}}}}{\frac{1}{N} \frac{I_{\text{sec}}}{I_{\text{pri}}}} = N^2 Z_{\text{sec}}$$

$$Z_{\text{pri}} = N^2 Z_{\text{sec}}$$

$$Z_{\text{pri}} = 100 \Omega$$

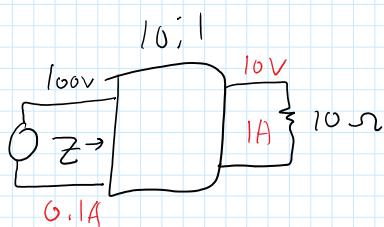

Given
Find


$$V_{\text{pri}} = TR \rightarrow V_{\text{sec}}$$

$$I_{\text{pri}} = \frac{I_{\text{sec}}}{TR}$$

$$Z_{\text{pri}} = |TR|^2 \times Z_{\text{sec}}$$

$$Z = (10)^2 \cdot 10 \Omega = 1000 \Omega$$

$$Z = \frac{100V}{0.1A} = 1000 \Omega$$

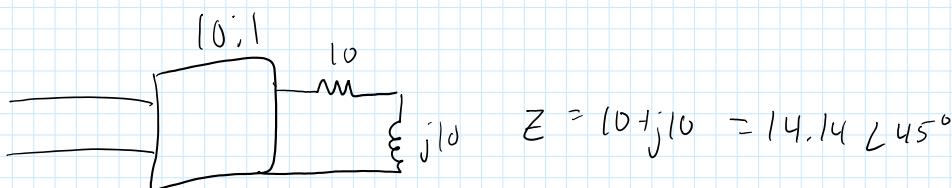


$$100(10 + j10) = 100 \times 14.14 \angle 45^\circ = 1000 + j1000 \text{ or } 1414 \angle 45^\circ$$

Transformer Problems

Monday, November 28, 2016 9:05 AM

want $Z = 200\Omega$

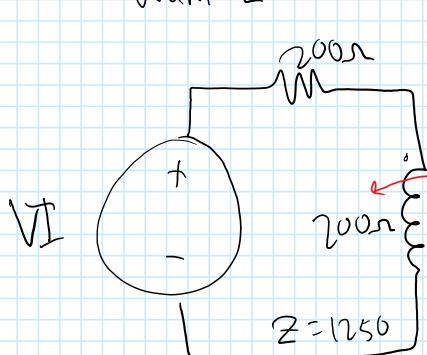

675:1




1:2500

1:2.5

1:1

turn
ratio

$$Z = (1:2.5)^2 \\ = 1.625$$

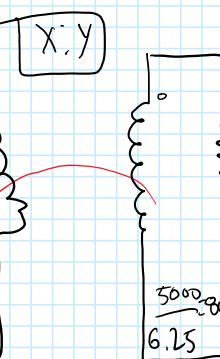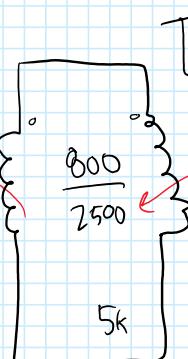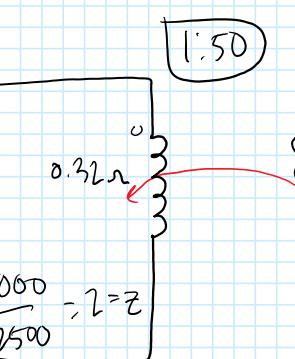


$6k\Omega$

$$\frac{\sqrt{1250}}{200} = \sqrt{6.25} = 2.5$$

$$Z_{pri} = Z_{sec} * (N_{ps})^2$$

$$Z_{sec} = \frac{Z_{pri}}{(N_{ps})^2}$$

$$I = 0.05A \leftarrow I = 1A / 20$$

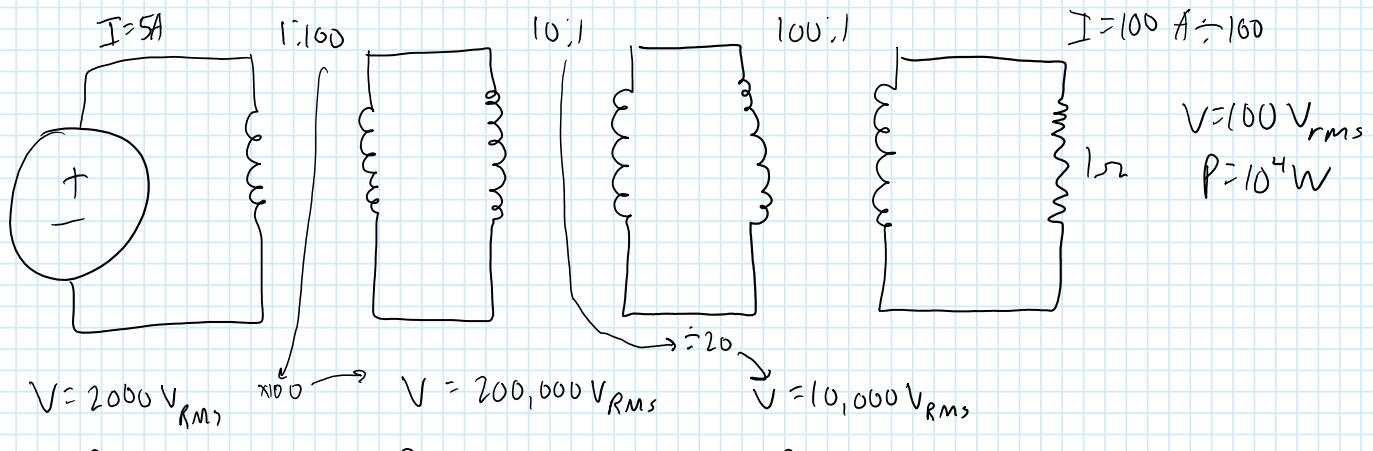

$$R = 400\Omega$$

$$R = 4M\Omega$$


$$R = 10^4\Omega$$


$$P = 10^4 W$$

$$P = 10^4 W$$

$$P = 10^4 W$$

$$(20)^2 * 10^4 = 4 * 10^6 = 4M\Omega$$

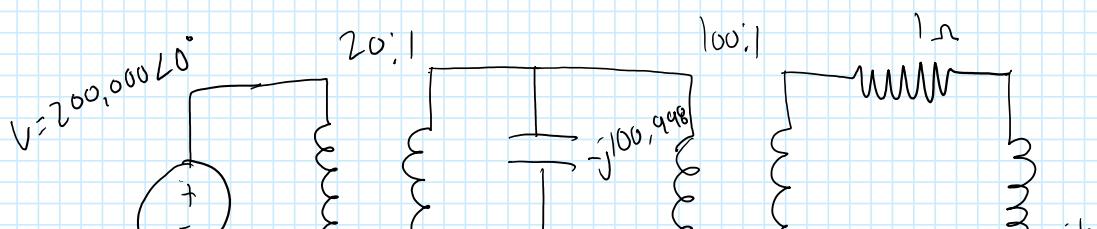

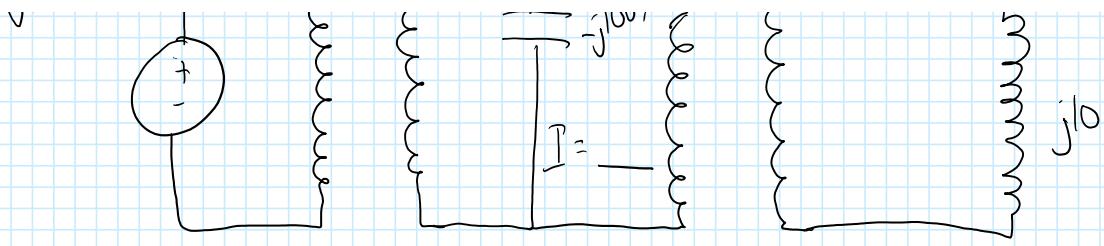

$$Z = \underline{\hspace{2cm}}$$

$$V = \underline{200,000}$$

$$I = \underline{\hspace{2cm}}$$

$$Z = \frac{1.01 \times 10^6}{\underline{10,000}}$$

$$V = \underline{10,000}$$

$$I = \underline{0.0095}$$

$$Z = \frac{10^4 + j10^5}{\underline{10,000}}$$

$$V = \underline{10,000}$$

$$I = \underline{0.0649 - j0.09}$$

$$Z = \frac{1 + j10}{\underline{100}}$$


$$V = \underline{100}$$

$$I = \underline{0.99 - j9.9}$$


$$I = \frac{V}{Z}$$

$$S = P \underline{\hspace{2cm}} + jQ \underline{\hspace{2cm}}$$
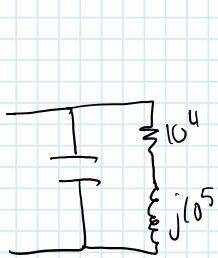
$$S = P \underline{9.84} + jQ \underline{98.4}$$



$$(10^4 + j10^5)^{-1}$$

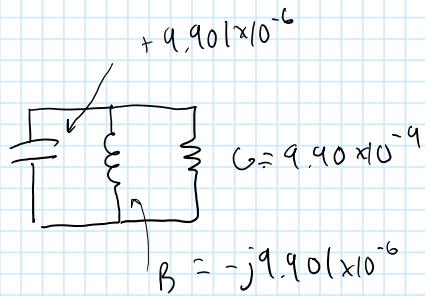

$$+ 9.901 \times 10^{-6}$$

$$G = 9.90 \times 10^{-9}$$


$$\beta = -j9.901 \times 10^{-6}$$

$$X_C = -j(9.901 \times 10^{-6})^{-1}$$


$$= -j100,998$$

3-Phase Delta and Wye

Wednesday, November 30, 2016 9:05 AM

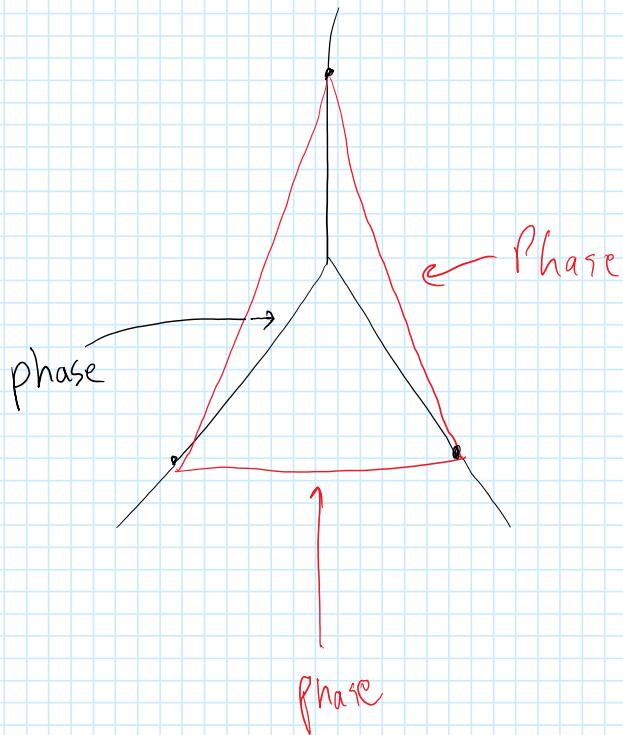

For Delta Config

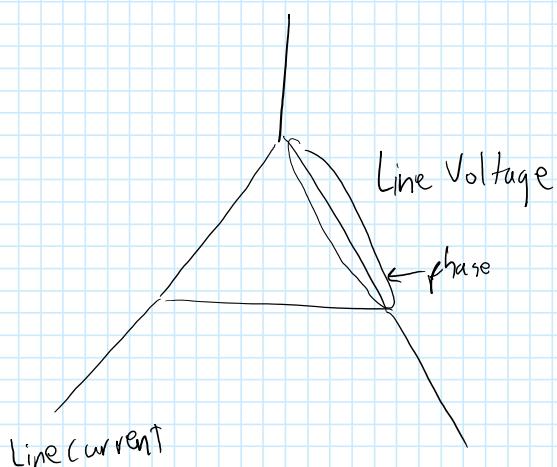


For Wye Config

The phase current = line current of the phase
voltage is vectorially related to the line-to-line voltage

Line-to-Line

Friday, December 2, 2016 9:03 AM

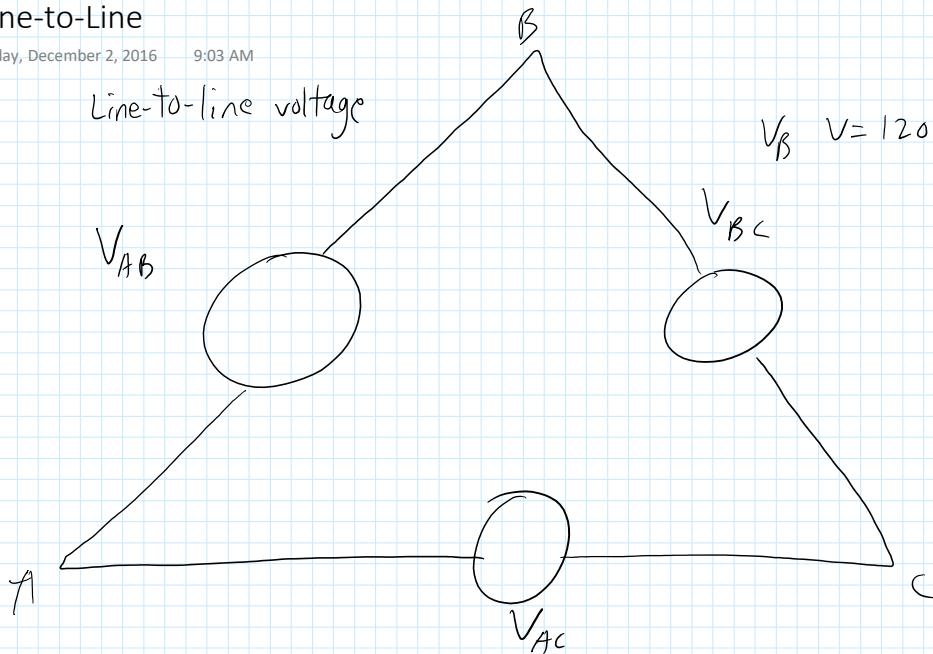

Line voltage = phase voltage

Line current = $\sqrt{3} \times$ phase current

phase current = $\frac{\text{Line current}}{\sqrt{3}}$

$$\begin{aligned}
 I_{\text{line } A} &= I_{AB} - I_{AC} = I_{\text{rms}} \angle -120^\circ = I_{\text{rms}} (e^{-j0^\circ} - e^{-j120^\circ}) \\
 &= I_{\text{rms}} (1 - \cos(-120) - j \sin(-120)) \\
 &= I_{\text{rms}} \left(1 - \left(-\frac{1}{2} - j \frac{\sqrt{3}}{2} \right) \right) = I_{\text{rms}} \left(\frac{3}{2} + j \frac{\sqrt{3}}{2} \right) \\
 &= (\sqrt{3})(I_{\text{rms}}) \left(\frac{\sqrt{3} + j}{2} \right) = \frac{\sqrt{3}}{2} + j \frac{1}{2}
 \end{aligned}$$

$$I_{\text{line } A} = \sqrt{3} \times I_{\text{rms}} \angle 30^\circ$$


$$I_{\text{line } B} = \sqrt{3} \times I_{\text{rms}} \angle 150^\circ$$

$$I_{\text{line } C} = \sqrt{3} \times I_{\text{rms}} \angle -90^\circ$$

Practice Final Exam Problems

Monday, December 5, 2016 9:03 AM

NODE VOLTAGE

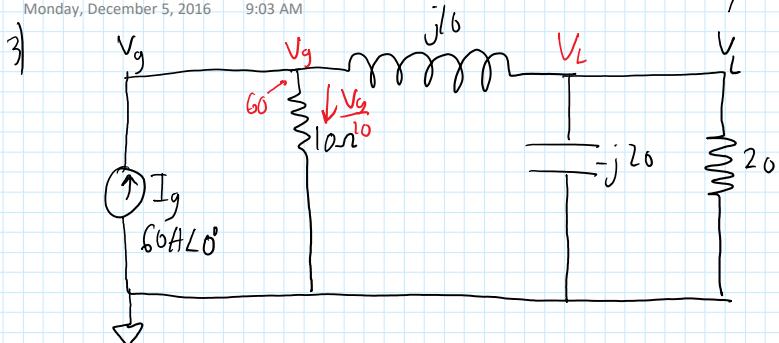

$$V_g =$$

$$V_L =$$

$$\text{Node } V_g: \frac{60 - V_g}{10} - \frac{V_g - V_L}{j10} = 0 \quad j100 [] = 6000j - j10(V_g) - 10V_g + 10V_L = 0$$

$$6000j - V_g(10 + j10) + 10V_L = 0$$

$$(1) \quad V_g(10 + j10) - 10V_L = 6000j$$

$$\text{Node } V_L: \frac{(V_g - V_L)}{j10} - \frac{V_L}{-j20} - \frac{V_L}{j20} \quad 200 [] \Rightarrow -20j(V_g - V_L) - 10jV_L - 10V_L = 0$$


$$-20j(V_g) + 20j(V_L) - 10j(V_L) - 10(V_L) = 0$$

$$(2) \quad -20j(V_g) + V_L(10j - 10) = 0$$

$$\text{Solve (1) and (2)} \Rightarrow V_g = 300 + j0 = 300 \angle 0^\circ$$

$$V_L = 300 - j300 = 424.3 \angle -45^\circ$$

MESH CURRENT

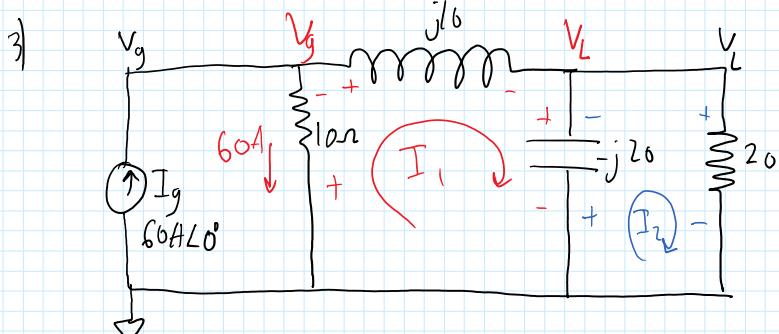

$$V_g =$$

$$V_L =$$

$$\text{Loop 1: } 10(I_1 - 60) + j10(I_1) - j20(I_1 - I_2) = 0$$

$$-600 + 10I_1 + j10(I_1) - j20(I_1) + j20(I_2) = 0$$

$$-600 + I_1(-j10 + 10) + I_2(j20) = 0$$

$$\textcircled{1} \quad I_1(10 - j10) + I_2(j20) = 600$$

$$\text{Loop 2: } -j20(I_2 - I_1) + 20(I_2) = 0$$

$$\textcircled{2} \quad I_1(j20) + I_2(20 - j20) = 0$$

Solve $\textcircled{1}$ and $\textcircled{2} \Rightarrow I_1 = 30 + j0$

$$I_2 = 15 - j15$$

$$V_g = 10(I_1 - 60) \quad V_g = 10(30 - 60) = -300$$

$$\begin{bmatrix} - \\ + \end{bmatrix} V_g = -300 \quad \text{Reality} \Rightarrow \begin{bmatrix} + \\ - \end{bmatrix} 300 = V_g$$



$$\boxed{V_g = 300V}$$

$$V_L = 20(15 - j15) = 300 - j300$$

$$\boxed{V_L = 300 - j300}$$



More Final Practice

Wednesday, December 7, 2016 9:08 AM

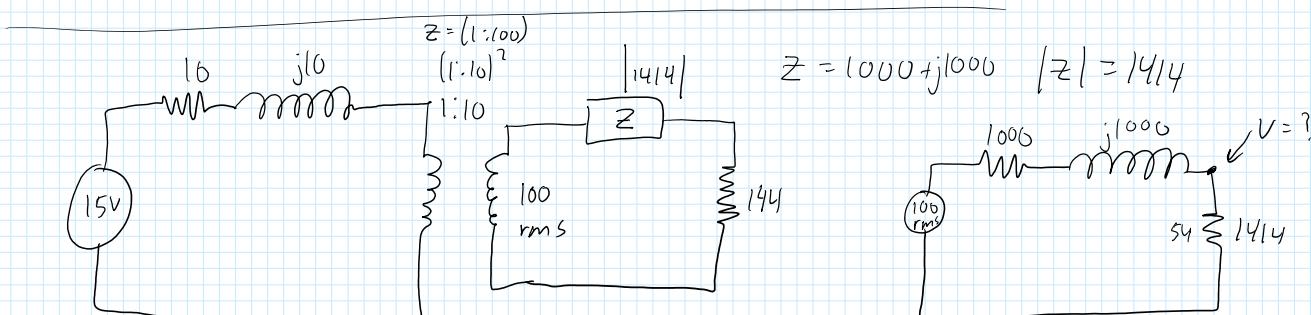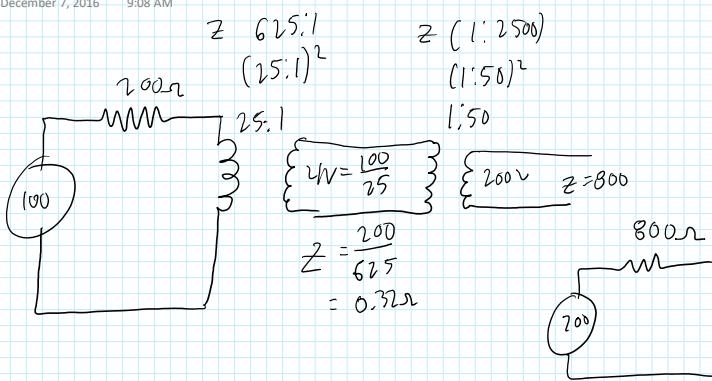


$$V = \frac{100(1414)}{2414+1000} = 44.9956 - 20.7j = \boxed{54.1 \angle -22^\circ}$$

Complex Conjugate

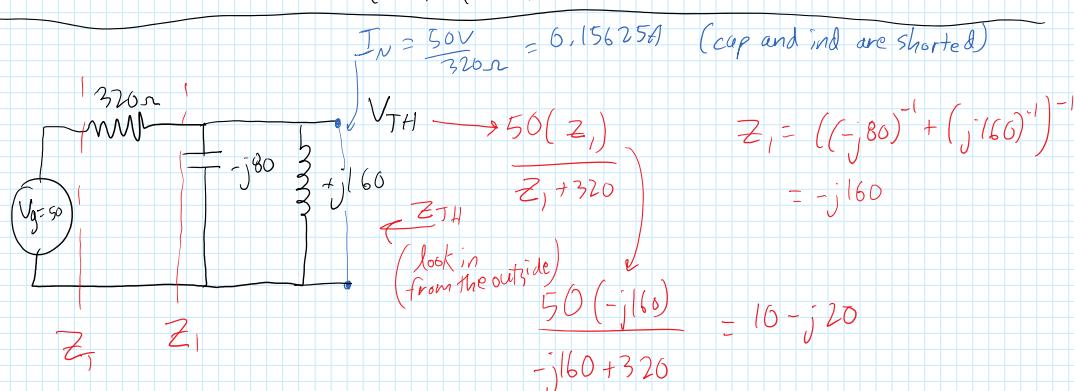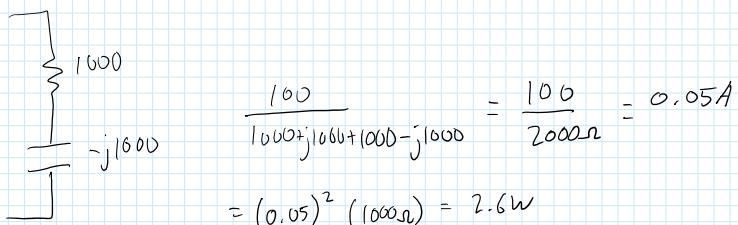



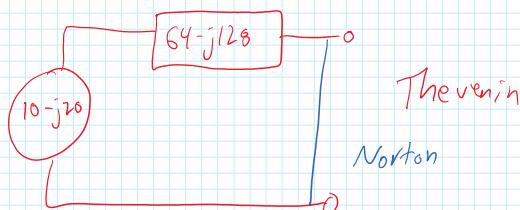
$$Z_{TH} = \left((320)^{-1} + (-80)^{-1} + (j80)^{-1} \right)^{-1} = 64 - j128$$






$$I_N = \frac{10 - j20}{64 - j128} \rightarrow I = \frac{V}{R}$$

$$I_N = 0.15625 A$$

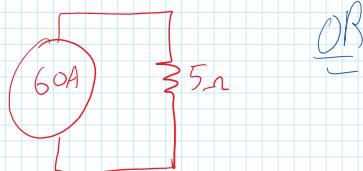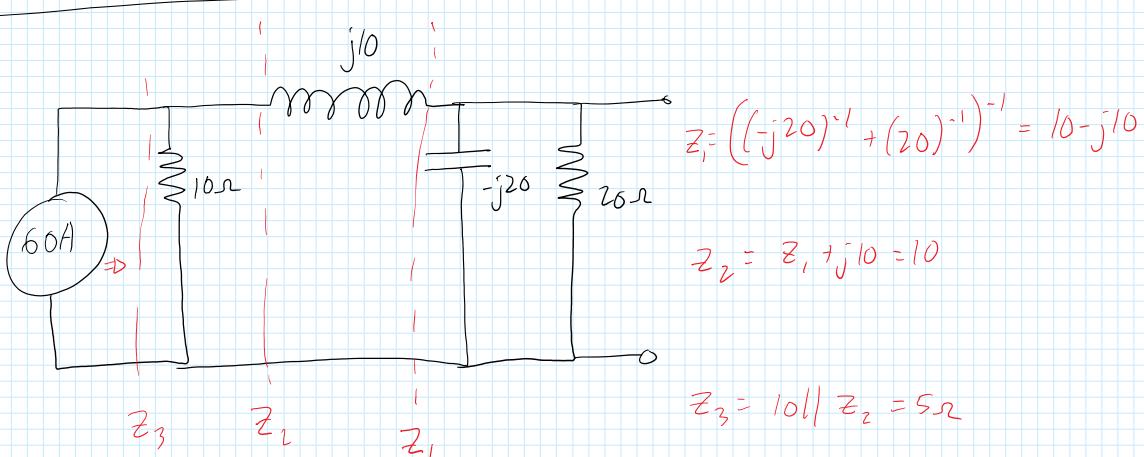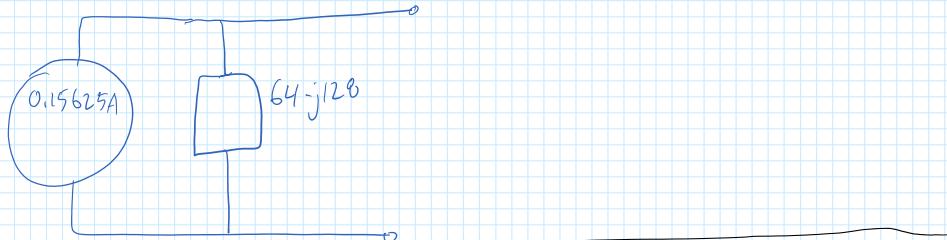

OR

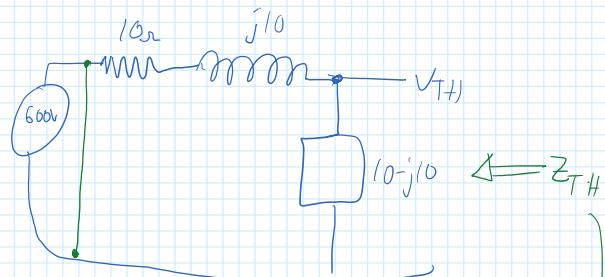


$$= \frac{600(10 - j10)}{10 - j10 + 10 + j10} = \frac{600(10 - j10)}{20 \Omega}$$


$$= 300 - j300$$

10Ω


= Thevenin

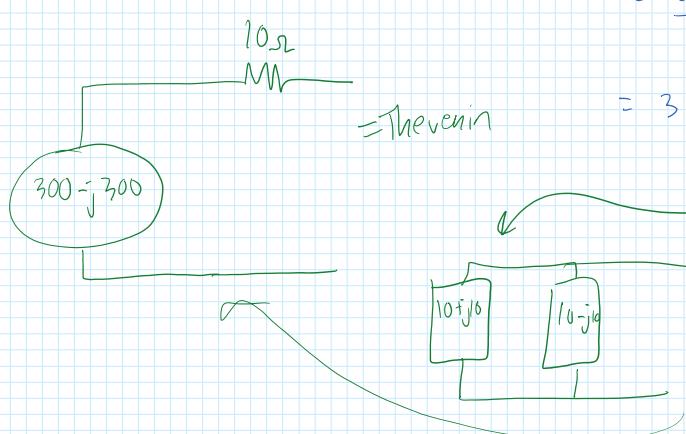

$$Z_{TH} = 10 \Omega$$

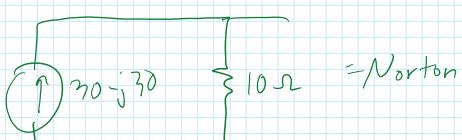

= Norton

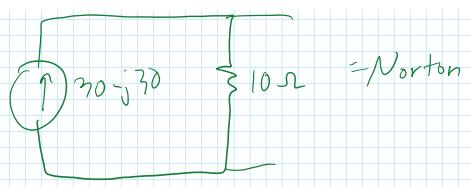

John Schad

E211

Dr. Galassi

HW #9

Review Problems

1) 120°

2) Delta, wye

3) $480V = V_{\text{Line}}$

$$V_{\text{phase}} = \frac{V_{\text{Line}}}{\sqrt{3}} \quad V_{\text{phase}} = \frac{480}{\sqrt{3}}$$

$$V_{\text{phase}} = 277.13V$$

4) $I_{\text{phase}} = 25A$ $I_{\text{line}} = I_{\text{phase}}$ $I_{\text{line}} = 25A$

5) $V_{\text{Line}} = 560V$ $V_{\text{phase}} = V_{\text{Line}}$ $V_{\text{phase}} = 560V$

6) $I_{\text{phase}} = 30A$ $I_{\text{line}} = I_{\text{phase}}(\sqrt{3})$ $I_{\text{line}} = 51.96A$

7) $V_{\text{phase}} = 240V$ $I_{\text{phase}} = 18A$ $VA = 3 \times V_{\text{phase}} \times I_{\text{phase}}$ $VA = 3(240)(18)$

$$VA = 12960 \text{ Watts}$$

8) $VA = \sqrt{3} \times I_{\text{line}} \times V_{\text{Line}}$ $V_{\text{phase}} = \frac{V_{\text{Line}}}{\sqrt{3}}$ $V_{\text{Line}} = V_{\text{phase}}(\sqrt{3})$ $V_{\text{Line}} = 240(\sqrt{3})$

$$I_{\text{line}} = \frac{VA}{\sqrt{3}(V_{\text{line}})}$$

$$I_{\text{line}} = \frac{12960}{(\sqrt{3})(415.69)} \quad I_{\text{line}} = 18A$$

$$V_{\text{Line}} = 415.69V$$

9) $V_L = 2400V$ $I_L = 40A$ $I_L = \frac{V_L}{Z}$ $Z = \frac{V_L}{I_L}$ $Z = \frac{2400}{40} \quad Z = 60\Omega$

10) $PF = 1$ $P = \sqrt{3} (PF) (V_L)(I_L)$ $P = \sqrt{3}(1)(2400)(40)$ $P = 166,276.88W$

Practice Problems

1) $V_p(A) = 138.56V$ $V_p(L) = 240V$
 $I_p(A) = 34.64A$ $I_p(L) = 20A$
 $V_L(A) = 240V$ $V_L(L) = 240V$
 $I_L(A) = 34.64A$ $I_L(L) = 34.64A$
 $P = 14399.58W$ $Z_{\text{phase}} = 12\Omega$

$$V_L(A) = V_L(L) \quad \text{alternator directly connected to load}$$

$$V_p(L) = V_L(L) \quad I_p(L) = \frac{V_p(L)}{Z} \quad I_p(L) = \frac{240}{12} = 20$$

$$I_L(L) = I_p(L) \times \sqrt{3} \quad I_L(L) = 34.64$$

$$I_L(L) = I_L(A) \quad I_p(A) = I_L(A) \quad V_p(A) = \frac{V_L(A)}{\sqrt{3}} \quad V_p(A) = \frac{240}{\sqrt{3}} \quad V_p(A) = 138.56$$

$$P = (\sqrt{3})(V_{L(A)}) (I_{L(A)}) \quad PF = 1 \quad P = (\sqrt{3})(240) (34.64)(1) = 14399.58$$

2)

$V_p(A) = 4160V$	$V_p(L) = 2401.78V$
$I_p(A) = 23.11A$	$I_p(L) = 40.03A$
$V_L(A) = 4160V$	$V_L(L) = 4160V$
$I_L(A) = 40.03A$	$I_L(L) = 40.03A$
$P = 288,429.41W$	$Z_{(phase)} = 60\Omega$

$$V_L(L) = V_L(A) \quad V_p(L) = \frac{V_L(L)}{\sqrt{3}} = \frac{4160}{\sqrt{3}} = 2401.78$$

$$I_p(L) = \frac{V_p(L)}{Z} = \frac{2401.78}{60} = 40.03 \quad I_p(L) = I_L(L) = I_L(A)$$

$$I_p(A) = \frac{I_L(A)}{\sqrt{3}} = \frac{40.03}{\sqrt{3}} = 23.11 \quad V_p(A) = V_L(A)$$

$$P = (\sqrt{3})(V_L(L))(I_L(L)) \quad PF = 1 \quad P = (\sqrt{3})(4160)(40.03)(1) = 288,429.41W$$

3)

$V_p(A) = 323.32V$	$V_p(L_1) = 323.32V$	$V_p(L_2) = 560V$
$I_p(A) = 185.9A$	$I_p(L_1) = 64.66A$	$I_p(L_2) = 70A$
$V_L(A) = 560V$	$V_L(L_1) = 560V$	$V_L(L_2) = 560V$
$I_L(A) = 185.9A$	$I_L(L_1) = 64.66A$	$I_L(L_2) = 121.24A$
$P = 180,313.42W$	$Z_{(phase)} = 5\Omega$	$Z_{(phase)} = 8\Omega$

$$V_L(A) = V_L(L_1) = V_L(L_2) = V_p(L_2)$$

$$I_p(L_2) = \frac{V_p(L_2)}{Z} = \frac{560V}{8\Omega} = 70 \quad I_L(L_2) = I_p(L_2)(\sqrt{3}) = 70(\sqrt{3}) = 121.24$$

$$I_p(l_2) = \frac{V_p(l_2)}{Z} = \frac{560V}{8\Omega} = 70 \quad I_c(l_2) = I_p(l_2)(\sqrt{3}) = 10(\sqrt{3}) = 141.44$$

$$V_p(l_1) = \frac{V_c(l_1)}{\sqrt{3}} = \frac{560}{\sqrt{3}} = 323.32 \quad I_p(l_1) = \frac{V_p(l_1)}{Z} = \frac{323.32}{5} = 64.66$$

$$I_p(l_1) = I_c(l_1) \quad I_c(A) = I_c(l_1) + I_c(l_2) = 64.66 + 121.24 = 185.9$$

$$I_p(A) = I_c(A) \quad V_p(A) = \frac{V_c(A)}{\sqrt{3}} = \frac{560}{\sqrt{3}} = 323.32$$

$$P = (\sqrt{3})(V_c)(I_c) \text{ (PF)} \quad P_F = 1 \quad P = (\sqrt{3})(560)(185.9)(1) = 180,313.42 \text{ W}$$

Three-Phase Power Practice

Friday, December 9, 2016 9:13 AM

8) Alternator

$$V_p = 508V$$

$$I_p = 381A$$

$$V_L = 880V$$

$$I_L = 381A$$

Load 1

$$V_p = 508V$$

$$I_p = 127A$$

$$V_L = 880V$$

$$I_L = 127A$$

Load 2

$$V_p = 880V$$

$$I_p = 146.7A$$

$$V_L = 880V$$

$$I_L = 254A$$

$$V_{\text{Line}} = \sqrt{3} (V_{\text{phase}}) \rightarrow \text{For } \text{Wye}$$

$$I_p = \frac{V_p}{Z}$$

$$I_{\text{Line}} = 254 + 127$$

$$I_{\text{Line}} = \sqrt{3} I_{\text{phase}} \rightarrow \text{For } \text{Delta}$$

$$\text{Power} = 580,644W$$

$$\text{Power} = (V_p)(I_p)(3) = 193,548W$$

$$\text{Power} = (V_p)(I_p)(3) = 387,288 \text{ Watts}$$