

# Syllabus

Monday, January 23, 2017 8:01 AM

[www.ecst.csuchico.edu/~hma](http://www.ecst.csuchico.edu/~hma) - class website

OCNL 317 Phone #: 898-4957 email: [hma@csuchico.edu](mailto:hma@csuchico.edu)

Office Hours: MTWTh 4:00 - 4:50 pm

Circuits: loop of electrical components

# Independent and Dependent Sources



Tuesday, January 24, 2017 8:02 AM

## I. Indep Sources

### A. Definition and Symbols

Indep source = source whose value does not depend in any way on the rest of the circuit

Symbols

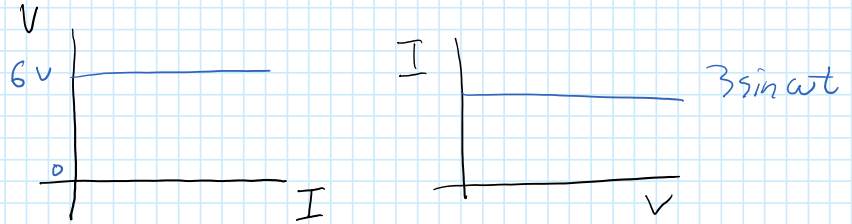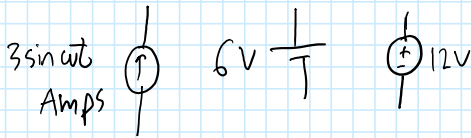


Ideal voltage source has  $\emptyset$  resistance

Short Circuit =  $\emptyset$  resis


Open Circuit =  $\infty$  resis
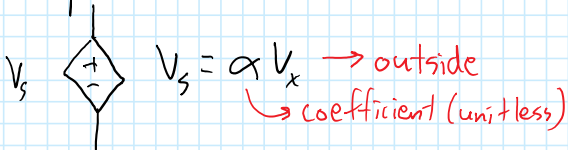
## II. Dependent Sources (controlled sources)




Voltage Controlled Voltage Source

Dependent Voltage Source

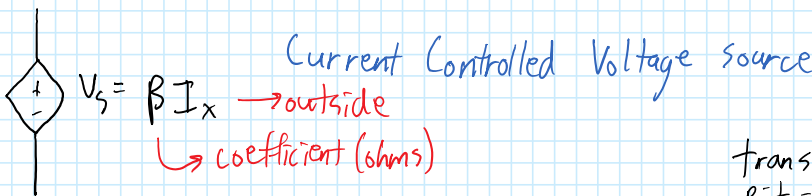


Current Controlled Voltage source

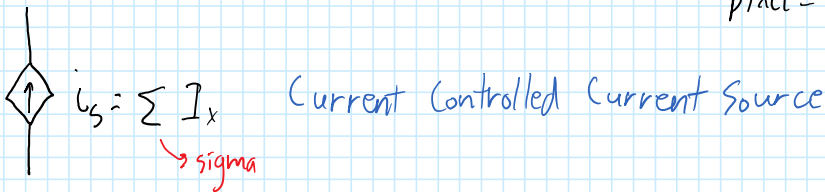transistor = transfer resistance  
Bit = binary digit  
pixel = picture element



Current Controlled Current Source

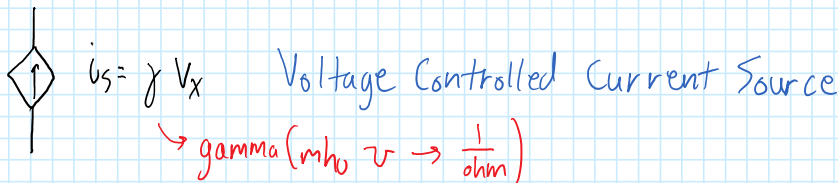




Voltage Controlled Current Source



## B. Circuit Applications

transistors act as dependent sources  
simulate transistors using dependent sources

Metal  
Oxide  
Semiconductor  
Field  
Effect  
Transistor

### 1. Transistor Small Signal

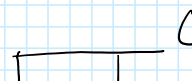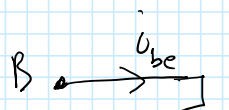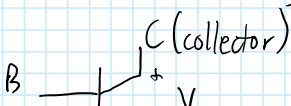

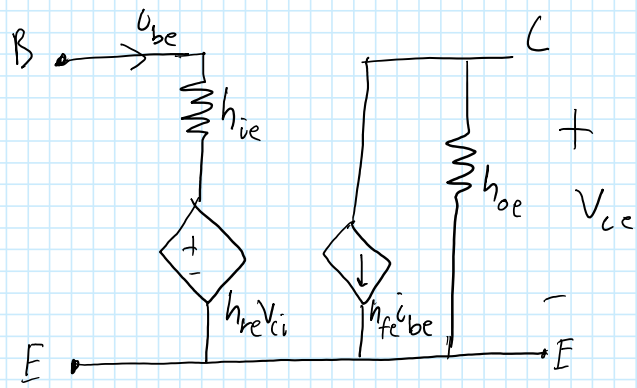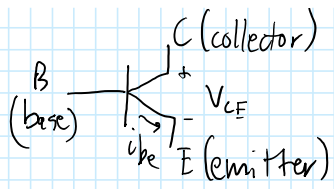




$$V_{CE} = h_{fe} i_{be} h_{oe}$$

$$V_{BE} = i_{be} h_{ie} + h_{re} V_{ce}$$


# MOSFET

Wednesday, January 25, 2017 8:02 AM

G = Gate  
D = Drain  
S = Source

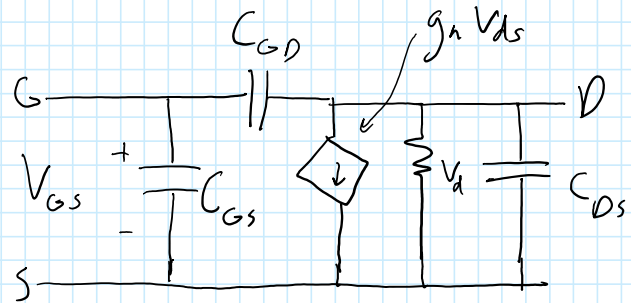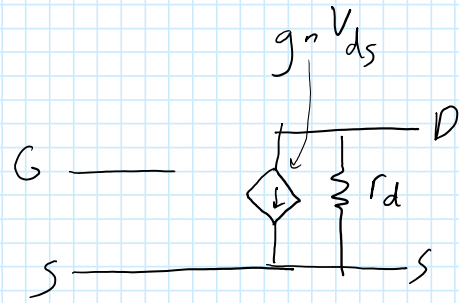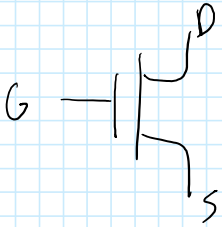

## Example 1:

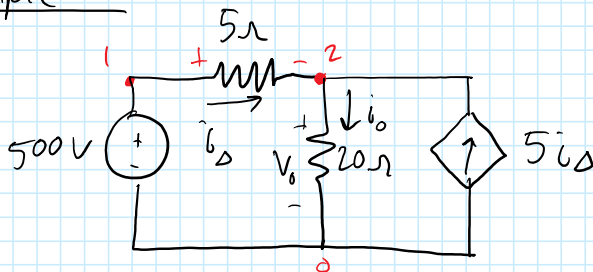

$i_D = ?$   
 $i_o = ?$   
 $V_o = ?$

Solve: Using KVL

$$\sum V = 0$$

$$\sum V_{\text{rises}} = \sum V_{\text{drops}}$$

$$\sum V_{\text{rises}} - \sum V_{\text{drops}} = 0$$

Using KCL at node 2:  $i_D + 5i_D = i_o$  (4)

$$6i_D = i_o \quad (5)$$

$$500 - 5i_D - 20(6i_D) = 0 \quad (6)$$

$$500 - 125i_D = 0 \quad (7)$$

$$125i_D = 500 \quad \boxed{i_D = 4A}$$

$$i_o = 6i_D \quad \boxed{i_o = 24A}$$





$$V_o = 20i_o \quad \boxed{V_o = 480V}$$

$V_{\text{rises}} \rightarrow "+"$        $V_{\text{drops}} \rightarrow "-"$

$$500V - 5i_D - V_o = 0 \quad (1)$$

$$V_o = 20i_o \quad (2)$$
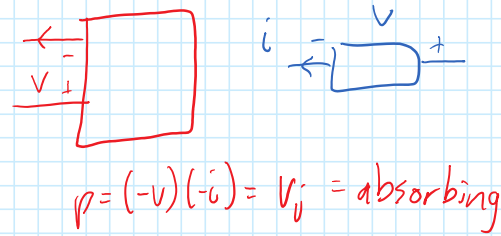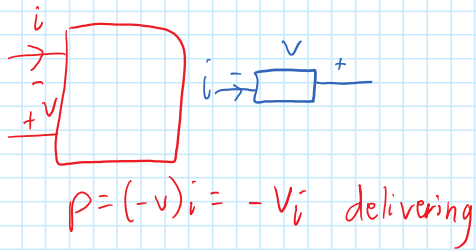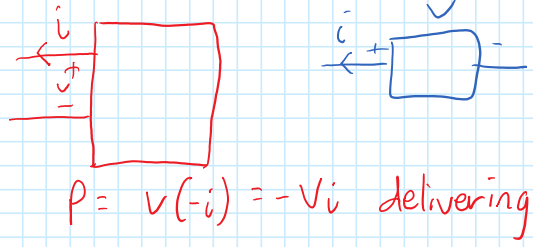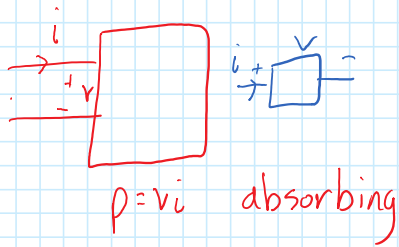
$$500 - 5i_D - 20i_o = 0 \quad (3) \quad 2 \rightarrow 1$$



$$P_{500V} = 500V(-i_d) = 500(4) = \boxed{-2000 \text{ W}} \text{ delivering}$$

$$P_{5\Omega} = V_{5\Omega}(i_d) \quad V_{5\Omega} = 5\Omega i_d \quad P = (5\Omega)(i_d)^2 \quad P = 5(4)^2 = \boxed{80 \text{ W}} \text{ absorbing}$$


$$P_{20\Omega} = (V_o)(i_s) = 480(24) = \boxed{11,520 \text{ W}} \text{ absorbing}$$

$$P_{5i_d} = (V_o)(-5i_d) = 480(-5)(4) = 480(-20) = \boxed{-9600 \text{ W}} \text{ delivery}$$

$$P_{500V} + P_{5\Omega} + P_{20\Omega} + P_{5i_d} = -2000 + 80 + 11520 - 9600 = 0$$

# Dependent Source Analysis

Thursday, January 26, 2017 8:02 AM

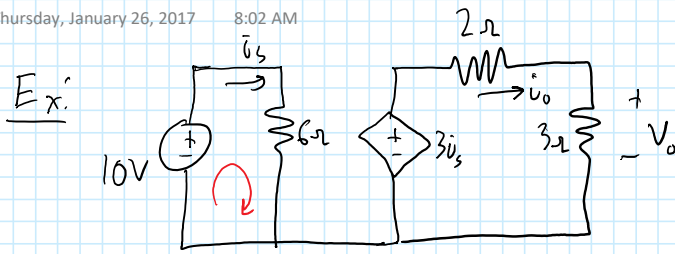

Solve: KVL at the left loop  
 Voltage rise = "+"  
 Voltage drop = "-"

$$10V - 6(i_s) = 0 \quad 6i_s = 10 \quad i_s = \frac{10}{6}$$

$$i_s = \frac{5}{3} \text{ A}$$

$$P_{10V} = V(-i) = 10(-i_s) = \frac{(10) \cdot (-5)}{3} = -\frac{50}{3} \text{ W}$$

$$P_{6\Omega} = V i = 10(i_s) = \frac{10 \cdot 5}{3} = \frac{50}{3} \text{ W}$$

$$P_{3i_s} = V(i) = \left(\frac{3}{1} \cdot \frac{5}{3}\right) \cdot (-1) = -5 \text{ W}$$

$$P_{2\Omega} = i^2 R = (1)^2 \cdot 2 = 2 \text{ W}$$

$$P_{3\Omega} = i^2 R = (1)^2 \cdot 3 = 3 \text{ W}$$

KVL at the right loop

$$3i_s - 2(i_o) - V_o = 0$$

$$V_o = 3\Omega(i_o)$$

$$3i_s - 2\Omega(i_o) - 3\Omega(i_o) = 0$$


$$3i_s - 5i_o = 0 \quad 5i_o = 3i_s$$

$$i_o = \frac{3}{5} i_s = \frac{3}{5} \cdot \frac{5}{3}$$

$$i_o = 1 \text{ A}$$

$$V_o = 3(i_o) = 3(1)$$

$$V_o = 3 \text{ V}$$

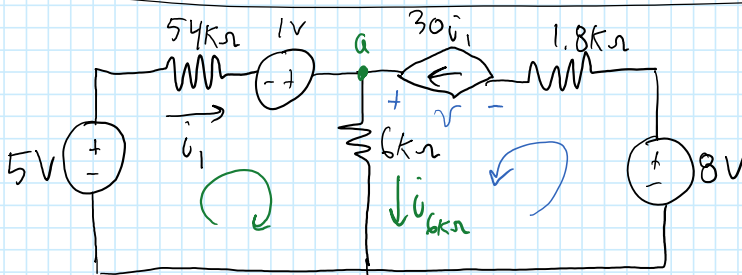

Solve: KVL at the left loop

$$5V - (54k\Omega)(i_1) + 1V$$

$$- (6k\Omega)(i_{6k\Omega}) = 0$$

$$i_{6k\Omega} = i_1 + 30i_1 \quad (\text{KCL at a})$$

$$5V - (54k\Omega)(i_1) + 1V - (6k\Omega)(31i_1) = 0$$

$$5 - 54000i_1 + 1 - 186000i_1 = 0$$

$$6 - 240000i_1 = 0$$

$$240000i_1 = 6 \quad i_1 = \frac{6}{240000}$$

$$= 0.000025 \text{ A} = 25 \mu\text{A} = i_1$$

KVL at the right loop:

$$8V - (1.8k\Omega)(30i_1) + V - (6k\Omega)(30i_1 + i_1) = 0$$

$$8V - (1800)(30i_1) + V - 186000i_1 = 0$$

$$V = -8 + 54000i_1 + 186000i_1$$

$$= -8 + 54000(25\mu A) + 186000(25\mu A)$$

$$= -2V$$

$$P_{5V} = V(-i) = (5V)(-i_1) = (5V)(25\mu A) = -125\mu W$$

$$P_{54k\Omega} = V(i) = (54k\Omega)(i_1)^2 = (54k\Omega)(25\mu A)^2 = 33.75\mu W$$

$$P_{1V} = V(-i) = (1V)(-i_1) = (1V)(-25\mu A) = -25\mu W$$

$$P_{6k\Omega} = V(i) = (6k\Omega)(31i_1)^2 = (6k\Omega)(31 \times 25\mu A)^2 = 3603.75\mu W$$

$$P_{30i_1} = V(-i) = (-2V)(-30i_1) = 1500\mu W$$

$$P_{1.8k\Omega} = V(i) = (1.8k\Omega)(30i_1)^2 = 1012.5\mu W$$

$$P_{8V} = V(-i) = 8V(-30i_1) = -6000\mu W$$

# Chapter 4: Techniques of Circuit Analysis


Monday, January 30, 2017 8:00 AM

- Read Ch 4.3, 4.4, 4.6, 4.7, 4.8
- Do Hw #2, due on wed. 2/8

## Node and Mesh Analysis
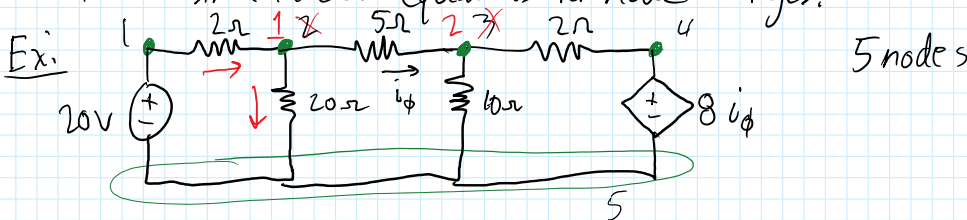
### I. Node Analysis

- Define Node - 2 or more branches merged together
- Pick Reference Node
- Define voltages relative to reference
- Apply KCL to all nodes except reference
- Solve simultaneous equations for node voltages.



$$\begin{aligned} V_1 &= 20V \\ V_4 &= 8i_\phi \\ V_5 &= 0V \end{aligned}$$

Solve: Node 1

Assume current entering "+"  
current leaving "-"

$$\rightarrow \downarrow \rightarrow \frac{20 - V_1}{2\Omega} - \frac{V_1}{20\Omega} - \frac{V_1 - V_2}{5\Omega} = 0 \quad \leftarrow \text{Use this one (1)}$$

$$\rightarrow \uparrow \rightarrow \frac{20 - V_1}{2} + \frac{0 - V_1}{20} - \frac{V_1 - V_2}{5} = 0$$

$$\leftarrow \downarrow \rightarrow \frac{-V_1 - 20}{2} - \frac{V_1}{20} - \frac{V_1 - V_2}{5} = 0$$

$$\leftarrow \uparrow \rightarrow \frac{-V_1 - 20}{2} + \frac{0 - V_1}{20} - \frac{V_1 - V_2}{5} = 0$$

Node 2:

$$\frac{V_1 - V_2}{5\Omega} + \frac{8i_\phi - V_2}{2\Omega} - \frac{V_2}{10\Omega} = 0 \quad (2)$$

$$i_\phi = \frac{V_1 - V_2}{5\Omega} \quad (3)$$

Solve 3 eq. 3 unknowns

cannot do  $i_\phi = V_1 - V_2$

Ask Clint to show how to solve eq




cannot do  $i_{\phi} = \frac{V_2 - V_1}{5}$

Ask client to show how to solve eq  
on calculator

# Supernode

Tuesday, January 31, 2017 8:04 AM

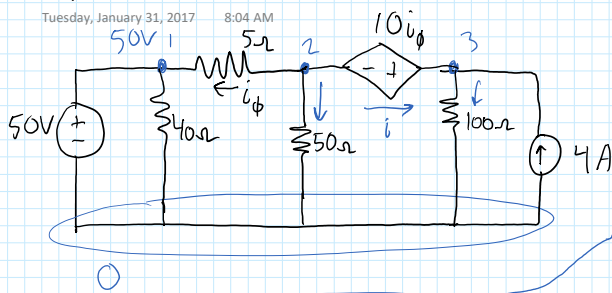

4 nodes

Node #1:  $V_1 = 50V$

Solve:  $I_{entering} \rightarrow "+"$

$I_{leaving} \rightarrow "-"$

Node #2: KCL

I. Using assumed  $i$

$$-\frac{V_2 - 50}{5} - \frac{V_2}{50} - i = 0 \quad (1)$$

Node 2:

$$i + 4A - \frac{V_3}{100\Omega} = 0 \quad (2)$$


Let (1) + (2)  $\Rightarrow -\frac{V_2 - 50}{5} - \frac{V_2}{50} (-i + i) + 4 - \frac{V_3}{100} = 0 \quad (3)$

$$V_3 - V_2 = 10i\phi \quad (4)$$

$$\frac{V_2 - 50}{5\Omega} = i\phi \quad (5)$$

Use (3), (4), (5) to solve for  $i\phi, V_2, V_3$

## II. Using supernode

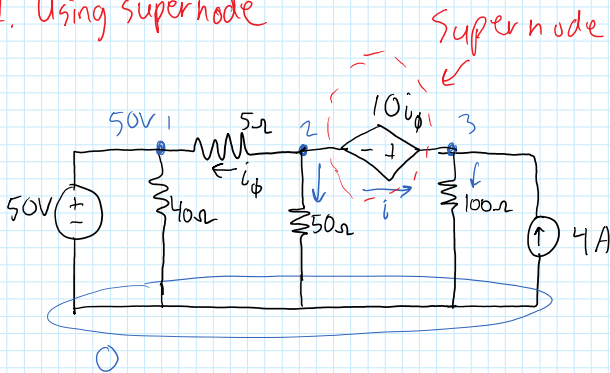

Looking at left side of supernode:

$$-\frac{V_2 - 50}{5\Omega} - \frac{V_2}{50\Omega} - \frac{V_3}{100} + 4A = 0 \quad \text{Same as (3)}$$

Looking at right side of supernode:

Substitute (5) into (4)

$$V_3 - V_2 = \left(\frac{V_2 - 50}{5}\right) 10 \quad V_3 - V_2 = 2V_2 - 100$$

$$V_3 = 3V_2 - 100 \quad (6)$$

Substitute (6) into (3):  $-\frac{V_2 - 50}{5} - \frac{V_2}{50} - \frac{3V_2 - 100}{100} + 4 = 0$

Mult 100 by both sides:

$$-20V_2 + 1000 - 2V_2 + 400 - 3V_2 + 100 = 0$$

$$-25V_2 + 1500 = 0$$

$$V_2 = 60 \text{ Volts}$$

$$V_3 = 3(60) - 100 = 180 - 100$$

$$V_3 = 80 \text{ Volts}$$

$$i\phi = \frac{V_2 - 50}{5}$$


$$i\phi = \frac{60 - 50}{5}$$

$$i\phi = \frac{10}{5}$$

$$i\phi = 2A$$

# More Supernode

Wednesday, February 1, 2017 8:02 AM

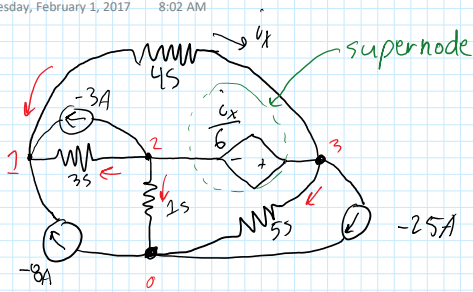

Use supernode only for voltage source  
- due to not knowing current thru voltage source

Solution:  $I_{entering} \rightarrow +$ ,  $I_{leaving} \rightarrow -$

At node 1:  $(V_2 - V_1)3S + (V_3 - V_1)4S + (-3A) + (-8A) = 0$

$3(V_2 - V_1) + 4(V_3 - V_1) - 11 = 0$

$3V_2 - 3V_1 + 4V_3 - 4V_1 - 11 = 0 \Rightarrow -7V_1 + 3V_2 + 4V_3 = 11$   $7V_1 - 3V_2 - 4V_3 = -11$  (1)

Supernode:  $(-3A) - (V_2 - V_1)3S - V_2(1S) - (V_3 - V_1)4S - (V_3)5S - (-25A)$

node 2:  $3 - 3(V_2 - V_1) - V_2 - 4(V_3 - V_1) - 5V_3 + 25 = 0$

$3 - 3V_2 + 3V_1 - V_2 - 4V_3 + 4V_1 - 5V_3 + 25 = 0$

$7V_1 - 4V_2 - 9V_3 = -28$  (2)

$V_3 - V_2 = \frac{v_x}{8} \Rightarrow -V_2 + V_3 = \frac{v_x}{8}$  (3)

$(V_1 - V_3)4S = i_x$


$4V_1 - 4V_3 - i_x = 0$  (4)

$V_1 = 1.4314V$

$V_2 = 3.3726V$

$V_3 = 2.7225V$

## Ex 2:

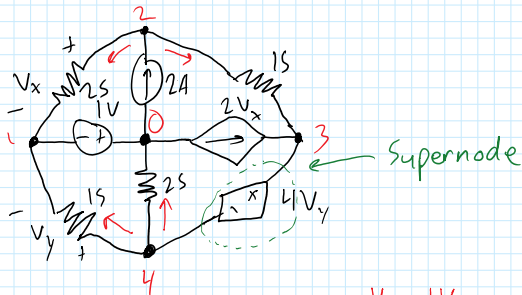

$V_1 = -1V$

$V_2 = \frac{17}{9}V$

$V_3 = \frac{17}{3}V$

$V_4 = -\frac{1}{3}V$

Solve: Node 1:  $V_1 = -1V$  (1)

Node 2:  $2A - (V_2 - V_1)2S - (V_2 - V_3)1S = 0$

$2 - 2V_2 + 2V_1 - V_2 + V_3 = 0$

$2V_1 - 3V_2 + V_3 = 0$  (2)

Supernode:  $(V_2 - V_3)1S + 2V_x - V_4(2S) - (V_4 - V_1)1S = 0$

$V_2 - V_3 + 2V_x - 2V_4 - V_4 + V_1 = 0$

$V_1 + V_2 - V_3 - 3V_4 + 2V_x = 0$  (3)

$V_2 - V_1 = V_x$

$-V_1 + V_2 - V_x = 0$  (4)

$V_3 - V_4 = 4V_y$

$V_3 - 4V_4 - 4V_y = 0$  (5)


$V_4 - V_1 = V_y$  (6)

# Mesh Analysis

Thursday, February 2, 2017 8:06 AM

## Procedure:

- Define a set of circuit paths
- Assign a direction to each loop-current
- Apply KVL to all loops
- Solve simultaneous equations for loop currents

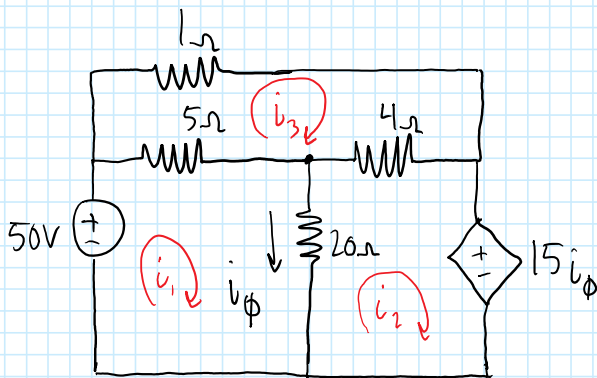

Loop 3:  $-(1\Omega)i_3 - (4\Omega)(i_3 - i_2) - (5\Omega)(i_3 - i_1) = 0$   
 $-i_3 - 4i_3 + 4i_2 - 5i_3 + 5i_1 = 0$   
 $5i_1 + 4i_2 - 10i_3 = 0 \quad (3) \quad \checkmark$

$$i_\phi = i_1 - i_2$$

$$i_1 - i_2 - i_\phi = 0 \quad (4)$$

$$20i_1 - 24i_2 + 4i_3 - 15(i_1 - i_2) = 0$$

$$20i_1 - 24i_2 + 4i_3 - 15i_1 + 15i_2 = 0$$

$$5i_1 - 9i_2 + 4i_3 = 0 \quad (2) \quad \checkmark$$

$$P_{50V} = (50V)(-i_1)$$

$$P_{5\Omega} = i^2 R = (5\Omega)(i_1 - i_3)^2$$

$$P_{20\Omega} = (20\Omega)(i_1 - i_2)^2$$

$$P_{4\Omega} = (4\Omega)(i_3 - i_2)^2$$

$$P_{1\Omega} = (1\Omega)(i_3)^2$$

order does not matter, due to the square

Solu:  $V_{rises} \rightarrow '+'$ ;  $V_{drops} \rightarrow '-'$


Loop 1:  $50V - (5\Omega)(i_1 - i_3) - (20\Omega)(i_1 - i_2) = 0$   
 $50 - 5i_1 + 5i_3 - 20i_1 + 20i_2 = 0$   
 $-25i_1 + 20i_2 + 5i_3 = -50 \quad (1) \quad \checkmark$

Loop 2:  $-20\Omega(i_2 - i_1) - 4\Omega(i_2 - i_3) - 15i_\phi = 0$   
 $-20i_2 + 20i_1 - 4i_2 + 4i_3 - 15i_\phi = 0$   
 $20i_1 - 24i_2 + 4i_3 - 15i_\phi = 0 \quad (2)$

$$P_{15i_\phi} = (15i_\phi)(i_2)$$

# Supermesh

Monday, February 6, 2017 8:02 AM

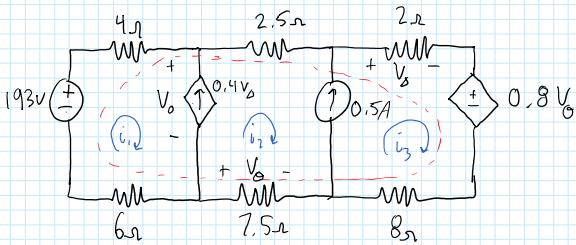

if  $i_2$  is assumed to go the opposite direction  
Supermesh:

$$193 - (4\Omega)i_1 + (2.5\Omega)i_2 - (2\Omega)i_3 - 0.8V_\Delta - (8\Omega)i_3 + (7.5\Omega)i_2 - (6\Omega)i_1 = 0 \quad (1)$$

$$V_\Delta = (7.5\Omega)i_2 \quad (2)$$

$$i_2 + i_3 = 0.5A \quad (3)$$

$$-i_1 - i_2 = 0.4V_\Delta \quad (4)$$

$$V_\Delta = 2i_3 \quad (5)$$

Solution:  $V_{rise} \Rightarrow '+'$ ;  $V_{drop} \Rightarrow '-'$

Supermesh:  $193V - (4\Omega)i_1 - (2.5\Omega)i_2 - (2\Omega)i_3 - 0.8V_\Delta - (8\Omega)i_3 - (7.5\Omega)i_2 - (6\Omega)i_1 = 0$   
or  $V_\Delta$ , but  $V_\Delta = (7.5)(-i_2)$

$$193 - 4i_1 - 7.5i_2 - 2i_3 - 0.8V_\Delta - 8i_3 - 7.5i_2 - 6i_1 = 0$$

$$193 - 10i_1 - 10i_2 - 10i_3 - 0.8V_\Delta = 0$$


$$10i_1 + 10i_2 + 10i_3 + 0.8V_\Delta = 193 \quad (1)$$

$$V_\Delta = -7.5i_2 \quad (2)$$

$$i_3 - i_2 = 0.5A \quad (3)$$

$$-i_1 + i_2 = 0.4V_\Delta \quad (4)$$

$$V_\Delta = 2i_3 \quad (5)$$

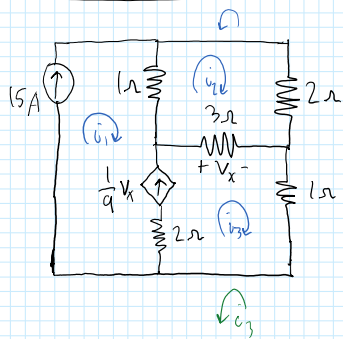

$$i_1 = 15A$$

Solu:

Mesh 2:  $(-1\Omega)(i_2 - 15A) - 2\Omega(i_2) - 3\Omega(i_2 - i_3) = 0 \quad (1)$

$$i_3 - i_1 = \frac{1}{9}V_x \quad (2)$$

$$V_x = (3\Omega)(i_3 - i_2) \quad (3)$$

$$\boxed{\begin{matrix} i_1 = 15A \\ i_2 = 11A \\ i_3 = 17A \end{matrix}}$$

Mesh 3:  $i_3 + i_1 = -\frac{1}{9}V_x \quad (1)$

$$V_x = (3\Omega)(i_2 + i_3) \quad (3)$$

Mesh 2:  $(-1\Omega)(i_2 - 15A) - 2\Omega(i_2) - 3\Omega(i_2 + i_3) = 0$

$$-i_2 + 15 - 2i_2 - 3i_2 - 3i_3 = 0 \Rightarrow -6i_2 - 3i_3 = -15 \quad (2)$$

$$i_3 + i_1 = \frac{1}{9}(-3i_2 - 3i_3) \quad i_3 + i_1 = \frac{1}{3}i_2 + \frac{1}{3}i_3 \quad \frac{2}{3}i_3 + i_1 - \frac{1}{3}i_2 = 0$$

$$15 - \frac{1}{3}i_2 + \frac{2}{3}i_3 = 0 \quad (3)$$

$$\boxed{i_1 = 15A}$$

$$\boxed{i_2 = 11A}$$

$$\boxed{i_3 = -17A}$$

Mesh 2:  $(-2\Omega)i_2 - (1\Omega)(i_2 + 15A) - (3\Omega)(i_2 + i_3) = 0$

$$-2i_2 - i_2 - 15 - 3i_2 - 3i_3 = 0 \Rightarrow -6i_2 - 3i_3 = 15 \quad (1)$$

Mesh 3:  $v_3 - v_1 = \frac{1}{a} V_x$  (2)

$$V_x = 3\Omega(i_2 + i_3) \quad (3)$$

$$v_3 - v_1 = \frac{1}{a} (3i_2 + 3i_3)$$

$$v_3 - v_1 = \frac{1}{3} v_2 + \frac{1}{3} v_3$$

$$\frac{2}{3} v_3 - \frac{1}{3} v_2 - 15 = 0 \quad (4)$$

$$i_1 = 15A$$

$$i_2 = -11A$$

$$i_3 = 17A$$

# Thevenin's and Norton's Theorem

Tuesday, February 7, 2017 8:09 AM

- 1) Read Section 4.11-4.13
  - 2) Do Hw#3, which will be due on Monday 2/20  
Hw#3: Ch 4 #79, 80, 81, 87, 88, 89, 97, 98, 99
  - 3) Quiz #1 Monday 2/13
  - 4) Test #1 Tuesday 2/28
- 

## Thevenin's Theorem


Given any linear circuit, rearrange it in the form of two networks A and B connected by two resistanceless conductors. If either network contains a dependent source, its control variable must be in the same network. Define a voltage  $V_{oc}$  as the open-circuit voltage which would appear across the terminals of A if B were disconnected so that no current is drawn from A. Then, all the currents and voltages in B will remain unchanged if all independent voltage sources in A are short circuited and all independent current sources in A are open circuits, and an independent voltage source  $V_{oc}$  is connected with proper polarity in series with the inactive A network.



# Pictorial Description of Thevenin and Norton Theorem



Wednesday, February 8, 2017 8:07 AM

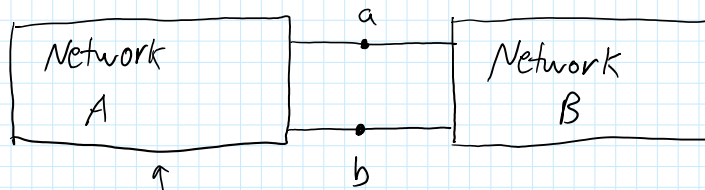1) Divide network into smaller networks A and B




If dependent source here, its control variable must be here also

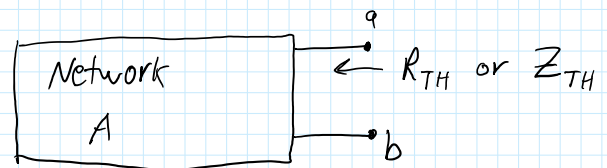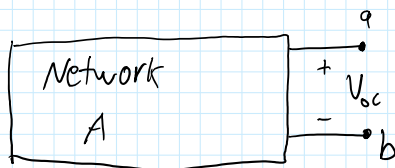2) Remove network A and tie  $V_{oc}$  and inactive A network (resistor for dc, impedance for ac)




↑  
short circuits all independent voltage sources and open circuits all indep. current sources

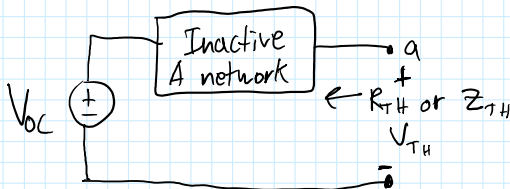3) Connect  $V_{oc}$  and Inactive network A in series.



$V_{oc} = V_{TH}$  since no current thru inactive A network (i.e. no voltage drop)

Ex:

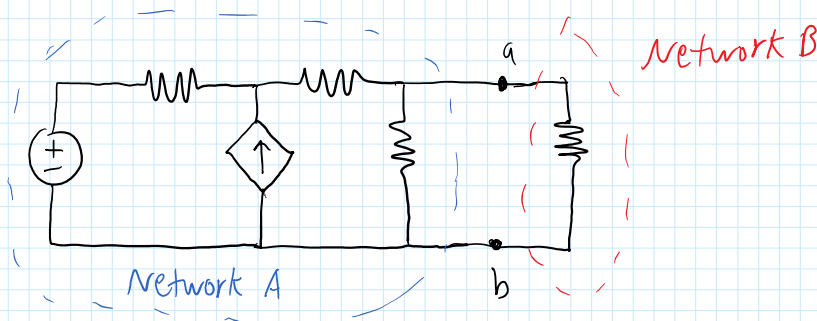


## Norton's Theorem

Given any linear circuit, rearrange it in the form of two networks A and B that are connected together by two resistanceless conductors. If either network contains a dependent source, its control variable must be in that same network. Define a

current  $i_{sc}$  as the short-circuit current which would appear at the terminals of A if B were short-circuited so that no voltage is provided by A. Then all the voltages and currents in B will remain unchanged if all independent voltage sources in A are short-circuited and all independent current sources in A are open-circuited, and an independent current source  $i_{sc}$  is connected with proper polarity in parallel with the inactive A network.


## Pictorial Description of Norton Theorem

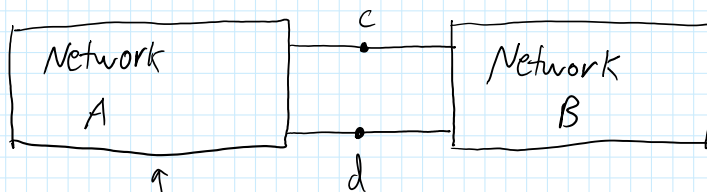1) Divide network into smaller networks A and B




If dependent source here, its control variable must be here also

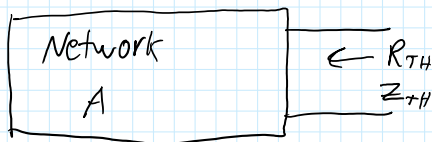2) Remove Network A and find  $i_{sc}$  and inactive network A (resistor for dc, impedance for ac).



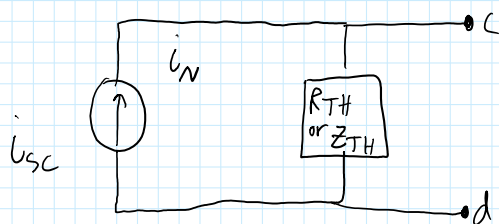
3) Connect  $i_{sc}$  and inactive A network in parallel.



Relationship btwn Thevenin and Norton theorems are:

$$V_{TH} = i_N \times R_N$$

$$i_N = \frac{V_{TH}}{R_{TH}}$$

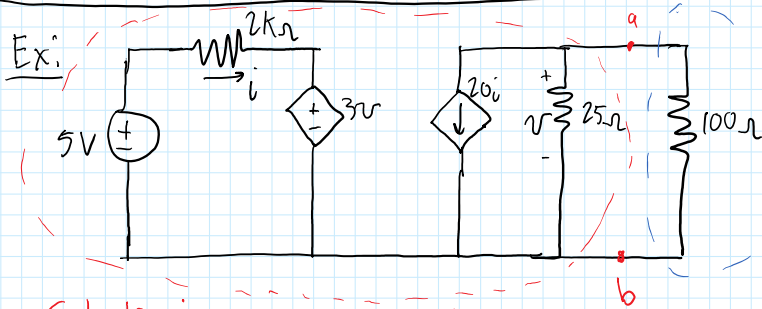


Find its Thevenin equivalent circuit

network B

Solution:

network A

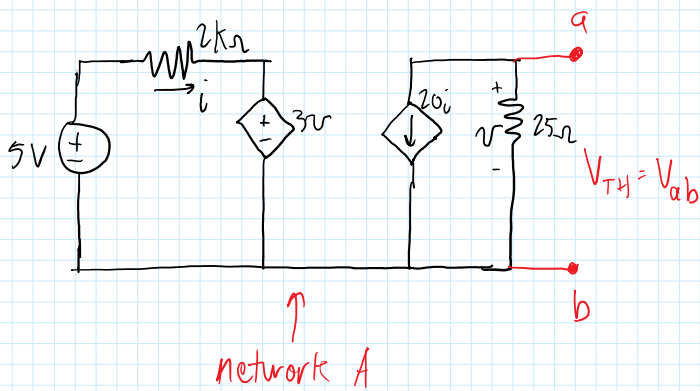

$$V_{TH} = V_{ab} = (-20i)(25\Omega)$$

$$i = \frac{5V - 3v}{2k\Omega} = \frac{5V - 3V_{TH}}{2k\Omega}$$

$$i = \frac{5 - 3V_{TH}}{2000}$$

$$V_{TH} = -20 \left( \frac{5 - 3V_{TH}}{2000} \right) (25)$$

$$V_{TH} = \left( \frac{-5}{100} + \frac{3V_{TH}}{100} \right) 25$$



$$V_{TH} = \frac{-5}{4} + \frac{3V_{TH}}{4}$$

$$4V_{TH} = -5 + 3V_{TH}$$

$$V_{TH} = -5 \text{ V}$$

# Thevenin Example

Thursday, February 9, 2017 8:07 AM

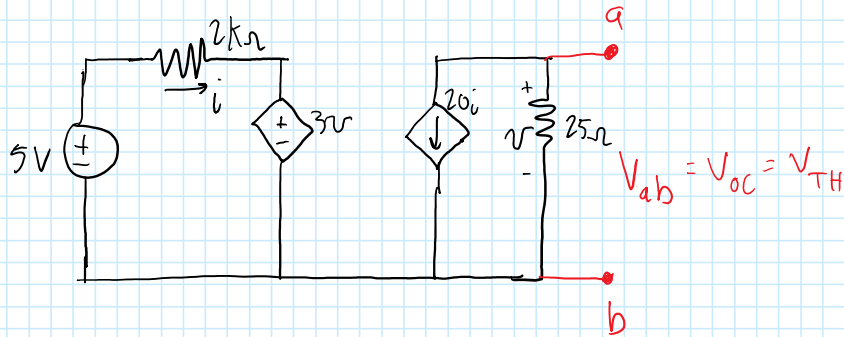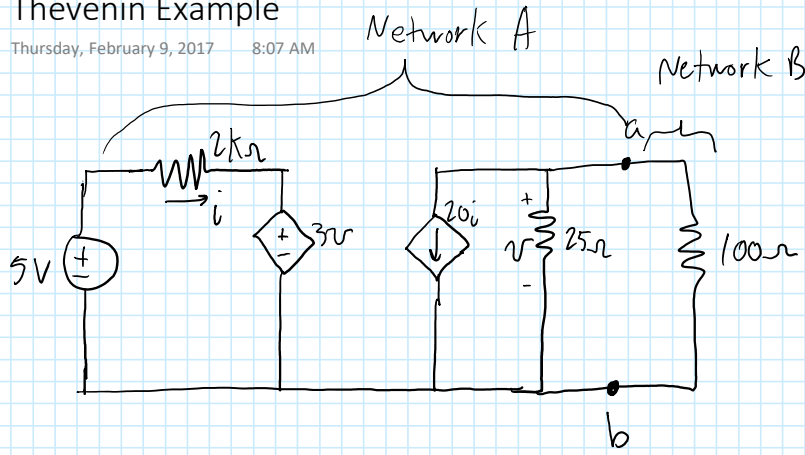

$$V_{TH} = V_{ab} = (-20i)(25\Omega) \quad (1)$$

$$i = \frac{5V - 3v}{2000\Omega} = \frac{5 - 3V_{TH}}{2000} \quad (2)$$

Substitute (2) → (1)

$$V_{TH} = \left(-20 \cdot \frac{5 - 3V_{TH}}{2000}\right)(25)$$


$$V_{TH} = -\left(\frac{5 - 3V_{TH}}{4}\right)$$

$$4V_{TH} = -5 + 3V_{TH}$$

$$V_{TH} = -5V$$

R<sub>TH</sub>

$$(1) R_{TH} = \frac{V_{TH}}{i_{sc}}$$

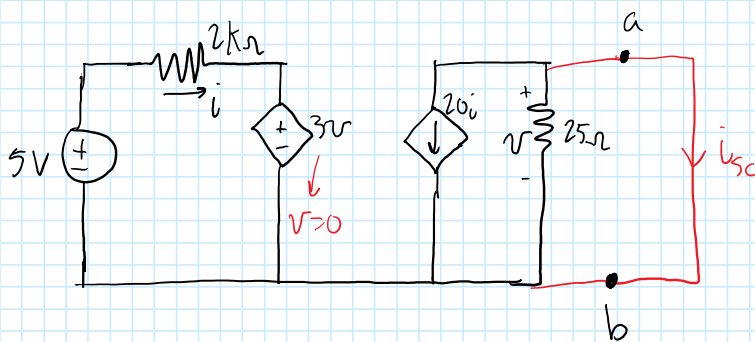

v = 0 (shorted)


$$i = \frac{5V}{2000\Omega} = 2.5\text{mA}$$

$$i_{sc} = -20i = -20(2.5\text{mA}) = -50\text{mA}$$

$$R_{TH} = \frac{-5V}{-50\text{mA}} = 100\Omega$$

$$(2) R_{TH} = V_T \text{ (using test voltage, } V_T)$$

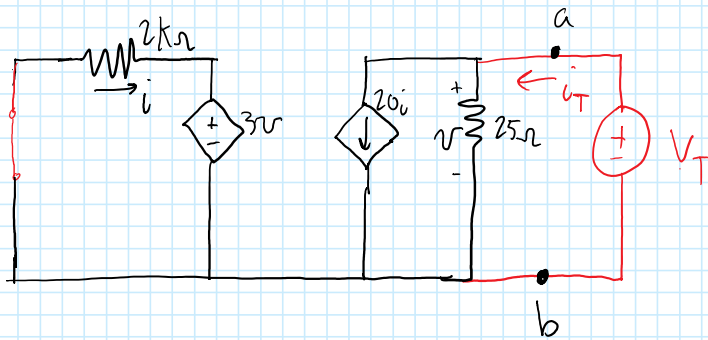②  $R_{TH} = \frac{V_T}{i_T}$  (using test voltage  $V_T$ )



$$3V = 3V_T$$

$$i_{\text{enter}} = '+' ; i_{\text{leave}} = '-'$$

KCL at a:

$$i_T - \frac{V_T}{25\Omega} - 20i = 0 \quad (1)$$

$$i = \frac{-3V_T}{2000\Omega} \quad (2)$$

Substitute (2) into (1)

$$i_T = \frac{V_T}{25} + 20 \left( \frac{-3V_T}{2000} \right)$$


$$i_T = \frac{V_T}{25} - \frac{3V_T}{100}$$

$$i_T = \frac{4V_T - 3V_T}{100}$$

$$i_T = \frac{V_T}{100}$$

$$\frac{V_T}{i_T} = 100\Omega = R_{TH}$$

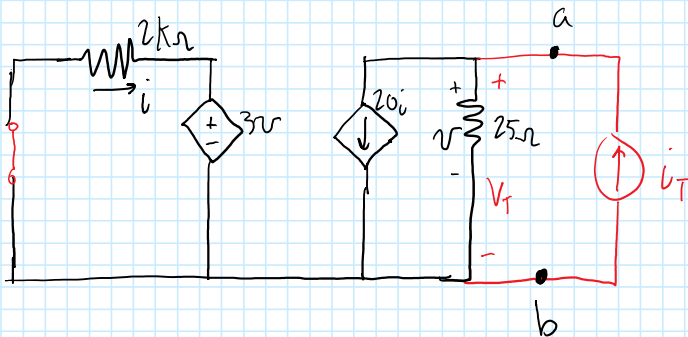③  $R_{TH} = \frac{V_T}{i_T}$  (using test current  $i_T$ )



$$V_T = 25\Omega(i_T - 20i)$$

$$V_T = (25)(i_T - 20i) \quad (1)$$

$$i = \frac{-3V_T}{2k\Omega} \quad (2)$$

$$V_T = 25 \left( i_T - 20 \left[ \frac{-3V_T}{2000} \right] \right)$$

$$V_T = 25i_T + 25(3V_T)$$

$$V_T = 25i_T + 25\left(\frac{3V_T}{100}\right)$$

$$V_T = 25i_T + \frac{3V_T}{4}$$

$$V_T - \frac{3V_T}{4} = 25i_T$$


$$\frac{1}{4}V_T = 25i_T$$

$$\frac{V_T}{i_T} = 100 \Omega$$


# Another Thevenin Example

Tuesday, February 14, 2017 7:57 AM

Find Thevenin equivalent for the circuit

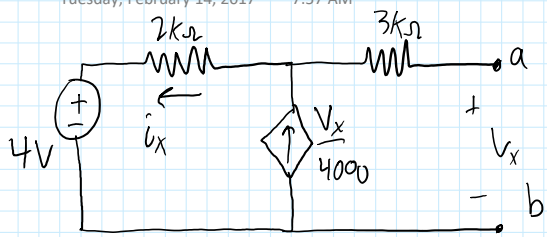

Solu:

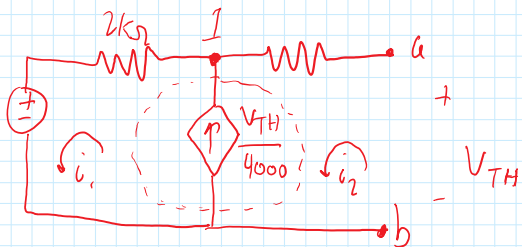

Using Supermesh:

$V_{rise} = '+'$ ;  $V_{drop} = '-'$   
 $I_{enter} = '+'$ ;  $I_{leave} = '-'$

$$-4V - (2k\Omega)i_1 - (3k\Omega)i_2 + V_{TH} = 0$$

$$-4 - 2000i_1 - 3000i_2 + V_{TH} = 0 \quad (1)$$

$$i_2 = 0 \quad (2)$$

At node 1:

$$i_x - \frac{V_{TH}}{4000} - i_2 = 0 \quad (3)$$

$$i_1 = i_x \quad (4)$$

Substitute (4) into (3)  $i_1 - \frac{V_{TH}}{4000} - i_2 = 0 \quad (5)$

substitute (2) into (5)

$$i_1 - \frac{V_{TH}}{4000} = 0 \quad (6)$$

Substitute (6) into (1)

$$-4 - 2000i_1 + V_{TH} = 0 \quad (7)$$

$$i_1 = \frac{V_{TH}}{4000} \quad (8)$$

Substitute (8) into (7)


$$-4 - 2000\left(\frac{V_{TH}}{4000}\right) + V_{TH} = 0$$

$$-4 - \frac{V_{TH}}{2} + V_{TH} = 0$$

$$\frac{V_{TH}}{2} = 4$$


$$V_{TH} = 8V$$

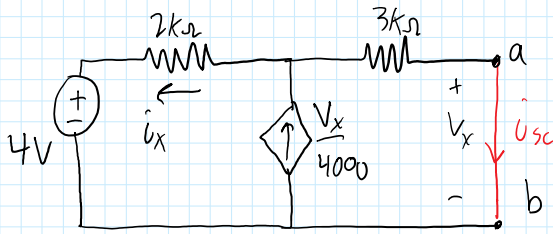$R_{TH}$ : 1)  $R_{TH} = \frac{V_{TH}}{i_{sc}} = \frac{8V}{0.8mA} = 10k\Omega$




$i_{sc} = \frac{4}{2k+3k} = 0.8mA$

$\therefore V_x = 0$

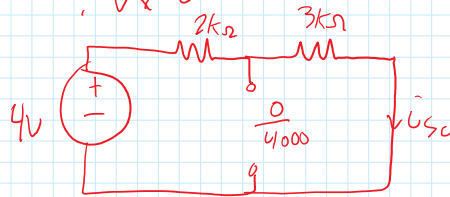

2)  $R_{TH} = \frac{V_T}{i_T}$

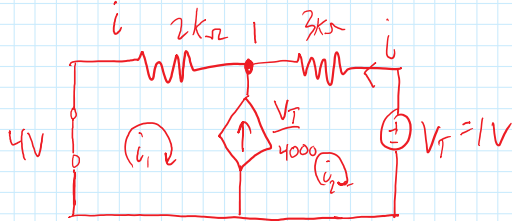

$V_{drop} = '+' ; V_{rise} = '-' ; I_{enter} = '+' ; I_{leave} = '-'$

Supermesh:  $2k\Omega(i_1) + 3k\Omega(i_2) + 1 = 0$

$2000i_1 + 3000i_2 = -1$  (1)

at node 1:  $i_1 + \frac{1}{4000} - i_2 = 0$

$i_1 = i_2 - \frac{1}{4000}$  (2)

Substitute (2) into (1)

$2000(i_2 - \frac{1}{4000}) + 3000i_2 = -1$

$2000i_2 - \frac{1}{2} + 3000i_2 = -1$


$5000i_2 = -\frac{1}{2}$

$i_2 = \frac{-1}{10,000} A$

$i = -i_2 = \frac{1}{10,000}$

$R_{TH} = \frac{V_T}{i} = \frac{1V}{\frac{1}{10,000} A} = 10k\Omega$

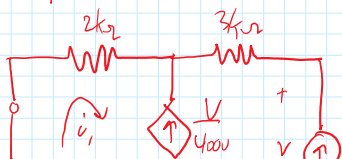3)  $R_{TH} = \frac{V}{i_T}$   $i_T = 1A$




Supermesh:

$2k\Omega(i_1) + (3k\Omega)i_2 + V = 0$

$2000i_1 + 3000i_2 + V = 0$  (1)



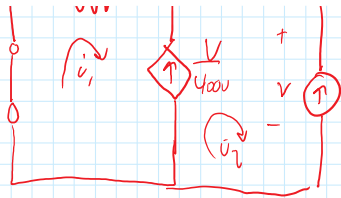

$$2k\Omega(i_1) + (5k\Omega)v_2 + V = 0$$

$$2000i_1 + 3000v_2 + V = 0 \quad (1)$$

Node 1:

$$i_1 + \frac{V}{4000} - i_2 = 0$$

$$i_1 = i_2 - \frac{V}{4000} \quad (2)$$

sub (2) into (1)

$$2000\left(i_2 - \frac{V}{4000}\right) + 3000v_2 + V = 0$$

$$2000i_2 - \frac{V}{2} + 3000v_2 + V = 0$$

$$5000v_2 + \frac{V}{2} = 0$$

$$\frac{V}{2} = -5000v_2$$

$$v_2 = -i_T = -1$$


$$\frac{V}{2} = 5000$$

$$V = 10,000 \text{ V}$$

$$R_{TH} = \frac{V}{i_T}$$

$$= \frac{10000}{1} = 10k\Omega$$


Thevenin Equivalent

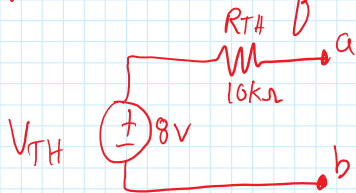
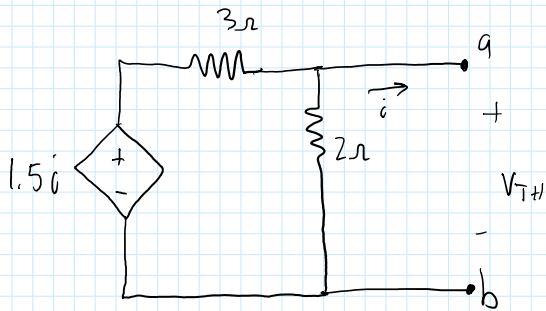
# Superposition

Wednesday, February 15, 2017 8:02 AM

Ex. Find the Thevenin Equivalent of the circuit shown below.



Soln:  $V_{TH} = V_{ab} = 0$

$\therefore i = 0$


or  $V_{TH} = (2\Omega)(i_1 - i) = 0$

$i = 0$

$i_1 = 0$

$R_{TH} = ?$

$R_{TH} = \frac{V_T}{i}$

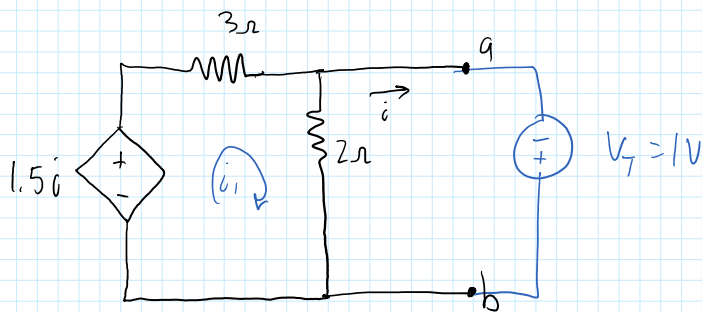

$V_{rises} = ' - ' ; V_{drops} = ' + '$

Left Mesh:  $-1.5i + 3\Omega(i_1) + 2\Omega(i_1 - i) = 0$   
 $-1.5i + 3i_1 + 2i_1 - 2i = 0$   
 $5i_1 - 3.5i = 0$  (1)

Right Mesh:  $2\Omega(i - i_1) - 1V = 0$   
 $2i - 2i_1 - 1 = 0$   
 $2i - 2i_1 = 1$  (2)  
 $i_1 = \frac{2i - 1}{2}$  (3)

Substitute (3) into (1)

$5\left(\frac{2i - 1}{2}\right) - 3.5i = 0$

$\frac{10i - 5}{2} - 3.5i = 0$


$10i - 5 - 7i = 0$

$3i = 5 \quad i = 5/3 A$

$R_{TH} = \frac{V_T}{i}$


$R_{TH} = \frac{1V}{5/3A}$

$R_{TH} = 0.6\Omega$

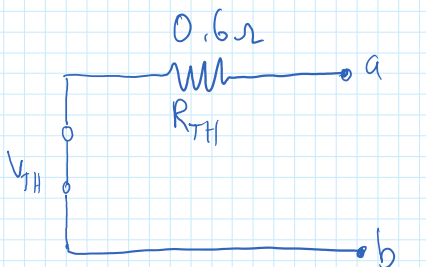



$V_{TH} = I_N R_N = (0)(0.6\Omega) = 0V$

$\Rightarrow$  Thevenin Equivalent

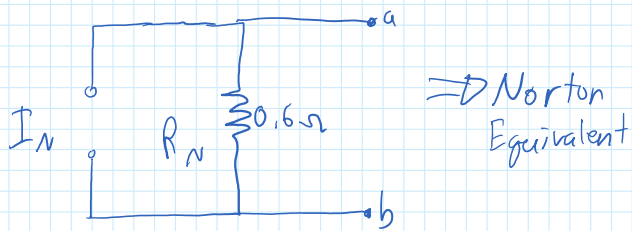


$$I_n = \frac{V_{TH}}{R_{TH}} = \frac{0V}{0.6\Omega} = 0A$$

Thevenin  $\rightarrow$  Norton Example

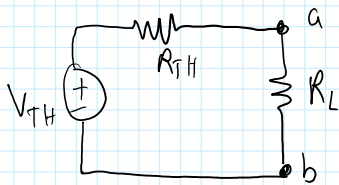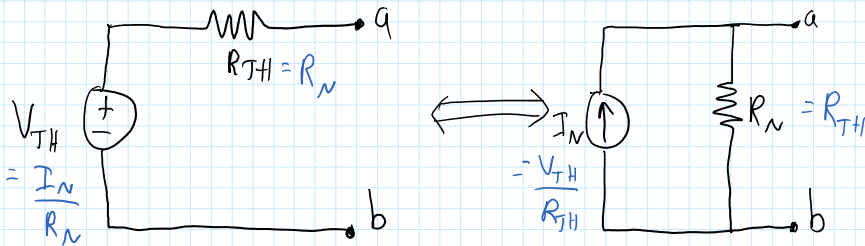

$$P_{R_L} = \left( \frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

Max Power transfer when  $R_L = R_{TH}$

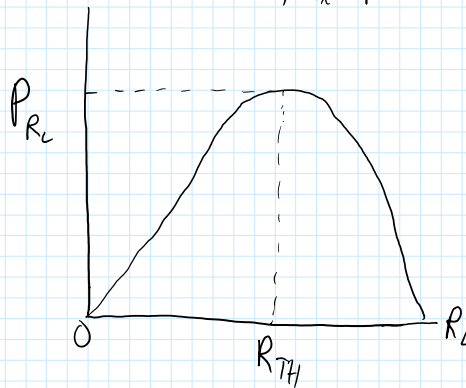

### Superposition Theorem


In any linear network containing several sources, the voltage across or the current through any passive element or source may be calculated by adding algebraically all the individual voltages or currents caused by each independent source acting alone, with all independent voltage sources replaced by short circuits and all other independent current sources replaced by open circuits. Dependent sources must be left in the network.

*x Cannot short dependent sources because we do not know the inner resistance*

# Superposition Examples

Thursday, February 16, 2017 8:04 AM

Ex:

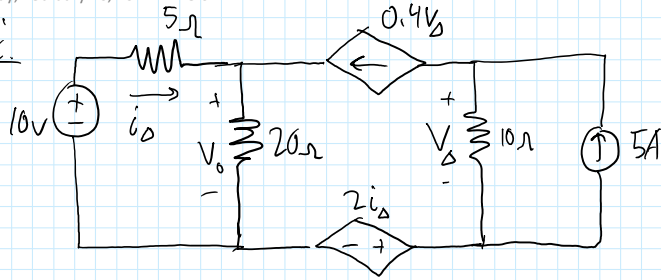


Use the principle of superposition to find  $V_0$ .

$$\begin{aligned} V_{\Delta}' &= -0.4V_{\Delta}'(10) \\ V_{\Delta}' &= -4V_{\Delta}' \\ V_{\Delta}' &= 0 \end{aligned}$$

Solution:

Consider 10V

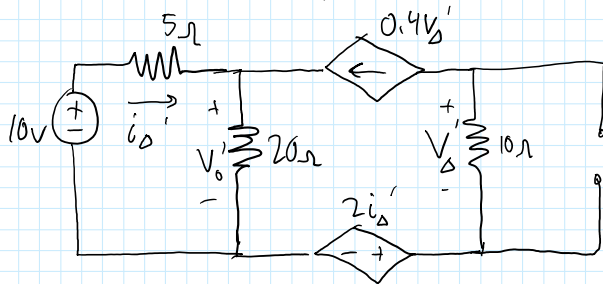

at  $V_0'$  (using node)

$$\frac{10V - V_0'}{5\Omega} - \frac{V_0'}{20\Omega} + 0.4V_{\Delta}' = 0 \quad (1)$$

$$V_{\Delta}' = -0.4V_{\Delta}'(10\Omega)$$

$$V_{\Delta}' = 0$$

(2)

Substitute (2) into (1)


$$\frac{10 - V_0'}{5} - \frac{V_0'}{20} + 0.4(0) = 0$$

$$4(10 - V_0') - V_0' = 0$$

$$40 - 4V_0' - V_0' = 0$$

$$5V_0' = 40 \quad \boxed{V_0' = 8V}$$

Consider 5A only:

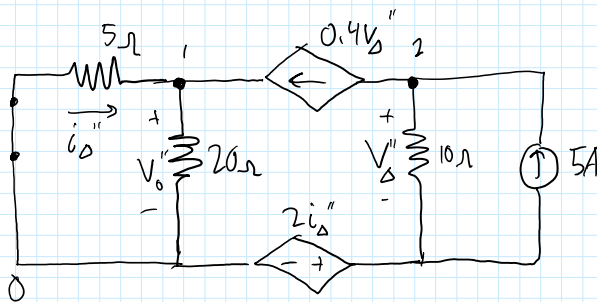

Node 1:  $I_{enter} = '+'$ ;  $I_{leave} = '-'$

$$i_{\Delta}'' - \frac{V_0''}{20\Omega} + 0.4V_{\Delta}'' = 0 \quad (1)$$

Node 2:

$$V_{\Delta}'' = V_2 - 2i_{\Delta}''$$

$$-0.4V_{\Delta}'' - \frac{V_0''}{10\Omega} + 5A = 0$$

$$i_{\Delta}'' = \frac{-V_0''}{5\Omega} \quad (3)$$

$$-4V_{\Delta}'' - V_{\Delta}'' + 50 = 0$$

$$V_{\Delta}'' = 10 \quad (2)$$

Substitute (2) and (3) into (1)

$$\frac{-V_0''}{5\Omega} - \frac{V_0''}{20\Omega} + 0.4(10) = 0$$

$$-4V_0'' - V_0'' + 80 = 0$$

$$5V_0'' = 80$$


$$V_0'' = 16V$$

$$V_0 = V_0' + V_0''$$

$$V_0 = 8V + 16V$$


$$V_0 = 24V$$

4.88

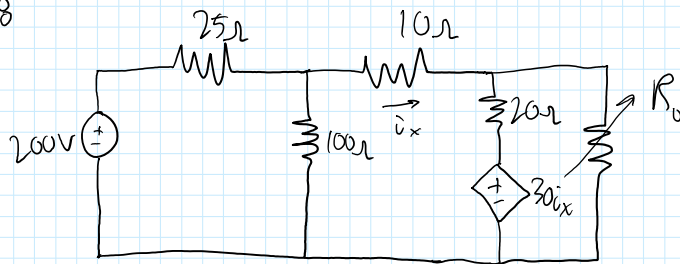

The  $R_o$  is adjusted until the  $P_{R_o} = 250W$   
Find  $R_o = ?$

Solution:

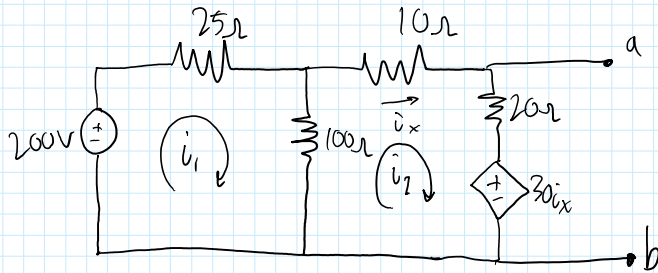

$$V_{th} = ?$$

$$R_{th} = ?$$

$$P_{R_o} = \left( \frac{V_{th}}{R_{th} + R_o} \right)^2 R_o$$

$$250 = \underline{\hspace{2cm}}$$

Mesh


Loop 1:  $200V - 25\Omega(i_1) - 100\Omega(i_1 - i_2) = 0$

Loop 2:  $-100\Omega(i_2 - i_1) - 10\Omega(i_2) - 20\Omega(i_2) - 30i_x = 0$


$$i_x = i_2$$

$$V_{th} = (20\Omega)(i_2) + 30i_x = C$$

Node

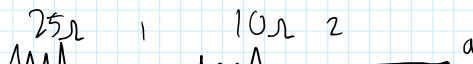

10000

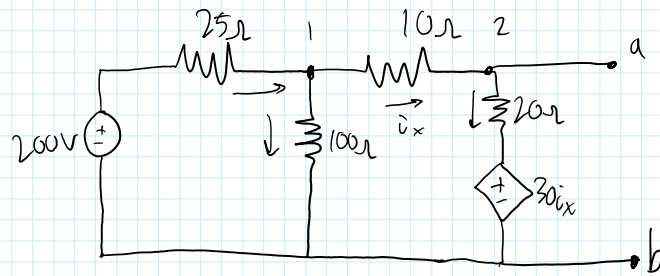

Node 1: 
$$\frac{200 - V_1}{25\Omega} - \frac{V_1}{100\Omega} - \frac{V_1 - V_2}{10\Omega} = 0 \quad (1)$$


Node 2: 
$$\frac{V_1 - V_2}{10\Omega} - \frac{V_2 - 30i_x}{20\Omega} = 0 \quad (2)$$

$$i_x = \frac{V_1 - V_2}{10\Omega} \quad (3)$$

$$V_2 = V_{th} = C$$

R<sub>Th</sub>:

C, d, e are just values when you solve the numbers

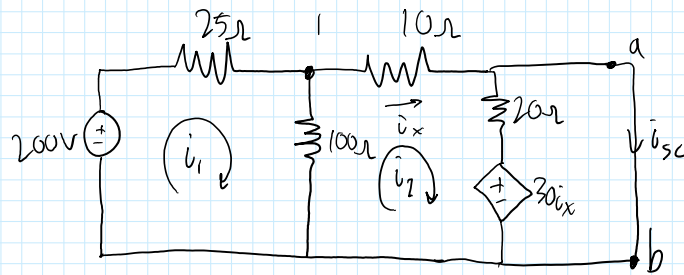

Node 1: 
$$\frac{200 - V_1}{25\Omega} - \frac{V_1}{100\Omega} - \frac{V_1}{10\Omega} = 0$$

$$V_1 = d$$

$$i_x = \frac{V_1}{10} = i_{sc} = e$$

$$R_{Th} = \frac{V_{th}}{i_{sc}} = \frac{C}{e}$$

Mesh: Loop 1: 
$$200 - 25i_1 - 100(i_1 - i_2) = 0$$

Loop 2: 
$$-100(i_2 - i_1) - 10(i_2) = 0$$

$$i_{sc} = i_2$$

# Intro to RL and RC Circuits

Monday, February 20, 2017 8:05 AM

No class this Wednesday

- 1.) Read Ch 7.
  - 2.) Do Hw #4 - Chapter 7: 1, 2, 3, 7, 8, 14, 15, 21, 23, 25, 28, 31, 35, 39, 44, 45, 60, 61, 85
  - 3.) Hw #4 due on Thursday, 3/09
  - 4.) Test 1: Hw #1-3
- 

## Ch. 7: RL + RC Circuits

### I. Basic Definition + concepts

#### A. Equivalent terminology

Natural response = transient response  
= source frequency = complementary function

#### B. Linear constant coefficient Differential Equations

##### 1. General Form

$$\frac{d^n y}{dt^n} + a_{n-1} \frac{d^{n-1} y}{dt^{n-1}} + \dots + a_0 y = m(t) \quad (1)$$

Where  $a_0, a_1, \dots, a_{n-1}$  are all constants

If  $m(t) = 0$ , equation (1) is called homogeneous, if not, it's called nonhomogeneous

## Example of RL Circuit

Tuesday, February 21, 2017 8:01 AM

$$\frac{d^n y}{dt^n} + a_{n-1} \frac{d^{n-1} y}{dt^{n-1}} + \dots + a_n y = m(t)$$


2. Solution of equation (1)

① Expression for  $y(t)$  that satisfies for all  $t > 0$ .

②  $y(t)$  satisfies the given initial conditions at  $t=0$ .

## II. Source-Free RL circuit

### A. Circuit Model

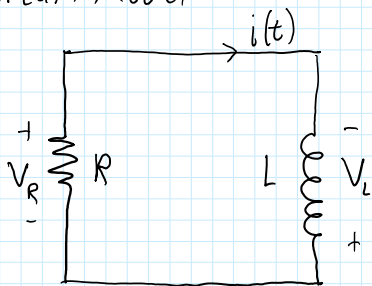

Let  $i(0) = I_0$  ← constant

$$V_L = L \frac{di}{dt}$$

KVL:

$$V_R + V_L = 0 = iR + L \frac{di}{dt} = 0$$

Lenz' Law

$$L \frac{di}{dt} + iR = 0$$

$$\frac{di}{dt} + \frac{R}{L} i = 0 \Rightarrow \text{1st order homogenous d.e.} \quad (1)$$

### B. Solution for $i(t)$

1. Method 1 - Substitute into general solution.

$$i(t) = I_0 e^{-(R/L)t} \quad \text{for } t \geq 0$$

comes from  $y(t) = Ae^{-st}$

2. Method 2 - Assume a solution with unknown coefficients

Let  $i(t) = Ae^{s_1 t}$  where  $A, s_1$  are unknown

Substitute  $i(t)$  into (1)

$$\frac{dAe^{s_1 t}}{dt} + \frac{R}{L} Ae^{s_1 t} = 0$$

$$s_1 Ae^{s_1 t} + \frac{R}{L} Ae^{s_1 t} = 0$$



$$s_1 A e^{s_1 t} + \frac{R}{L} A e^{s_1 t} = 0$$

$$(s_1 + \frac{R}{L}) A e^{s_1 t} = 0$$

$$s_1 + \frac{R}{L} = 0$$

$$s_1 = -\frac{R}{L}$$

$$\therefore i(t) = A e^{(-\frac{R}{L})t} \text{ for } t \geq 0$$


$$\text{at } t=0, i(0) = A e^{(-\frac{R}{L})0} = A = I_0$$

$$\therefore i(t) = I_0 e^{(-\frac{R}{L})t}, t \geq 0$$


C. RL Circuit Sample Problems

1. Case I: Problem reduces to one resistor and one inductor.

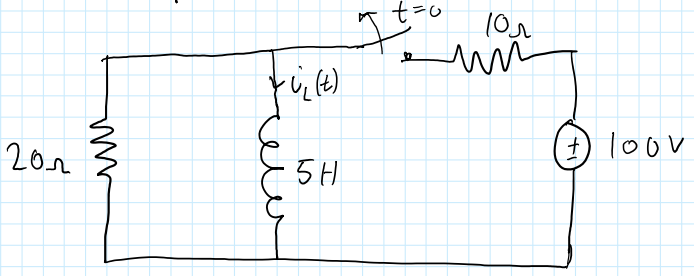
a) Example 1. Find  $i_L(t)$  for  $t \geq 0$  in the circuit below



Solution:  $t \geq 0$

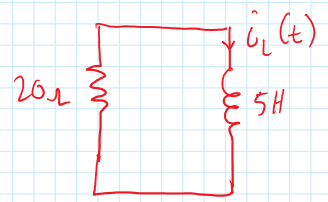
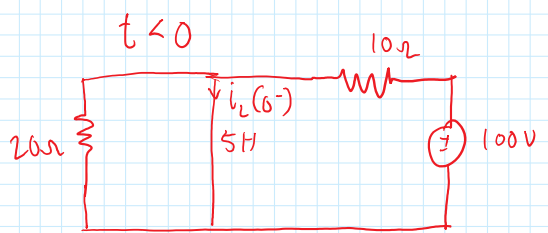
$$i_L(t) = I_0 e^{(-\frac{R}{L})t} = I_0 e^{-\frac{20}{5}t} = I_0 e^{-4t}, t \geq 0$$



inductor is short circuit since  $\frac{di}{dt}$  is  $\phi$ , meaning  $V_{\text{drop across } L}$  is  $\phi$ , meaning it is a short.

$V_{\text{drop across } L}$  is  $\phi$ , meaning it is a short.


$$i_L(0^-) = \frac{100V}{10\Omega} = 10A = I_0$$

Current cannot be changed instantaneously on an inductor, but voltage can

$$i_L(t) = 10e^{-4t}, t \geq 0$$

$$\underline{R} = \tau$$

$$i_L(t) = 10e^{-4t}, t \geq 0$$

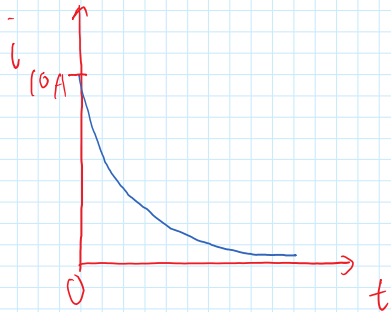

$$\frac{R}{L} = \tau$$

finished after  $5 \tau$ , since  $e^{-5}$  is less than 1%

$$i_L(t) = 10 \left( \frac{1}{e^{4t}} \right) \rightarrow \text{never goes to } \emptyset$$

①  $t = 0.25$

$$e^{-1} = 0.67$$

⑤  $t = 1.25$

$$e^{-5} = 0.0067$$


# More RL Examples

Thursday, February 23, 2017 8:05 AM

## 2.) Case 2: One inductor and several resistors


a) Approach - find equivalent resistance and time constant

b) Illustration

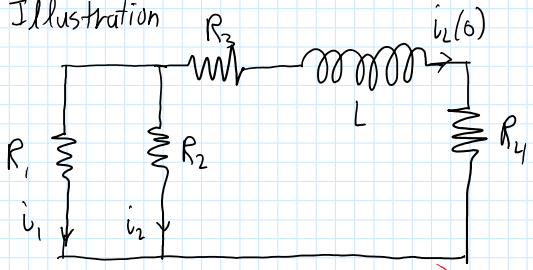


Let  $t=0$  and  $i_L(0) = I_0$   
Find  $i_1(t)$  and  $i_2(t)$  for  $t \geq 0$


Remember:

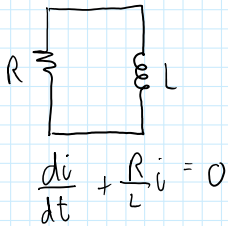

Solution:

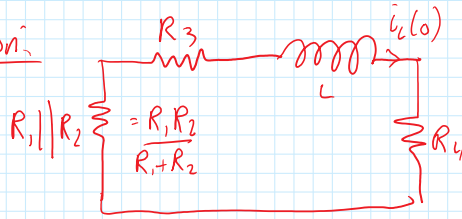
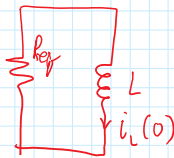
$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} + R_3 + R_4$$



$$i_L(t) = i_L(0) e^{-t/\tau}$$


$$\tau = \frac{L}{R_{eq}}$$

$$i_L(t) = i_L(0) e^{-\left(\frac{R_{eq}}{L}\right)t}, t \geq 0$$


$$i_1(t) = \frac{R_2}{R_1 + R_2} i_L(t)$$

$$= \frac{R_2}{R_1 + R_2} \left[ i_L(0) e^{-t/\tau} \right] A, t \geq 0$$
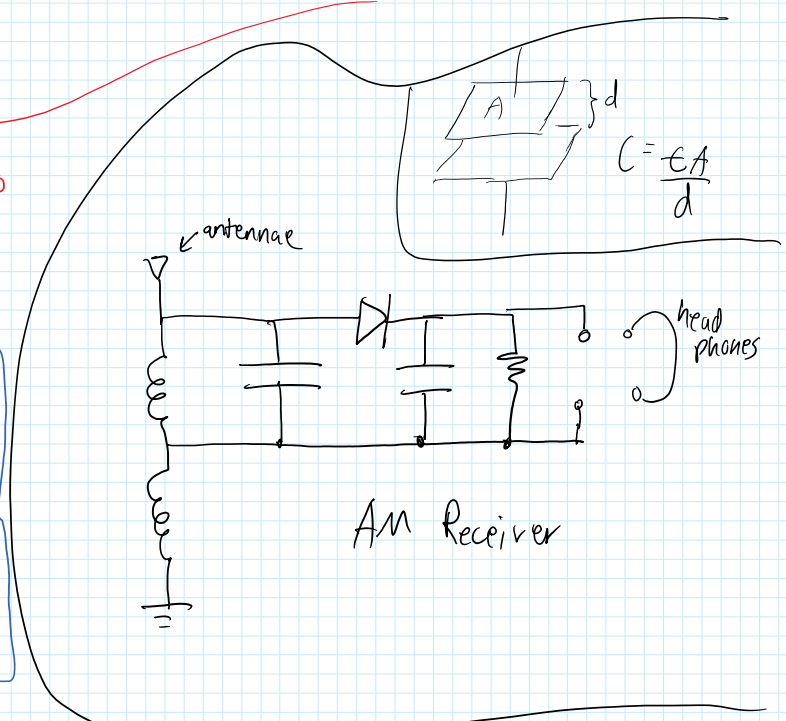
$$i_2(t) = \frac{R_1}{R_1 + R_2} \left[ i_L(0) e^{-t/\tau} \right] A, t \geq 0$$



## Current Divider

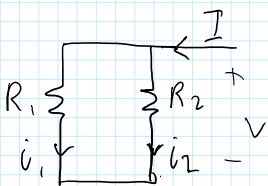

$$I = i_1 + i_2$$


$$i_1 = \frac{V}{R_1} = \frac{(R_1 || R_2) I}{R_1} = \frac{R_1 R_2}{R_1 + R_2} I = \frac{R_2}{R_1 + R_2} (I)$$

$$i_2 = \frac{V}{R_2} = \frac{(R_1 || R_2) I}{R_2} = \frac{R_1 R_2}{R_1 + R_2} I = \frac{R_1}{R_1 + R_2} (I)$$




$$i_2 = \frac{R_1}{R_2} = \frac{(R_1 // R_2) I}{R_2} = \frac{R_1 R_2}{R_1 + R_2} (I) = \frac{R_1}{R_1 + R_2} (I)$$

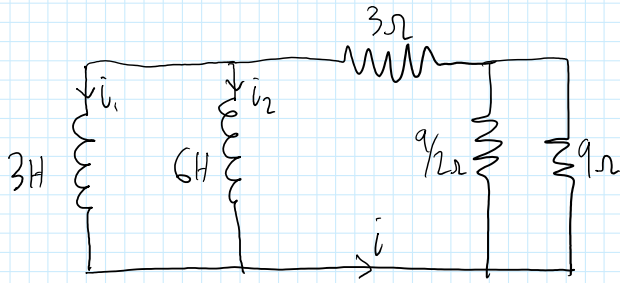3) Case 3: Serial Inductors and Resistors reduceable to one inductor and resistor



Find  $i(t) = ?$  for  $t \geq 0$   
when  $i_1(0) = 1A$ ,  $i_2(0) = 2A$

Solution:

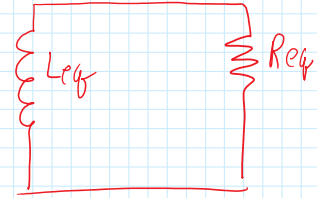

$$Leq = 3H // 6H = \frac{3 \times 6}{3+6} = 2H$$

$$Req = \left( \frac{9}{2} // 9 \right) + 3\Omega = 3 + \left( \frac{\frac{9}{2} \cdot 9}{\frac{9}{2} + 9} \right)$$

$$= 3 + \left( \frac{\frac{81}{2}}{\frac{27}{2}} \right) = 3 + 3 = 6\Omega$$

$$\tau = \frac{Leq}{Req} = \frac{2H}{6\Omega} = \frac{1}{3}$$

$$i(t) = i(0) e^{-t/\tau}$$

$$= i(0) e^{-t/\tau}$$

$$= (i_1(0) + i_2(0)) e^{-3t}$$

$$= (1+2) e^{-3t}$$


$$= 3e^{-3t} A, t \geq 0$$

# Source-Free RC Circuits

Monday, February 27, 2017 8:04 AM

## III. Source-Free RC Circuits

### A. Circuit Model

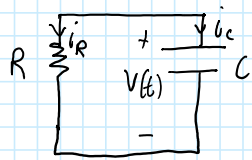

$$i_R + i_C = 0 \quad (\text{KCL})$$

$$\frac{V}{R} + C \frac{dV}{dt} = 0$$

$$\frac{dV}{dt} + \frac{1}{RC} (V) = 0$$

where  $V(0) = V_0$

$$Q = CV$$

$$I = \frac{Q}{t} = C \frac{V}{t}$$


$$\frac{di}{dt} = C \frac{dV}{dt}$$

### B. Solution for $V(t)$

$$V(t) = V_0 e^{-t/\tau} = V_0 e^{-t/RC}, \quad t \geq 0$$

$\tau = RC \rightarrow$  time constant, how long it takes to charge/discharge [s]  
 [s] [Ω] [F]
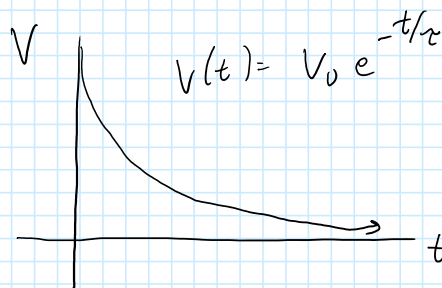
$$= \frac{V}{I} \cdot \frac{Q}{V} = \frac{Q}{I} = t$$





### C. RC Circuit Sample Problem

1. Case 1: One Capacitor and one or more resistors


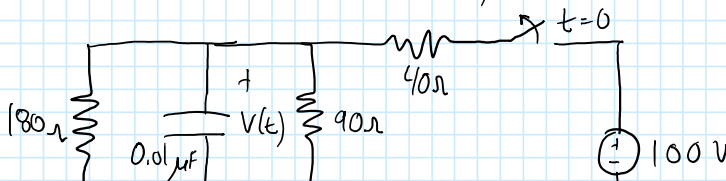
a) Example 1:

Find  $V(t)$  for  $t \geq 0$  in the circuit below



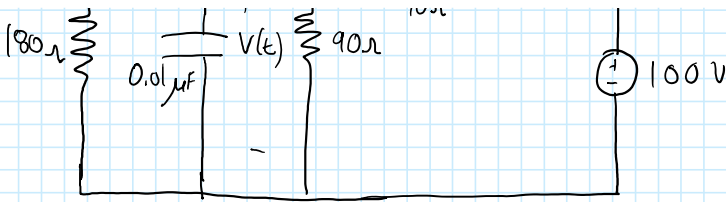



Solu:  $t \geq 0$

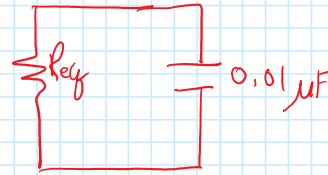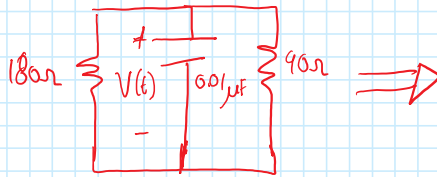

$$R_{eq} = 180\Omega // 90\Omega = \frac{180 \cdot 90}{180 + 90} = 60\Omega$$

$$\tau = R_{eq}(C) = (60\Omega)(0.01 \times 10^{-6} \text{ F}) = 0.6 \mu\text{s}$$

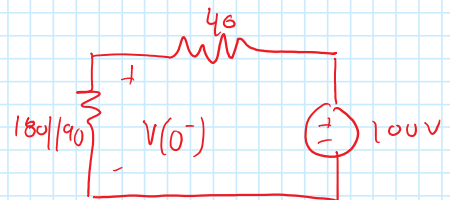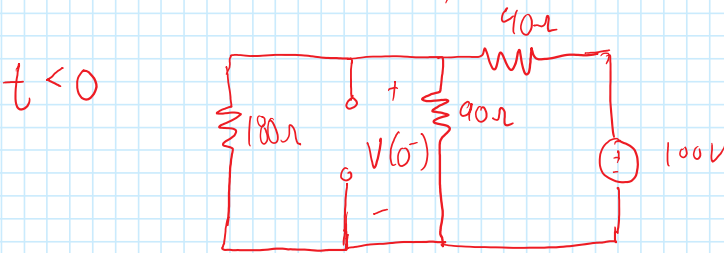
$$V(t) = V_0 e^{-t/0.6 \times 10^{-6} \text{ s}}, t \geq 0$$



$$V(0^-) = 100\text{V} \left( \frac{180 // 90}{(180 // 90) + 40} \right)$$

$$= 100 \left( \frac{60}{60 + 40} \right) = 60\text{V} = V(0)$$
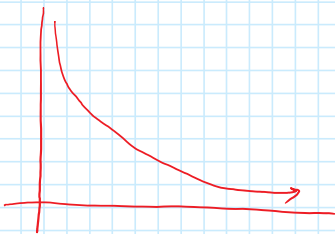
$$V(t) = 60 e^{-t/0.6 \times 10^{-6}}, t \geq 0$$



## Several Caps and Resistors



Wednesday, March 1, 2017 8:28 AM

2) Case 2: Several Capacitors and Resistors reducible to one capacitor and resistor

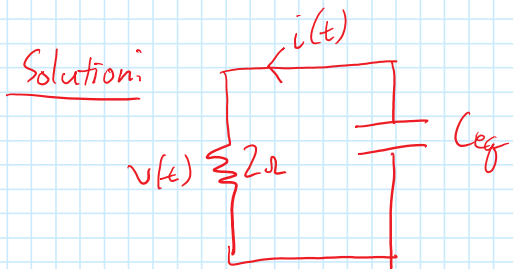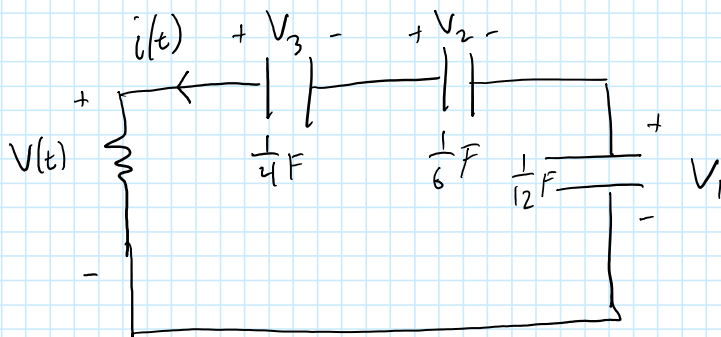a) Example

$$\text{Let } V_1(0) = 6V, V_2(0) = 4V, V_3(0) = 1V$$

Find  $V_1(t), V_2(t), V_3(t), i(t)$  for  $t \geq 0$



$$\frac{1}{C_{eq}} = \frac{1}{\frac{1}{4}F} + \frac{1}{\frac{1}{6}F} + \frac{1}{\frac{1}{12}F}$$

$$= 4 + 6 + 12 = 22F$$

$$C_{eq} = \frac{1}{22}F$$

$$\tau = RC_{eq} = (2\Omega) \left(\frac{1}{22}F\right) = \frac{1}{11} s$$

$$V(t) = V(0)e^{-t/\tau} = V(0)e^{-t/1/11}$$

$$= V(0)e^{-11t}$$

$$= [V_1(0) + V_2(0) + V_3(0)] e^{-11t}$$

$$= [6 + 4 + 1] e^{-11t} \quad V, t \geq 0$$

$$i(t) = \frac{V(t)}{R} = \frac{11e^{-11t}}{2} = \frac{11}{2} e^{-11t} A, t \geq 0$$

$$Q = CV$$

$$i(t) = C \frac{dV}{dt}$$

$$i(t) = -\frac{1}{12} \frac{dV_1}{dt} \Rightarrow 12i(t) = -\frac{dV_1}{dt} \quad 12i(t)dt = -dV_1$$

$$V_1(t) = \int -12i(t) dt + V_1(0)$$

$$\begin{aligned}
 V_1(t) &= -\int_0^t 12i(t)dt + V_1(0) \\
 &= -\int_0^t 12 \cdot \frac{11}{2} e^{-11t} dt + 6 \\
 &= \frac{(12)11e^{-11t}}{-2(11)} \Big|_0^t + 6 \\
 &= 6(e^{-11t} - 1) + 6 \\
 &= 6e^{-11t} \quad V, t \geq 0
 \end{aligned}$$

$$\begin{aligned}
 V_2(t) &= -\int_0^t 6i(t)dt + V_2(0) \\
 &= -\int_0^t 6 \cdot \frac{11}{2} e^{-11t} dt + 4 \\
 &= 3e^{-11t} + 1 \quad V, t \geq 0
 \end{aligned}$$

$$\begin{aligned}
 V_3(t) &= -\int_0^t 4i(t)dt + V_3(0) \\
 &= -\int_0^t 4 \cdot \frac{11}{2} e^{-11t} dt + 1 \\
 &= 2e^{-11t} - 1 \quad V, t \geq 0
 \end{aligned}$$



# Complete Response for RL Circuits

Thursday, March 2, 2017 8:03 AM

## I. General Form of Complete Response

### A. Definition

Complete Response = natural response + forced response

For example:  $i = i_n + i_f$  or  $V = V_n + V_f$

where  
 $i_n$  = natural response  
 $i_f$  = forced response  
 $i$  = complete response

### B. Relation to Differential Equation

$$\frac{d^k i}{dt^k} + a_{k-1} \frac{d^{k-1} i}{dt^{k-1}} + \dots + a_0 i = f(t)$$


Solution consists of homogenous (transient) part =  $i_n$  plus particular integral (forced response) part =  $i_f$ .

### C. Analysis Procedure


1. Find general form of natural response ( $i_n$ ) without solving all unknown coefficients (set all independent sources to  $\emptyset$ ).
2. Find forced or steady-state response ( $i_f$ )
3. Add the two expressions:  $i = i_n + i_f$
4. Adjust unknown coefficients to satisfy initial conditions

### D. RL Example

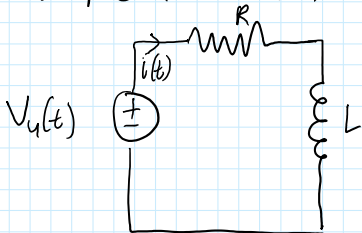1. Example 1: Find  $i(t)$  for  $t \geq 0$  in the circuit below



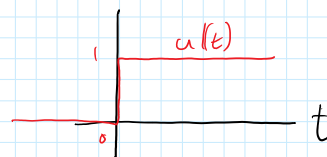
$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t \geq 0 \end{cases}$$



Solution:


step 1: Set sources = 0

This gives the network below

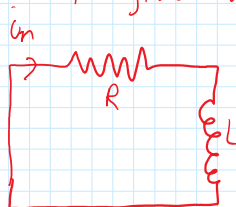

$$i_n(t) = A e^{-\frac{R}{L}t}, t \geq 0 \quad \gamma = \frac{L}{R}$$

step 2: Find forced response  $t \geq 0$

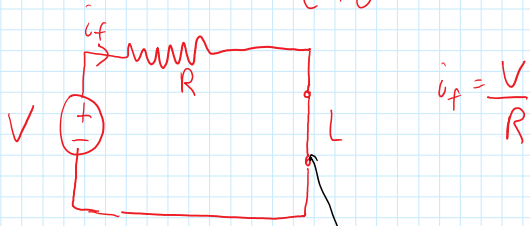


$$i_f = \frac{V}{R}$$

in steady state  $v_L = L \frac{di}{dt}$   
 $= L \frac{di_f}{dt}$   
 $= L \times 0 = 0$

step 3:  $i = i_n + i_f$   
 $= (A e^{-R/L t}) + (\frac{V}{R}) \quad t \geq 0$

step 4:  $t < 0$

$i(0^-)$

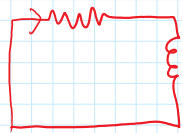

$$i(0^-) = 0 = i(0)$$


$$i(0) = A e^{-R/L(0)} + \frac{V}{R} = 0$$

$$A + \frac{V}{R} = 0$$


$$A = -\frac{V}{R}$$

$$i(t) = -\frac{V}{R} e^{-R/L(t)} + \frac{V}{R}$$


$$= \frac{V}{R} (1 - e^{-R/L(t)}) \text{ A, } t \geq 0$$

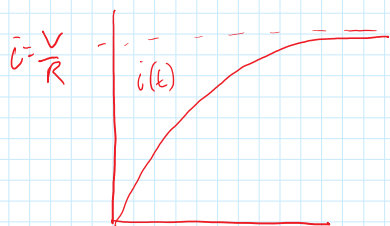

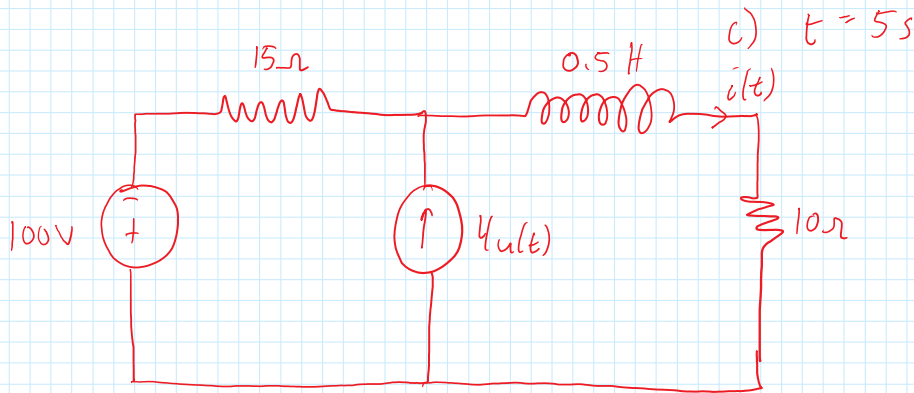Example 2: Find energy stored in the inductor at a)  $t = -10 \text{ ms}$   
 b)  $t = 20 \text{ ms}$



Solution: a)  $t = -10ms$

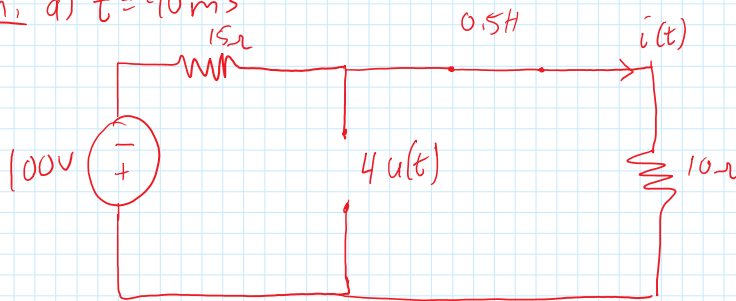


$$\bar{v} = \frac{-100V}{15\Omega + 10\Omega}$$

$$\bar{v} = -4A$$

$$\begin{aligned} \therefore W_L(-10ms) &= \frac{1}{2} L \bar{i}^2 \\ &= \frac{1}{2} (0.5H) (-4A)^2 \\ &= 4J \text{ stored} \end{aligned}$$

(b) and (c) must find complete response  
( $\because t \geq 0$ )


Step 1: find natural response

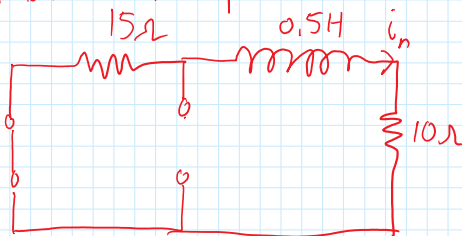

$$\tau = \frac{L}{R_{eq}} = \frac{0.5H}{15\Omega + 10\Omega} = 0.02s$$

$$i_n = Ae^{-t/\tau} = Ae^{-50t}$$

Step 2: Find forced response

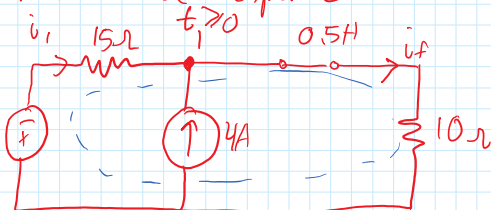

Supermesh

$$100V + 15i_1 + 10i_f = 0$$

KCL at 1

$$i_1 + 4A = i_f$$

$$i_f = -1.6A$$

Step 3:  $i = i_n + i_f = Ae^{-50t} - 1.6 \quad t \geq 0$

Step 4: Solve for A from initial conditions

$$i(0^-) = -4A = i(0) \quad \leftarrow \text{from step 1}$$

$$i(0) = -4 = A - 1.6$$

$$A = -2.4$$

$$i(t) = -2.4e^{-50t} - 1.6 \text{ A}, t \geq 0$$

at  $t = 20 \text{ ms}$

$$i(20 \text{ ms}) = -2.4e^{-50(0.02)} - 1.6$$

$$= -2.483 \text{ A}$$

$$W_L(20 \text{ ms}) = \frac{1}{2} L i^2 = \frac{1}{2} (0.5 \text{ H}) (-2.483 \text{ A})^2 \\ = 1.541 \text{ J}$$

at  $t = 5 \text{ s}$

$$i(5 \text{ sec}) = -2.4e^{-50(5)} - 1.6$$

$$= -1.6 \text{ A}$$

$$W_L(5 \text{ s}) = \frac{1}{2} L i^2 = \frac{1}{2} (0.5 \text{ H}) (-1.6 \text{ A})^2 \\ = 0.64 \text{ J}$$


# RC Examples

Monday, March 6, 2017 8:08 AM


## E: RC Examples
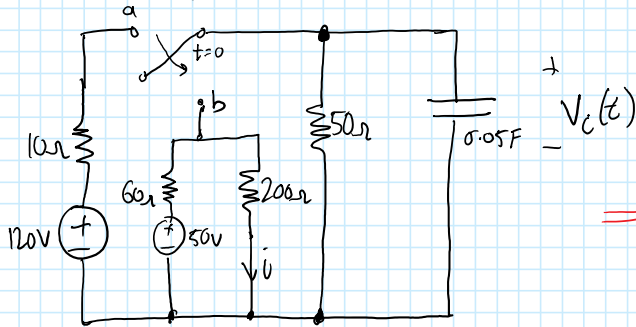
### I. Example 1:

Find  $V_c(t)$  for  $t \geq 0$  in the circuit below



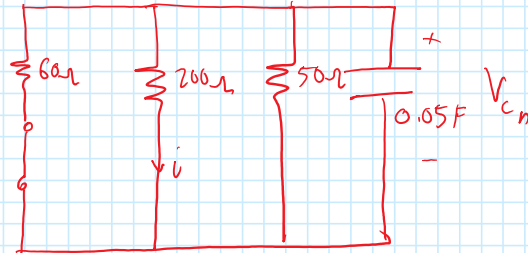Solution: Source free  
Step 1: Find natural response with switch in position b





$$\left(\frac{1}{60} + \frac{1}{200} + \frac{1}{50}\right)^{-1} = R_{eq}$$

$$R_{eq} = 24\Omega \quad \tau = R_{eq}C = (24\Omega)(0.05F) = 1.2 \text{ sec}$$

$$V_{cn}(t) = Ae^{-t/\tau}, t \geq 0$$

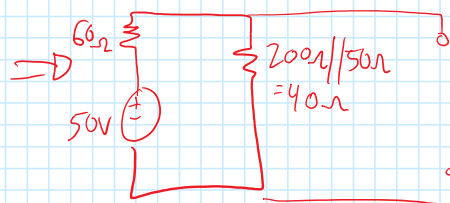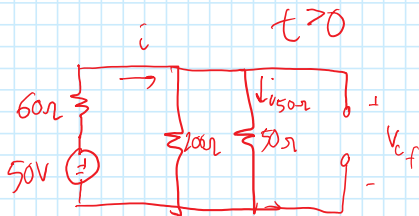Step 2: Find forced or steady-state response



$$i = \frac{50V}{60\Omega + (200\Omega + 50\Omega)} = 0.5A$$

$$V_{cf} = 50V \left( \frac{40\Omega}{40\Omega + 60\Omega} \right) = 20V$$

$$i_{50\Omega} = i \cdot \left( \frac{200\Omega}{200\Omega + 50\Omega} \right) = 0.5 \left( \frac{4}{5} \right) = 0.4 A$$

$$V_{cf} = (50\Omega)(i_{50\Omega}) = 50(0.4) = 20V$$

Step 3: Add the two expressions


$$V_c = V_{cn} + V_{cf} = Ae^{-t/\tau} + 20$$

Step 4: Determine A from initial conditions

At  $t=0^-$


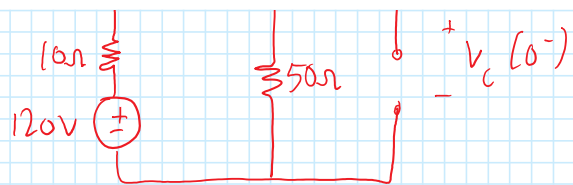
$$V_c(0^-) = 120V \left( \frac{50\Omega}{10\Omega + 50\Omega} \right) = 100V = V_c(0^+) = V_c(0)$$



$$v_c(0^-) = 120V \left( \frac{50\Omega}{10\Omega + 50\Omega} \right) = 100V = v_c(0^-)$$

$$v_c(0) = 100 = Ae^{-0} + 20$$

$$= A + 20$$


$$A = 80 \text{ V}$$

$$v_c(t) = 80e^{-t/1.2} + 20 \text{ Volts}, t \geq 0$$

# Test 1 Review

Tuesday, March 7, 2017 8:03 AM

HW#4 due 3/23

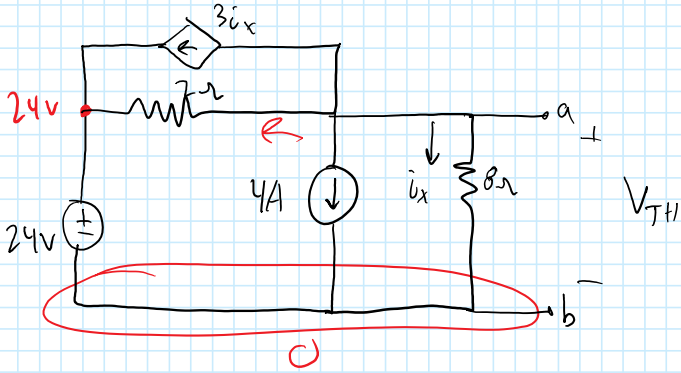


Solu: at  $V_{TH} = V_{ab}$

$$\frac{V_{TH}}{8\Omega} + 4A + 3i_x + \frac{V_{TH} - 24}{2\Omega} = 0 \quad (1)$$

$$i_x = \frac{V_{TH}}{8\Omega} \quad (2)$$


$$V_{TH} = 8V$$

$$R_{TH} = \frac{V_{TH}}{i_{sc}}$$

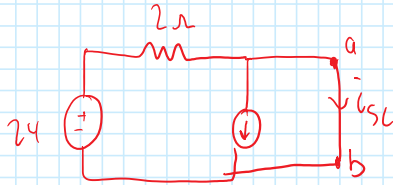


$$4A + i_{sc} - \frac{24}{2\Omega} = 0 \quad i_{sc} = 8A$$

$$R_{TH} = \frac{8V}{8A} = 1\Omega$$

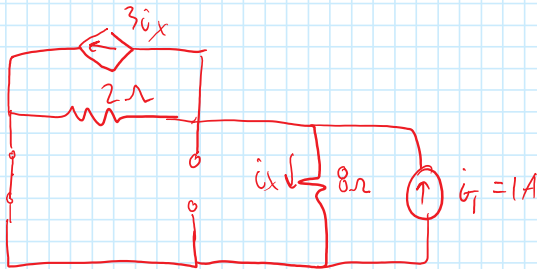


$$\frac{V_T}{2\Omega} + 3i_x + \frac{V_T}{8\Omega} - 1A = 0$$
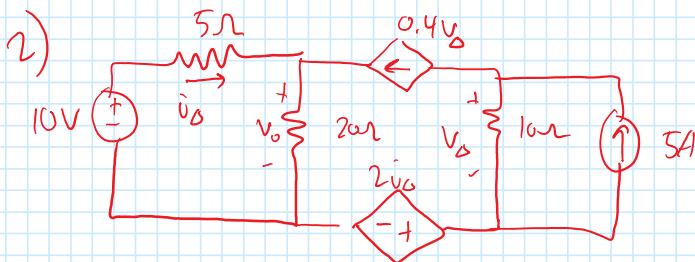
$$i_x = \frac{V_T}{8\Omega} \quad V_T = 1V \quad R_{TH} = \frac{V_T}{i_T} = 1\Omega$$




Consider 10V only

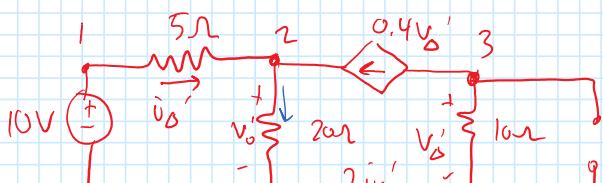

Node 1 = 10V

$$\text{Node 2: } V_1 - V_2 - V_2, 0.4V_1' = 0 \quad (1)$$

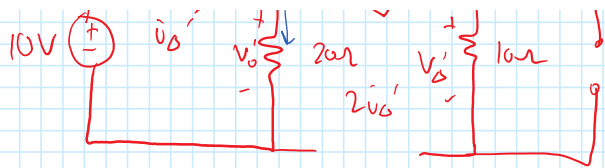


Node 2:  $\frac{V_1 - V_2}{5\Omega} - \frac{V_2}{20\Omega} + 0.4V_{\Delta}' = 0$  (1)

$V_{\Delta}' = -0.4V_{\Delta}' (10\Omega)$  (2)

$V_{\Delta}' = 0$

$V_2 = 0V = V_0'$

Consider SA only:

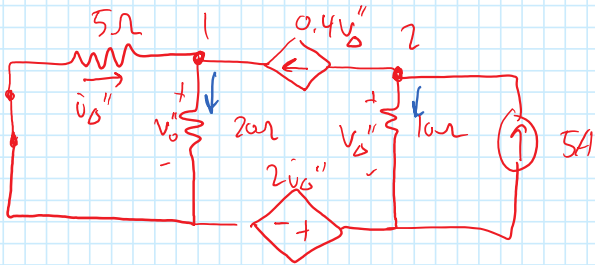


Node 1:  $\frac{V_1}{20\Omega} - \frac{0 - V_1}{5\Omega} - 0.4V_{\Delta}'' = 0$

Node 2:  $0.4V_{\Delta}'' + \frac{V_2 - 2i_0''}{10\Omega} - 5 = 0$

$V_{\Delta}'' = V_2 - 2i_0''$

$i_0'' = \frac{-V_1}{5\Omega}$


$V_1 = 16V = V_0''$

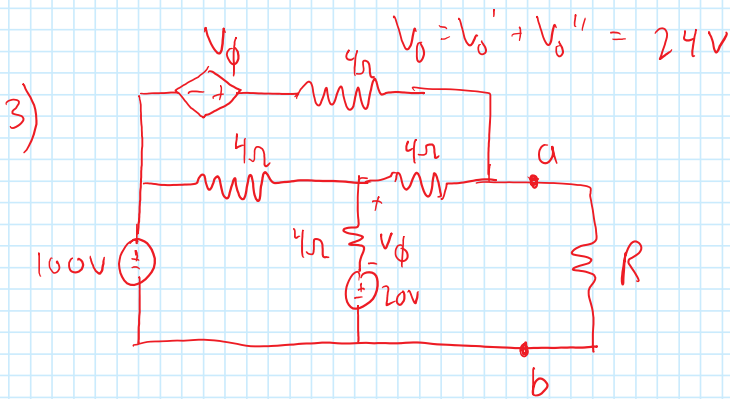

$R = ?$  if max power delivered

$R = R_{TH}$

Solution:

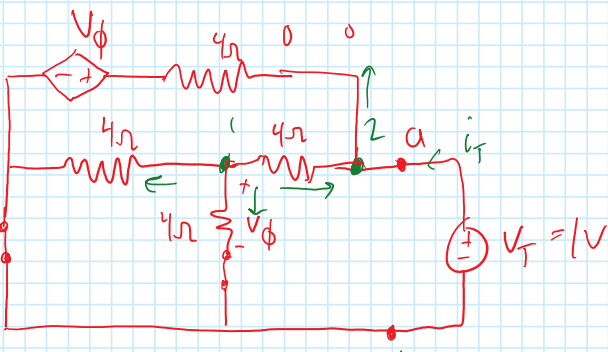


$V_{\phi} = 1V$ , since  $v_{\phi} \parallel V_T$

Node 1:  $\frac{V_1}{4\Omega} + \frac{V_1}{4\Omega} + \frac{V_1 - V_T}{4\Omega} = 0$  (1)

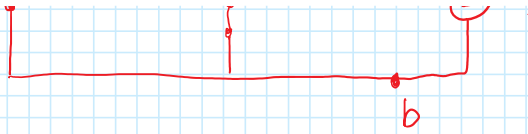Node 2:  $-\left(\frac{V_1 - V_T}{4\Omega}\right) - i_T + \frac{V_T - V_{\phi}}{R} = 0$  (1)






$$\text{Node } 2: \left( \frac{V_1 - V_T}{4\Omega} \right) - i_T + \frac{V_T - V_\phi}{4\Omega} = 0 \quad (1)$$

$$V_1 = 0.333V$$

$$i_T = 0.333A$$

$$R_{TH} = \frac{V_T}{i_T} = \frac{1V}{0.333A} = 3\Omega$$

$$R_{TH} = \frac{V_{TH}}{i_{sc}}$$

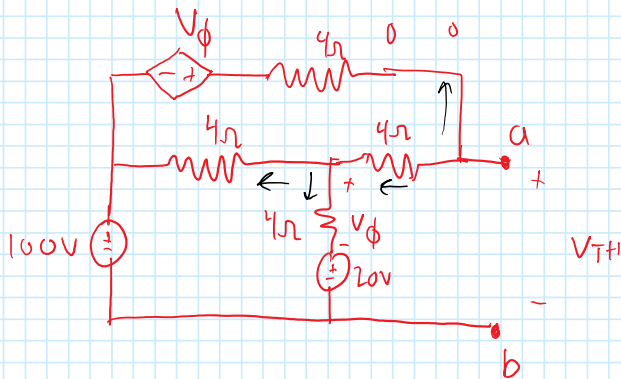


$$\text{At } V_{TH}: \frac{V_{TH} - (100V + V_\phi)}{4\Omega} + \frac{V_{TH} - V_1}{4\Omega} = 0 \quad (1)$$

$$\text{at } V_1: \frac{V_1 - 100}{4\Omega} + \frac{V_1 - 20}{4\Omega} + \frac{V_1 - V_{TH}}{4\Omega} = 0 \quad (2)$$

$$V_\phi = V_1 - 20V$$

$$V_{TH} = 120V$$

$$(3)$$

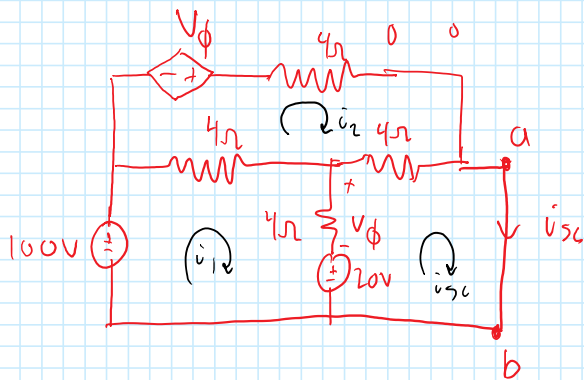

$$\text{Mesh 1: } -100 + 4(i_1 - i_2) + V_\phi + 20 = 0$$

$$\text{Mesh 2: } -V_\phi + 4i_2 + 4(i_2 - i_{sc}) + 4(i_2 - i_1) = 0$$

$$\text{Mesh } i_{sc}: -20 - V_\phi + 4(i_{sc} - i_2) = 0$$

$$V_\phi = 4(i_1 - i_{sc})$$

$$i_{sc} = -40A$$


$$i_1 = 45A$$

$$i_2 = 30A$$

# Complete Response for RC Circuits


Wednesday, March 8, 2017 8:12 AM

Example 2:

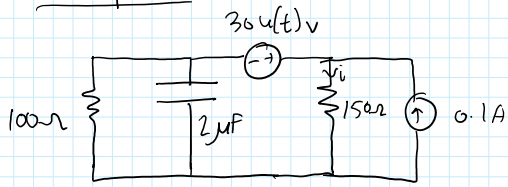

Find  $i(t)$  for  $t \geq 0$

Solu: step 1: Natural response

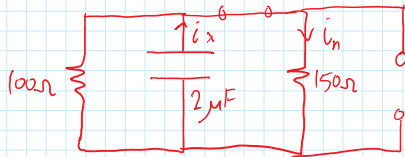

$$i_x = -C \frac{dv_{cn}}{dt} = (-2 \times 10^{-6}) \frac{d}{dt} A e^{-t/\tau} = (2 \times 10^6) = \frac{A}{\tau} e^{-t/\tau}$$

$$R_{eq} = 100\Omega \parallel 150\Omega = 60\Omega$$


$$\tau = R_{eq} C = (2\mu F)(60\Omega) = 1.2 \times 10^{-4} \text{ sec}$$

$$V_{cn} = A e^{-t/\tau} = A e^{-t/1.2 \times 10^{-4} \text{ sec}}$$

$$i_n = i_x \cdot \frac{100\Omega}{100\Omega + 150\Omega} = \frac{4 \times 10^{-2} A}{6} e^{-t/\tau}$$

$$i_n = 0.8 \times 10^{-6} A \frac{e^{-t/\tau}}{\tau}$$

Step 2: Forced Response

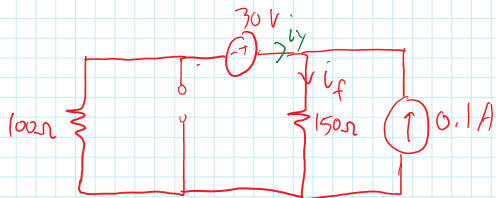


Mesh:  $100i_y - 30V + 150i_f = 0$

KCL:  $i_y + 0.1 = i_f$


$i_f = 0.16A$

or (Source Trans)

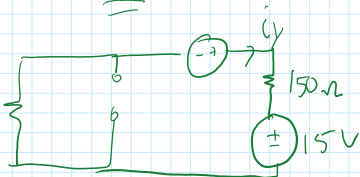

Step 3:  $i = i_n + i_f = 0.8 \times 10^{-6} \frac{A}{\tau} e^{-t/\tau} + 0.16 \quad t \geq 0$

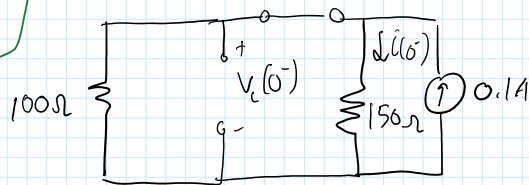Step 4: Solve for A from initial conditions ( $t = 0^-$ )




$$V_c(0^-) = (100\Omega \parallel 150\Omega)(0.1A)$$


$$= 6V$$

$$i(0^-) = \frac{V_c(0^-)}{150\Omega}$$

$$= 0.04A$$

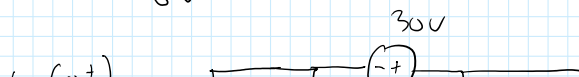

$$= 6V$$

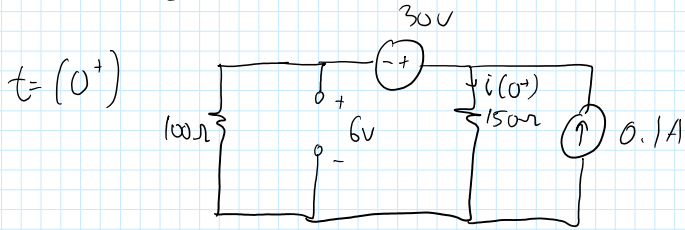

$$6V + 30V - (150)i(0^+) = 0$$

$$i(0^+) = \frac{36V}{150\Omega} = 0.24A = i(0)$$

Pick up  $i(0^+)$  since looking for  $t \geq 0$

greater  
than or  
equal to

$$i(0) = 0.24 = 0.8 \times 10^{-6} \frac{A}{\tau} + 0.16$$


$$\frac{A}{\tau} = 10^5$$

$$i(t) = 0.8 \times 10^{-6} (10^5) e^{-t/1.2 \times 10^{-4}} + 0.16$$

$$i(t) = 0.08 e^{-t/1.2 \times 10^{-4}} + 0.16 \text{ A}, t \geq 0$$



# More RC Examples

Thursday, March 9, 2017 8:00 AM

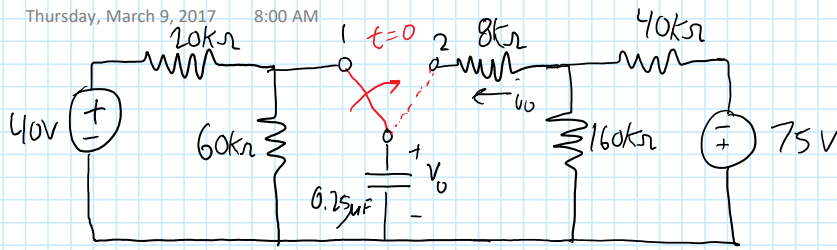

Find  $V_o(t)$  and  $i_o(t)$  for  $t \geq 0$ .

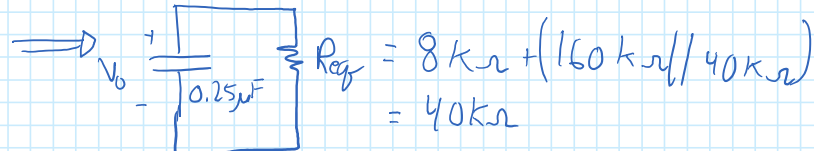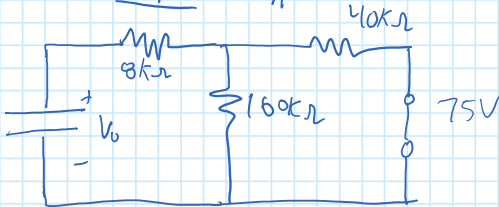Solution - Step 1:  $V_n = ?$  for  $t \geq 0$




$$R_{eq} = 8k\Omega + (160k\Omega // 40k\Omega) = 40k\Omega$$

$$\tau = RC = 40k\Omega (0.25\mu F) = 10 \times 10^{-3} = 0.01$$

$$V_n = Ae^{-t/0.01} = Ae^{-100t}$$


Step 2:  $V_f = ?$

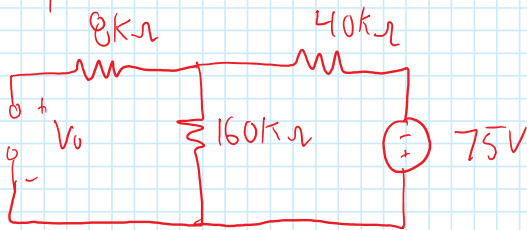

$$V_f = -75 \left( \frac{160k\Omega}{160k\Omega + 40k\Omega} \right) = -60V$$

Step 3:  $V_o = V_n + V_f = Ae^{-100t} - 60, t \geq 0$

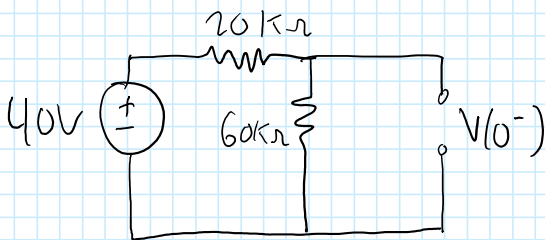Step 4: Find A from initial conditions  $t = 0^-$




$$V(0^-) = 40 \left( \frac{60k\Omega}{20k\Omega + 60k\Omega} \right) = 30V = V(0)$$


$$V(0) = 30 = Ae^0 - 60$$

$$30 = A - 60 \quad A = 90$$
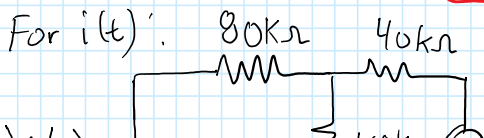
$$V(t) = 90e^{-100t} - 60 \text{ volts, } t \geq 0$$



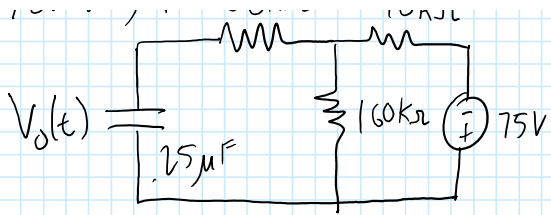
$$i_o(t) = \left( \frac{dv_o(t)}{dt} \right)$$



$$\begin{aligned}
 i_0(t) &= \left( \frac{dV_0(t)}{dt} \right) \\
 &= (0.25 \mu\text{F}) \frac{d}{dt} (90e^{-100t} - 60) \\
 &= (-9000 e^{-100t}) (0.25 \times 10^{-6})
 \end{aligned}$$


# RC With Dependent Source

Monday, March 20, 2017 8:10 AM

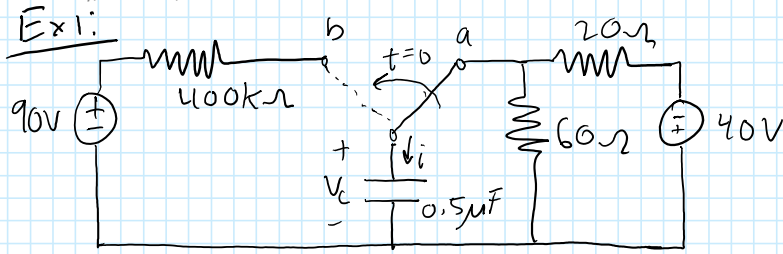

$V_c(t)$  and  $i(t) = ? \quad t \geq 0$

Solution:

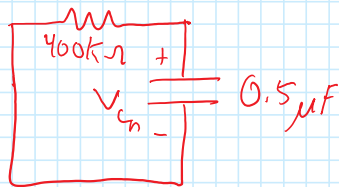


Step 1: Natural Response

$\tau = 400k\Omega (0.5\mu F) = 200 \text{ ms}$


$V_c(t) = Ae^{-t/\tau} = Ae^{-5t} \text{ Volts}$

Step 2: Forced Response

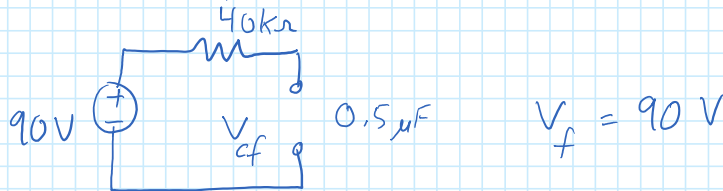

Step 3:  $V_c(t) = V_{cn} + V_{cf} = Ae^{-5t} + 90V, \quad t \geq 0$

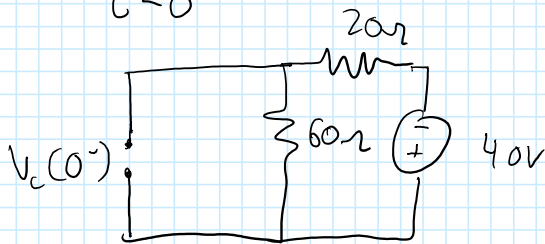Step 4: Using initial conditions to adjust unknown parameter  $t < 0$



$V_c(0^-) = (-40V) \left( \frac{60\Omega}{20\Omega + 60\Omega} \right) = -30V$

$-30V = V_c(0)$

$V_c(0) = Ae^0 + 90 = -30$

$A = -120$

$V_c(t) = 90 - 120e^{-5t} \text{ Volts}, \quad t \geq 0$


$i(t) = C \frac{dV_c(t)}{dt} = (0.5\mu F) \frac{d}{dt} (90 - 120e^{-5t}) = (0.5\mu F) (600e^{-5t})$

$i(t) = (300 \times 10^{-6}) e^{-5t} \text{ Amps}, \quad t \geq 0$

Ex 7.13





$v(t) = ? \quad t \geq 0$

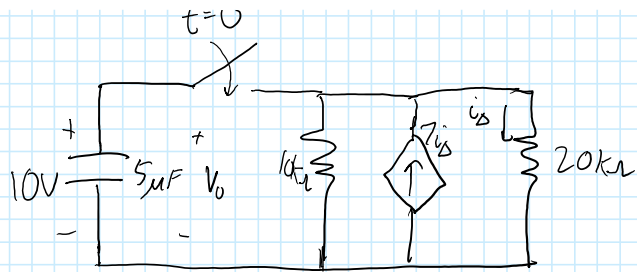


$$V_o(t) = ? \quad t \geq 0$$

Solu:

Step 1: Natural Response  $V_{on}$

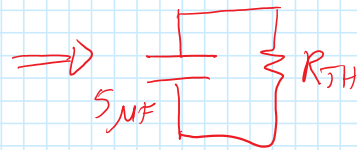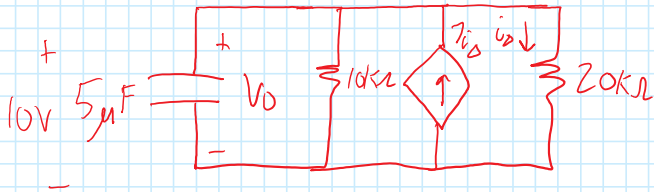

$$\tau = (5\mu F)(R_{TH})$$

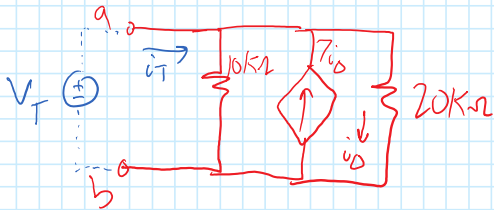

Node A:

$$\dot{i}_T - \frac{V_T}{10k} + 7\dot{i}_D - \dot{i}_D = 0$$

$$\dot{i}_D = \frac{V_T}{20k}$$

$$\dot{i}_T - \frac{V_T}{10k} + \frac{6V_T}{20k} = 0$$

$$\dot{i}_T + \frac{3V_T}{10k} - \frac{V_T}{10k} = 0$$

$$10k \dot{i}_T + 2V_T = 0$$

$$2V_T = -10k \dot{i}_T$$

$$\frac{V_T}{\dot{i}_T} = \frac{-10k}{2} = -5k$$

$$R_{TH} = \frac{V_T}{\dot{i}_T} = -5000\Omega$$

$$\tau = (5\mu F)(-5000) = -0.025$$


$$V_{on} = A e^{-t/\tau} = A e^{40t} \text{ Volts, } t \geq 0$$

Step 2: Forced Response  $V_{of}$

$V_{of} = 0 \text{ V} \rightarrow$  no indep source

Step 3:  $V_{on} + V_{of} = Ae^{40t}$  Volts,  $t \geq 0$

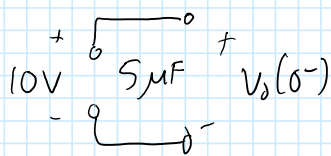Step 4: Use initial conditions to adjust  $A$   
 $t < 0$



$$V_o(0^-) = V_c(0^-) = 10 \text{ V} = V_o(0)$$


$$V_o(0) = 10 \text{ V} = Ae^0 \quad A = 10$$

$$V_o(t) = 10e^{40t} \text{ Volts, } t \geq 0$$




# Find V(t) Across Resistor

Tuesday, March 21, 2017 8:29 AM

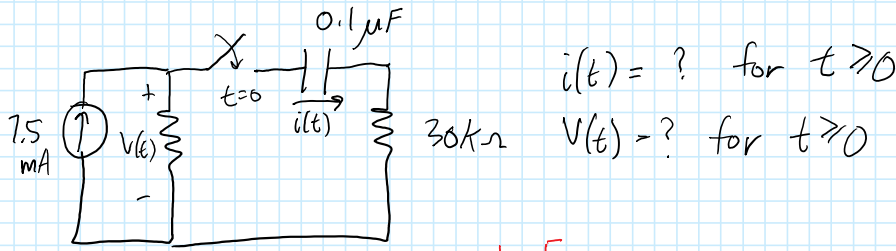


Solu: step 1:

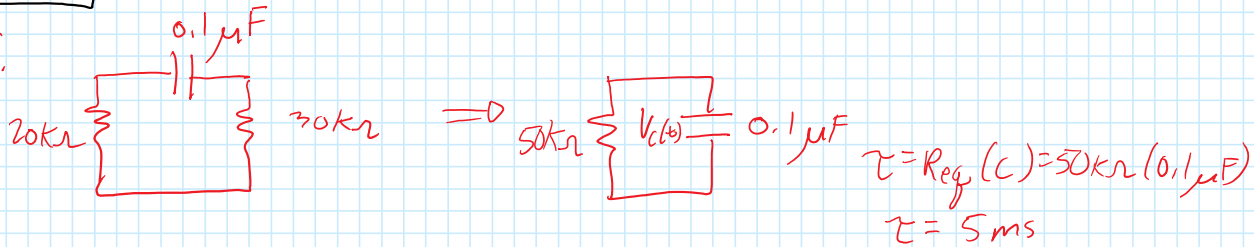

$$V_{cn} = Ae^{-200t}$$


Step 2:

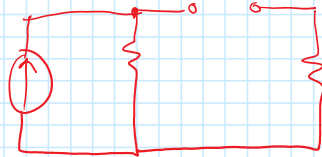

$$V_{cf} = 7.5mA (20k\Omega) = 150V$$

Step 3:  $V_c(t) = V_{cn} + V_{cf} = Ae^{-200t} + 150$  Volts,  $t \geq 0$

Step 4:  $t < 0$

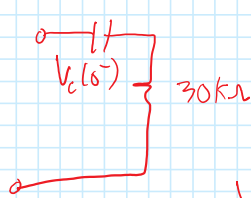


$$V_c(0^-) = 0 = V_c(0)$$



$$0 = A + 150 \quad A = -150$$

$$V_c(t) = 150 - 150e^{-200t} \text{ Volts, } t \geq 0$$

$t \geq 0^+$

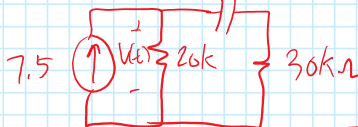

$$V(t) = V_c(t) + i(t) 30k\Omega$$

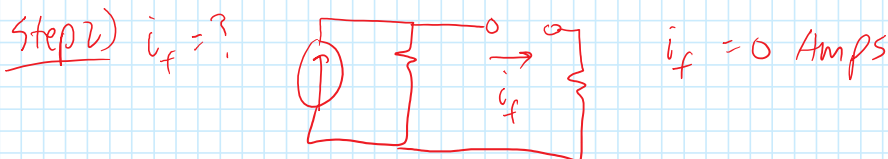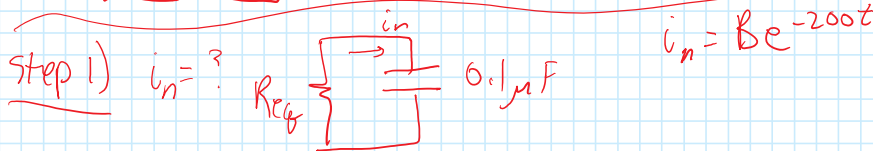


Step 3)  $i(t) = i_n + i_f = B e^{-200t}$

Step 4)



$i_0^- = 0 \text{ Amps} \neq i_0^+$

$t \geq 0^+$

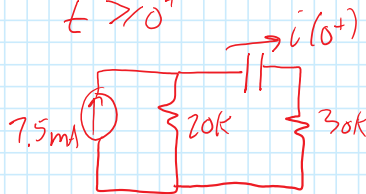

$i(0^+) = 7.5 \text{ mA} \left( \frac{20k\Omega}{50k\Omega} \right) = 3 \text{ mA}$

$i(0^+) = 3 \text{ mA} = B e^{0^+}$

$B = 3 \text{ mA}$

$i(t) = 3 e^{-200t} \text{ mA}, t \geq 0^+$

$V(t) = 150 - 150 e^{-200t} + (0.003 e^{-200t}) (30,000)$

$V(t) = 150 - 150 e^{-200t} + 90 e^{-200t} = \boxed{150 - 60 e^{-200t} \text{ Volts}, t \geq 0^+}$


# Intro to RLC Circuits

Wednesday, March 22, 2017 8:04 AM

- 1) HW#5 due on Tuesday, 4/11 Ch 8: 6, 8, 10, 14, 19, 27, 30, 31, 35, 37, 42, 45, 47, 49, 52, 53
- 2) Read Ch. 8
- 3) Test #2 on Tuesday, 4/18 (16 problems, do 4 a day)

## Ch 8: Transient RLC Networks

### I. Source free Parallel Circuits

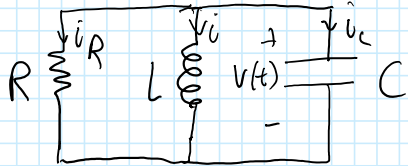

$$v = L \frac{di}{dt}$$

$$v dt = L di$$

$$di = \frac{1}{L} v dt \Rightarrow i = \frac{1}{L} \int_0^t v dt + i(0)$$

### A. Differential Equations

KCL:  $i_R + i_L + i_C = 0$

$$\frac{v(t)}{R} + C \frac{dv(t)}{dt} + \frac{1}{L} \int_0^t v dt + i(0) = 0$$

$$C \frac{d^2 v(t)}{dt^2} + \frac{1}{R} \frac{dv(t)}{dt} + \frac{1}{L} v(t) = 0$$

$$\boxed{\frac{d^2 v(t)}{dt^2} + \frac{1}{RC} \frac{dv(t)}{dt} + \frac{1}{LC} v(t) = 0}$$

### 3 Types of Oscillations

Thursday, March 23, 2017 8:00 AM

$$\frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0 \quad (1)$$

B. Solution of Eq. (1)

1. Characteristic Roots, (eigenvalue)

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0 \quad (2)$$

$$ax^2 + bx + c$$
$$x_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$s_{1,2} = \frac{-\frac{1}{RC} \pm \sqrt{\left(\frac{1}{RC}\right)^2 - 4(1)\left(\frac{1}{LC}\right)}}{2(1)} = \frac{-1}{2RC} \pm \sqrt{\frac{1}{4}\left(\frac{1}{RC}\right)^2 - \frac{1}{LC}} = \frac{-1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$s_1 = \frac{-1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} \quad (3)$$

$$s_2 = \frac{-1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} \quad (4)$$

2. Three Possible Solution Forms


a) Case 1: Overdamped ( $\alpha > \omega_0$ )

$$\alpha = \frac{1}{2RC} \Rightarrow \text{"exponential damping factor"}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow \text{"resonant frequency"}$$

Eq. (3) and (4) have distinct real roots
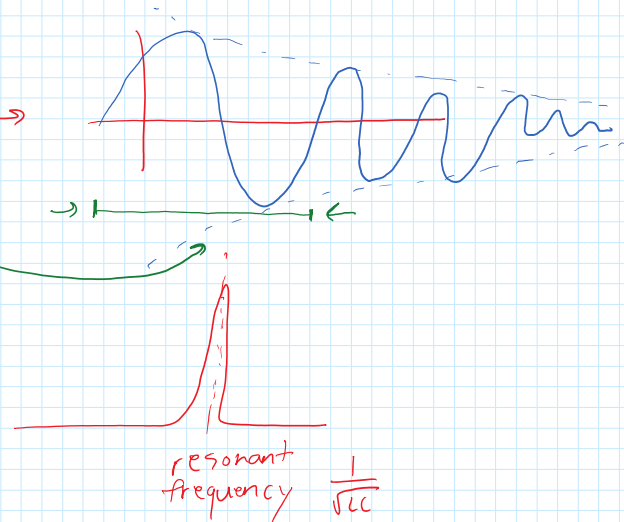
$$\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC} > 0 \quad \alpha^2 > \omega_0^2$$



$$V(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}, \quad t \geq 0$$

where  $s_1 < 0$  and  $s_2 < 0$  (both real)

$A_1$  and  $A_2$  determined by initial conditions

b) Case 2: Critically Damped

Eq. (3) and (4) have same value

$$(s_1 = s_2 \text{ or } \alpha = \omega_0)$$

$$\left(\frac{1}{2RC}\right)^2 = \frac{1}{LC}$$

Solution  $s$  to (1) for this case is

$$V(t) = (A_1 t + A_2) e^{-\alpha t}$$

where  $A_1$  and  $A_2$  are determined by initial conditions

c) Case 3: Underdamped ( $\alpha < \omega_0$ )

Eqs (3) and (4) are complex numbers

$$\left(\frac{1}{2RC}\right)^2 < \frac{1}{LC} \text{ or } \alpha < \omega_0$$

$$s_1 = s_2^* \text{ (complex conjugates)}$$

$$j = \sqrt{-1}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$V(t) = e^{-\alpha t} (\beta_1 \cos \omega_d t + \beta_2 \sin \omega_d t)$$

# Overdamped RLC Parallel

Monday, March 27, 2017 8:00 AM


## II. Circuit Example for Source-Free RLC Networks

### A. Overdamped Case
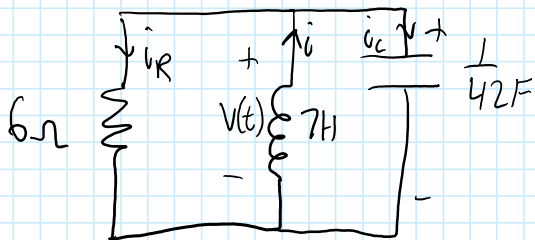
#### 1. Example 1

$$\text{Let } v(0) = 15\text{V}, \quad i(0) = -6\text{A}$$

Find  $A_1, A_2, v(t)$  and  $V_{\min}$  for the following circuit



Solu:

$$\frac{dv^2}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

$$\frac{dv^2}{dt^2} + \frac{1}{6(\frac{1}{42})} \frac{dv}{dt} + \frac{1}{7(\frac{1}{42})} v = 0$$

$$\frac{dv^2}{dt^2} + 7 \frac{dv}{dt} + 6v = 0$$

$$s^2 + 7s + 6$$

$$s_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = \frac{-7 \pm \sqrt{7^2 - 4(1)(6)}}{2(1)} = \frac{-7 \pm \sqrt{25}}{2} = \frac{-7 \pm 5}{2}$$

$$s_1 = \frac{-7+5}{2} = \frac{-2}{2} = -1$$

$$s_2 = \frac{-7-5}{2} = \frac{-12}{2} = -6$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2(6)(\frac{1}{42})} = \frac{7}{2} = 3.5$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{7(1/42)}} = \frac{1}{\sqrt{1/6}} \approx 2.4$$

$\alpha > \omega_0$  Overdamped

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$= A_1 e^{-t} + A_2 e^{-6t}$$

$$v(0) = 15 = A_1 + A_2$$

$$A_1 + A_2 = 15$$

$$i_c = C \frac{dv}{dt} = C \frac{d}{dt} (A_1 e^{-t} + A_2 e^{-6t})$$

$$= C [-A_1 e^{-t} - 6A_2 e^{-6t}]$$

$$i = i_R + i_c$$

$$i_c = i - i_R$$

$$i_c(0) = i(0) - i_R(0)$$

$$\frac{1}{42} [-A_1 - 6A_2] = -6 - \left( \frac{15V}{6\Omega} \right)$$

$$-A_1 - 6A_2 = -6(42) - \left[ \frac{15 \cdot 42}{6} \right]$$

$$-A_1 - 6A_2 = -252 - 105$$

$$-A_1 - 6A_2 = -357$$

$$A_1 + A_2 = 15 \quad (1)$$

$$-A_1 - 6A_2 = -357 \quad (2)$$

$$A_1 = \frac{-267}{5} = -53.4$$

$$A_2 = \frac{342}{5} = 68.4$$

$$v(t) = -53.4 e^{-t} + 68.4 e^{-6t} \text{ Volts, } t \geq 0$$

Shortcut:  $i_c = C \frac{dv}{dt}$

$$\frac{dv}{dt} = \frac{i_c}{C} = \frac{i - i_R}{C}$$

$$\boxed{\frac{dv}{dt} = \frac{i - i_R}{C}} \text{ at } t=0$$

→ natural response of circuit

$$V_{\min} : V'(t) = 0$$

$$\frac{dV}{dt} = 53.4e^{-t} - 6(68.4)e^{-6t}$$

$$53.4e^{-t} - 410.4e^{-6t} = 0$$

$$53.4e^{-t} = 410.4e^{-6t}$$

$$53.4 = 410.4e^{-5t}$$

$$e^{-5t} = \frac{53.4}{410.4}$$

$$-5t = \ln \left[ \frac{53.4}{410.4} \right]$$

$$-5t = -2.0393$$

$$t = 0.40786 \text{ sec (time at } V_{\min})$$

$$V(0.40786) = -53.4e^{-0.40786} + 68.4e^{-6(0.40786)}$$


$$V_{\min} = -29.6 \text{ Volts}$$



# Critically Damped RLC Parallel

Tuesday, March 28, 2017 8:06 AM

## B. Critically Damped 1. Example 1

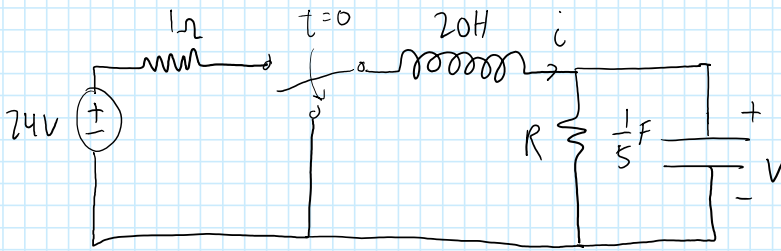

Given that the circuit is critically damped,  
Find  $R$ ,  $i(0^+)$ ,  $V(0^+)$ ,  $v(t)$

Solu:  $\alpha = \omega_0$

$$\frac{1}{2RC} = \frac{1}{\sqrt{LC}}$$

$$\frac{1}{(2RC)^2} = \frac{1}{LC}$$

$$LC = 4R^2C^2$$

$$R^2 = \frac{LC}{4C^2} = \frac{L}{4C}$$


$$R = \frac{1}{2} \sqrt{\frac{L}{C}} = \frac{1}{2} \sqrt{\frac{20}{1/5}} = 5\Omega$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2(5)(1/5)} = 0.5$$

$$V(t) = (A_1 t + A_2) e^{-\alpha t}$$

$$V(t) = (A_1 t + A_2) e^{-0.5t}$$

Assume  $t=0^-$

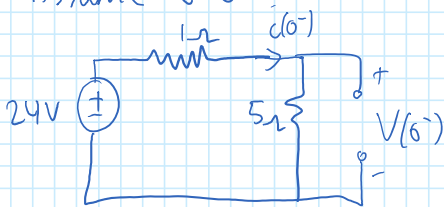


$$i = \frac{24V}{6\Omega} \quad i(0^-) = 4A$$

$$V = 24V \left( \frac{5\Omega}{5\Omega + 1\Omega} \right) = 24 \left( \frac{5}{6} \right) = 20V$$

$$V(0^-) = 20V$$

Now, let  $t=0^+$

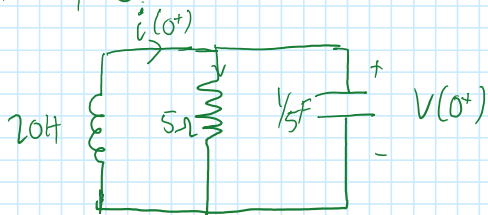

$$i(0^+) = i(0^-) = 4A = i(0)$$

$$V(0^+) = V(0^-) = 20V = V(0)$$

$$V(0) = 20 = (A_1 \cdot 0 + A_2) e^{-\alpha \cdot 0}$$

$$A_2 = 20$$

$$V(t) = (A_1 t + 20) e^{-0.5t}$$

$$i_C = C \frac{dV}{dt} \Rightarrow \frac{dV}{dt} \Big|_{t=0} = \frac{i_C(0)}{C} = \frac{i(0) - i_R(0)}{C} = \frac{4A - \frac{20V}{5\Omega}}{1/5F} = 0$$

$$\frac{dV}{dt} = \frac{d}{dt} (A_1 t + 20) e^{-0.5t} = A_1 [t(-0.5e^{-0.5t}) + e^{-0.5t}] + 20(-0.5)e^{-0.5t} \Big|_{t=0}$$

$$\frac{dV}{dt} = \frac{d}{dt} (A_1 t + 20) e^{-0.5t} = A_1 \left[ t(-0.5e^{-0.5t}) + e^{-0.5t} \right] + 20(-0.5)e^{-0.5t} \Big|_{t=0}$$
$$= A_1 - 10 = 0$$
$$A_1 = 10$$



$$V(t) = (10t + 20) e^{-0.5t} \text{ Volt}, t \geq 0$$

$$V(2) = (10 \cdot 2 + 20) e^{-0.5(2)} = 14.72 \text{ V}$$

# Underdamped RLC Parallel

Wednesday, March 29, 2017 8:03 AM

C. Underdamped  
1. Example 1

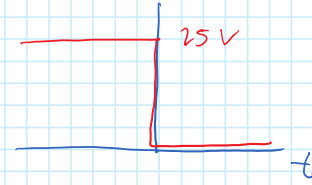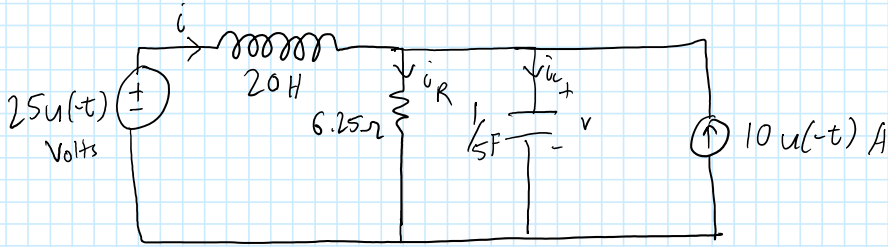

Solution: Let  $t > 0$ , then  $u(-t) = 0$



$$\alpha = \frac{1}{2RC} = \frac{1}{2(6.25\Omega)(1/5F)} = 0.4$$


$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20H(1/5F)}} = 0.5$$

Since  $\alpha < \omega_0$ , circuit is underdamped

$$V(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{(0.5)^2 - (0.4)^2} = 0.3$$

At  $t = 0^-$ ,

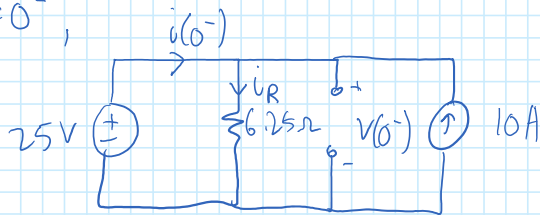

$$V(0^-) = 25V$$


$$i_R(0^-) = \frac{25V}{6.25\Omega} = 4A$$

$$i(0^-) + 10A - i_R(0^-) = 0$$

$$i(0^-) = i_R(0^-) - 10 = 4 - 10$$

$$i(0^-) = -6A$$

Let  $t = 0^+$

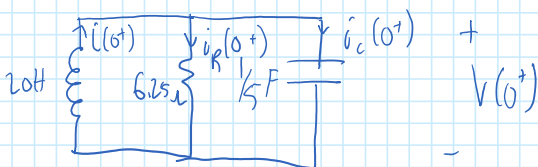

$$i(0^-) = i(0^+) = i(0) = -6A$$

$$V(0^+) = V(0^-) = V(0) = 25V$$

$$v(0) = e^0 (B_1 \cos 0 + B_2 \sin 0) = 25$$

$$B_1 = 25$$

$$v(t) = e^{-0.4t} (25 \cos 0.3t + B_2 \sin 0.3t)$$

$$i_C = C dv$$

$$\left. \frac{dV}{dt} \right|_{t=0} = \frac{i_C(0)}{C} = \frac{i(0) - i_R(0)}{C} = \frac{-6 - \frac{25V}{6.25\Omega}}{1/5F} = -50$$

$$\begin{aligned} \frac{dV}{dt} &= \frac{d}{dt} \left[ e^{-0.4t} (25 \cos 0.3t + B_2 \sin 0.3t) \right] \\ &= e^{-0.4t} (-7.5 \sin 0.3t + 0.3B_2 \cos 0.3t) - 0.4e^{-0.4t} (25 \cos 0.3t + B_2 \sin 0.3t) \end{aligned}$$

$$\text{at } t=0, \frac{dV}{dt} = 0.3B_2 - 0.4(25)$$

$$0.3B_2 - 0.4(25) = -50$$

$$B_2 = -133.3$$

$$V(t) = e^{-0.4t} (25 \cos(0.3t) - 133.3 \sin(0.3t)) \text{ Volts, } t \geq 0$$

$$V(2) = e^{-0.4(2)} (25 \cos(0.3 \cdot 2) - 133.3 \sin(0.3 \cdot 2))$$

$$V(2) = -24.5 \text{ Volts}$$


## Overdamped RLC Series

Thursday, March 30, 2017 8:14 AM

### III. Source-Free Series Circuit
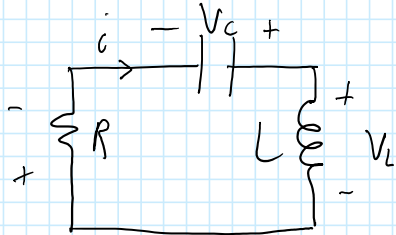
#### A. Differential equation

$$\text{Let } v_c(t_0) = V_0, \quad i(t_0) = I$$



$$L \frac{di}{dt} + Ri + \frac{1}{C} \int_0^t i dt + v_c(t_0) = 0$$

$\underbrace{\hspace{1.5cm}}_{V_L} \quad \underbrace{\hspace{1.5cm}}_{V_R} \quad \underbrace{\hspace{2.5cm}}_{V_C}$

KVL:  $CV = Q \quad V = \frac{1}{C} Q$

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0 \quad (1)$$

#### B. Solution of Equ (1)

##### 1. Characteristic Roots

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

Roots are

$$s = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - 4\left(\frac{1}{LC}\right)}}{2}$$

$$\text{or } s_1 = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \quad (2)$$

$$s_2 = \frac{-R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \quad (3)$$

$$\alpha = \frac{R}{2L} \quad \text{exponential damping factor}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \text{resonant frequency}$$

## 2. Three Possible Solutions

a) Case 1: Overdamped ( $\alpha > \omega_0$ )

(2) and (3) have distinct real roots

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

b) Case 2: Critically Damped ( $\alpha = \omega_0$ )

$$i(t) = (A_1 t + A_2) e^{-\alpha t}$$

c) Case 3: Underdamped ( $\alpha < \omega_0$ )


$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

## IV. Circuit Example for Source-Free series RLC network

A. Overdamped Case

1. Example 1

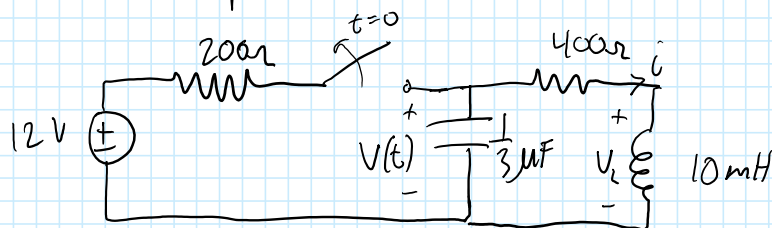

Find  $V(0^+)$ ,  $i(0^+)$ ,  $v(0.1 \text{ ms})$

Solu: By (1) when  $t > 0$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

check with case:

$$\alpha = \frac{R}{2L} = \frac{400\Omega}{2(10 \times 10^{-3} \text{H})} = 20,000$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(10 \times 10^{-3} \text{H})(1/3 \times 10^{-6} \text{F})}} = 17,320.5$$

$\therefore \alpha > \omega_0 \rightarrow$  overdamped


$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\text{where } s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -2 \times 10^4 + \sqrt{(2 \times 10^4)^2 - (1.73205 \times 10^4)^2} = -1 \times 10^4$$

$$\text{where } s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -2 \times 10^4 + \sqrt{(2 \times 10^4)^2 - (1.73205 \times 10^4)^2} = -1 \times 10^4$$


$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -2 \times 10^4 - \sqrt{(2 \times 10^4)^2 - (1.73205 \times 10^4)^2} = -3 \times 10^4$$

Determine initial conditions

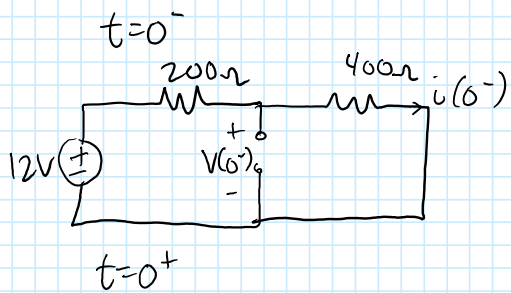

$$V(0^-) = 12V \left( \frac{400\Omega}{400\Omega + 200\Omega} \right) = 8V$$
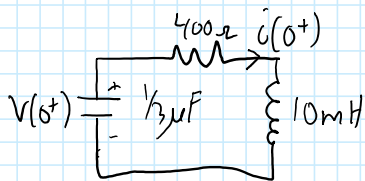
$$i(0^-) = \frac{12V}{200\Omega + 400\Omega} = 0.02A$$



$$V(0^+) = V(0^-) = 8V = V(0)$$

$$i(0^+) = i(0^-) = 0.02A = i(0)$$

$$i(0) = 0.02 = A_1 e^0 + A_2 e^0$$

$$A_1 + A_2 = 0.02$$

$$A_2 = 0.02 - A_1$$

$$i(t) = A_1 e^{s_1 t} + (0.02 - A_1) e^{s_2 t}$$

$$V_L = L \frac{di}{dt} \quad \left. \frac{di}{dt} \right|_{t=0} = \frac{1}{L} V_L \Big|_{t=0} = \frac{V_L}{L} \Big|_{t=0} = \frac{V(0) - 400\Omega [i(0^+)]}{10 \times 10^{-3} H} = \frac{8 - 400(0.02)}{10 mH} = 0$$

## Critically Damped RLC Series

Monday, April 3, 2017 8:03 AM

$$i(t) = A_1 e^{s_1 t} + \underbrace{(0.02 - A_1)}_{A_2} e^{s_2 t}$$

$$\left. \frac{di}{dt} \right|_{t=0} = \frac{V_L(0)}{L} = \frac{V(0) - 400 \Omega (i_L(0))}{0.01 \text{ H}} = \frac{8 - (400)(0.02)}{0.01} = 0$$

$$\text{also: } \left. \frac{di}{dt} \right|_{t=0} = \left. \frac{d}{dt} \left( A_1 e^{s_1 t} + (0.02 - A_1) e^{s_2 t} \right) \right|_{t=0}$$

$$= s_1 A_1 e^{s_1 t} + (0.02 - A_1) s_2 e^{s_2 t} \Big|_{t=0}$$

$$= s_1 A_1 + (0.02 - A_1) s_2$$

$$0 = -10^4 A_1 + (0.02 - A_1) (-3 \times 10^4)$$

$$A_1 + (0.02 - A_1) 3 = 0$$

$$A_1 = 0.03$$

$$i(t) = 0.03 e^{-10^4 t} - 0.01 e^{-3 \times 10^4 t} \quad \text{Amps, } t \geq 0$$

$$V_L(t) = L \frac{di}{dt} = (0.01 \text{ H}) \frac{d}{dt} \left( 0.03 e^{-10^4 t} - 0.01 e^{(-3 \times 10^4)t} \right)$$

$$= (0.01) \left[ -3 \times 10^2 e^{-10^4 t} + 3 \times 10^2 e^{(-3 \times 10^4)t} \right]$$

$$V_L(t) = 3 \left( -e^{-10^4 t} + e^{(-3 \times 10^4)t} \right)$$

$$V(t) = (400 \Omega) i(t) + V_L(t)$$

$$= 400 \left[ 0.03 e^{-10^4 t} - 0.01 e^{(-3 \times 10^4)t} \right] + 3 \left( -e^{-10^4 t} + e^{(-3 \times 10^4)t} \right)$$

$$V(t) = 9 e^{-10^4 t} - e^{(-3 \times 10^4)t} \quad \text{Volts, } t \geq 0$$

$$V(0.1 \text{ ms}) = 9 e^{-10^4 (0.1 \times 10^{-3})} - e^{(-3 \times 10^4) (0.1 \times 10^{-3})}$$


$$= 3.31083 \text{ Volts} - 0.649787 \text{ Volts}$$

$$V(0.1 \text{ ms}) = 3.261 \text{ V}$$

B. Critically Damped Case



1. Example 1:

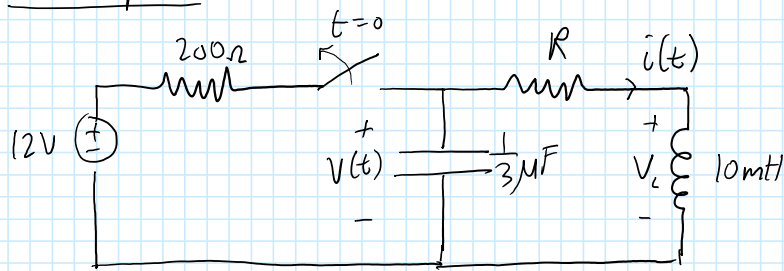

Find  $R = ?$   
 $i(t) = ? \quad t \geq 0$

Solu:

$$\alpha = \omega_0$$

$$\frac{R}{2L} = \frac{1}{\sqrt{LC}}$$


$$R = \frac{2L}{\sqrt{LC}} = 2\sqrt{\frac{L}{C}} = 2\sqrt{\frac{10 \times 10^{-3} \text{H}}{1/3 \times 10^{-6} \text{F}}}$$

$$R = 346.41 \Omega$$

Since critically damped:

$$i(t) = (A_1 t + A_2) e^{-\alpha t}, \quad t \geq 0$$
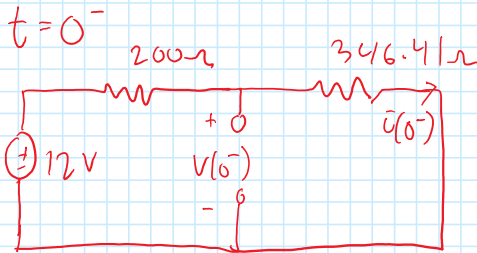
$$\text{where } \alpha = \frac{R}{2L} = \frac{346.41 \Omega}{2(10 \times 10^{-3} \text{H})} = 17,320.5$$




$$v(0^-) = 12V \left( \frac{346.41 \Omega}{200 \Omega + 346.41 \Omega} \right)$$

$$v(0^-) = 7.6077 \text{ V}$$

$$i(0^-) = \frac{12V}{200 \Omega + 346.41 \Omega}$$

$$i(0^-) = 0.022 \text{ A}$$

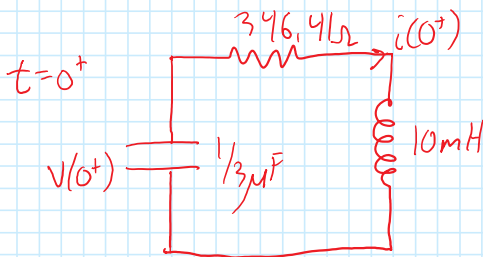

$$v(0^+) = v(0^-) = 7.6077 \text{ V} = v(0)$$

$$i(0^+) = i(0^-) = 0.022 \text{ A} = i(0)$$

$$i(0) = 0.022 \text{ A} = (A_1(0) + A_2) e^{-0}$$

$$A_2 = 0.022$$

$$\therefore i(t) = (A_1 t + 0.022) e^{-17,320.5 t}$$

$$\left. \frac{di}{dt} \right|_{t=0} = \left. \frac{v_L}{L} \right|_{t=0} = \frac{v(0) - (346.41 \Omega) i(0)}{L} = \frac{7.6077 - 346.41(0.022)}{0.01} = -1.332$$

$u = 0 \quad L \quad t > 0$

$L$

$0.01$

$$\frac{di}{dt} = \frac{d}{dt} \left[ (A_1 t + 0.022) e^{-17,320.5t} \right]$$

$$= (A_1 t + 0.022)(-17,320.5) e^{-17,320.5t} + A_1 e^{-17,320.5t} \Big|_{t=0}$$

$$= -381.05 + A_1$$

$$-381.05 + A_1 = -1.332$$

$$A_1 = 379.7$$

$$i(t) = (379.7t + 0.022) e^{-17,320.5t} \quad \text{Amps, } t \geq 0$$

# Complete Response of RLC Circuits

Tuesday, April 4, 2017 8:12 AM

## IV. Complete Response of RLC Circuits

### A. Analysis Procedure

1. Find general form of natural response ( $V_n$  or  $i_n$ ) without solving for all unknown coefficients (set all independent sources =  $\emptyset$ )
2. Find forced or steady-state response ( $V_f$  or  $i_f$ )
3. Add the two expressions


$$V = V_n + V_f$$

or,  $i = i_n + i_f$

4. Adjust unknown coefficients to satisfy initial condition.


### B. Sample Problems

#### 1. Example 1

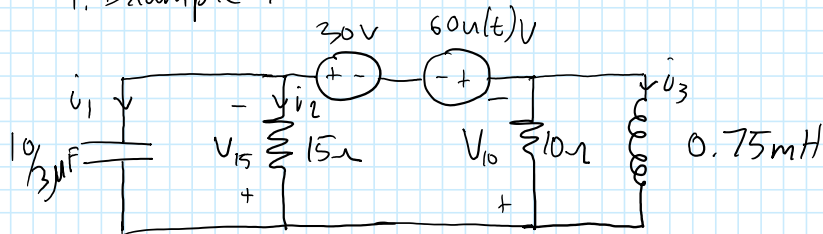

Solve for  $i_1, i_2, i_3, t \geq 0$

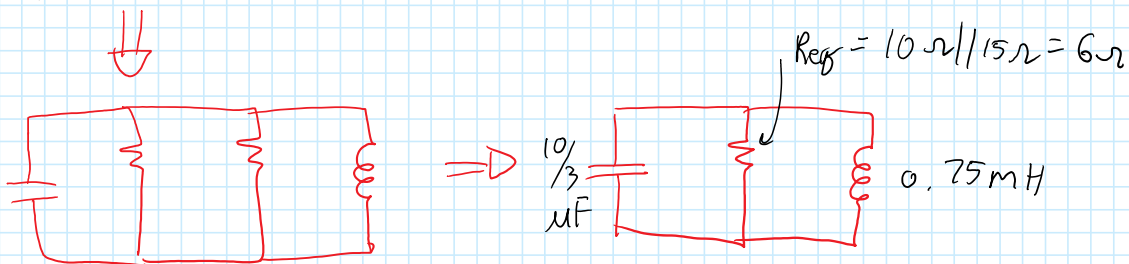Solu: Step 1: Natural Response for  $t > 0$  parallel RLC form



Parallel RLC, so  $\alpha = \frac{1}{2RC} = \frac{1}{2(6\Omega)(10/3\mu F)} = 2.5 \times 10^4$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(0.75mH)(10/3\mu F)}} = 2 \times 10^4$$

Since  $\alpha > \omega_0$ , response is overdamped


$$V_n(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -(2.5 \times 10^4) + \sqrt{(2.5 \times 10^4)^2 - (2 \times 10^4)^2} = -10^4$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -(2.5 \times 10^4) - \sqrt{(2.5 \times 10^4)^2 - (2 \times 10^4)^2} = -4 \times 10^4$$

$$V_h(t) = A_1 e^{(-10^2)t} + A_2 e^{(-4 \times 10^4)t}$$

Step 2: Find forced response

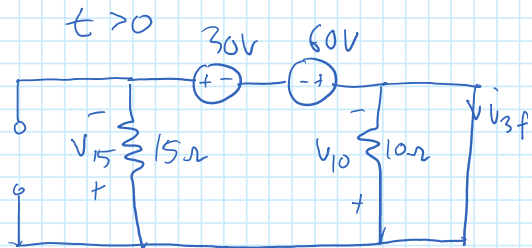

$$V_{10f} = 0 \text{ V, due to short}$$

$$V_{15f} = 30 \text{ V}$$

$$i_{3f} = \frac{(-30 \text{ V}) - (-60 \text{ V})}{15 \Omega} = \frac{30}{15} = 2 \text{ A}$$


$$i_{2f} = -i_{3f} = -2 \text{ A}$$

$$i_{1f} = 0$$

# Cont. of Complete RLC Response

Wednesday, April 5, 2017 8:04 AM

## Example 1:

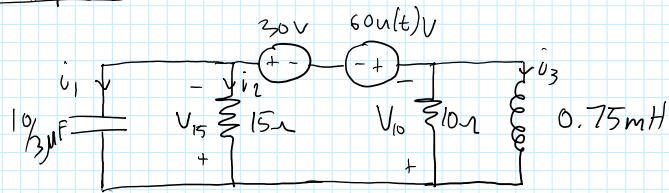

Solve for  $i_1, i_2, i_3, t \geq 0$

Solution:

Step 1: Natural response

$$\alpha = \frac{1}{2RC} = 2.5 \times 10^4$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 2 \times 10^4$$


$\alpha > \omega_0$  overdamped

$$s_1 = \alpha + \sqrt{\alpha^2 - \omega_0^2} = -10^4$$

$$s_2 = \alpha - \sqrt{\alpha^2 - \omega_0^2} = -4 \times 10^4$$

$$V_n(t) = A_1 e^{-10^4 t} + A_2 e^{(-4 \times 10^4)t}$$

Step 2: Forced Response

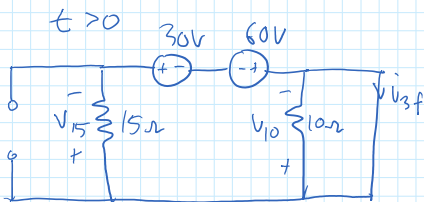

$$V_{10f} = 0V$$

$$V_{15f} = 30V$$

$$i_{2f} = 2A$$


Step 3: Add responses

$$V_{10}(t) = V_{10f} + V_n = A_1 e^{-10^4 t} + A_2 e^{(-4 \times 10^4)t}$$

$$V_{15}(t) = V_{15f} + V_n = A_1' e^{-10^4 t} + A_2' e^{(-4 \times 10^4)t} + 30$$

Step 4: Adjust  $A_1, A_2, A_1', A_2'$  to satisfy initial conditions

$t = 0^-$

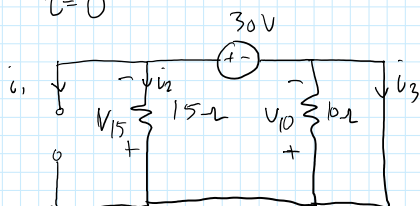


$$i_3(0^-) = \frac{-30V}{15\Omega} = -2A$$

$$V_{15}(0^-) = -30V$$

$$V_{10}(0^-) = 0V$$

$t=0^+$

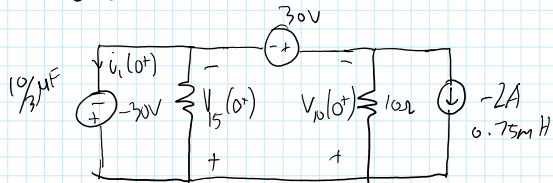

$$i_3(0^+) = -2A$$

$$V_{15}(0^+) = -30V$$

$$-V_{15}(0^+) + 30V + V_{10}(0^+) = 0 \quad (\text{KVL})$$

$$-(-30V) + 30V + V_{10}(0^+) = 0$$

$$V_{10}(0^+) = -60V$$

$$V_{10}(0^+) = A_1 e^{0^+} + A_2 e^{0^+} = -60$$

$$A_1 + A_2 = -60$$

$$A_2 = -A_1 - 60$$

$$V_{10}(t) = A_1 e^{-10^4 t} - (A_1 + 60) e^{(-4 \times 10^4)t}$$

$$V_{15}(0^+) = 30 + A_1' e^{0^+} + A_2' e^{0^+} = -30$$

$$30 + A_1' + A_2' = -30$$

$$A_1' + A_2' = -60$$

$$A_2' = -A_1' - 60$$

$$V_{15}(t) = 30 + A_1' e^{-10^4 t} - (A_1' + 60) e^{(-4 \times 10^4)t}$$

$$i_1 = -C \frac{dV_{15}}{dt} \Rightarrow \left. \frac{dV_{15}}{dt} \right|_{t=0^+} = \frac{-i_1(0^+)}{C} = - \frac{\left[ \frac{V_{15}(0^+)}{15\Omega} + \frac{V_{10}(0^+)}{10\Omega} + 2 \right]}{10/3 \times 10^{-6}} = - \frac{\left[ \frac{-30V}{15\Omega} + \frac{-60V}{10\Omega} + 2 \right]}{10/3 \times 10^{-6}}$$

$$= 1.8 \times 10^6$$

$$\left. \frac{dV_{15}}{dt} \right|_{t=0} = \frac{d(30 + A_1' e^{-10^4 t} + A_2' e^{(-4 \times 10^4)t})}{dt} = (-10^4 t)(A_1') e^{-10^4 t} + A_2' (-4 \times 10^4) e^{(-4 \times 10^4)t} \Big|_{t=0}$$

$$= 3 \times 10^4 A_1' + 2.4 \times 10^6$$

$$3 \times 10^4 A_1' + 2.4 \times 10^6 = 1.8 \times 10^6 \Rightarrow A_1' = -20$$

# Finished Complete RLC Response

Thursday, April 6, 2017 8:02 AM


$$V_{15}(t) = 30 - 20e^{-10^4 t} - 40e^{(-4 \times 10^4)t} \text{ Volts, } t \geq 0$$

$$v_2(t) = \frac{-V_{15}(t)}{15\Omega} = \frac{30 - 20e^{-10^4 t} - 40e^{(-4 \times 10^4)t}}{15}$$

$$i_2(t) = -2 + \frac{4}{3}e^{-10^4 t} - \frac{8}{3}e^{(-4 \times 10^4)t} \text{ Amps, } t \geq 0$$

$$\dot{i}_1(t) = C \frac{dV_{15}}{dt} = \left(\frac{-10}{3} \times 10^6\right) \frac{d}{dt} \left(30 - 20e^{-10^4 t} - 40e^{(-4 \times 10^4)t}\right)$$

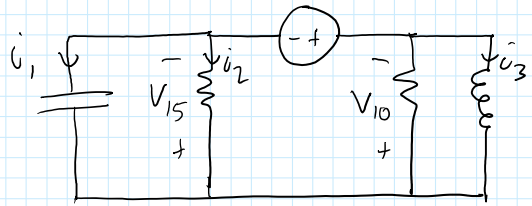
$$i_1(t) = \frac{-2}{3}e^{-10^4 t} - \frac{16}{3}e^{(-4 \times 10^4)t} \text{ Amps, } t \geq 0$$



Since  $V_{10}(t) = -L \frac{di_3}{dt}$  negative due to polarity of 10Ω resistor

$$\begin{aligned} i_3(t) &= \frac{-1}{L} \int_0^t V_{10}(t) dt + i_3(0^+) \\ &= \frac{-1}{L} \int_0^t [A_1 e^{-10^4 t} - (A_1 + 60) e^{-4 \times 10^4 t}] dt + i_3(0^+) \\ &= \frac{-1}{L} \left[ \frac{A_1 (e^{-10^4 t} - 1)}{-10^4} - \frac{(A_1 + 60) (e^{-4 \times 10^4 t} - 1)}{-4 \times 10^4} \right] - 2 \end{aligned}$$
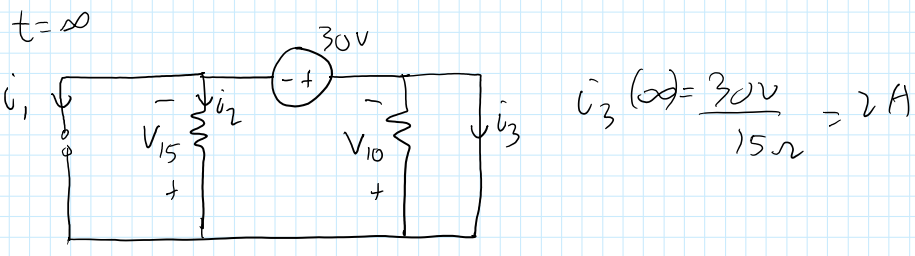
$$i_3(\infty) = 2A = \frac{30V}{15\Omega}$$



$$i_3(\infty) = \frac{-1}{L} \left[ \frac{A_1 (e^{-\infty} - 1)}{-10^4} - \frac{(A_1 + 60) (e^{-\infty} - 1)}{-4 \times 10^4} \right] - 2$$

$$i_3(\infty) = -\frac{1}{L} \left[ \frac{A_1(e^{-\infty} - 1)}{-10^4} - \frac{(A_1 + 60)(e^{-\infty} - 1)}{-4 \times 10^4} \right] - 2$$



$$i_3(\infty) = -\frac{1}{L} \left[ \frac{A_1}{10^4} - \frac{A_1 + 60}{4 \times 10^4} \right] - 2 = 2$$

$$\frac{-1}{0.75 \times 10^{-3}} \left[ \frac{A_1}{10^4} - \frac{A_1 + 60}{4 \times 10^4} \right] - 2 = 2$$


$$A_1 = -20$$

$$i_3(t) = -\frac{1}{0.75 \times 10^{-3}} \left[ \frac{-20(e^{-10^4 t} - 1)}{-10^4} - \frac{(-20 + 60)(e^{-4 \times 10^4 t} - 1)}{-4 \times 10^4} \right] - 2$$
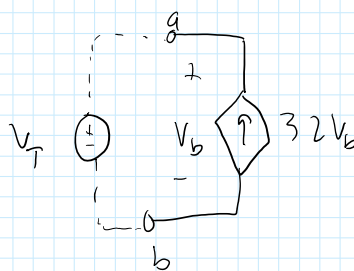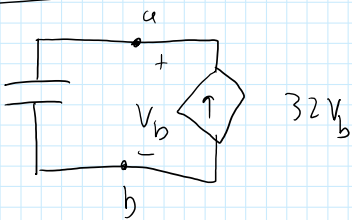
$$i_3(t) = -\frac{8}{3} e^{-10^4 t} - \frac{4}{3} e^{-4 \times 10^4 t} + 2 \text{ Amps, } t > 0$$



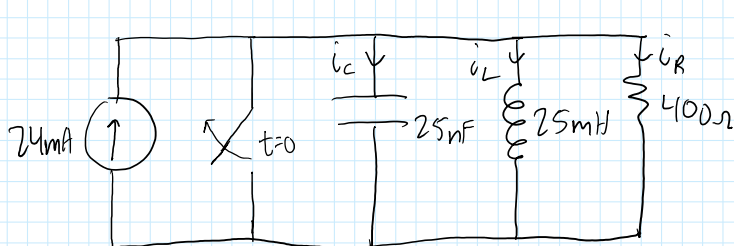
$$R_{TH} = \frac{V_T}{i_T} = \frac{V_b}{32V_b} = \frac{1}{32} \Omega$$



$$i_L(t) = ? , t \geq 0$$

Soln:

Step 1:

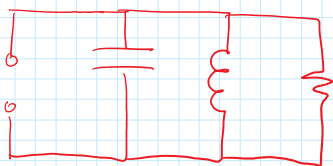

$\alpha > \omega_0$  overdamped

$$\alpha = \frac{1}{2RC} = \frac{1}{2(400)(25nF)} = 5 \times 10^4$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(25mH)(25nF)}} = 4 \times 10^4$$




$$\hat{i}_{L_n}(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

# Finding Current in Parallel RLC

Monday, April 10, 2017 8:24 AM

## Example 8.6

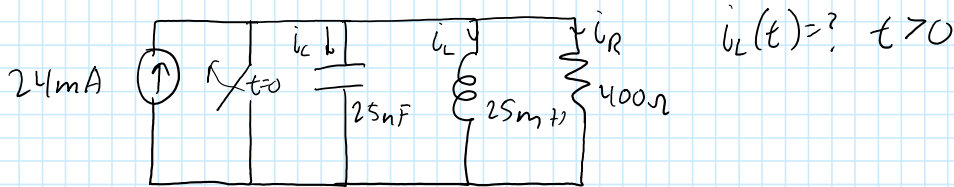

Solution:

step 1)

$$\alpha = \frac{1}{2RC} = 5 \times 10^4$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 4 \times 10^4$$

$\alpha > \omega_0$  overdamped


$$i_{L_n}(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_1 = -20,000$$

$$s_2 = -80,000$$

$$i_{L_n}(t) = A_1 e^{-20000t} + A_2 e^{-80000t}$$

step 2)

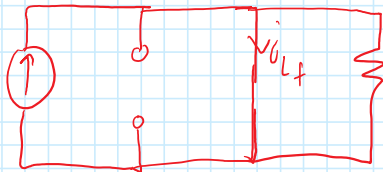

$$i_{LF} = 24 \text{ mA}$$

Step 3)

$$i_L(t) = i_{L_n} + i_{LF}$$


$$= 24 + A_1 e^{-20000t} + A_2 e^{-80000t}$$

Step 4)

$t = 0^-$

$$i_L(0^-) = 0$$

$$V_L(0^-) = 0$$

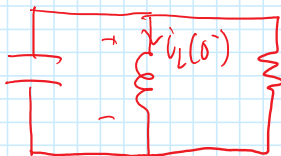

$t = 0^+$



$$i_L(0^+) = i_L(0^-) = i_L(0) = 0$$

$$V_L(0^+) = V_L(0^-) = V_L(0) = 0$$

$$i_L(0) = 0 = 24 + A_1 + A_2$$

$$A_1 + A_2 = -24 \quad (1)$$

$$A_1 + A_2 = -24 \quad (1)$$

$$V_L = L \frac{di_L}{dt} \quad \left. \frac{di_L}{dt} \right|_{t=0} = \frac{V_L}{L} = 0$$

$$\frac{di_L}{dt} = \frac{d}{dt} \left( 24 + A_1 e^{-20000t} + A_2 e^{-80000t} \right)$$

$$= \left( -20,000 A_1 e^{-20000t} - 80000 A_2 e^{-80000t} \right) \Big|_{t=0} = -20000 A_1 - 80000 A_2$$

$$20000 A_1 + 80000 A_2 = 0 \quad (2)$$

Solve eq (1) and (2)

$$A_1 = -32 \text{ mA}$$

$$A_2 = 8 \text{ mA}$$

$$\boxed{i_L(t) = 24 - 32e^{-20000t} + 8e^{-80000t} \text{ mA}, t > 0}$$

Intro to Ch 12

Tuesday, April 11, 2017 8:03 AM

Hw#6 - Chapter 12: 3, 8, 12, 14, 20, 26, 27, 29, 30, 34, 40, 46, 55

1. Read Ch. 12
2. Do Hw #6
3. Hw #6 due Wed, 4/26

1.) Definition of the Laplace Transform

$$\mathcal{L}\{f(t)\} = \int_0^{\infty} f(t)e^{-st} dt = F(s)$$


if  $f(t)=1$

$$\int_0^{\infty} e^{-st} dt = -\frac{1}{s} e^{-st} \Big|_0^{\infty} = \frac{1}{s} [0 - 1] = \frac{1}{s}$$

damping factor  $\downarrow$   
 resonant frequency  $\downarrow$   
 $s = \alpha + j\omega$


$$\mathcal{L}\{f(t)\} = F(s)$$

2.) Step Function

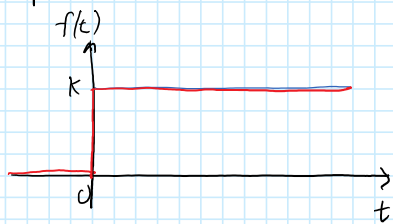


$$k u(t) = 0, t < 0$$

$$k u(t) = k, t > 0$$

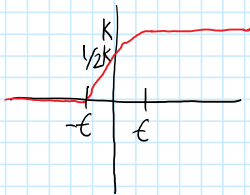


$$k u(0) = 0.5k$$

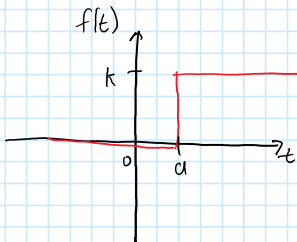


$$k u(t-a) = 0, t < a$$

$$k u(t-a) = k, t > a$$

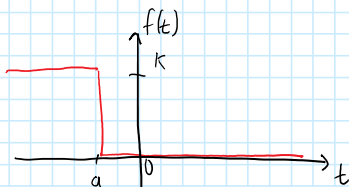

$$k u(a-t) = 0, t < a$$

$$k u(a-t) = k, t > a$$

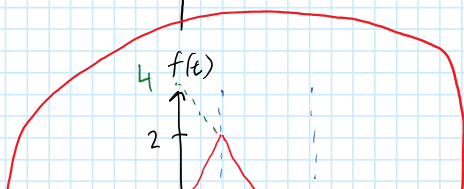


$$f(t) = mt + b$$

$$[0, 1]$$

$$f(t) = 2t$$

[1, 3]

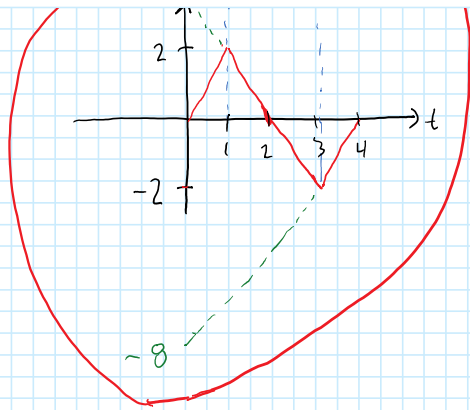

represents

$[0, 1]$

$$f(t) = 2t$$

$$\textcircled{1} m = \frac{2-0}{1-0} = 2$$

$$\textcircled{2} f(0) = 0 = 2(0) + b$$

$$b = 0$$

$$\therefore f(t) = 2t$$

$[1, 3]$

$$\textcircled{1} m = \frac{-2-2}{3-1} = \frac{-4}{2} = -2 = m$$

$$\textcircled{2} f(0) = 4 = -2 \cdot 0 + b$$

$$b = 4$$

$$\therefore f(t) = -2t + 4$$

$[3, 4]$

$$\textcircled{1} m = \frac{0-(-2)}{4-3} = 2 = m$$

$$\textcircled{2} f(0) = -8 = 2(0) + b$$

$$b = -8$$

$$\therefore f(t) = 2t - 8$$

or  $f(4) = 0 = 2(4) + b$

$$0 = 8 + b$$


$$b = -8$$

$$f(t) = 2t - 8$$

$$f(t) = 2t[u(t) - u(t-1)] + (-2t + 4)[u(t-1) - u(t-3)] + (2t - 8)[u(t-3) - u(t-4)]$$


# Intro to Laplace Transform

Wednesday, April 12, 2017 7:59 AM

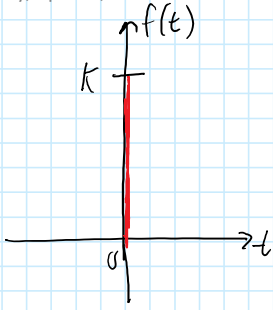


$$\delta(t) = k, t = 0$$

$$\delta(t) = 0, t \neq 0$$

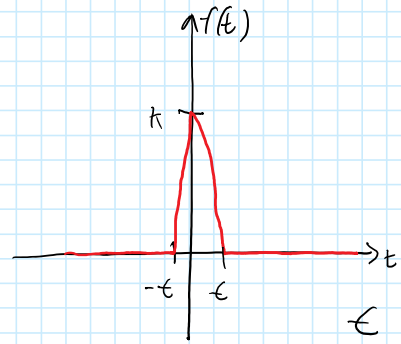

$\epsilon$  is infinitesimal

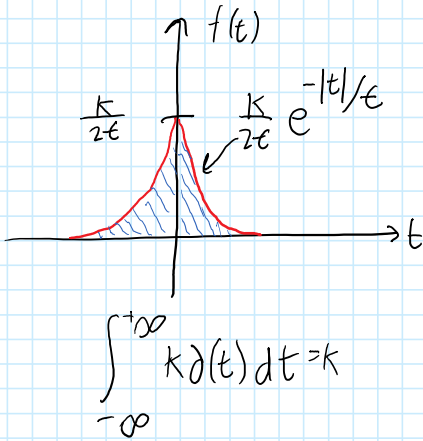

$$\int_{-\infty}^{+\infty} k \delta(t) dt = k$$

$$\text{Area} = \int_{-\infty}^0 \frac{k}{2\epsilon} e^{t/\epsilon} dt + \int_0^{\infty} \frac{k}{2\epsilon} e^{-t/\epsilon} dt$$

$$= \frac{k}{2\epsilon} \cdot \frac{e^{t/\epsilon}}{1/\epsilon} \Big|_{-\infty}^0 + \frac{k}{2\epsilon} \cdot \frac{e^{-t/\epsilon}}{-1/\epsilon} \Big|_0^{\infty}$$

$$= \frac{k}{2\epsilon} \left( \frac{e^0}{1/\epsilon} - \frac{e^{-\infty}}{1/\epsilon} \right) + \frac{k}{2\epsilon} \left( \frac{e^{-\infty}}{-1/\epsilon} - \frac{e^0}{-1/\epsilon} \right)$$

$$= \frac{k}{2\epsilon} \left( \frac{1}{1/\epsilon} - 0 \right) + \frac{k}{2\epsilon} \left( 0 + \frac{1}{1/\epsilon} \right)$$

$$= \frac{k\epsilon}{2\epsilon} + \frac{k\epsilon}{2\epsilon} = \frac{k}{2} + \frac{k}{2} = k$$

$$\mathcal{L}\{\delta(t)\} = 1$$


$$\mathcal{L}\{u(t)\} = \int_{0^-}^{\infty} f(t) e^{-st} dt$$

$$= \int_{0^-}^{\infty} 1 \cdot e^{-st} dt$$

$$= -\frac{1}{s} \int_{0^-}^{\infty} 1 \cdot e^{-st} d(-st)$$

$$= -\frac{1}{s} \left[ e^{-st} \right]_{0^-}^{\infty} = -\frac{1}{s} \left[ e^{-\infty} - e^{0^-} \right] = -\frac{1}{s} \left[ 0 - 1 \right] = \frac{1}{s}$$
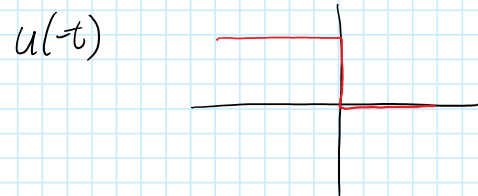
$$u(t) \begin{cases} 1, t \geq 0 \\ 0, t < 0 \end{cases}$$



$$u(-t)$$



f(t) = e^{-at}

$$f(t) = e^{-at} \quad \mathcal{L}\{f(t)\} = \mathcal{L}\{e^{-at}\} = \int_0^{\infty} e^{-at} \cdot e^{-st} dt = \int_0^{\infty} e^{-(s+a)t} dt$$

$$= \frac{1}{s+a}$$

$$f(t) = \sin \omega t \quad \mathcal{L}\{f(t)\} = \mathcal{L}\{\sin(\omega t)\} = \int_0^{\infty} (\sin \omega t) \cdot e^{-st} dt$$

$$= \int_0^{\infty} \frac{e^{j\omega t} - e^{-j\omega t}}{2j} e^{-st} dt$$

$$= \int_0^{\infty} \frac{e^{-(s-j\omega)t} - e^{-(s+j\omega)t}}{2j} dt$$

$$= \frac{1}{2j} \left( \frac{1}{s-j\omega} - \frac{1}{s+j\omega} \right)$$

$$= \frac{1}{2j} \cdot \frac{(s+j\omega) - (s-j\omega)}{(s-j\omega)(s+j\omega)} = \frac{1}{2j} \cdot \frac{s+j\omega - s+j\omega}{s^2 + \omega^2} = \frac{1}{\cancel{2j}} \cdot \frac{\cancel{2}j\omega}{s^2 + \omega^2}$$

$$= \frac{\omega}{s^2 + \omega^2}$$

# Using Laplace Transforms

Thursday, April 13, 2017 8:11 AM

## Table 12.1 - Laplace transforms

$$\cos \omega t \longrightarrow \frac{s}{s^2 + \omega^2}$$

$$te^{-at} \longrightarrow \frac{1}{(s+a)^2}$$

$$e^{-at} \sin \omega t \longrightarrow \frac{\omega}{(s+a)^2 + \omega^2}$$

$$e^{-at} \cos \omega t \longrightarrow \frac{s+a}{(s+a)^2 + \omega^2}$$

## Table 12.2 $\implies$ P.440

### Operational Transforms

$$\mathcal{L}\{f(t)\} = F(s)$$

$$\mathcal{L}\{k f(t)\} = k F(s)$$

### Addition + Subtraction

$$\mathcal{L}\{f_1(t) + f_2(t) - f_3(t)\} = F_1(s) + F_2(s) - F_3(s)$$

### Differentiation

$$\mathcal{L}\left\{\frac{df(t)}{dt}\right\} = \int_0^{\infty} \frac{df(t)}{dt} e^{-st} dt = f(t)e^{-st} \Big|_0^{\infty} - \int_0^{\infty} f(t)(-se^{-st}) dt$$

$$= (0 - f(0)) + s \underbrace{\int_0^{\infty} f(t)e^{-st} dt}_{F(s)} = \boxed{sF(s) - f(0)}$$

### Integration

$$\mathcal{L}\left\{\int_0^t f(x) dx\right\} = \int_0^{\infty} \left[\int_0^t f(x) dx\right] e^{-st} dt$$

$$\text{Let } u = \int_0^t f(x) dx$$

$$du = f(t) dt$$

$$dv = e^{-st} dt$$

$$v = \frac{-e^{-st}}{s}$$




$$= uv - \int v du = \frac{-e^{-st}}{s} \int_0^t f(x) dx \Big|_0^{\infty} + \int_0^{\infty} \frac{e^{-st}}{s} f(t) dt$$

$$= \frac{1}{s} \int_0^{\infty} e^{-st} f(t) dt = \frac{F(s)}{s}$$

2nd order differentiation - p. 437

$$\mathcal{L} \left\{ \frac{d^2 f(t)}{dt^2} \right\} = s^2 F(s) - s f(0) - \frac{df(0)}{dt}$$

Applying the Laplace Transform

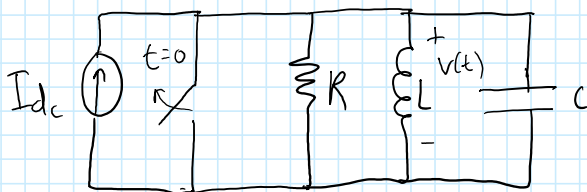

Time domain:  $i_R + i_L + i_C = I_{dc}$

$$\frac{v(t)}{R} + \frac{1}{L} \int_0^t v(t) dt + C \frac{dv(t)}{dt} = I_{dc} u(t)$$

Frequency domain (Laplace Transform):

$$\frac{V(s)}{R} + \frac{1}{L} \frac{V(s)}{s} + C [sV(s) - V(0)] = I_{dc} \left( \frac{1}{s} \right)$$

$$V(0) = 0 \text{ V}$$

$$V(s) \left( \frac{1}{R} + \frac{1}{sL} + sC \right) = \frac{I_{dc}}{s}$$

$$V(s) = \frac{I_{dc}/s}{s^2 + \frac{1}{RC}(s) + \frac{1}{LC}}$$

# Partial Fraction Method

Monday, April 17, 2017 8:05 AM

$$F(s) = \frac{96s^2 + 1652s + 5760}{s^3 + 14s^2 + 48s}$$

$$= \frac{96(s^2 + 17s + 60)}{s(s^2 + 14s + 48)}$$

$$s = \frac{-14 \pm \sqrt{14^2 - 4(1)(48)}}{2}$$

$$= \frac{-14 \pm \sqrt{49}}{2}$$

$$= \frac{-14 \pm 7}{2}$$

$$s_1 = -6 \Rightarrow s_1 + 6 = 0$$

$$s_2 = -8 \Rightarrow s_2 + 8 = 0$$

$$s = \frac{-17 \pm \sqrt{17^2 - 4(1)(60)}}{2}$$

$$= \frac{-17 \pm \sqrt{49}}{2}$$

$$= \frac{-17 \pm 7}{2}$$

$$s_1 = -5$$

$$s_2 = -12$$

$$= \frac{96(s+5)(s+12)}{s(s+6)(s+8)}$$

$$= \frac{K_1}{s} + \frac{K_2}{s+8} + \frac{K_3}{s+6}$$

$$s \rightarrow \frac{96(s+5)(s+12)}{s(s+6)(s+8)} \Big|_{s=0} = \frac{K_1}{s+8} + \frac{K_3}{s+6} \Big|_{s=0}$$

$$K_1 = \frac{96(0+5)(0+12)}{(0+6)(0+8)} = \frac{96(60)}{48} = 120$$

$$(s+8) \frac{96(s+5)(s+12)}{s(s+6)(s+8)} \Big|_{s=-8} = \frac{(s+8)K_1}{s} \Big|_{s=-8} + \frac{(s+8)K_2}{s+8} \Big|_{s=-8} + \frac{(s+8)K_3}{s+6} \Big|_{s=-8}$$

$$\frac{96(s+5)(s+12)}{s(s+6)} \Big|_{s=-8} = 0 + K_2 + 0$$

$$\frac{96(-8+5)(-8+12)}{-8(-8+6)} = K_2 \quad K_2 = \frac{96(-12)}{16} = -72$$

$$(s+6) \frac{96(s+5)(s+12)}{s(s+6)(s+8)} \Big|_{s=-6} = \frac{(s+6)K_1}{s} \Big|_{s=-6} + \frac{(s+6)K_2}{s+8} \Big|_{s=-6} + \frac{(s+6)K_3}{s+6} \Big|_{s=-6}$$

$$\frac{96(s+5)(s+12)}{s(s+8)} \Big|_{s=-6} = 0 + 0 + K_3$$

$$\frac{96(-6+5)(-6+12)}{-6(-6+8)} = \frac{96(-6)}{-12} = 48 = K_3$$

$$\therefore \frac{120}{s} - \frac{72}{s+8} + \frac{48}{s+6}$$

$$\therefore \frac{120}{s} - \frac{72}{s+8} + \frac{48}{s+6}$$

$$\mathcal{L}^{-1} \left\{ \frac{96s^2 + 1652s + 5760}{s^3 + 14s^2 + 48s} \right\} =$$

$$120 u(t) - 72e^{-8t} u(t) + 48e^{-6t} u(t)$$

$$= (120 - 72e^{-8t} + 48e^{-6t}) u(t)$$

# Inverse Laplace Transform of Imaginary Numbers

Wednesday, April 19, 2017 8:02 AM

$$F(s) = \frac{100(s+3)}{(s+6)(s^2+6s+25)}$$

$$s_{1,2} = \frac{-6 \pm \sqrt{6^2 - 4(1)(25)}}{2(1)} = \frac{-6 \pm \sqrt{-64}}{2} = \frac{-6 \pm j8}{2} = -3 \pm j4$$

$$= \frac{100(s+3)}{(s+6)(s+3-j4)(s+3+j4)}$$

$$= \frac{k_1}{s+6} + \frac{k_2}{s+3-j4} + \frac{k_3}{s+3+j4}$$

$$k_1 = \frac{100(s+3)}{s^2+6s+25} \Big|_{s=-6} = \frac{100(-3)}{25} = -12$$

$$\frac{(s+3-j4)[100(s+3)]}{(s+6)(s+3-j4)(s+3+j4)} \Big|_{s=-3+j4} = \frac{(s+3-j4)k_1}{s+6} \Big|_{s=-3+j4}$$

||  
0

$$+ \frac{(s+3-j4)k_2}{s+3-j4} \Big|_{s=-3+j4}$$

$$+ \frac{(s+3-j4)k_3}{s+3+j4} \Big|_{s=-3+j4}$$

||  
0

$$k_2 = \frac{100(s+3)}{(s+6)(s+3+j4)} \Big|_{s=-3+j4} = \frac{100(-3+j4+3)}{(-3+j4+6)(-3+j4+3+j4)} = \frac{100 \cdot j4}{(3+j4)(j4)} = \frac{50}{3+j4}$$

$$= \frac{50(3-j4)}{(3+j4)(3-j4)} = \frac{150-j200}{9+16} = 6-j8 \rightarrow \text{convert to polar form}$$

$$= \sqrt{6^2 + (-8)^2} \tan^{-1}\left(\frac{-8}{6}\right)$$

$$a+jb = \sqrt{a^2+b^2} \tan^{-1} \angle \frac{b}{a}$$

$$= c \angle \theta = c \cos \theta + j \sin \theta = a+jb$$

$$c_1 e^{j\theta_1} \cdot c_2 e^{j\theta_2} = c_1 \cdot c_2 e^{j(\theta_1 + \theta_2)} = c_1 \angle \theta_1 \cdot c_2 \angle \theta_2 = c_1 \cdot c_2$$

$$= 10e^{-j53.13^\circ}$$

$$k_3 = \frac{100(s+3)}{(s+6)(s+3-j4)} \Big|_{s=-3-j4} = \frac{100(-3-j4+3)}{(-3-j4+6)(-3-j4+3-j4)} = 6+j8 = 10e^{j53.13^\circ}$$

$$= \frac{-12}{s+6} + \frac{10e^{-j53.13^\circ}}{s+3-j4} + \frac{10e^{j53.13^\circ}}{s+3+j4} = \frac{-12}{s+6} + \frac{10 \angle -53.13^\circ}{s+3-j4} + \frac{10 \angle 53.13^\circ}{s+3+j4}$$

$$= \frac{-12}{s+6} + \frac{10e^{-j53.13^\circ}}{s+3-j4} + \frac{10e^{j53.13^\circ}}{s+3+j4} = \frac{-12}{s+6} + \frac{10\angle -53.13^\circ}{s+3-j4} + \frac{10\angle 53.13^\circ}{s+3+j4}$$

$$\mathcal{L}^{-1} \left\{ \frac{100(s+3)}{(s+6)(s^2+6s+25)} \right\} = \mathcal{L}^{-1} \left\{ \frac{-12}{s+6} + \frac{10\angle -53.13^\circ}{s+3-j4} + \frac{10\angle 53.13^\circ}{s+3+j4} \right\}$$

$$= \left( -12e^{-6t} + 10\angle -53.13^\circ \cdot e^{-(3-j4)t} + 10\angle 53.13^\circ \cdot e^{-(3+j4)t} \right) u(t)$$

$$\mathcal{L} \{ e^{-at} \} = \frac{1}{s+a}$$

$$= \left( -12e^{-6t} + 10e^{-j53.13^\circ} \cdot e^{-(3-j4)t} + 10e^{j53.13^\circ} \cdot e^{-(3+j4)t} \right) u(t)$$

$$= \left( -12e^{-6t} + 10e^{-3t} \cdot e^{j(4t-53.13^\circ)} + 10e^{-3t} \cdot e^{-j(4t-53.13^\circ)} \right)$$

Note:  $e^a \cdot e^b \cdot e^c = e^{(a+b+c)}$

$e^a \cdot e^{(bt)} = e^c \cdot e^{(at)}$

$$= \left( -12e^{-6t} + \frac{2 \cdot 10e^{-3t} (e^{j(4t-53.13^\circ)} + e^{-j(4t-53.13^\circ)})}{2} \right) u(t)$$

$$= \left( -12e^{-6t} + 20e^{-3t} \cos(4t - 53.13^\circ) \right) u(t)$$

↑  
phase

# Laplace Real Repeated Roots

Monday, April 24, 2017 8:04 AM

## Repeated Real Roots of $F(s)$

$$\frac{100(s+25)}{s(s+5)^3} = \frac{K_1}{s} + \frac{K_2}{(s+5)^3} + \frac{K_3}{(s+5)^2} + \frac{K_4}{(s+5)}$$

$$K_1 = \left. \frac{100(s+25)}{(s+5)^3} \right|_{s=0} = \frac{100(0+25)}{(0+5)^3} = \frac{2500}{125} = 20$$

To find  $K_2$ , we multiply both sides by  $(s+5)^3$  and then evaluate both sides at  $-5$ :

$$\left. \frac{100(s+25)}{s} \right|_{s=-5} = \left. \frac{K_1(s+5)^3}{s} \right|_{s=-5} + \left. K_2 + K_3(s+5) \right|_{s=-5} + \left. K_4(s+5)^2 \right|_{s=-5}$$

$$\frac{100(-5+25)}{-5} = 0 + K_2 + 0 + 0 \quad K_2 = \frac{2000}{-5} = -400$$

To find  $K_3$ , we first must multiply both sides by  $(s+5)^3$ . Next we differentiate both sides once with respect to  $s$  and then evaluate at  $s=-5$ .

$$\left. \frac{d}{ds} \left[ \frac{100(s+25)}{s} \right] \right|_{s=-5} = \left. \frac{d}{ds} \left[ \frac{K_1(s+5)^3}{s} \right] \right|_{s=-5} + \left. \frac{d}{ds} [K_2] \right|_{s=-5} + \left. \frac{d}{ds} [K_3(s+5)] \right|_{s=-5} + \left. \frac{d}{ds} [K_4(s+5)^2] \right|_{s=-5}$$

$$100 \left[ \frac{s - (s+25)}{s^2} \right]_{s=-5} = 0 + 0 + K_3 + 0$$

$$K_3 = 100 \left[ \frac{-5 - (-5+25)}{(-5)^2} \right] = 100 \left[ \frac{-25}{25} \right] = -100$$

To find  $K_4$ , we first multiply both sides by  $(s+5)^3$ . Next, we differentiate both sides twice with respect to "s" and then evaluate both sides at  $s=-5$ . After simplifying the first derivative, the second derivative becomes:

$$100 \left. \frac{d}{ds} \left[ \frac{-25}{s^2} \right] \right|_{s=-5} = K_1 \left. \frac{d}{ds} \left[ \frac{(s+5)^2(25-5)}{s^2} \right] \right|_{s=-5} + \left. \frac{d}{ds} [K_3] \right|_{s=-5} + \left. \frac{d}{ds} [2K_4(s+5)] \right|_{s=-5}$$

$$\begin{aligned} -40 &= 2K_4 \\ K_4 &= -20 \end{aligned}$$

$$= \frac{20}{s} - \frac{400}{(s+5)^3} - \frac{100}{(s+5)^2} - \frac{20}{(s+5)}$$

$$\mathcal{L}^{-1} \left\{ \frac{100(s+5)}{s(s+5)^3} \right\} = \left[ 20 - 200t^2 e^{-5t} - 100t e^{-5t} - 20e^{-5t} \right] u(t)$$

Time domain result

$$F(s) = \frac{s^4 + 13s^3 + 66s^2 + 200s + 300}{s^2 + 9s + 20}$$

$$\begin{array}{r} s^2 + 9s + 20 \overline{) s^4 + 13s^3 + 66s^2 + 200s + 300} \\ \underline{-(s^4 + 9s^3 + 20s^2)} \phantom{+ 300} \\ 4s^3 + 46s^2 + 200s \phantom{+ 300} \\ \underline{-(4s^3 + 36s^2 + 80s)} \phantom{+ 300} \\ 10s^2 + 120s + 300 \phantom{+ 300} \\ \underline{-(10s^2 + 90s + 200)} \\ 30s + 100 \end{array}$$

$$F(s) = s^2 + 4s + 10 + \frac{30s + 100}{s^2 + 9s + 20}$$

$$= s^2 + 4s + 10 + \frac{30s + 100}{(s+5)(s+4)}$$

$$= s^2 + 4s + 10 + \frac{k_1}{s+4} + \frac{k_2}{s+5}$$

$$\frac{30s + 100}{(s+4)(s+5)} = \frac{k_1}{s+4} + \frac{k_2}{s+5}$$

$$\frac{(30s+100)}{(s+5)} \Big|_{s=-4} = k_1 + \frac{k_2(s+4)}{(s+5)} \Big|_{s=-4}$$

$$\frac{-20}{1} = k_1 \quad k_1 = -20$$

$$k_2 = \frac{30s+100}{s+4} \Big|_{s=-5} = \frac{-50}{-1} \quad k_2 = 50$$

$$= s^2 + 4s + 10 \frac{-20}{s+4} + \frac{50}{s+5}$$

$$\mathcal{L}^{-1} \left[ \frac{s^4 + 13s^3 + 66s^2 + 200s + 300}{s^2 + 9s + 20} \right] = \mathcal{L}^{-1} \left[ s^2 + 4s + 10 \frac{-20}{s+4} + \frac{50}{s+5} \right]$$

$$= \left[ \frac{d^2 \delta(t)}{dt^2} + \frac{4 d \delta(t)}{dt} + 10 \delta(t) - (20 e^{-4t} - 50 e^{-5t}) \right] u(t)$$

Tables 12.1, 12.2, 12.3



# Applying Laplace Transform

Tuesday, April 25, 2017 8:04 AM

Polar and Zeros of  $F(s)$


$$F(s) = \frac{4(s+5)(s+10)}{(s+1)(s+2)(s+3)(s+4)}$$

Numerator:  $(s+5)(s+10)$

$$s_1 = -5, s_2 = -10 \Rightarrow \text{Zeros}$$

Denominator:  $(s+1)(s+2)(s+3)(s+4)$
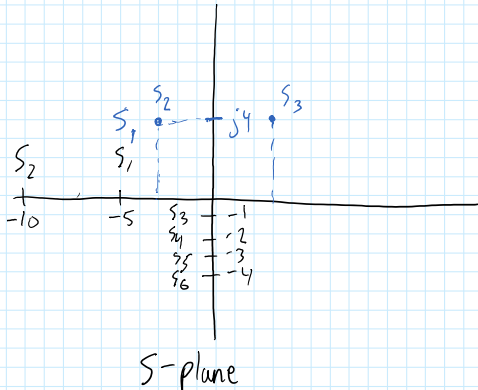
$$s_3 = -1, s_4 = -2, s_5 = -3, s_6 = -4 \Rightarrow \text{Poles}$$




$$F(s) = \frac{9(s+5)}{(s+3-j4)(s-3-j4)}$$

Zero:  $s_1 = -5$

Poles:  $s_2 = -3 + j4$

$s_3 = -3 - j4$

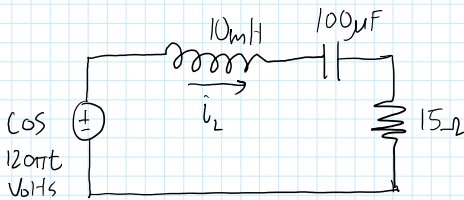

Use Laplace Transform to determine the complete response of  $i_L(t)$

Solu: KVL:  $(15\Omega) i_L(t) + (10 \times 10^{-3} \text{H}) \frac{di_L(t)}{dt} + \left(\frac{1}{100 \times 10^{-6} \text{F}}\right) \int_0^t i_L(t) dt$   
 $-\cos 120\pi t = 0$

$$15i_L(t) + 0.01 \frac{di_L(t)}{dt} + 10^4 \int_0^t i_L(t) dt = \cos 120\pi t$$



Using Table 12.1 and 12.2

$$15I_L(s) + 0.01sI_L(s) + 10^4 \frac{I_L(s)}{s} = \frac{s}{s^2 + (120\pi)^2}$$

$$I_L(s) \left[ 15 + 0.01s + \frac{10^4}{s} \right] = \frac{s}{s^2 + (120\pi)^2}$$

$$I_L(s) = \frac{s}{s^2 + (120\pi)^2} \cdot \frac{s}{15 + 0.01s + \frac{10^4}{s}} = \frac{s^2}{15s + 0.01s^2 + 10^4} = \frac{100s^2}{1500s + s^2 + 10^6} = \frac{100s^2}{(s^2 + 1500s + 10^6)(s^2 + (120\pi)^2)}$$

$$I_L(s) = \frac{100s^2}{(s + 750 + j661.44)(s + 750 - j661.44)(s - j120\pi)(s + j120\pi)} \quad s_{1,2} = -1500 \pm \sqrt{1500^2 - 4(1)(10^6)}$$

$$I_L(s) = \frac{100s}{(s+750+j661.44)(s+750-j661.44)(s-j120\pi)(s+j120\pi)}$$

$$s_{1,2} = \frac{-1500 \pm \sqrt{1500^2 - 4(1)(10^6)}}{2(1)}$$

$$s_{1,2} = -750 \pm j661.44$$

$$\begin{cases} s_1 = -750 - j661.44 \\ s_2 = -750 + j661.44 \end{cases}$$

$$= \frac{K_1}{(s+750+j661.44)} + \frac{K_1^*}{(s+750-j661.44)} + \frac{K_2}{(s-j120\pi)} + \frac{K_2^*}{(s+j120\pi)}$$

$$K_1 = \frac{100s^2}{(s+750-j661.44)(s-j120\pi)(s+j120\pi)} \Big|_{s=-750-j661.44} = 0.07357 \angle 97.89^\circ$$

$$K_2 = \frac{100s^2}{(s+750-j661.44)(s+750+j661.44)(s+j120\pi)} \Big|_{s=j120\pi} = 0.018345 \angle 56.61^\circ$$

$$= \frac{0.07357 \angle 97.89^\circ}{(s+750+j661.44)} + \frac{0.07357 \angle -97.89^\circ}{(s+750-j661.44)} + \frac{0.018345 \angle 56.61^\circ}{s-j120\pi} + \frac{0.018345 \angle -56.61^\circ}{s+j120\pi}$$


$$\mathcal{L}^{-1}[I_L(s)] = 147.14e^{-750t} \cos(661.44t - 97.89^\circ) + 36.69 \cos(120\pi t + 56.61^\circ) \text{ mA}$$

# HW #7


Wednesday, April 26, 2017 8:04 AM

1. Read Ch 17
  2. Do HW #7 - Chapter 13: 4, 7, 8, 9, 10, 11, 17, 21, 23, 25, 27, 57
- Due Monday 5/08

Time Domain

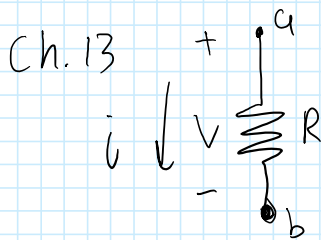


Frequency Domain

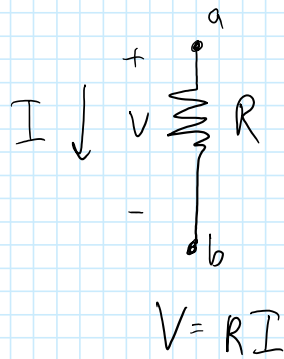

# Frequency Domain Models for Elements

Thursday, April 27, 2017 8:00 AM

An inductor in the s-domain

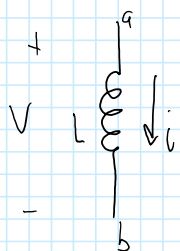


$$V = L \frac{di}{dt}$$

Table 12.2

$$\mathcal{L}\left\{L \frac{di}{dt}\right\} = L[sI - I_0]$$

$$= sLI - LI_0 = V$$

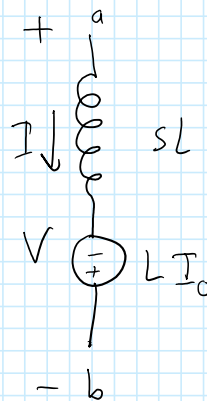



$$V = sLI - LI_0$$

$$V + LI_0 = sLI$$

$$I = \frac{V + LI_0}{sL}$$

$$= \frac{V}{sL} + \frac{I_0}{s}$$

impedance(ind) = sL

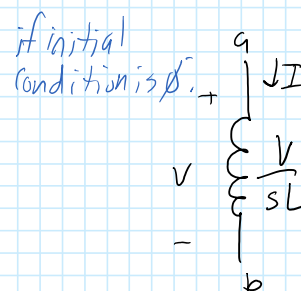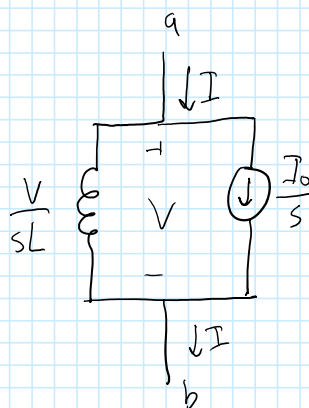

A capacitor in the s-domain


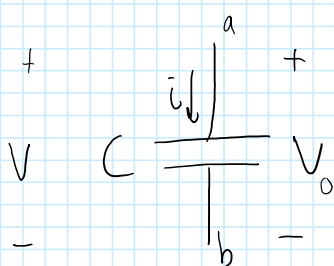
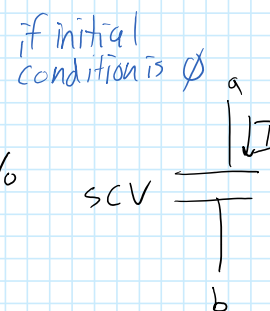


Table 12.2

$$I = C[sV - V(0^-)]$$

$$= sCV - CV_0$$

impedance(cap) =  $\frac{1}{sC}$

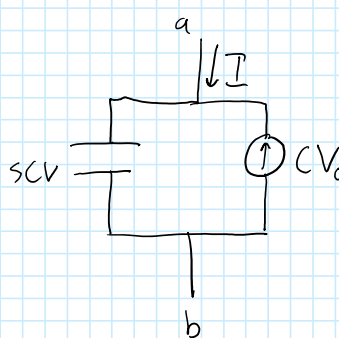


$$i = C \frac{dV}{dt}$$


$$I = sCV - CV_0$$

$$sCV = I + CV_0$$
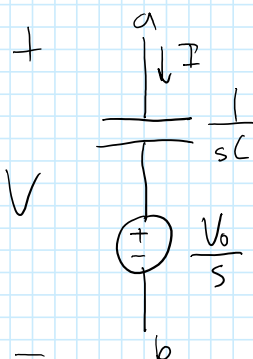
$$V = \frac{I + CV_0}{sC} = \frac{I}{sC} + \frac{V_0}{s}$$





if initial conditions =  $\emptyset$

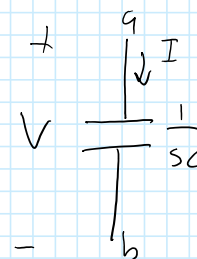

Natural Response of an RC circuit

# Natural Response of an RC circuit

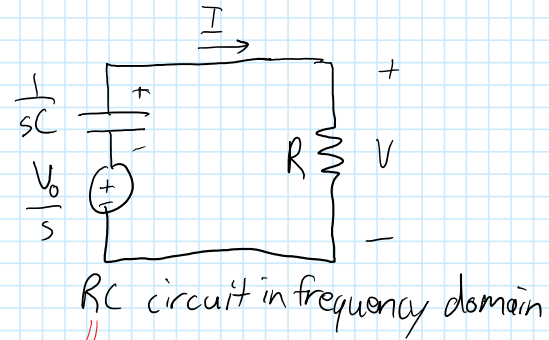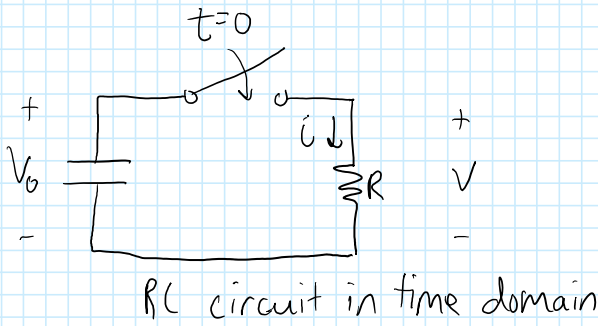

KVL:  $\frac{V_0}{s} - \frac{1}{sC} I - RI = 0$

$$\frac{1}{sCI} + RI = \frac{V_0}{s}$$

$$I \left( \frac{1}{sC} + R \right) = \frac{V_0}{s}$$

$$I = \frac{\frac{V_0}{s}}{\left( \frac{1}{sC} + R \right)} \cdot \frac{s}{s} = \frac{V_0}{\frac{1}{C} + sR} \cdot \frac{\frac{1}{R}}{\frac{1}{R}} = \frac{\frac{V_0/R}{1}}{\frac{1}{RC} + s}$$

Using Table 12.1:  $i(t) = \mathcal{L}^{-1}\{I\}$



$$i = \frac{V_0}{R} e^{-t/RC}$$

$$V = Ri = V_0 e^{-t/RC}$$

# Step Response of a parallel RLC circuit

$i_L(t) = ?$

Solu: frequency domain

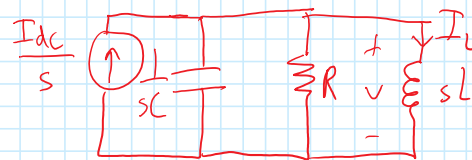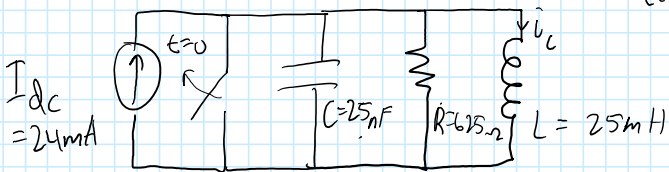

KCL:  $\frac{I_{dc}}{s} - V_s C - \frac{V}{R} - \frac{V}{sL} = 0$

$$\frac{I_{dc}}{s} = sVC + \frac{V}{R} + \frac{V}{sL}$$

$\dots - I_{dc}$

$$s \quad R \quad sL$$

$$V \left( sC + \frac{1}{R} + \frac{1}{sL} \right) = \frac{I_{dc}}{s}$$

$$V = \frac{I_{dc}/s}{sC + \frac{1}{R} + \frac{1}{sL}} \cdot \frac{s}{s} = \frac{I_{dc}}{s^2C + \frac{s}{R} + \frac{1}{L}} \cdot \frac{1}{C} = \frac{I_{dc}}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

$$I_L = \frac{V}{sL} = \frac{\frac{I_{dc}}{C}}{sL \left( s^2 + \frac{1}{RC}s + \frac{1}{LC} \right)} = \frac{I_{dc}/LC}{s \left( s^2 + \frac{1}{RC}s + \frac{1}{LC} \right)} = \frac{384 \times 10^5}{s \left( s^2 + 64,000s + 16 \times 10^8 \right)}$$

$$I_L = \frac{384 \times 10^5}{s \left( s + 32,000 - j24,000 \right) \left( s + 32,000 + j24,000 \right)}$$



$$= \frac{k_1}{s} + \frac{k_2}{(s + 32,000 - j24,000)} + \frac{k_2^*}{(s + 32,000 + j24,000)}$$

# Examples of S-domain Circuits

Tuesday, May 2, 2017 8:03 AM

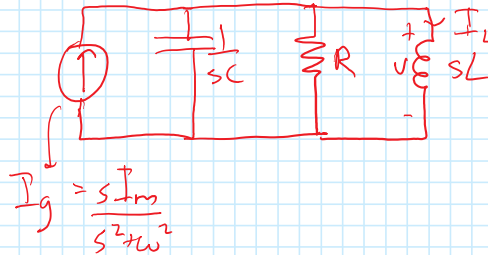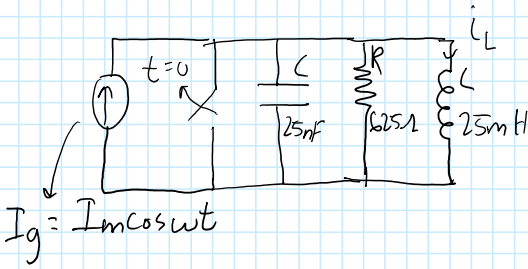Example: 8.7 in book

Sdu in S domain :  $I_m = 24\text{mA}$   
 $\omega = 40,000 \text{ rad/sec}$



$$V = \frac{(I_g/c)s}{s^2 + (1/RC)s + 1/LC} = \frac{\left(\frac{sI_m}{s^2 + \omega^2}\right) \cdot \frac{s}{C}}{s^2 + \left(\frac{1}{RC}\right)s + \frac{1}{LC}} = \frac{(I_m/c)s^2}{(s^2 + \omega^2)\left(s^2 + \frac{1}{RC}s + \frac{1}{LC}\right)}$$

$$I_L = \frac{V}{sL} = \frac{(I_m/c)s^2}{(s^2 + \omega^2)\left(s^2 + \frac{1}{RC}s + \frac{1}{LC}\right)sL} = \frac{(I_m/Lc)s}{(s^2 + \omega^2)\left(s^2 + \frac{1}{RC}s + \frac{1}{LC}\right)}$$


$$= \frac{(384 \times 10^5)s}{(s^2 + 16 \times 10^8)(s^2 + 64000s + 16 \times 10^8)}$$

$$= \frac{k_1}{s + j40000} + \frac{k_1^*}{s - j40000} + \frac{k_2}{s + 32000 - j24000} + \frac{k_2^*}{s + 32000 + j24000}$$


$$= \frac{7.5 \times 10^3 \angle -90^\circ}{s - j40000} + \frac{7.5 \times 10^3 \angle 90^\circ}{s + j40000} + \frac{12.5 \times 10^{-3} \angle 90^\circ}{s + 32000 - j24000} + \frac{12.5 \times 10^{-3} \angle -90^\circ}{s + 32000 + j24000}$$

$$i_L(t) = \mathcal{L}^{-1}\{I_L\} = \left[ 15 \cos(40000t - 90^\circ) + 25e^{-32000t} \cos(24000t + 90^\circ) \right] \text{ mA}$$

Example:

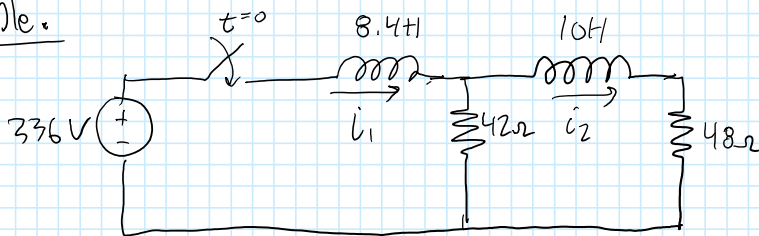

Sdu:

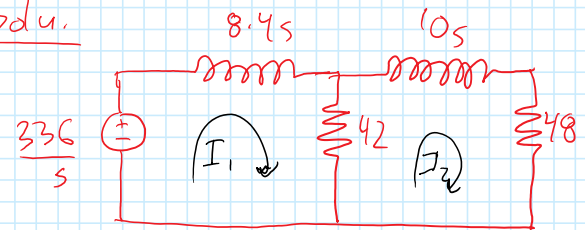

S domain

Mesh 1:  $\frac{336}{s} - 8.4sI_1 - 42(I_1 - I_2) = 0$

$$\frac{336}{s} = (42 + 8.4s)I_1 - 42I_2 \quad (1)$$

Mesh 2:  $-42(I_2 - I_1) - 10s(I_2) - 48(I_2) = 0$

Mesh 2:  $-42(I_2 - I_1) - 10s(I_2) - 48(I_2) = 0$   
 $0 = -42I_1 + (90 + 10s)I_2$  (2)

$$(42 + 8.4s)I_1 - 42I_2 = \frac{336}{s}$$

$$-42I_1 + (90 + 10s)I_2 = 0$$

$$I_1 = \frac{\begin{vmatrix} \frac{336}{s} & -42 \\ 0 & 90+10s \end{vmatrix}}{\begin{vmatrix} 42+8.4s & -42 \\ -42 & 90+10s \end{vmatrix}}$$

$$= \frac{\frac{336}{s}(90+10s)}{84(s^2+14s+24)} = \frac{336(90+10s)}{84s(s^2+14s+24)}$$

$$= \frac{3360(s+9)}{84s(s^2+14s+24)}$$

$$= \frac{40(s+9)}{s(s^2+14s+24)} = \frac{40(s+9)}{s(s+2)(s+12)} = \frac{k_1}{s} + \frac{k_2}{s+2} + \frac{k_3}{s+12} = \frac{15}{s} - \frac{14}{s+2} - \frac{1}{s+12}$$

$$I_2 = \frac{\begin{vmatrix} 42+8.4s & \frac{336}{s} \\ -42 & 0 \end{vmatrix}}{\begin{vmatrix} 42+8.4s & -42 \\ -42 & 90+10s \end{vmatrix}}$$

$$= \frac{168}{s(s+2)(s+12)} = \frac{k_1}{s} + \frac{k_2}{s+2} + \frac{k_3}{s+12}$$

$$= \frac{7}{s} - \frac{8.4}{s+2} + \frac{1.4}{s+12}$$

$$i_1(t) = \mathcal{L}^{-1}\{I_1\}$$

$$= (15 - 14e^{-2t} - e^{-12t})u(t) \text{ Amps}$$

$$i_2(t) = \mathcal{L}^{-1}\{I_2\}$$

$$= (7 - 8.4e^{-2t} + 1.4e^{-12t})u(t) \text{ Amps}$$

Cramer's Rule

$$aI_1 + bI_2 = e$$

$$cI_1 + dI_2 = 0$$

$$I_1 = \frac{\begin{vmatrix} e & b \\ 0 & d \end{vmatrix}}{\begin{vmatrix} a & b \\ c & d \end{vmatrix}}$$


$$I_2 = \frac{\begin{vmatrix} a & e \\ c & 0 \end{vmatrix}}{\begin{vmatrix} a & b \\ c & d \end{vmatrix}}$$



# Transfer Function


Wednesday, May 3, 2017 8:04 AM

Example:

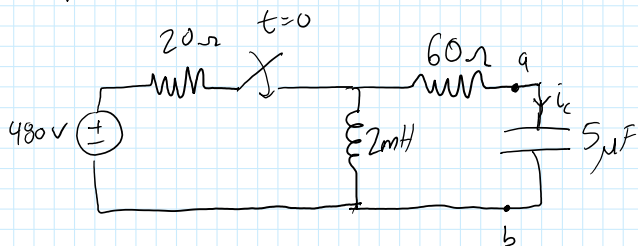


Use Thevenin equivalent to find  $V_{TH}$  and  $Z_{TH}$  at a and b, in s domain.

Soln:

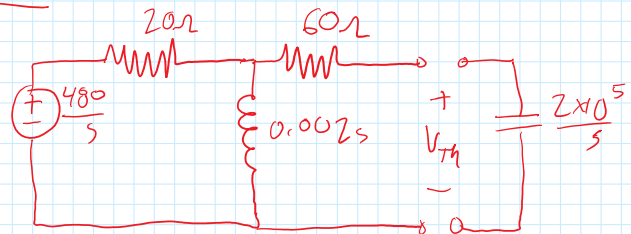

$$V_{TH} = \frac{480}{s} \left( \frac{0.002s}{20 + 0.002s} \right) = \frac{480}{5 \times 10^4}$$
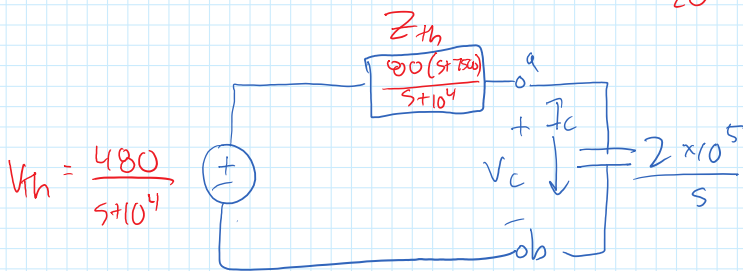
$$Z_{TH} = 60 + 20 // 0.002s = 60 + \frac{20(0.002s)}{20 + 0.002s} = \frac{80(s + 7500)}{5 \times 10^4}$$



$$I_c = \frac{V_{TH}}{Z_{TH} + \frac{2 \times 10^5}{s}}$$


$$V_c = I_c \left( \frac{2 \times 10^5}{s} \right)$$

The transfer function


$$H(s) = \frac{Y(s)}{X(s)}$$

↖ output  
↖ input

Example (3.1)

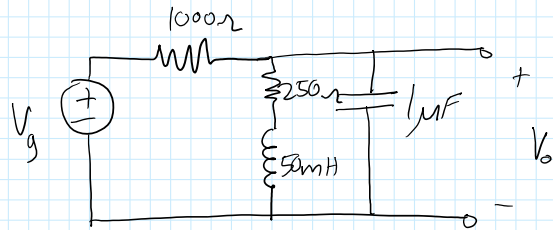

Solution:

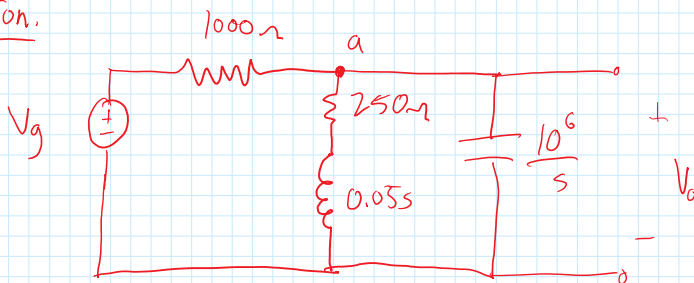

$$H(s) = \frac{V_o(s)}{V_g(s)}$$

KCL at a:  $I_{\text{leaving}} = +$ ;  $I_{\text{entering}} = -$

$$\frac{V_o - V_g}{1000} + \frac{V_o}{250 + 0.05s} + \frac{V_o}{10^6/s} = 0$$

$$\frac{V_o}{1000} + \frac{V_o}{250 + 0.05s} + \frac{V_o s}{10^6} = \frac{V_g}{1000}$$

$$V_o \left( \frac{1}{1000} + \frac{1}{250 + j0.05s} + \frac{5}{10^6} \right) = \frac{V_g}{1000}$$

$$\frac{V_o}{V_g} = \frac{\frac{1}{1000}}{\left( \frac{1}{1000} + \frac{1}{250 + j0.05s} + \frac{5}{10^6} \right)} = \frac{1000(s) \dots}{s^2 + 6000s \dots}$$

---


HW #8 Chapter 18: 2, 4, 6, 7, 9, 10, 12, 13, 18, 19, 21, 29, 31, 33, 36, 37

Due Thursday, 5/11

# Two-Port Circuits

Thursday, May 4, 2017 8:03 AM
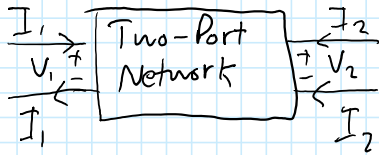
## Four Common Two-Port Network Parameters



### 1. Admittance Parameters

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

short circuit input admittance

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

short circuit output admittance


$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

short circuit transfer admittance


$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

short circuit transfer admittance

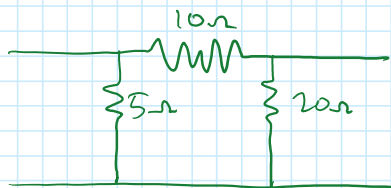Example 1: Find the  $y$ -parameter for the network shown below



short output to find  $y_{11} + y_{21}$

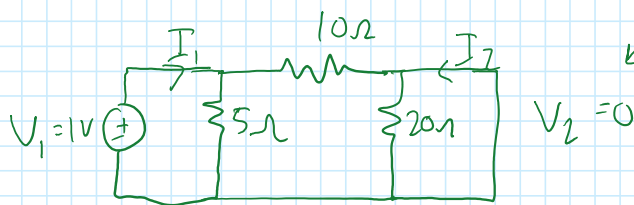

$$I_1 = \frac{V_1}{5\Omega \parallel 10\Omega} = 0.3 V_1$$


$$Y_{11} = \frac{I_1}{V_1} = \frac{0.3 V_1}{V_1} = \boxed{0.3 \text{ S}}$$

$$I_2 = -I_1 \left( \frac{5}{15} \right) = -0.1 V_1 \text{ Amps}$$

$$Y_{21} = \frac{I_2}{V_1} = \frac{-0.1 V_1}{V_1} = \boxed{-0.1 \text{ S}}$$

Short out input to find  $Y_{22} + Y_{12}$

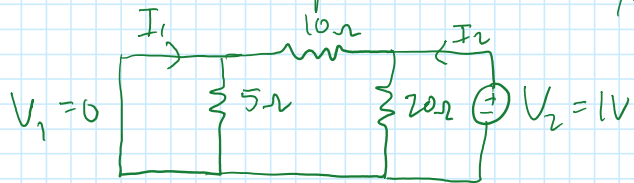Short out input to find  $Y_{22} + Y_{12}$



$$Y_{22} = \frac{I_2}{V_2} \quad I_2 = \frac{V_2}{20\Omega \parallel 10\Omega} = \frac{30V_2}{200} = 0.15V_2$$

$$Y_{22} = \frac{0.15V_2}{V_2} = \boxed{0.15 \text{ S}} \text{ or } 0.15 \text{ S}$$


$$I_1 = -I_2 \left( \frac{20}{30} \right) = -0.15V_2 \left( \frac{20}{30} \right) = -0.1V_2$$

$$Y_{12} = \frac{I_1}{V_2} = \frac{-0.1V_2}{V_2} = \boxed{-0.1 \text{ S}}$$

For first (total network):

$$\begin{cases} I_1 = 0.3V_1 - 0.1V_2 \\ I_2 = -0.1V_1 + 0.15V_2 \end{cases}$$

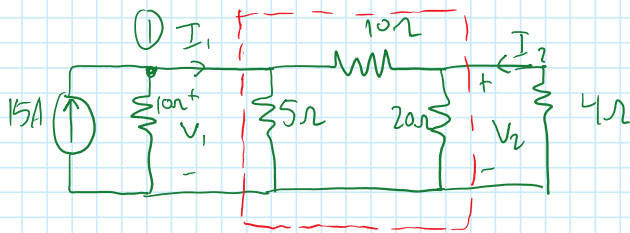Example 2: Use the result of example 1 to find  $I_1$  and  $I_2$  in the circuit shown below



KCL at ①

$$15 - I_1 - \frac{V_1}{10\Omega} = 0$$

$$15 - I_1 - 0.1V_1 = 0$$

$$I_1 = 15 - 0.1V_1$$

ohm's law at the output

$$I_2 = \frac{-V_2}{4\Omega} = -0.25V_2 \text{ from ex. 1}$$

$$I_1 = 15 - 0.1V_1 = 0.3V_1 - 0.1V_2$$

$$I_1 = -0.25V_2 = -0.1V_1 + 0.15V_2 \text{ from ex. 1}$$

$$15 = 0.4V_1 - 0.1V_2$$

$$0 = -0.1V_1 + 0.4V_2$$

$$V_1 = 40V$$

$$V_2 = 10V$$

$$I_1 = 15 - 0.1V_1 = 15 - 0.1(40) = 11A$$

$$I_2 = -0.25V_2 = -0.25(10) = -2.5A$$

## Impedance Parameters

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \quad \text{open circuit input impedance}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} \quad \text{open circuit output impedance}$$


$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} \quad \text{open circuit transfer impedance}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} \quad \text{open circuit transfer impedance}$$

## Two Port Examples

Monday, May 8, 2017 8:08 AM

Example:

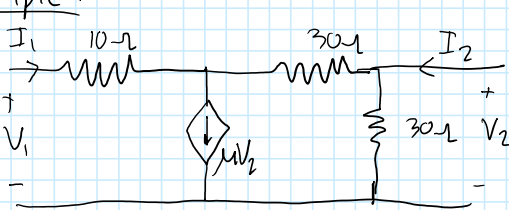


$$\mu = \frac{1}{60}$$

Find  $Z$  parameters

Solu:

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

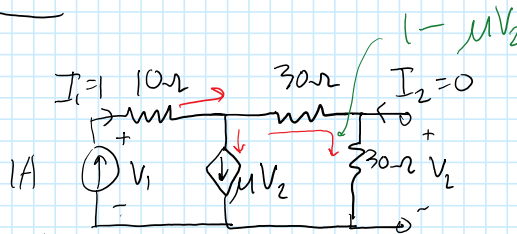

Ohm's Law

$$V_2 = 30 \Omega (1 - \mu V_2)$$

$$V_2 = 30 - 30 \mu V_2$$

$$V_2 + 30 \mu V_2 = 30$$

$$V_2 (1 + 30 \mu) = 30$$

$$V_2 = \frac{30}{1 + 30 \mu} = \frac{30}{1 + \frac{30}{60}} = \frac{30}{1.5} = 20$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{20\text{V}}{1\text{A}} = 20 \Omega$$

Supermesh:

$V_{\text{rise}} = \text{"+"}$ ;  $V_{\text{drop}} = \text{"-"}$

$$V_1 - 10 \Omega (1\text{A}) - (30 \Omega + 30 \Omega)(1 - \mu V_2) = 0$$

$$V_1 - 10 - 60(1 - \mu V_2) = 0$$

$$V_1 = 10 + 60(1 - \mu V_2)$$


$$= 10 + 60 \left(1 - \frac{1}{60} \cdot 20\right)$$

$$= 10 + 60 \left(\frac{2}{3}\right) = 10 + 40 = 50 = V_1$$

$$Z_{11} = \frac{V_1}{I_1} = \frac{50\text{V}}{1\text{A}} = 50 \Omega$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

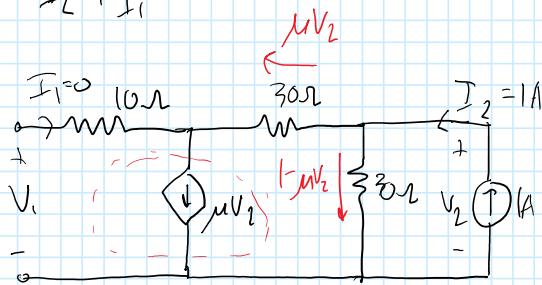

$$V_2 = 30(1 - \mu V_2)$$

$$V_2 = 30 - 30\mu V_2$$

$$V_2 + 30\mu V_2 = 30$$

$$V_2(1 + 30\mu) = 30$$

$$V_2 = \frac{30}{1 + \frac{30}{60}} = \frac{30}{1.5} = 20V$$

$$V_2 = 20V$$

$$Z_{22} = \frac{V_2}{I_2} = \frac{20V}{1A} = 20\Omega$$

Supermesh:

$$V_1 - I_1(10\Omega) + 30\Omega(\mu V_2) - 30\Omega(1 - \mu V_2) = 0$$

$$V_1 + 30\mu V_2 - 30 + 30\mu V_2 = 0$$

$$V_1 = 30 - 60\mu V_2 = 30 - \frac{60}{60} V_2 = 30 - 20 = 10V$$

$$Z_{12} = \frac{V_1}{I_2} = \frac{10V}{1A} = 10\Omega$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$


$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$V_1 = 50I_1 + 10I_2$$

$$V_2 = 20I_1 + 20I_2$$

Loading Effect on Two-Port Network

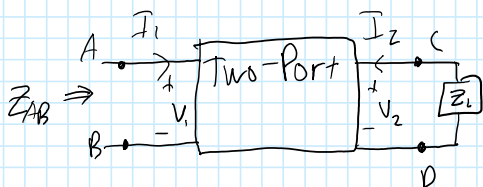a.) Input Impedance  $Z_{AB}$  for the following network



$$Z_L = \frac{V_2}{I_2} \quad \therefore V_2 = -Z_L I_2$$

$$-I_2 \\ V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{also}$$

$$-Z_L I_2 = Z_{21} I_1 + Z_{22} I_2$$

$$-Z_L I_2 - Z_{22} I_2 = Z_{21} I_1$$

$$-(Z_L + Z_{22}) I_2 = Z_{21} I_1$$

$$\frac{I_2}{I_1} = \frac{-Z_{21}}{Z_L + Z_{22}}$$

$$Z_{AB} = Z_{11} - \frac{Z_{12} Z_{21}}{Z_L + Z_{22}}$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$Z_{AB} = \frac{V_1}{I_1}$$

$$Z_{AB} = \frac{Z_{11} I_1 + Z_{12} I_2}{I_1}$$

$$= Z_{11} + Z_{12} \frac{I_2}{I_1}$$


$$= Z_{11} + Z_{12} \left( \frac{-Z_{21}}{Z_L + Z_{22}} \right)$$

$$= Z_{11} - \frac{Z_{12} Z_{21}}{Z_L + Z_{22}}$$



# Output Impedance

Tuesday, May 9, 2017 8:01 AM

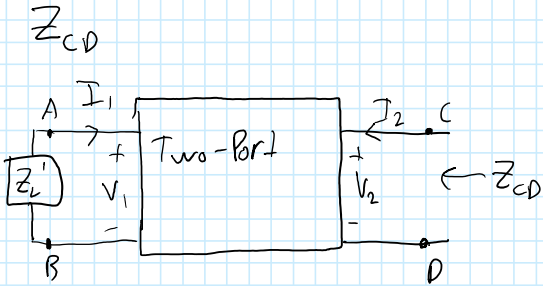

$$Z'_L = \frac{V_1}{-I_1} = \frac{-V_1}{I_1} \Rightarrow V_1 = -Z'_L I_1$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$-Z'_L I_1 = Z_{11} I_1 + Z_{12} I_2$$

$$-Z'_L I_1 - Z_{11} I_1 = Z_{12} I_2$$

$$-(Z'_L + Z_{11}) I_1 = Z_{12} I_2$$


$$\frac{I_1}{I_2} = \frac{-Z_{12}}{Z'_L + Z_{11}}$$

$$Z_{CD} = \frac{V_2}{I_2} \quad V_2 = Z_{22} I_2 + Z_{21} I_1$$

$$Z_{CD} = \frac{Z_{22} I_2 + Z_{21} I_1}{I_2} = Z_{22} + Z_{21} \frac{I_1}{I_2}$$

$$Z_{CD} = Z_{22} - \frac{Z_{21} Z_{12}}{Z_{11} + Z'_L}$$
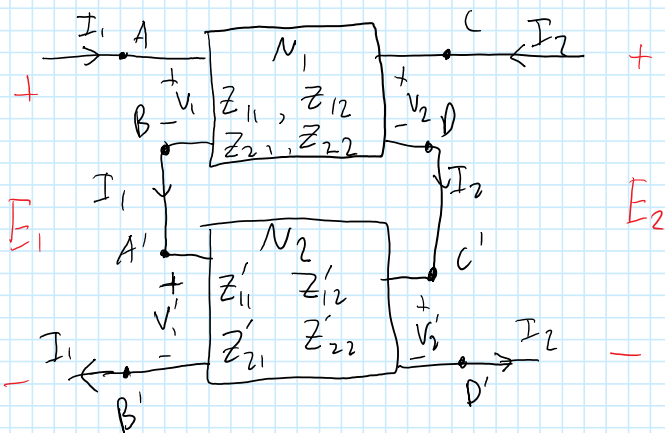
## Series Connections of Two-Port Network



Using KVL:

$$\begin{bmatrix} E_1 \\ E_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + \begin{bmatrix} V'_1 \\ V'_2 \end{bmatrix}$$

$$= \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} + \begin{bmatrix} Z'_{11} & Z'_{12} \\ Z'_{21} & Z'_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$= \begin{bmatrix} Z_{11} + Z'_{11} & Z_{12} + Z'_{12} \\ Z_{21} + Z'_{21} & Z_{22} + Z'_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

## Relation Between Y and Z parameters

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\therefore \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}^{-1} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\frac{1}{Y_{11}Y_{22} - Y_{12}Y_{21}} \begin{bmatrix} Y_{22} & -Y_{12} \\ -Y_{21} & Y_{11} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$Z_{11} = \frac{Y_{22}}{Y_{11}Y_{22} - Y_{12}Y_{21}}$$


$$Z_{12} = \frac{-Y_{12}}{Y_{11}Y_{22} - Y_{12}Y_{21}}$$

$$Z_{21} = \frac{-Y_{21}}{Y_{11}Y_{22} - Y_{12}Y_{21}}$$

$$Z_{22} = \frac{Y_{11}}{Y_{11}Y_{22} - Y_{12}Y_{21}}$$

A parameters
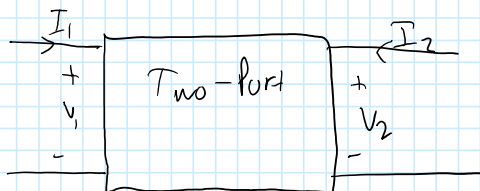
$$\begin{aligned} V_1 &= a_{11}V_2 - a_{12}I_2 \\ I_1 &= a_{21}V_2 - a_{22}I_2 \end{aligned} \Rightarrow \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$




$$a_{11} = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$a_{12} = \left. \frac{-V_1}{I_2} \right|_{V_2=0}$$

$$a_{21} = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$a_{22} = \left. \frac{-I_1}{V_1} \right|_{V_2=0}$$


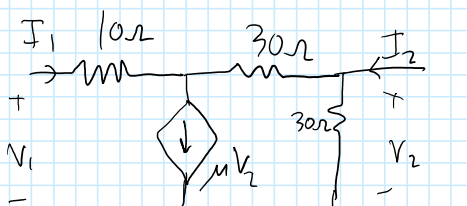
Example: Determine A parameters for the following circuit



Solution:

$$a_{11} = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$a_{21} = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

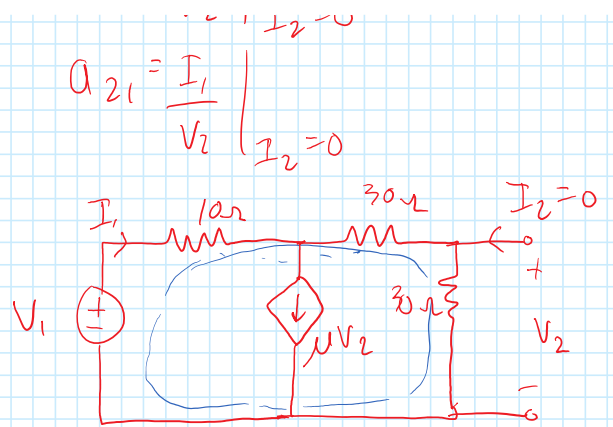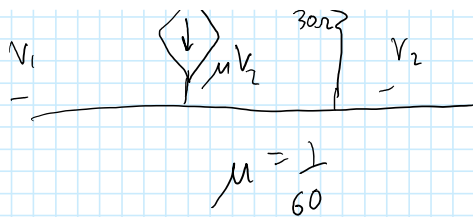

Supermesh:

$$V_1 - 10\Omega (I_1) - 30\Omega (I_1 - \mu V_2) - 30\Omega (I_1 - \mu V_2) = 0$$

$$V_1 - 10I_1 - 60(I_1 - \mu V_2) = 0 \quad (1)$$

$$V_2 = 30(I_1 - \mu V_2)$$

$$V_2 = 30I_1 - 30\mu V_2$$

$$V_2 + 30\mu V_2 = 30I_1$$

$$I_1 = \frac{(1 + 30\mu)V_2}{30} \quad (2)$$

$$a_{21} = \frac{I_1}{V_2} = \frac{1 + 30\mu V_1 / V_2}{30} = \frac{1 + 30 \cdot \frac{1}{60}}{30} = \frac{1.5}{30} = 0.05 \text{ Amps}$$

Substitute (2) into (1)

$$V_1 - 70 \frac{(1 + 30\mu)V_2}{30} + 60\mu V_2 = 0$$

$$V_1 - 70 \frac{(1 + 30\mu)}{30} - 60\mu + 30 V_2 = 0$$

$$V_1 - 7 \left(1 + 30 \cdot \frac{1}{60}\right) - 180 \cdot \frac{1}{60} V_2 = 0$$

$$V_1 - 7 + \frac{210}{60} - 3 V_2 = 0$$


$$V_1 - 2.5V_2 = 0 \quad V_1 = 2.5V_2 \quad \underline{V_1 = 2.5}$$

$$V_1 - 2.5V_2 = 0 \quad V_1 = 2.5V_2 \quad \frac{V_1}{V_2} = 2.5$$

$$a_{11} = 2.5$$

$$a_{12} = \frac{V_1}{I_2} \Big|_{V_2=0} = -40$$

$$a_{22} = \frac{-I_1}{I_2} \Big|_{V_2=0} = \frac{-I_1}{\mu V_2 - I_1} = \frac{-I_1}{-I_1} = 1$$

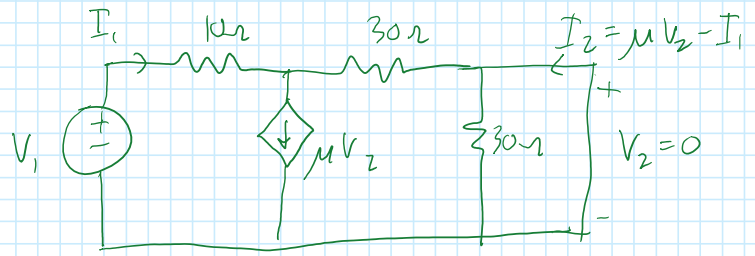

Supermesh

$$V_1 - 10i_1 + 30i_2 = 0$$

$$\therefore i_1 = -i_2$$

$$V_1 + 10I_2 + 30I_2 = 0$$

$$V_1 + 40I_2 = 0$$

$$V_1 + 40I_2 = 0$$



$$V_1 = -40I_2$$

$$\frac{V_1}{I_2} = -40$$

# Cascade Connections

Wednesday, May 10, 2017 8:04 AM

## Cascade Connections

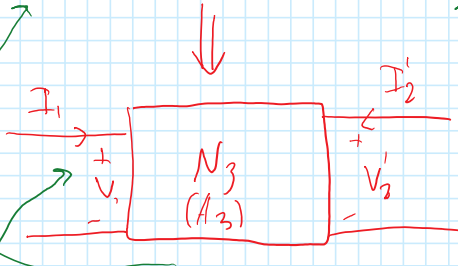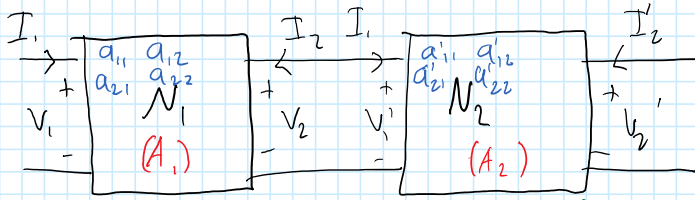

$$\text{Let } \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = A_1 \begin{bmatrix} V_1' \\ -I_2' \end{bmatrix}, \quad \begin{bmatrix} V_1' \\ I_1' \end{bmatrix} = A_2 \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix}$$


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = A_3 \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix}$$

$$\therefore V_2 = V_1'$$

$$I_2 = -I_1'$$

$$\therefore \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = A_1 \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = A_1 \begin{bmatrix} V_1' \\ -I_1' \end{bmatrix} = A_1 A_2 \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix} = A_3 \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix} \quad \text{where } A_3 = A_1 A_2$$
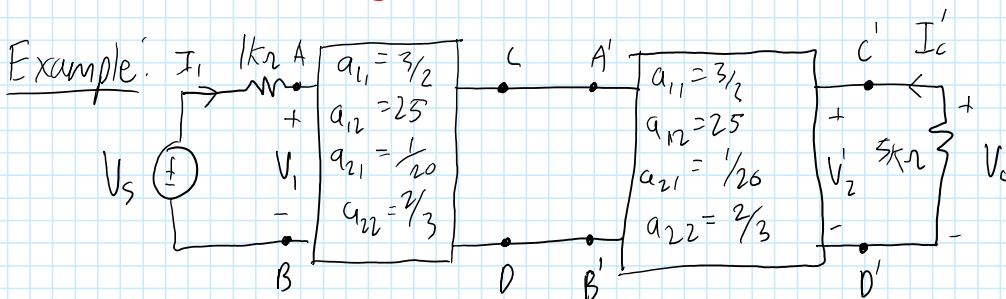
$$A_3 = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} a'_{11} & a'_{12} \\ a'_{21} & a'_{22} \end{bmatrix}$$



A Two-stage amplifier is shown above in terms of "a" parameters

Find the voltage gain of the amplifier

$$\text{Solu: } A_3 = A_1 A_2 = \begin{bmatrix} 3/2 & 25 \\ 1/20 & 2/3 \end{bmatrix} \cdot \begin{bmatrix} 3/2 & 25 \\ 1/20 & 2/3 \end{bmatrix} = \begin{bmatrix} 3/2 \cdot 3/2 + 25 \cdot 1/20 & 3/2 \cdot 25 + 25 \cdot 2/3 \\ 1/20 \cdot 3/2 + 2/3 \cdot 1/20 & 1/20 \cdot 25 + 2/3 \cdot 2/3 \end{bmatrix}$$

$$\begin{aligned} \text{Solu: } A_3 = A_1 \cdot A_2 &= \begin{bmatrix} 3/2 & 25 \\ 1/20 & 2/3 \end{bmatrix} \cdot \begin{bmatrix} 3/2 & 25 \\ 1/20 & 2/3 \end{bmatrix} = \begin{bmatrix} 3/2 \cdot 3/2 + 25 \cdot 1/20 & 3/2 \cdot 25 + 25 \cdot 2/3 \\ 1/20 \cdot 3/2 + 2/3 \cdot 1/20 & 1/20 \cdot 25 + 2/3 \cdot 2/3 \end{bmatrix} \\ &= \begin{bmatrix} 9/4 + 25/20 & 75/2 + 50/3 \\ 3/40 + 2/60 & 25/20 + 4/9 \end{bmatrix} \\ &= \begin{bmatrix} 3.5 & 54.1667 \\ 0.10833 & 1.6944 \end{bmatrix} \end{aligned}$$

$$\therefore \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 3.5 & 54.1667 \\ 0.10833 & 1.6944 \end{bmatrix} \begin{bmatrix} V_0 \\ -I_2' \end{bmatrix}$$

$$\text{gain? } \frac{V_0}{V_s} = ?$$

$$\text{KVL: } V_s - 1000I_1 - V_1 = 0 \Rightarrow V_s = 1000I_1 + V_1$$

$$V_0 = -5000I_2' \Rightarrow$$

$$\frac{V_0}{V_s} = \frac{-5000I_2'}{1000I_1 + V_1} = \frac{-5000I_2'}{1000[0.10833 \cdot V_0 - 1.6944I_2'] + [3.5 \cdot V_0 - 54.1667I_2']}$$

$$\frac{V_0}{V_s} = \frac{-5000I_2'}{108.33V_0 - 1694.4I_2' + 3.5V_0 - 54.1667I_2'}$$

$$= \frac{-5000I_2'}{111.83V_0 - 1748.57I_2'}$$

$$= \frac{-5000I_2'}{111.83(-5000I_2') - 1748.57I_2'}$$

$$\boxed{\frac{V_0}{V_s} = 0.00891 = \text{gain}}$$

Hybrid Parameters  $\rightarrow$  H parameters

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad \text{short circuit input impedance}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} \quad \text{short circuit forward current gain}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad \text{open circuit reverse voltage gain}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} \quad \text{open circuit output admittance}$$

$$\left. \begin{array}{l} h_{11} \approx h_{ie} \\ h_{12} \approx h_{re} \\ h_{21} \approx h_{fe} \\ h_{22} \approx h_{oe} \end{array} \right\} \text{for E315}$$