



What Every Electrical Engineer Should Know about *Nonlinear* Circuits and Systems

Michael Peter Kennedy FIEEE
University College Cork, Ireland



*IEEE CAS Society, Santa Clara Valley Chapter
05 August 2013*



www.tyndall.ie




Outline

2/168

- Part 1: Motivation and Key Concepts (70)
- Part 2: Examples (5 x 18)
 - SPIKE DC Analysis
 - Schmitt Trigger
 - Colpitts Oscillator
 - Injection-Locking
 - Digital Delta-Sigma Modulator




www.tyndall.ie




3/168

Part 1

Motivation and Key Concepts




www.tyndall.ie



Motivation and Key Concepts

4/168

- **Motivation**
 - Linear Systems
 - Nonlinear Systems
 - Nonlinear Effects
- **Key Concepts in Nonlinear Dynamical Systems**



www.tyndall.ie



Motivation

5/168

“It doesn’t matter how beautiful your theory is, it doesn’t matter how smart you are. If it doesn’t agree with experiment, it’s wrong.”

Richard P. Feynman



www.tyndall.ie




Linear Systems

6/168

- Global behavior
Unique solution; independent of initial conditions
- Frequencies don’t mix
- Tractable
- Exact solution
- Quantitative analysis




www.tyndall.ie




Nonlinear Systems

7/168

- Local and global behavior
 - Coexisting solutions; dependence on initial conditions
 - Small- and large-signal behavior
- What does “frequency” mean?
- Normally intractable
- Approximate solutions
- *Qualitative* analysis




www.tyndall.ie




“Static” (Memoryless) Nonlinearities

8/168

- “Weak” and “strong” nonlinearities
 - Harmonic distortion
 - Saturation
 - Non-monotonicity
 - Hysteresis?




www.tyndall.ie




Nonlinear Effects

9/168

- Harmonic distortion (superharmonics)
- Saturation
- Amplitude limiting
- Bistability
- “Hysteresis”
- Subharmonics
- Synchronization



www.tyndall.ie




Motivation

10/168


“...even the theory of the simplest valve oscillator cannot *in principle* be reduced to the investigation of a linear differential equation and *requires the study of a nonlinear equation.*”

...a linear equation, for example, cannot explain the fact that a valve oscillator, independently of the initial conditions, has a tendency to reach determined steady-state conditions.”

A.A. Andronov, A.A. Vitt, and S.E. Khaikin,
Theory of Oscillators, Pergamon Press, 1966




www.tyndall.ie




Examples

11/168

- SPICE DC Analysis
- Schmitt Trigger
- Colpitts Oscillator
- Injection-Locking
- Digital Delta-Sigma Modulator




www.tyndall.ie



Examples

12/168

- SPICE DC analysis: Why does my simulation not converge? Why does my oscillator not start in simulation?




www.tyndall.ie



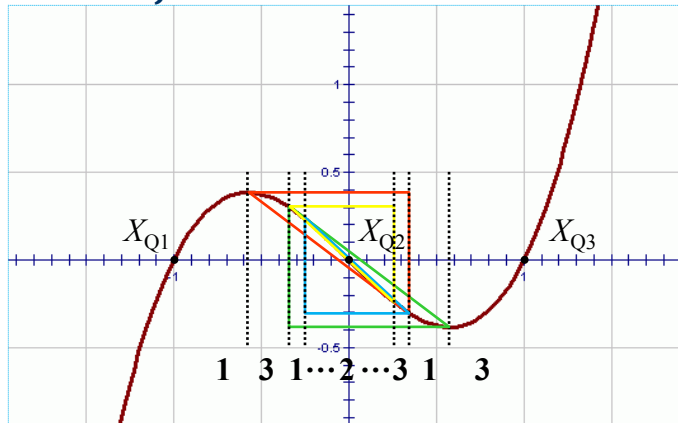Example: SPICE DC analysis

13/168

- The *basins of attraction* are intertwined...



www.tyndall.ie



Examples

14/168

- Schmitt Trigger: What happens between the switching thresholds?





www.tyndall.ie



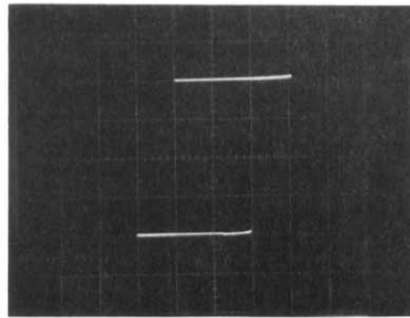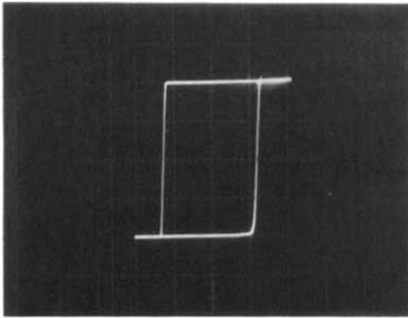Example: Schmitt trigger

15/168

- Voltage transfer characteristic (measured)



www.tyndall.ie



Examples

16/168

- Colpitts Oscillator: How large should the loop gain be?




www.tyndall.ie



Example: Colpitts Oscillator

17/168

- Design space

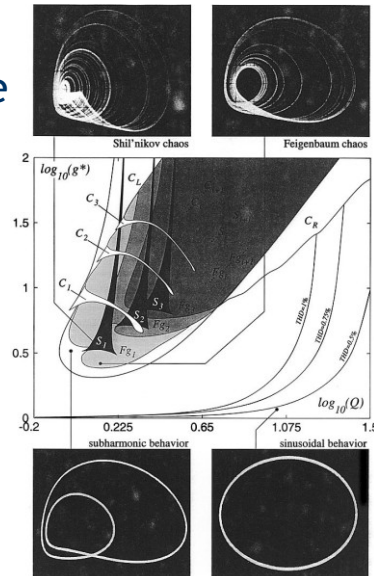

www.tyndall.ie




Examples

18/168

- Injection-Locking: What's the division ratio?



www.tyndall.ie




Example: Injection-Locking

19/168

- A point on line (d) of the sensitivity lines (Q=40).

$f_{in} = 20 \text{ MHz}$


 $f_{out} = 5 \text{ MHz}$

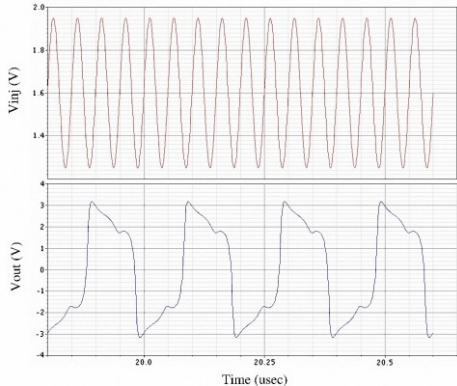

$V_{in} @ f_{in}$


Divide-by-4
ILFD

$V_{out} @ f_{out}$



$$f_0 = \frac{1}{2\pi\sqrt{LC}} = 10 \text{ MHz}$$

www.tyndall.ie



Examples

20/168

- Digital Delta Sigma Modulator: why do different values of the input yield different quantization noise spectra?


www.tyndall.ie



Example: DDSM

21/168

- Different *inputs* produce different spectra

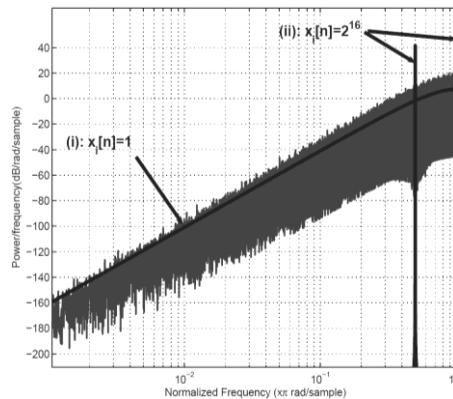

MASH 1-1-1

wordlength: 17 bits

- (i) $X=1$
- (ii) $X=2^{16}$



www.tyndall.ie



Motivation


22/168

“I've wondered why it took us so long to catch on.
We saw it and yet we didn't see it.
Or rather *we were trained not to see it...*
The truth knocks on the door and you say, 'Go
away, I'm looking for the truth,' and so it goes
away...”

Robert M. Pirsig,
Zen and the Art of Motorcycle Maintenance, Corgi, 1974




www.tyndall.ie




Motivation

23/168

The “truths” of
Nonlinear Circuits and Systems
can provide some valuable insights...




www.tyndall.ie



Nonlinear Dynamical Systems

24/168

- **Dynamical System**
 - State
 - State equations
 - Trajectories
- **Phase Portrait (effect of initial conditions)**
 - Non-wandering sets
 - Attractors
 - Basins of attraction
- **Bifurcation Diagram (parameters)**
 - Local and global bifurcations



www.tyndall.ie



Nonlinear Dynamical Systems

25/168

- A dynamical system comprises a *state space* and a *dynamic*
- The *state space* is the set of possible states of the system; it is also called the “phase space”
- The *dynamic* describes the evolution of the state with time; it is also called the “state equations” or the “equations of motion”



www.tyndall.ie



State Equations (Dynamic)

26/168

- Continuous time

$$\dot{\mathbf{X}}(t) = \mathbf{F}(\mathbf{X}(t); \mu)$$

- Discrete time

$$\mathbf{X}[n + 1] = \mathbf{G}(\mathbf{X}[n]; \mu)$$



www.tyndall.ie



Nonlinear Dynamical Systems

27/168

- The continuous- (discrete-) time system is *nonlinear* if \mathbf{F} (\mathbf{G}) is not linear in \mathbf{X}



www.tyndall.ie



Nonlinear Dynamical Systems

28/168

- A dynamical system follows a *trajectory* (orbit) through the state space
- The *flow* describes the evolution of all trajectories in the state space



www.tyndall.ie




Trajectories (Orbits)

29/168


- Continuous time
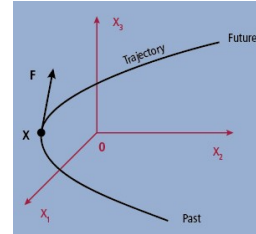
$$\mathbf{X}(t) = \phi_t(\mathbf{X}(0); \mu)$$



- Discrete time
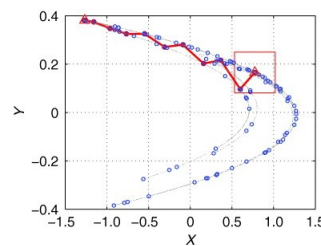
$$\mathbf{X}[n] = \phi_n(\mathbf{X}(0); \mu)$$



www.tyndall.ie



Nonlinear Dynamical Systems

30/168

- Nonlinear dynamics is concerned with:
 - (a) the *structure of the flow* (types of trajectories and their stability)
 - (b) its *dependence on the parameters* of the system (structural stability and bifurcations)



www.tyndall.ie



Phase Portrait and Bifurcation Diagram

31/168

- Phase portrait: Structure of the flow
- Bifurcation diagram: Dependence of the flow on the parameters




www.tyndall.ie



Phase Portrait

32/168

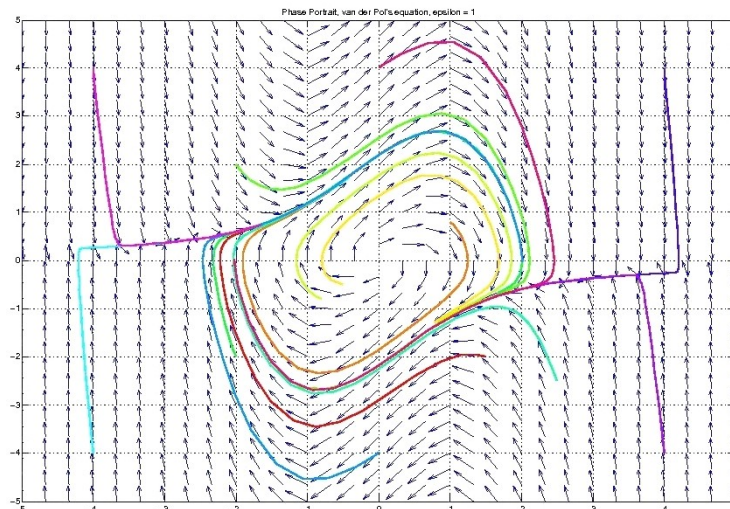


www.tyndall.ie



Phase Portrait

33/168

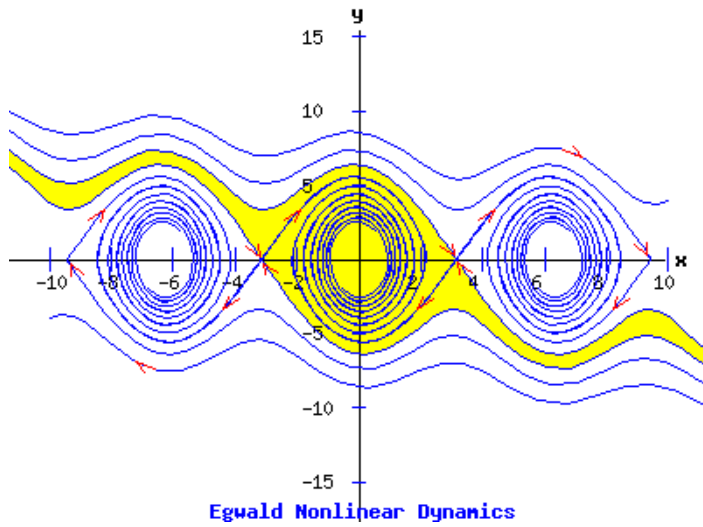


www.tyndall.ie



Phase Portrait

34/168

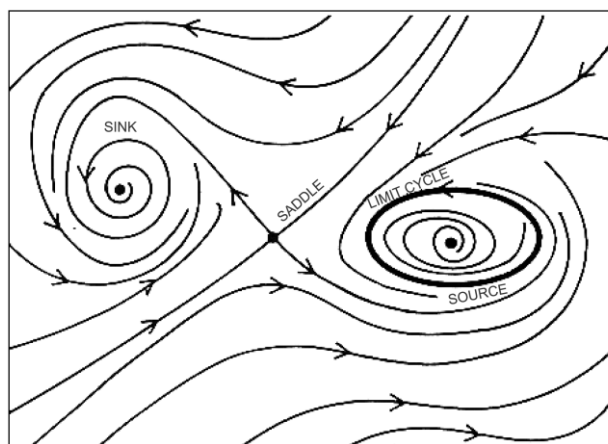

Source: Stewart (1989)




www.tyndall.ie



Bifurcation Diagram

35/168

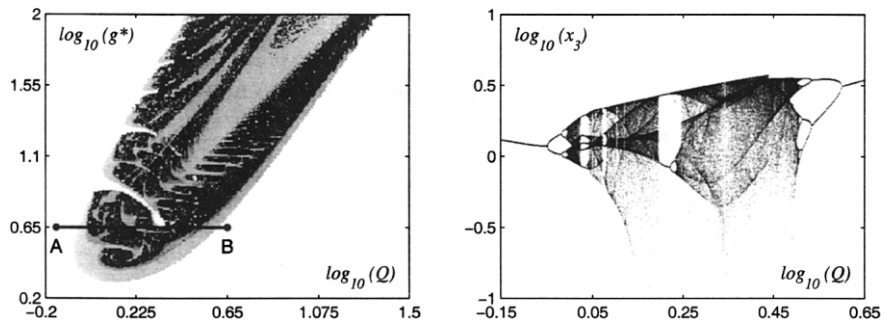


www.tyndall.ie



Bifurcation Diagram

36/168

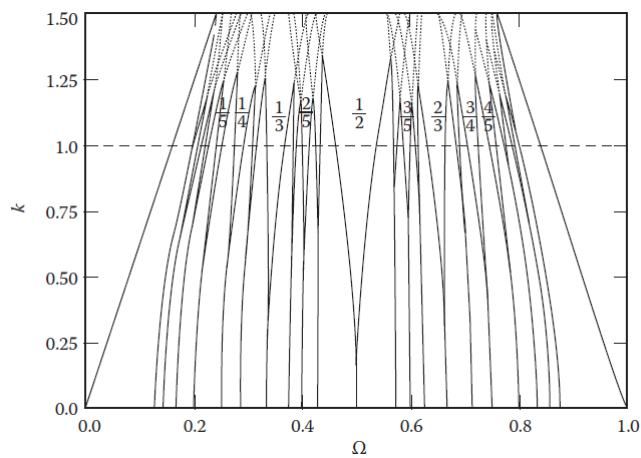

www.tyndall.ie



Structure of the Flow

37/168

- Types of trajectories
- Limit sets
- Stability of limit sets
- Attractors (“steady-state”)
- Basins of attraction/separatrices




www.tyndall.ie



Special Types of Trajectories

38/168

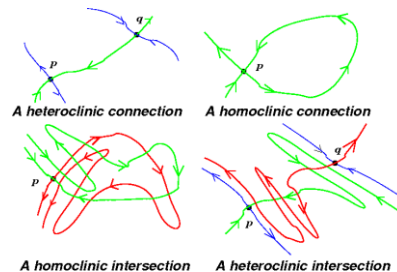- Equilibrium (fixed) point
- Periodic trajectory (cycle)
- Quasiperiodic trajectory (torus)
- Chaotic trajectory
- Heteroclinic trajectory
- Homoclinic trajectory



www.tyndall.ie



Non-Wandering Sets

39/168

- Equilibrium (fixed) point
- Periodic trajectory (cycle)
- Quasiperiodic trajectory (torus)
- Chaotic trajectory



www.tyndall.ie



Equilibrium (Fixed) Point

40/168

- Continuous time $\dot{\mathbf{X}}(t) = \mathbf{F}(\mathbf{X}(t); \mu)$

$$\mathbf{X}(t) = \mathbf{X}_Q$$

$$\mathbf{F}(\mathbf{X}_Q; \mu) = 0$$

- Discrete time $\mathbf{X}[n + 1] = \mathbf{G}(\mathbf{X}[n]; \mu)$

$$\mathbf{X}[n + 1] = \mathbf{X}_Q$$

$$\mathbf{G}(\mathbf{X}_Q; \mu) = \mathbf{X}_Q$$



www.tyndall.ie





Periodic Trajectory (Cycle)

41/168

- Continuous time $\dot{\mathbf{X}}(t) = \mathbf{F}(\mathbf{X}(t); \mu)$

$$\mathbf{X}(t + T) = \mathbf{X}(t)$$

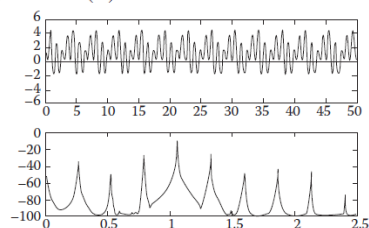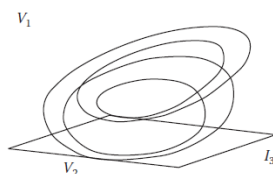

- Discrete time $\mathbf{X}[n + 1] = \mathbf{G}(\mathbf{X}[n]; \mu)$

$$\mathbf{X}[n + N] = \mathbf{X}[n]$$





www.tyndall.ie



Quasiperiodic Trajectory (Torus)

42/168

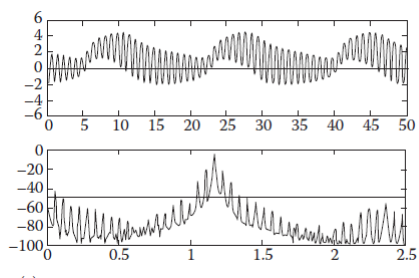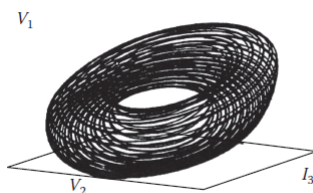- Continuous time $\dot{\mathbf{X}}(t) = \mathbf{F}(\mathbf{X}(t); \mu)$



www.tyndall.ie





Chaotic Trajectory

43/168

- Continuous time
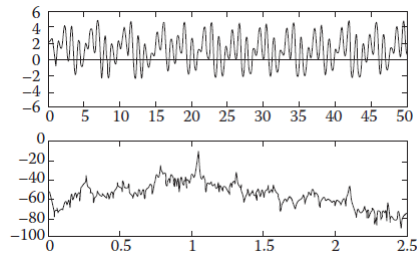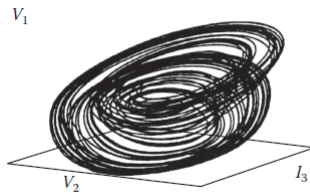
$$\dot{\mathbf{X}}(t) = \mathbf{F}(\mathbf{X}(t); \mu)$$




www.tyndall.ie



Stability of Non-Wandering Sets

44/168

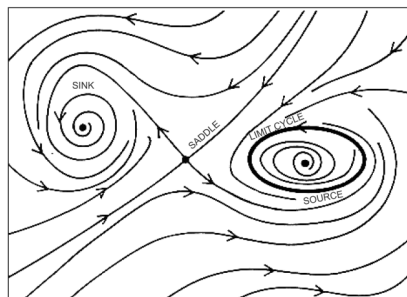- ω limit sets
- Attracting (or not)
- Basin of attraction



Source: Stewart (1989)



www.tyndall.ie



Stability of Non-Wandering Sets: Techniques

45/168

- Linearization (local behavior; “small-signal” analysis)
- Eigenvalues (negative or positive real parts [CT]; magnitudes less than or greater than unity [DT])



www.tyndall.ie



Stability of Non-Wandering Sets: Techniques

46/168

- Poincaré maps (reduce CT system to equivalent lower order DT system)
- Lyapunov exponents (generalized notion of stability)



www.tyndall.ie



Equilibrium (Fixed) Point

47/168

- Continuous time $\dot{\mathbf{X}}(t) = \mathbf{F}(\mathbf{X}(t); \mu)$

$$\dot{\mathbf{x}}(t) = D_{\mathbf{X}}\mathbf{F}(\mathbf{X}_Q; \mu) \mathbf{x}(t)$$

- Discrete time $\mathbf{X}[n+1] = \mathbf{G}(\mathbf{X}[n]; \mu)$

$$\mathbf{x}[n+1] = D_{\mathbf{X}}\mathbf{G}(\mathbf{X}_Q; \mu) \mathbf{x}[n]$$



www.tyndall.ie



Linearization (Jacobian)

48/168

$$D_{\mathbf{X}}\mathbf{F} = \begin{pmatrix} \frac{\partial F_1}{\partial X_1} & \frac{\partial F_1}{\partial X_2} & \cdots & \frac{\partial F_1}{\partial X_N} \\ \frac{\partial F_2}{\partial X_1} & \frac{\partial F_2}{\partial X_2} & \cdots & \frac{\partial F_2}{\partial X_N} \\ \vdots & \vdots & \ddots & \vdots \\ \frac{\partial F_N}{\partial X_1} & \frac{\partial F_N}{\partial X_2} & \cdots & \frac{\partial F_N}{\partial X_N} \end{pmatrix}$$



www.tyndall.ie




Equilibrium (Fixed) Point

49/168

- Continuous time $\dot{\mathbf{X}}(t) = \mathbf{F}(\mathbf{X}(t); \mu)$
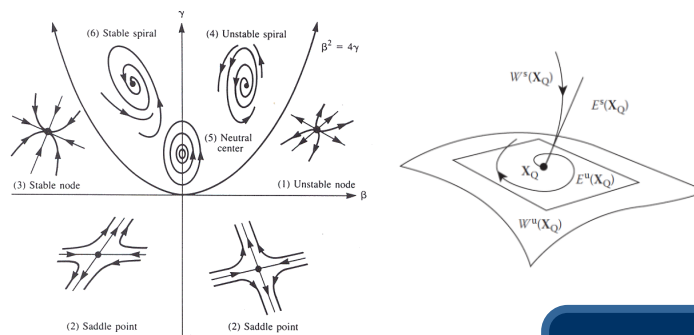
$$\dot{\mathbf{x}}(t) = D_{\mathbf{X}}\mathbf{F}(\mathbf{X}_Q; \mu) \mathbf{x}(t)$$



www.tyndall.ie




Periodic Trajectory (Cycle)

50/168

- Continuous time $\dot{\mathbf{X}}(t) = \mathbf{F}(\mathbf{X}(t); \mu)$

Poincaré map

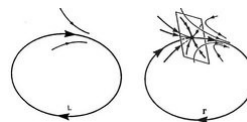


- Discrete time $\mathbf{X}[n+1] = \mathbf{G}(\mathbf{X}[n]; \mu)$

$$\mathbf{x}[n+1] = D_{\mathbf{X}}\mathbf{G}^N(\mathbf{X}_Q; \mu) \mathbf{x}[n]$$



www.tyndall.ie






Poincaré Map

51/168


- Continuous time $\dot{\mathbf{X}}(t) = \mathbf{F}(\mathbf{X}(t); \mu)$

Poincaré map
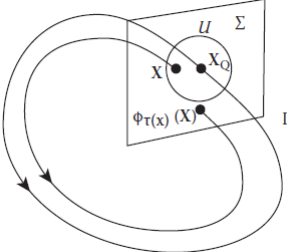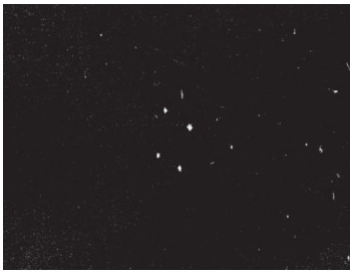
$$\mathbf{X}[n + 1] = \mathbf{G}(\mathbf{X}[n]; \mu)$$


www.tyndall.ie





Quasiperiodic Trajectory (Torus)

52/168

- Continuous time $\dot{\mathbf{X}}(t) = \mathbf{F}(\mathbf{X}(t); \mu)$

Poincaré map

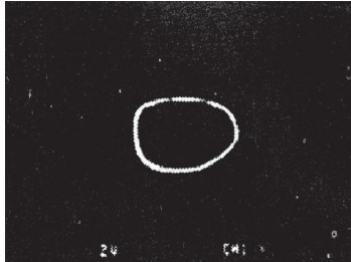

$$\mathbf{X}[n + 1] = \mathbf{G}(\mathbf{X}[n]; \mu)$$


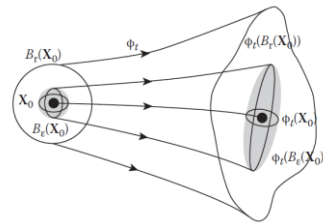
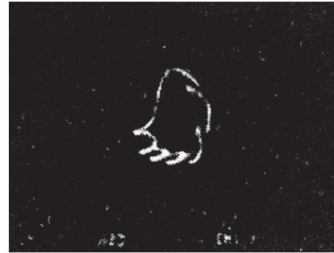
www.tyndall.ie



Chaotic Trajectory

53/168

- Poincaré map
- Lyapunov exponents



www.tyndall.ie




Summary: Phase Portrait

54/168


- Flow
- Non-wandering sets
- Special trajectories (heteroclinic and homoclinic connections)
- Separatrices
- ω limit sets (attractors; “steady states”)
- Basins of attraction



www.tyndall.ie

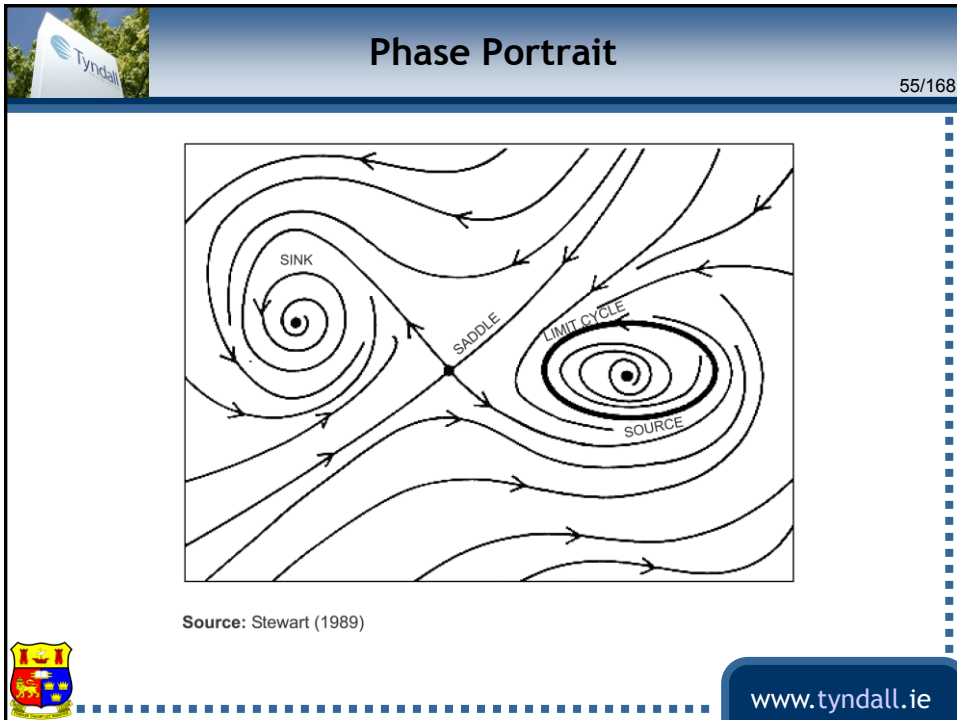


- ## Structural Stability
- 56/168
- A *structurally stable* dynamical system is one for which a small change in a parameter does not change the dynamics qualitatively
 - A *bifurcation* occurs if the qualitative dynamics change; the system is not structurally stable at the bifurcation point
- www.tyndall.ie




Bifurcations

57/168

- Local bifurcation: The stability of an equilibrium (or fixed) point changes
- Global bifurcation: A 'larger' invariant set, such as a periodic orbit, collides with an equilibrium



www.tyndall.ie




Bifurcations

58/168

- Local bifurcations
 - Saddle-node (fold, tangent) [Schmitt trigger]
 - Transcritical
 - Pitchfork [Bistable]
 - Period-doubling (flip)
 - Hopf ["Sinusoidal" oscillator]
- Global bifurcations
 - Homoclinic: limit cycle collides with a saddle
 - Heteroclinic: limit cycle collides with two or more saddles
 - Blue sky catastrophe: limit cycle collides with an unstable cycle


www.tyndall.ie



Local Bifurcations


59/168

- ### Saddle-node (fold, tangent)


A stable and an unstable equilibrium point collide and disappear

- ### Pitchfork

A stable equilibrium point goes unstable and two new stable equilibria appear



www.tyndall.ie



Local Bifurcations

60/168


- ### Period-doubling (flip)

A stable fixed point goes unstable with an eigenvalue equal to -1


- ### Hopf


A stable equilibrium point becomes unstable and a stable cycle appears

period doubling bifurcation

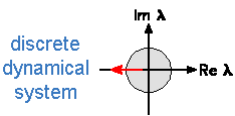

Hopf bifurcation

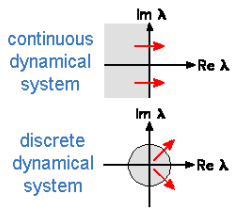



www.tyndall.ie



Saddle-Node Bifurcation [CT]

61/168


- State equation
- Equilibrium points
- Stability

$$\dot{X}(t) = \mu - X^2(t)$$

$$X_Q = \pm\sqrt{\mu}$$

$$\dot{x}(t) = (-2X_Q) x(t)$$

saddle-node bifurcation

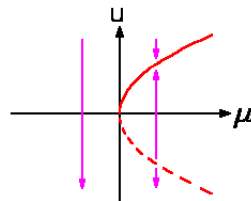

$$\dot{X}(t) = \mu - X^2(t)$$



www.tyndall.ie



Saddle-Node Bifurcation [DT]

62/168

- State equation
- Equilibrium points
- Stability

$$X[n+1] = X[n] + \mu - X^2[n]$$

$$X_Q = \pm\sqrt{\mu}$$

$$x[n+1] = (1 - 2X_Q) x[n]$$



www.tyndall.ie



Pitchfork Bifurcation [CT]


63/168

- State equation
- Equilibrium points
- Stability

$$\dot{X}(t) = \mu X(t) - X^3(t)$$

$$X_Q = 0, \pm\sqrt{\mu}$$

$$\dot{x}(t) = (\mu - 3X_Q^2) x(t)$$

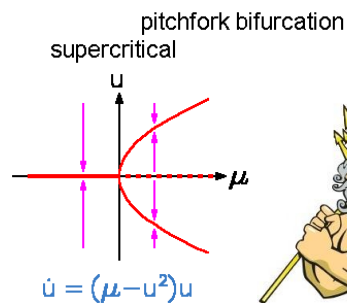

www.tyndall.ie



Pitchfork Bifurcation [DT]

64/168

- State equation
- Equilibrium points
- Stability

$$X[n+1] = X[n] + \mu X[n] - X^3[n]$$

$$X_Q = 0, \pm\sqrt{\mu}$$

$$x[n+1] = (1 + \mu - 3X_Q^2) x[n]$$





www.tyndall.ie



Period-Doubling Bifurcation [DT]

65/168

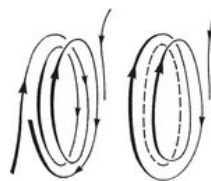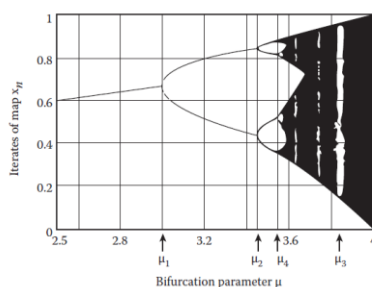- State equation $X[n+1] = \mu - X[n] - X^2[n]$
- Equilibrium point(s) $X_Q = -1 \pm \sqrt{1 + \mu}$
- Stability $x[n+1] = (-1 - 2X_Q)x[n]$



www.tyndall.ie




Hopf Bifurcation [CT]

66/168


- State equation

$$\begin{aligned}\dot{X}_1(t) &= \mu X_1(t) - \omega X_2(t) + (-X_1(t) - \beta X_2(t))(X_1^2(t) + X_2^2(t)) \\ \dot{X}_2(t) &= \omega X_1(t) + \mu X_2(t) + (\beta X_1(t) - X_2(t))(X_1^2(t) + X_2^2(t))\end{aligned}$$
- Equilibrium point
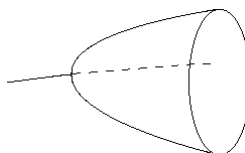
$$\begin{aligned}X_{1Q} &= 0 \\ X_{2Q} &= 0\end{aligned}$$
- Stability



www.tyndall.ie



Local Bifurcations

67/168


- Saddle-node (fold, tangent)**


A stable and an unstable equilibrium point collide and disappear
- Pitchfork**

A stable equilibrium point goes unstable and two new stable equilibria appear
- Period-doubling (flip)**

A stable fixed point goes unstable with eigenvalue equal to -1
- Hopf**

A stable equilibrium point becomes unstable and a stable cycle appears



www.tyndall.ie



Summary

68/168

- Part 1: Motivation and Basic Concepts**
 - Coexisting solutions
 - Bistability
 - “Hysteresis”
 - Synchronization
 - State space trajectories
 - Limit sets (steady-state solutions) and basins of attraction
 - Structural stability
 - Bifurcations (saddle-node, pitchfork, period-doubling, Hopf)


www.tyndall.ie



References: Nonlinear Dynamics

69/168

- [K93a] M.P. Kennedy. Three steps to chaos part I: Evolution. *IEEE Trans. Circuits and Systems-Part I: Fundamental Theory and Applications*, 40(10):640-656, October 1993.
- [K93b] M.P. Kennedy. Three steps to chaos part II: A Chua's circuit primer. *IEEE Trans. Circuits and Systems-Part I: Fundamental Theory and Applications*, 40(10):657-674, October 1993.
- [K94] M.P. Kennedy. Basic concepts of nonlinear dynamics and chaos. In C. Toumazou, editor, *Circuits and Systems Tutorials*, pages 289-313. IEEE Press, London, 1994.



www.tyndall.ie




References: Nonlinear Dynamics

70/168

- [NBb] A.H. Nayfeh and B. Balachandran. *Applied Nonlinear Dynamics*. Wiley, 1995.
- [S01] S.H. Strogatz. *Nonlinear Dynamics And Chaos: With Applications To Physics, Biology, Chemistry, And Engineering*. Perseus Books, 2001.




www.tyndall.ie



Part 2: Examples

71/168

- SPICE DC Analysis (intertwined basins of attraction)
- Schmitt Trigger (Saddle-node bifurcation)
- Colpitts Oscillator (Hopf bifurcation)
- Injection-Locking (Arnold tongues)
- Digital Delta-Sigma Modulator (Coexisting solutions)



www.tyndall.ie



Acknowledgements

72/168


- FIRB Italian National Research Program RBAP06L455
- Science Foundation Ireland Grant 08/IN1/I1854



Fondúireacht Eolaíochta Éireann
Science Foundation Ireland




www.tyndall.ie




73/168

Part 2

Examples




www.tyndall.ie



Examples

74/168

- SPICE DC Analysis (intertwined basins of attraction)
- Schmitt Trigger (Saddle-node bifurcation)
- Colpitts Oscillator (Hopf bifurcation)
- Injection-Locking (Arnold tongues)
- Digital Delta-Sigma Modulator (Coexisting solutions)



www.tyndall.ie



Example: SPICE DC analysis

75/168

- Local: Equilibrium (“operating”) point
- Global: Coexisting stable equilibrium points; multiple basins of attraction; complex separatrices



www.tyndall.ie



Example: SPICE DC analysis


76/168

- At each time point, SPICE solves a nonlinear circuit using Modified Nodal Analysis (MNA) and the Newton-Raphson algorithm

```
Transient loop :  
while the simulation is not over  
  Formulate companion models for energy storage  
  components, using current operating point  
  Newton loop :  
    while the convergence is not achieved  
      Formulate companion models for non-linear components,  
      using current operating point  
      Solve for new operating point  
    end while  
  end while
```



www.tyndall.ie

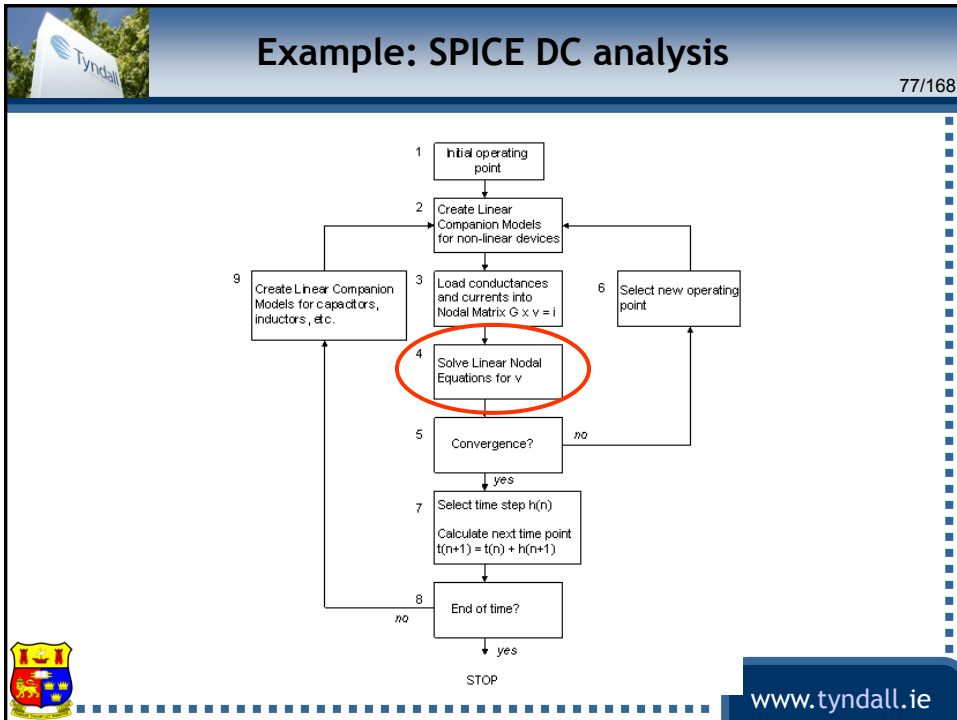

Example: SPICE DC analysis 78/168

- Modified Nodal Analysis (MNA)

$$M(X) = S$$

www.tyndall.ie



Example: SPICE DC analysis

79/168

- Use Newton-Raphson to solve

$$\mathbf{F}(\mathbf{X}) = \mathbf{0}$$

where

$$\mathbf{F}(\mathbf{X}) = \mathbf{M}(\mathbf{X}) - \mathbf{S}$$



www.tyndall.ie



Example: SPICE DC analysis

80/168

- Newton-Raphson is a *dynamical system*

$$\mathbf{X}[n+1] = \mathbf{X}[n] - D_{\mathbf{X}}\mathbf{F}^{-1}(\mathbf{X}[n])\mathbf{F}(\mathbf{X}[n])$$

with equilibrium (fixed) point(s) at

$$\mathbf{F}(\mathbf{X}) = \mathbf{0}$$




www.tyndall.ie



Example: SPICE DC analysis

81/168

- CMOS ILFD with direct injection

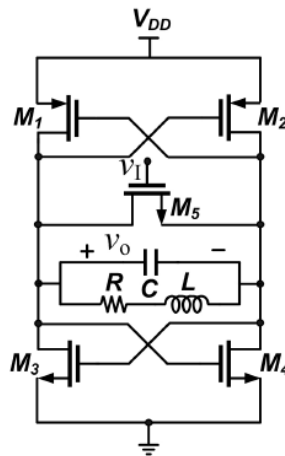

www.tyndall.ie




Example: SPICE DC analysis

82/168

- Simplified model
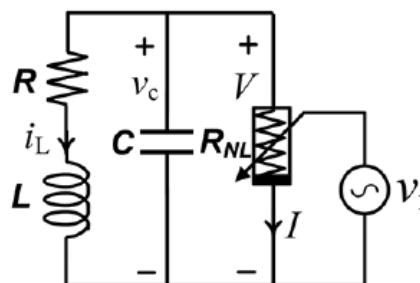
$$C \frac{dv_C}{dt} = -i_L - f(v_C, v_I),$$
$$L \frac{di_L}{dt} = v_C - R i_L,$$




www.tyndall.ie



Example: SPICE DC analysis

83/168

- Nonlinear resistor

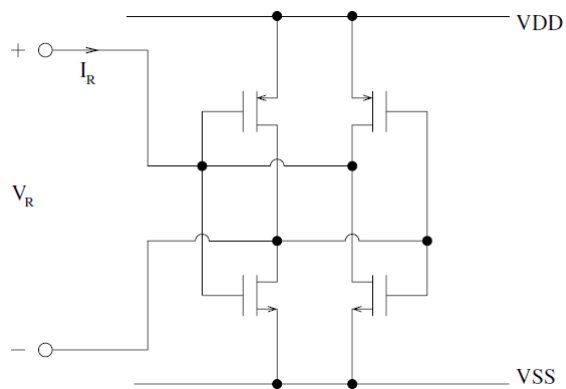



www.tyndall.ie



Example: SPICE DC analysis

84/168

- Nonlinear resistor

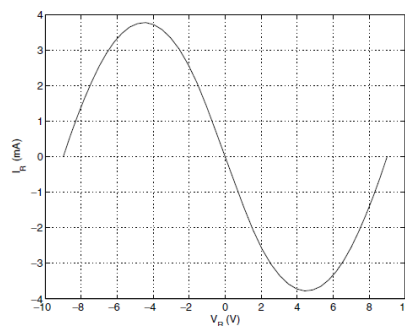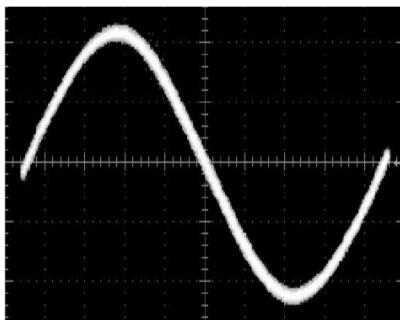

$$f(V) = G_a V \left(1 - \frac{V^2}{V_{\max}^2} \right)$$



www.tyndall.ie



Example: SPICE DC analysis

85/168

- Modified Nodal Analysis (MNA)

$$\frac{1}{R}V + f(V) = 0$$

where

$$f(V) = G_a V \left(1 - \frac{V^2}{V_{\max}^2} \right)$$



www.tyndall.ie



Example: SPICE DC analysis

86/168

- Use Newton-Raphson to solve

$$F(V) = 0$$

where

$$F(V) = \left(\frac{1}{R} + G_a \right) V + \left(- \frac{G_a}{V_{\max}^2} \right) V^3$$



www.tyndall.ie



Example: SPICE DC analysis

87/168

- Newton-Raphson is a dynamical system

$$X[n+1] = X[n] - \frac{F(X[n])}{\frac{d}{dX}F(X[n])}$$

with

$$F(X) = c_1X + c_3X^3$$

and

$$c_1 = \left(\frac{1}{R} + G_a \right), \quad c_3 = \left(-\frac{G_a}{V_{\max}^2} \right)$$



www.tyndall.ie



Example: SPICE DC analysis

88/168

- State equation

$$X[n+1] = X[n] - \left(\frac{c_1X[n] + c_3X^3[n]}{c_1 + 3c_3X^2[n]} \right)$$

- Equilibrium (fixed) points

$$X_Q = 0, \pm V_{\max} \sqrt{1 + \frac{1}{G_a R}}$$



www.tyndall.ie




Example: SPICE DC analysis

89/168

- The next state is obtained from the current state by following the tangent...
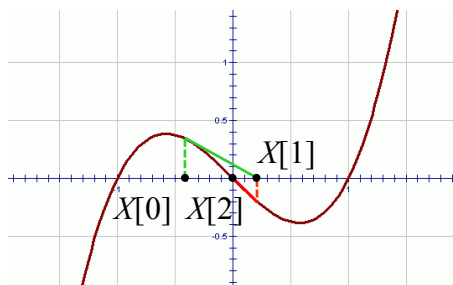
$$X[n+1] = X[n] - \frac{F(X[n])}{\frac{d}{dX}F(X[n])}$$




www.tyndall.ie



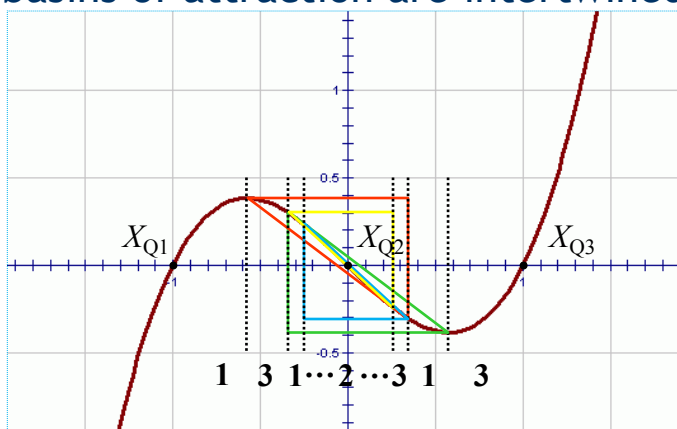
Example: SPICE DC analysis

90/168

- The basins of attraction are intertwined...




www.tyndall.ie



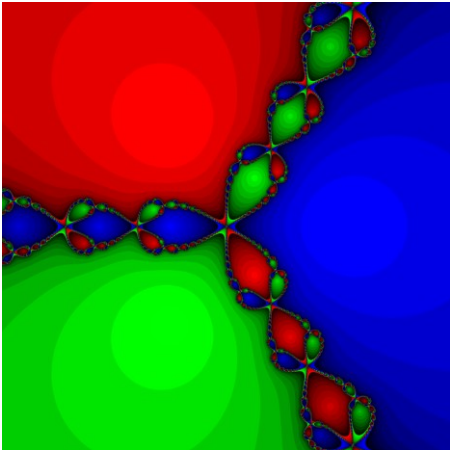
Example: SPICE DC analysis


91/168

- Intertwining can be very complicated...






www.tyndall.ie



Example: SPICE DC analysis

92/168

- Issues
 - Oscillation (of algorithm)
 - Unboundedness
 - “Missed” solution
 - No oscillation (of circuit)



www.tyndall.ie



Example: SPICE DC analysis

93/168

- Local: Equilibrium (“operating”) point
- Global: Coexisting stable equilibrium points; multiple basins of attraction; complex separatrices



www.tyndall.ie



Example: Schmitt trigger

94/168

- Local: Stable equilibrium point
- Global: Coexisting stable and unstable equilibrium points (“bistable”)
- Structural: Saddle-node (fold) bifurcations at transition points




www.tyndall.ie



Example: Schmitt trigger

95/168

- Circuit diagram

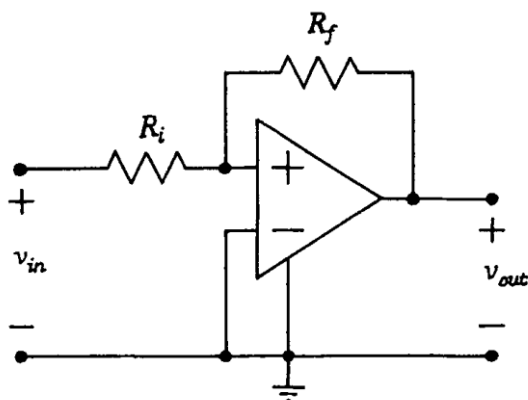


www.tyndall.ie



Example: Schmitt trigger

96/168

- Voltage transfer characteristic

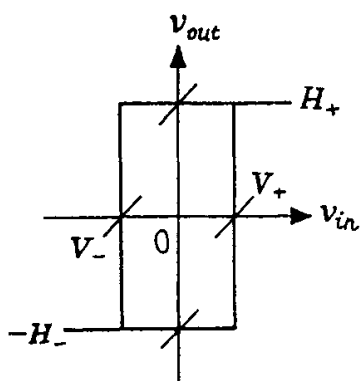



www.tyndall.ie



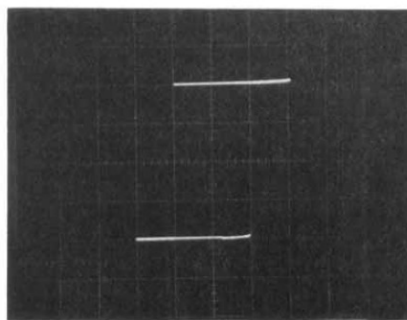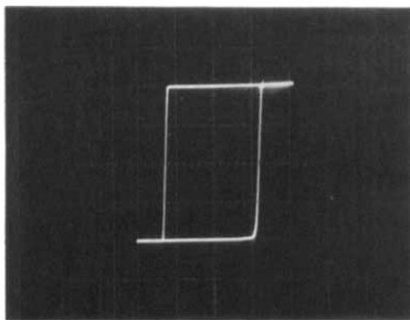Example: Schmitt trigger

97/168

- Voltage transfer characteristic (measured)




www.tyndall.ie




Example: Schmitt trigger

98/168

- Simplified model

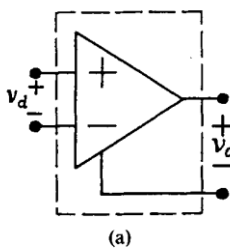

(a)

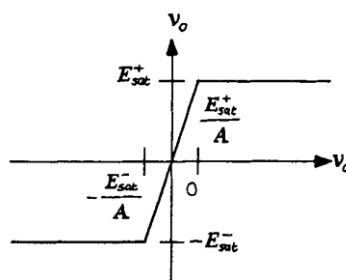

(b)

Figure 10. (a) Finite gain op amp model¹² and (b) its three-segment PWL voltage transfer characteristic




www.tyndall.ie



Example: Schmitt trigger

99/168

- Simplified model

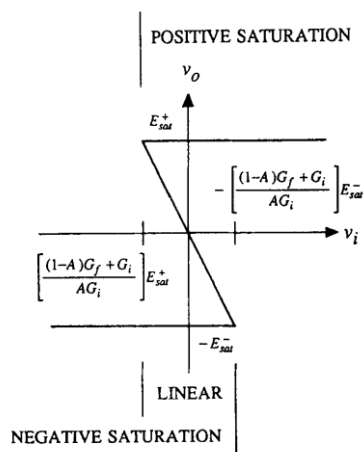


www.tyndall.ie



Example: Schmitt trigger

100/168

- Experimental verification

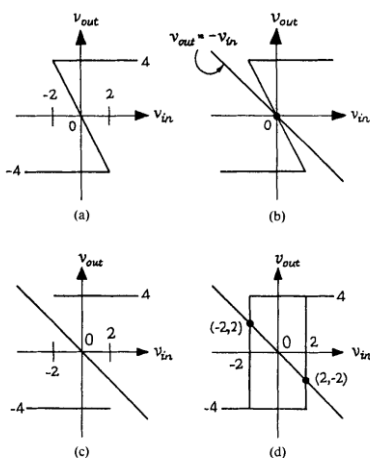

www.tyndall.ie



Example: Schmitt trigger

101/168

- Measurement circuit

$$u = -(v_{\text{out}} + v_{\text{in}})$$

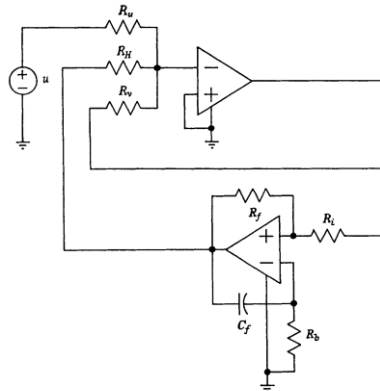


Figure 14. Op amp network for determining the TC of the Schmitt trigger of Figure 6. The circuit consists of an independent voltage source u (top left), an inverting summer (top) and a Schmitt trigger with AC feedback (bottom). $R_u = 20 \text{ k}\Omega$, $R_H = 20 \text{ k}\Omega$, $R_v = 20 \text{ k}\Omega$, $R_f = 20 \text{ k}\Omega$, $R_i = 20 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$, $R_3 = 470 \text{ }\Omega$, $C_f = 470 \text{ pF}$, op amps are 1/4 TL074




www.tyndall.ie



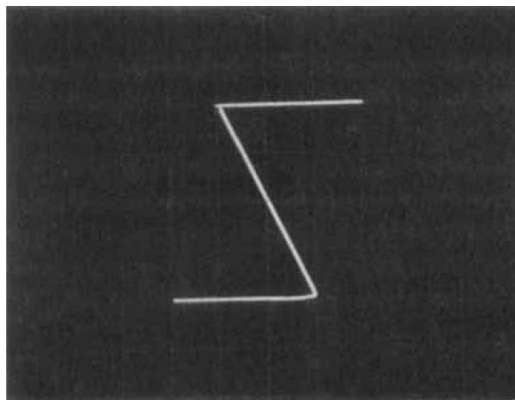Example: Schmitt trigger

102/168

- Voltage transfer characteristic (measured)




www.tyndall.ie



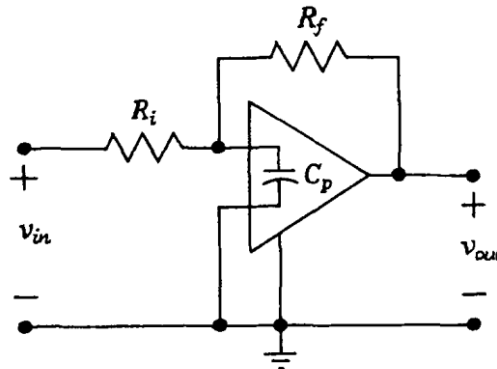Example: Schmitt trigger

103/168

- One parasitic capacitor is sufficient to explain the switching mechanism...




www.tyndall.ie



Example: Schmitt trigger

104/168

- Equivalent circuit

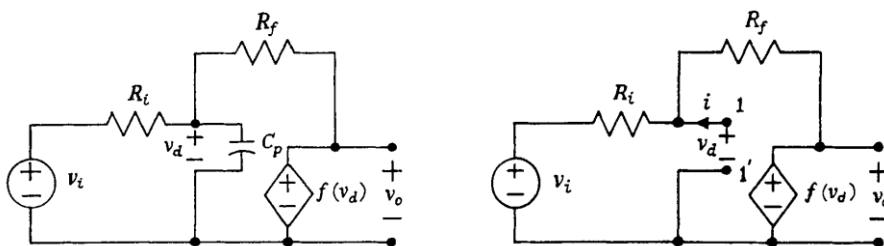

www.tyndall.ie




Example: Schmitt trigger

105/168

- Equivalent circuit
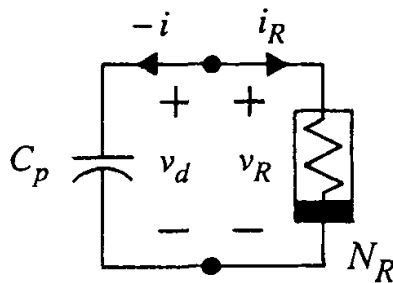
$$C_p \frac{dv_d}{dt} = G_i v_i + [G_f f(v_d) - G_f v_d - G_i v_d] = -g(v_d, v_i)$$




www.tyndall.ie



Example: Schmitt trigger

106/168



- Nonlinear resistor seen by parasitic

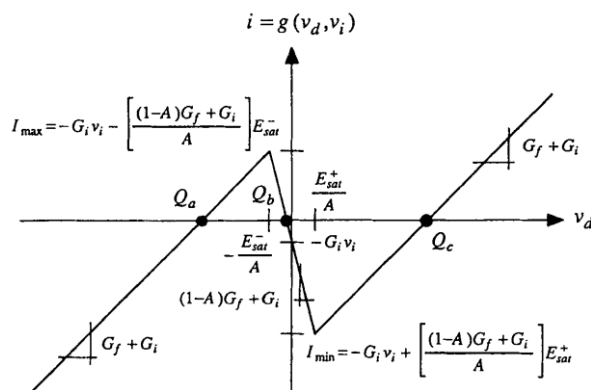

$$C_p \frac{dv_d}{dt} = G_i v_i + [G_f f(v_d) - G_f v_d - G_i v_d] = -g(v_d, v_i)$$



www.tyndall.ie

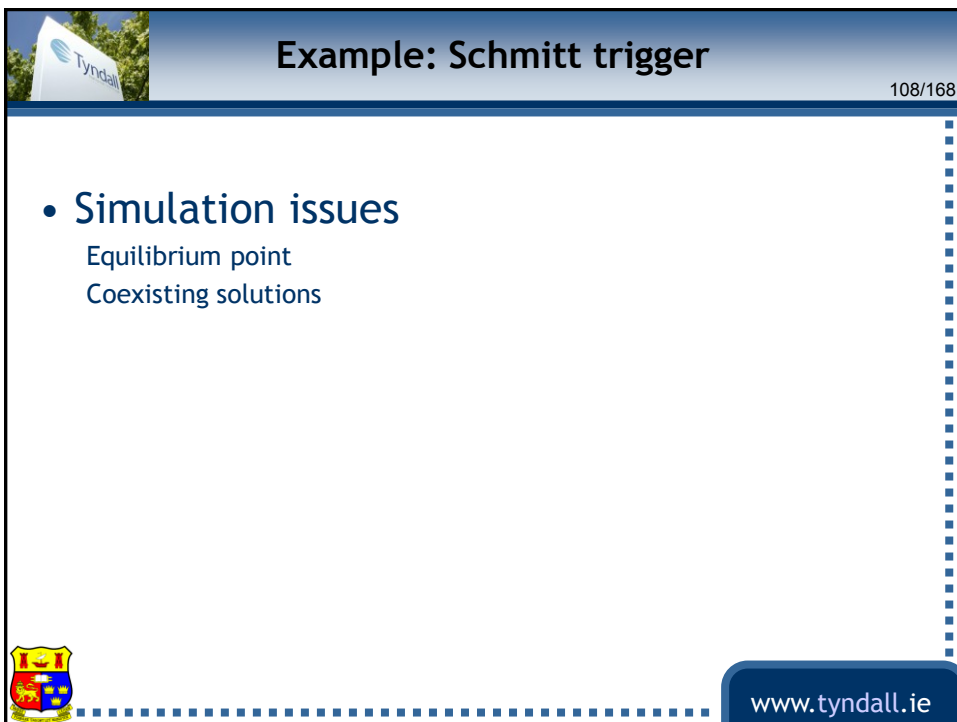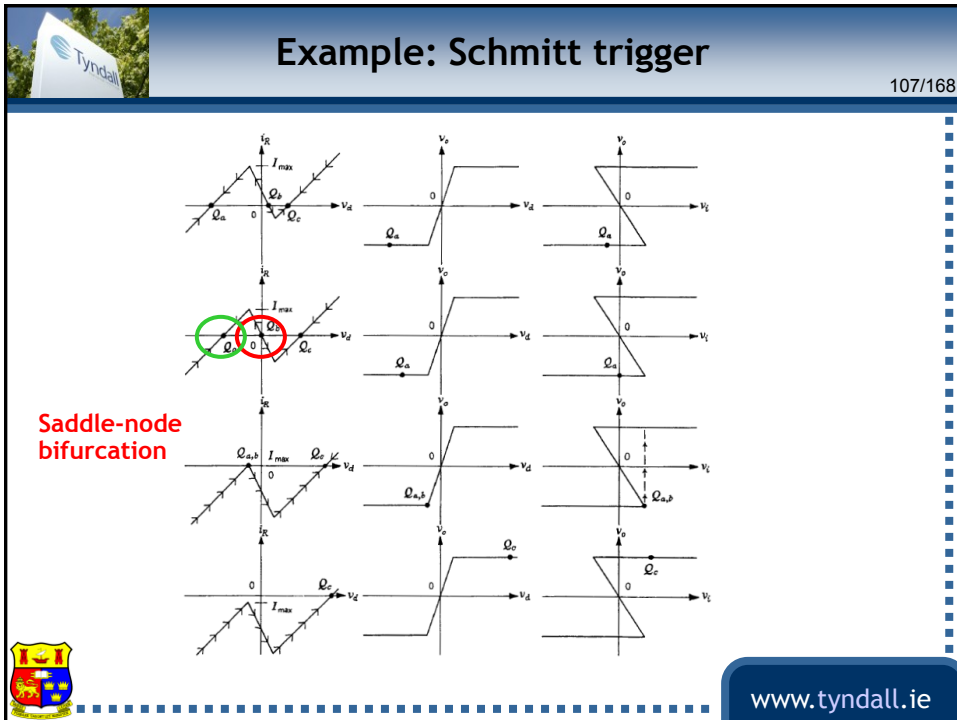



Example: Schmitt trigger

109/168

- Local: Stable equilibrium point
- Global: Coexisting stable and unstable equilibrium points (“bistable”)
- Structural: Saddle-node (fold) bifurcations at transition points



www.tyndall.ie



References: Hysteresis

110/168

[KC91] M.P. Kennedy and L.O. Chua. Hysteresis in electronic circuits: A circuit theorist's perspective. *Int. J. Circuit Theory Appl.*, 19(5):471-515, 1991.



www.tyndall.ie



Example: Colpitts Oscillator

111/168

- Local: Unstable equilibrium point; stable limit cycle
- Global: Amplitude-limiting mechanism
- Structural: Hopf bifurcation; period-doubling (flip) bifurcation




www.tyndall.ie



Example: Colpitts Oscillator

112/168

- Circuit diagram

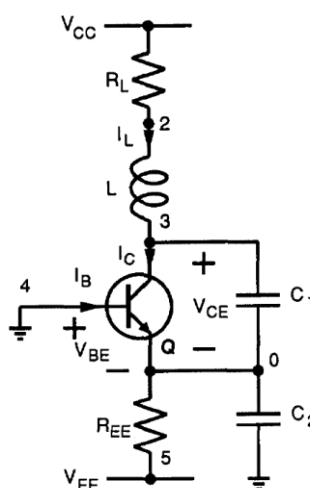

www.tyndall.ie



Example: Colpitts Oscillator

113/168

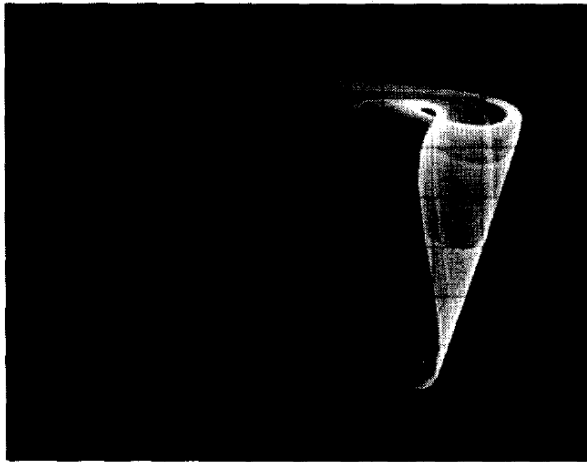


Fig. 2. Suspected chaotic attractor in the BJT Colpitts oscillator of Fig. 1.
Horizontal axis: V_{CE} (V); vertical axis V_{BE} (V).



www.tyndall.ie



Example: Colpitts Oscillator

114/168

- SPICE deck

```
vcc 1 4 pw1(0 0 1n 5 5m 5)
vee 5 4 dc -5
q1 3 4 0 Q2N2222A
rl 1 2 35
l1 2 3 98.5u
c1 3 0 54n
c2 4 0 54n
ree 0 5 400
```

```
.model Q2N2222A NPN(Is=14.34f
+ Xti=3 + Eg=1.11 Vaf=74.03
+ Bf=255.9 Ne=1.307 Ise=14.34f
+ Ikf=.2847 Xtb=1.5 Br=6.092
+ Nc=2 Isc=0 Ikr=0 Rc=1
+ Cjc=7.306p Mjc=.3416 Vjc=.75
+ Fc=.5 Cje=22.01p Mje=.377
+ Vje=.75 Tr=46.91n Tf=411.1p
+ Itf=.6 Vt=1.7 Xtf=3 Rb=10)

.options reltol=1e-4
.tran 10n 4m 3m
.end
```



www.tyndall.ie



Example: Colpitts Oscillator

117/168

- State equations

$$C_1 \frac{V_{CE}}{dt} = I_L - I_C$$

$$C_2 \frac{V_{BE}}{dt} = -\frac{V_{EE} + V_{BE}}{R_{EE}} - I_L - I_B$$

$$L \frac{I_L}{dt} = V_{CC} - V_{CE} + V_{BE} - I_L R_L.$$

$$I_B = \begin{cases} 0 & \text{if } V_{BE} \leq V_{TH} \\ \frac{V_{BE} - V_{TH}}{R_{ON}} & \text{if } V_{BE} > V_{TH}, \end{cases}$$

$$I_C = \beta_F I_B$$



www.tyndall.ie



Example: Colpitts Oscillator

118/168

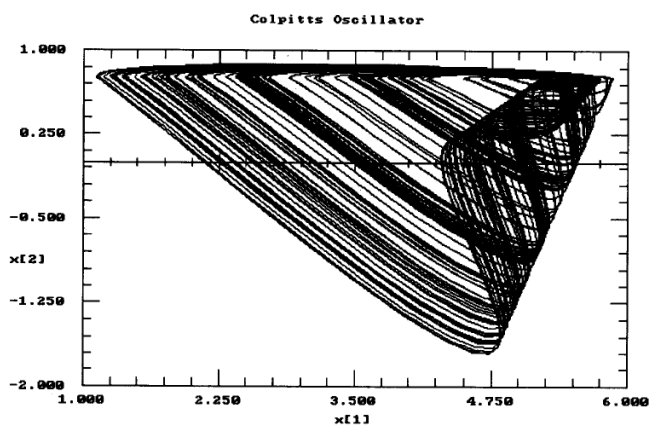


Fig. 5. INSITE simulation of the piecewise-linear BJT Colpitts oscillator model. Model parameters are: $V_{CC} = 5$ V, $R_L = 35$ Ω , $L = 98.5$ μ H, $C_1 = 54$ nF, $C_2 = 54$ nF, $R_{EE} = 400$ Ω , and $V_{EE} = -5$ V. The BJT is specified by three parameters: $V_{TH} = 0.75$ V, $R_{ON} = 100\Omega$, and $\beta_F = 200$. Horizontal axis: $x[1] = V_{CE}$ (V); vertical axis: $x[2] = V_{BE}$ (V).




www.tyndall.ie



Example: Colpitts Oscillator

119/168

- Alternative topology

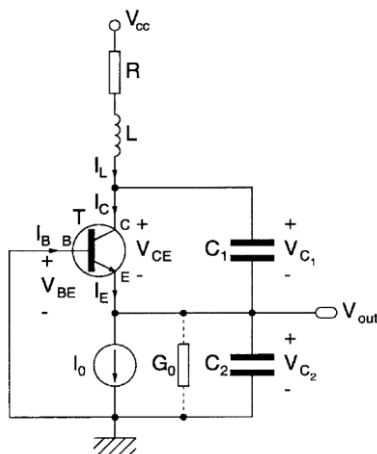

www.tyndall.ie



Example: Colpitts Oscillator

120/168

- State equations

$$C_1 \frac{dV_{C_1}}{dt} = -f(V_{C_2}) + I_L$$

$$C_2 \frac{dV_{C_2}}{dt} = I_L - I_0$$

$$L \frac{dI_L}{dt} = -V_{C_1} - V_{C_2} - RI_L + V_{CC}$$

$$f(V_{C_2}) = I_S \exp\left(-\frac{V_{C_2}}{V_T}\right)$$



www.tyndall.ie



Example: Colpitts Oscillator

121/168

- Normalized state equations

$$\begin{pmatrix} \dot{x}_1 \\ \dot{x}_2 \\ \dot{x}_3 \end{pmatrix} = \begin{pmatrix} \frac{g^*}{Q(1-k)}[-n(x_2) + x_3] \\ \frac{g^*}{Qk}x_3 \\ -\frac{Qk(1-k)}{g^*}[x_1 + x_2] - \frac{1}{Q}x_3 \end{pmatrix}$$

$$n(x_2) = \exp(-x_2) - 1$$

$$k = C_2/(C_1 + C_2)$$




www.tyndall.ie





Example: Colpitts Oscillator


122/168

- Phase portrait

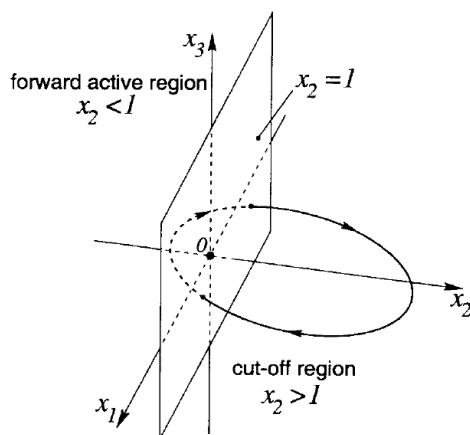

www.tyndall.ie

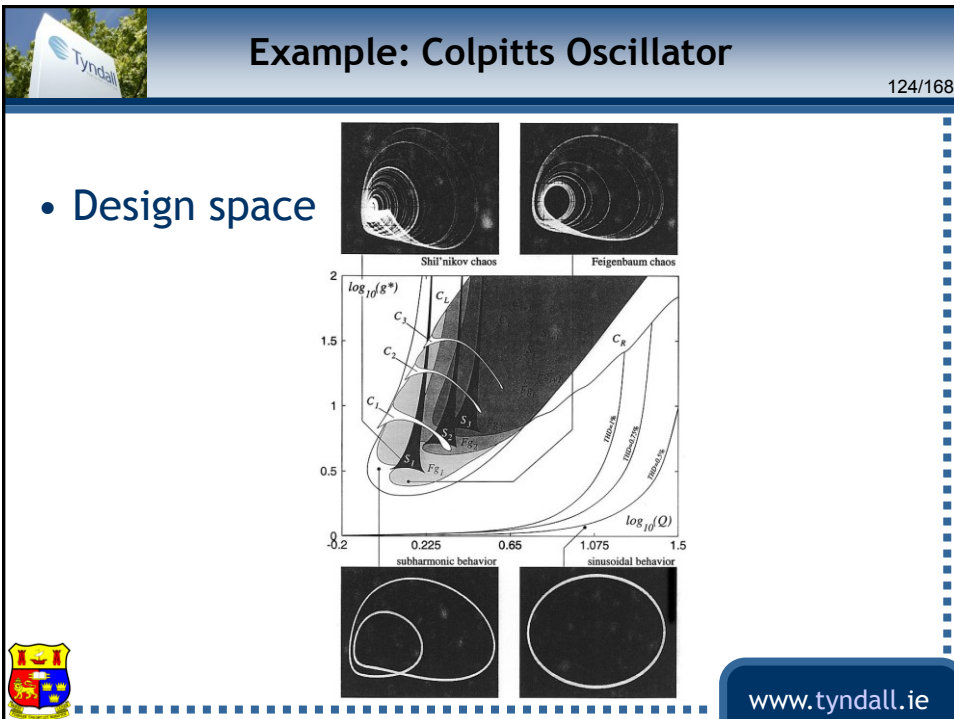
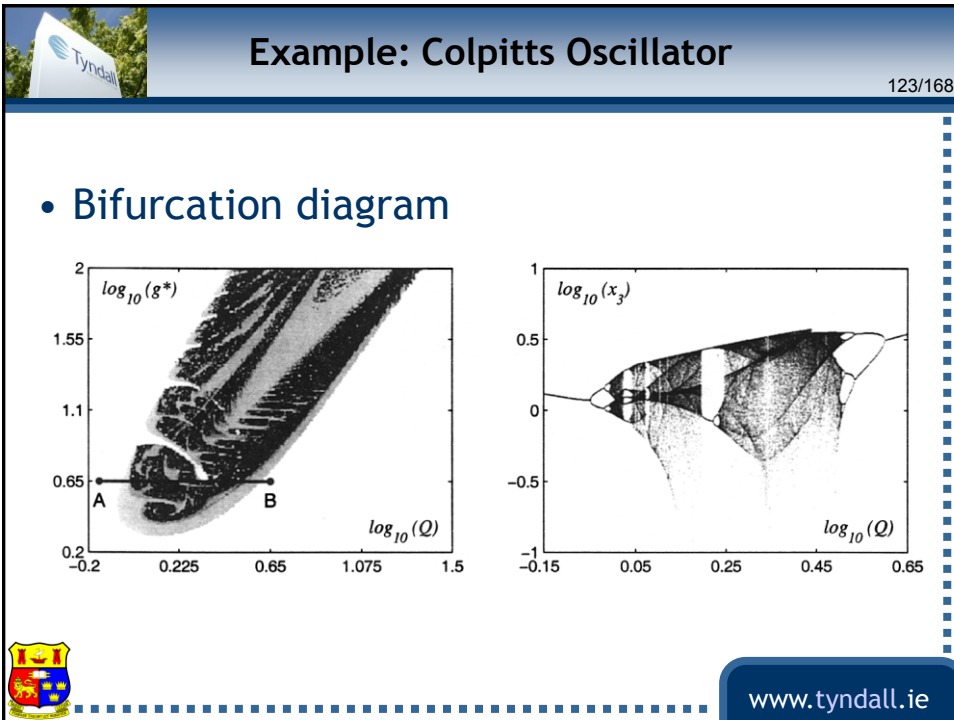




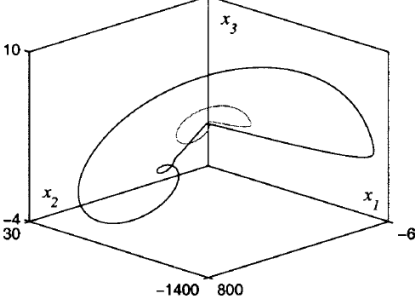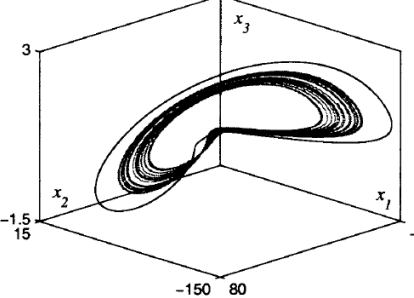
Example: Colpitts Oscillator


125/168

- Simulation issues
 - Equilibrium point
 - Coexisting solutions




www.tyndall.ie



Example: Colpitts Oscillator

126/168

- Local: Unstable equilibrium point; stable limit cycle
- Global: Amplitude-limiting mechanism
- Structural: Hopf bifurcation; period-doubling (flip) bifurcation



www.tyndall.ie



References: Colpitts Oscillator

127/168

- [K94] M.P. Kennedy. Chaos in the Colpitts oscillator. *IEEE Trans. Circuits and Systems-Part I*, 41(11):771-774, November 1994.
- [MdeFK99] G.M. Maggio, O.de Feo, and M.P. Kennedy. Nonlinear analysis of the Colpitts oscillator with applications to design. *IEEE Trans. Circuits and Systems-Part I: Fundamental Theory and Applications*, CAS-46(9):1118-1130, September 1999.



www.tyndall.ie



Example: Injection-Locking

128/168

- Local: Stable limit cycle
- Global: Arnold tongues
- Structural: Fold (?) bifurcation




www.tyndall.ie



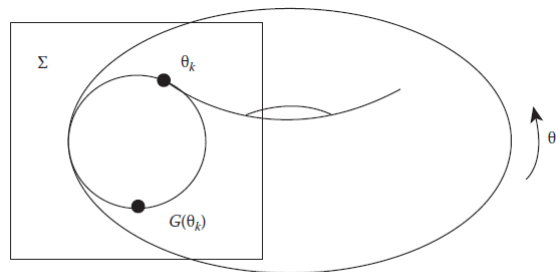Example: Injection-Locking

129/168

- Model of injection-locking: The Circle map



$$\theta_{k+1} = \left(\theta_k + \frac{K}{2\pi} \sin(2\pi\theta_k) + \Omega \right) \bmod 1, \quad k = 0, 1, 2, \dots$$




www.tyndall.ie



Example: Injection-Locking

130/168

- Bifurcation diagram (Arnold tongues)

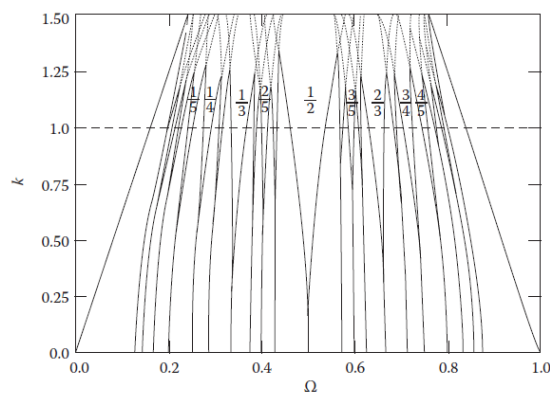


www.tyndall.ie



Example: Injection-Locking

131/168

- Devil's staircase

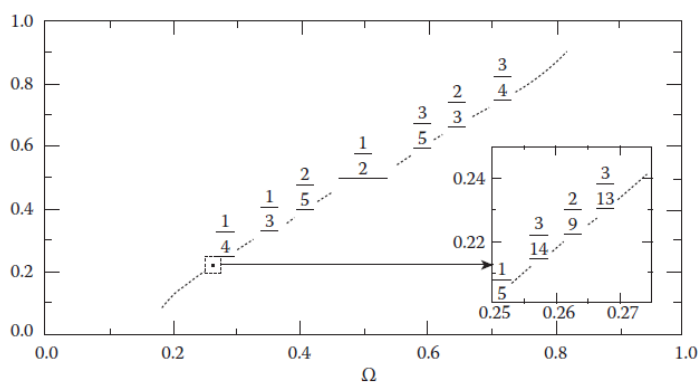


www.tyndall.ie



Example: Injection-Locking

132/168

- CMOS ILFD with tail coupling

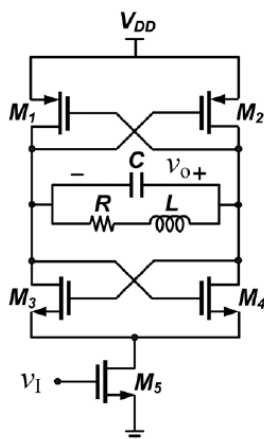

www.tyndall.ie




Example: Injection-Locking

133/168

- Simplified model

$$C \frac{dv_C}{dt} = -i_L - f(v_C, v_I),$$

$$L \frac{di_L}{dt} = v_C - R i_L,$$

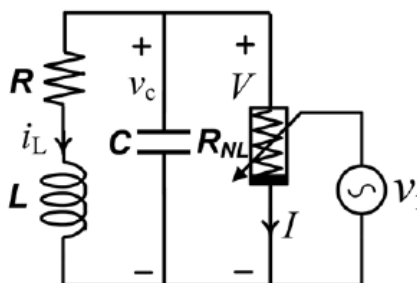

www.tyndall.ie




Example: Injection-Locking

134/168

- Nonlinearity
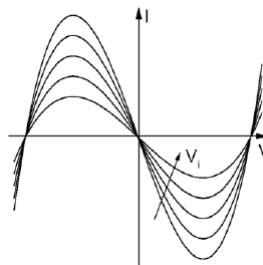
$$I_N = f(V_N, v_I) = -a(v_I) \cdot V_N \cdot \left(1 - \left(\frac{V_N}{V_{DD}}\right)^2\right)$$



$$a(v_I) \approx a(V_{dc}) + \left. \frac{\partial a(v_I)}{\partial v_I} \right|_{v_I=V_{dc}} \cdot V_i \cdot g(\omega_i t)$$

$$= a(V_{dc}) \left(1 + m_f \cdot g(\omega_i t)\right),$$



www.tyndall.ie



Example: Injection-Locking

135/168

- Normalized model $x = \frac{v_C}{V_{DD}}, \quad y = \frac{R i_L}{V_{DD}}, \quad \tau = \frac{t}{\sqrt{LC}},$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}, \quad G = R \cdot a(V_{dc}), \quad \omega = \omega_i \sqrt{LC},$$

$$\begin{aligned} \frac{dx}{d\tau} &= Q [-y + \mathcal{G}(\tau) x (1 - x^2)], \\ \frac{dy}{d\tau} &= \frac{1}{Q} (x - y), \end{aligned}$$



$$\mathcal{G}(\tau) = G (1 + m_f \cdot g(\omega\tau))$$

www.tyndall.ie




Example: Injection-Locking

136/168

$$\begin{cases} \frac{dx}{d\tau} = Q [-y + Gx(1 - x^2)] \\ \frac{dy}{d\tau} = \frac{1}{Q} (x - y) \end{cases}$$

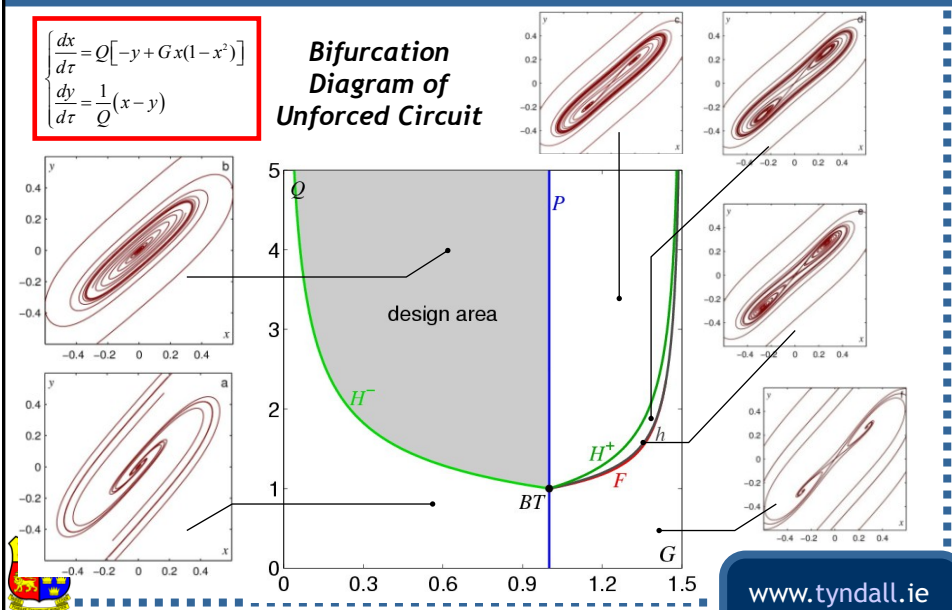**Bifurcation
Diagram of
Unforced Circuit**




www.tyndall.ie



Example: Injection-Locking

137/168

- Bifurcation diagram (simulated)

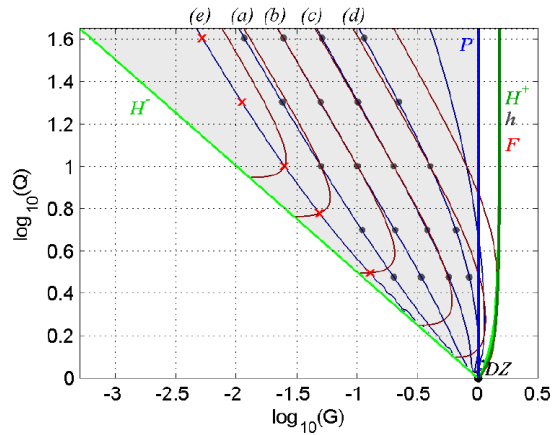


www.tyndall.ie




Example: Injection-Locking

138/168

- Bifurcation diagram (simulated)

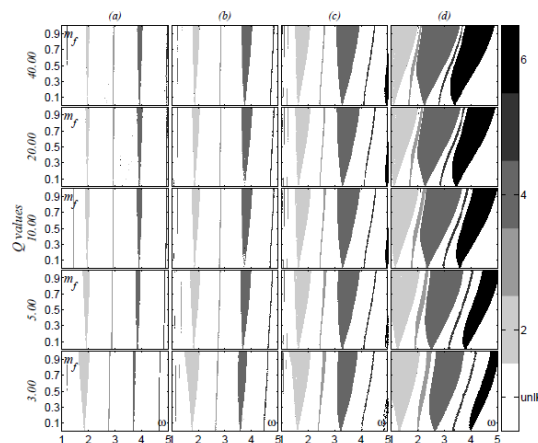

www.tyndall.ie



Example: Injection-Locking

139/168

- A point on line (d) of the sensitivity lines (Q=40).


$f_{in} = 20 \text{ MHz}$

$f_{out} = 5 \text{ MHz}$

$V_{in} @ f_{in}$


Divide-by-4
ILFD


$V_{out} @ f_{out}$



$$f_0 = \frac{1}{2\pi\sqrt{LC}} = 10 \text{ MHz}$$

www.tyndall.ie

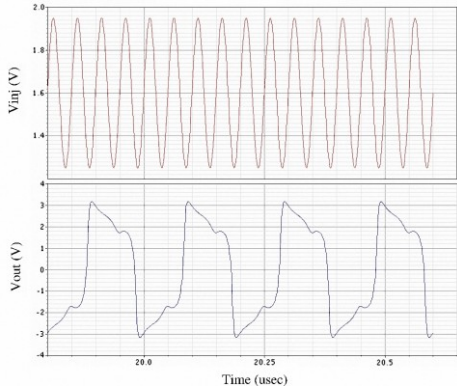





Example: Injection-Locking

140/168

- Experimental measurements

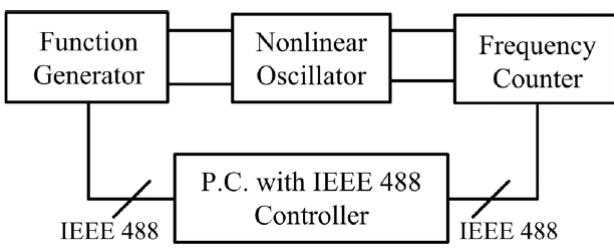




www.tyndall.ie



Example: Injection-Locking

141/168

- Bifurcation diagram (measured)

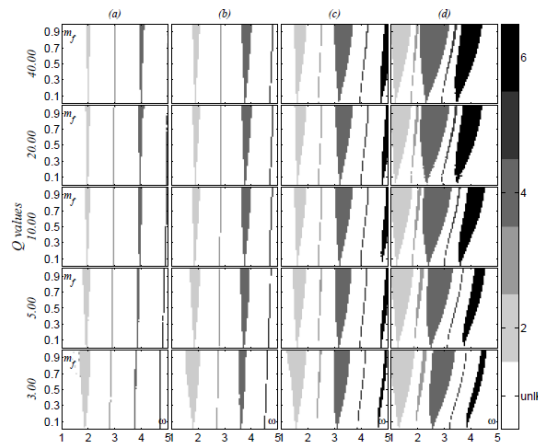


www.tyndall.ie



Example: Injection-Locking

142/168

- CMOS ILFD with direct injection

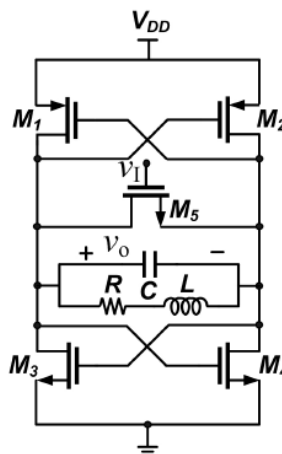


www.tyndall.ie



Example: Injection-Locking

143/168

- Bifurcation diagram (measured)

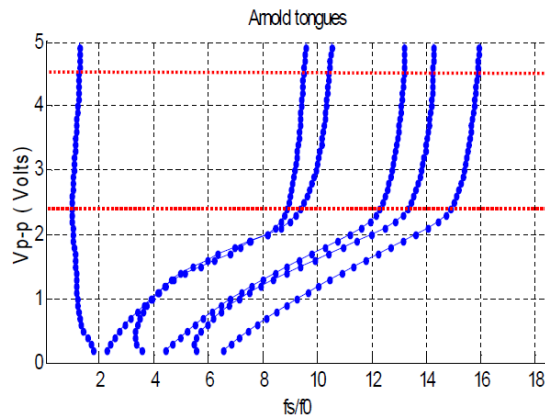


www.tyndall.ie




Example: Injection-Locking

144/168

- “Devil’s staircase” (measured)

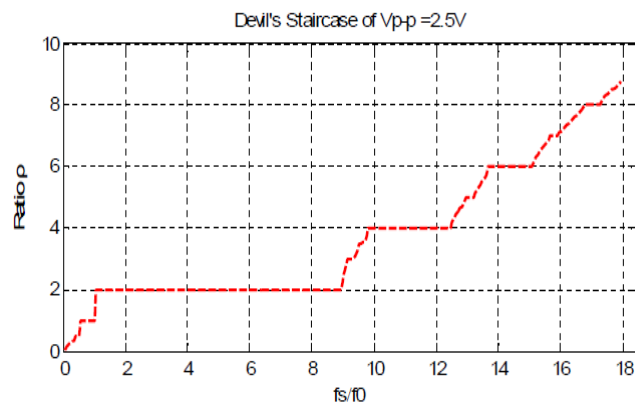


www.tyndall.ie




Example: Injection-Locking

145/168

- Simulation issues
 - Coexisting solutions
 - Long transients
 - Calculation of frequency ratio
 - Detecting periodicity




www.tyndall.ie



Example: Injection-Locking

146/168

- Local: Stable limit cycle
- Global: Arnold tongues
- Structural: Fold (?) bifurcation



www.tyndall.ie



References: Injection-Locking

147/168

- [O'DKFQJ05] K. O'Donoghue, M.P. Kennedy, P. Forbes, M. Qu, and S. Jones. A Fast and Simple Implementation of Chua's Oscillator with Cubic-like Nonlinearity. *Int. J. Bif. Chaos*. 15(9):2959-2971, September 2005.
- [DdeFK10] S. Daneshgar, O. De Feo and M.P. Kennedy. Observations Concerning the Locking Range in the Complementary Differential LC Injection-Locked Frequency Divider Part I: Qualitative Analysis. *IEEE Trans. Circuits and Systems-Part I*, 57(1):179-188, Jan. 2010.



www.tyndall.ie




Example: Digital Delta Sigma Modulator

148/168

- Local: unstable equilibrium
- Global: cycles; complex basins of “attraction”
- Structural: multiple nonlinearities




www.tyndall.ie




The ideal DDSM


149/168

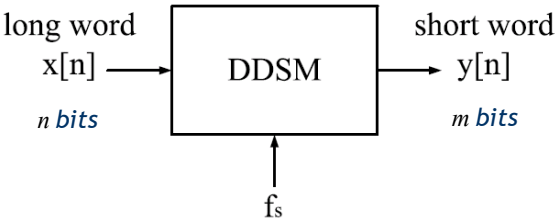- A bandlimited digital signal x (n bits) is requantized to a shorter word y (m bits)
- The additive quantization noise e is highpass filtered for later removal by a lowpass filter






www.tyndall.ie




The ideal DDSM

150/168

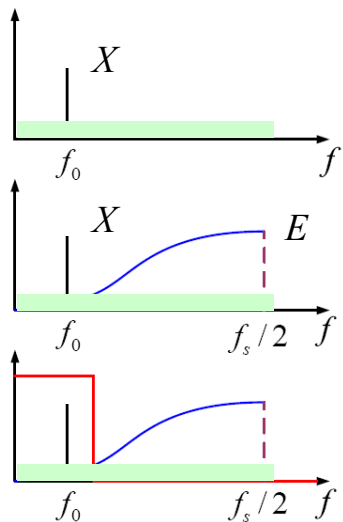- x is bandlimited
- y includes highpass filtered quantization noise
- quantization noise can be removed by lowpass filtering





www.tyndall.ie




Example: DDSM

151/168

- MASH: Higher order filtering with *exact* cancellation of intermediate errors

$$Y(z) = X(z) + E_l(z) (1-z^{-1})^l$$

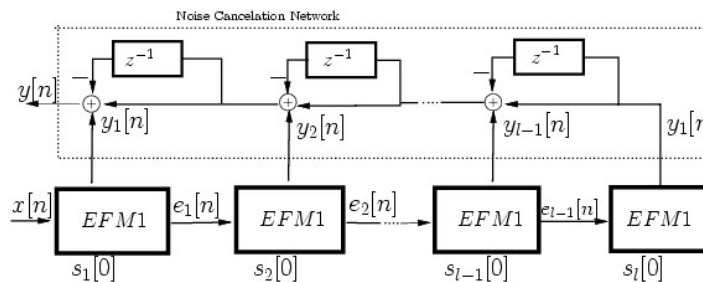

www.tyndall.ie



Example: DDSM

152/168

- 3rd order MASH

$$Y_1(z) = X(z) + E_1(z) (1-z^{-1})$$

$$Y_2(z) = -E_1(z) + E_2(z) (1-z^{-1})$$

$$Y_3(z) = -E_2(z) + E_3(z) (1-z^{-1})$$

$$\begin{aligned} Y(z) &= Y_1(z) + Y_2(z) (1-z^{-1}) + Y_3(z) (1-z^{-1})^2 \\ &= X(z) + E_3(z) (1-z^{-1})^3 \end{aligned}$$




www.tyndall.ie



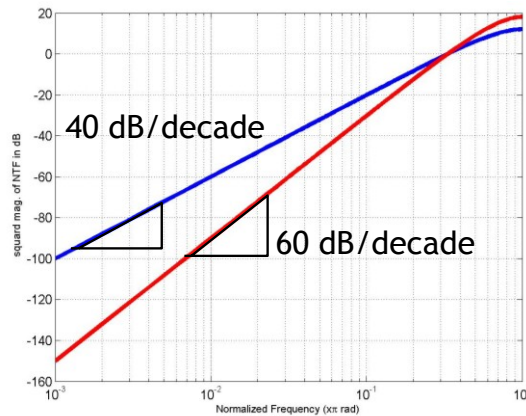Example: DDSM

153/168

- MASH: Idealized power spectra (white noise with 2nd and 3rd order filters)




www.tyndall.ie



Example: DDSM

154/168

- A MASH 1-1-1 with a constant input can produce *spurious tones* (spurs)

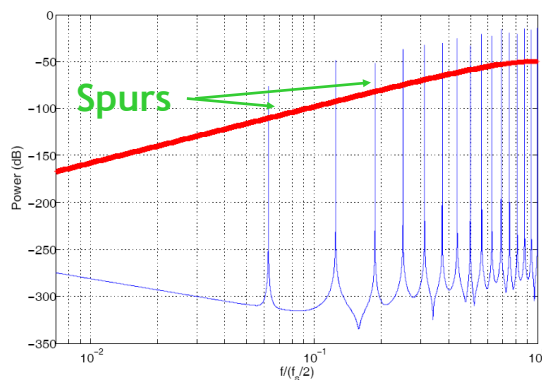

MASH 1-1-1

wordlength: 18 bits



www.tyndall.ie



Example: DDSM

155/168

- Different *wordlengths* can produce different spectra
- Different *initial conditions* can produce different spectra
- Different *inputs* can produce different spectra
- *All of the above* can cause spurs!




www.tyndall.ie



Example: DDSM

156/168

- Different *wordlengths* produce different spectra

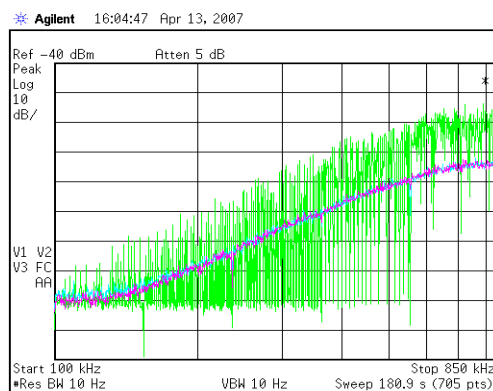

MASH 1-1-1

green plot: 9 bits

blue plot: 18 bits




www.tyndall.ie



Example: DDSM

157/168

- Different *initial conditions* produce different spectra

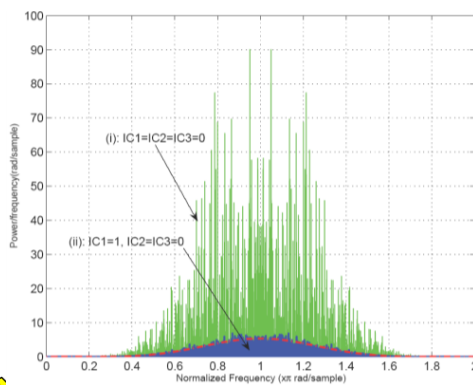

MASH 1-1-1

Input = 8 (decimal)

accumulator word length: 14 bits

cycle length for green plot: 4096

cycle length for blue plot: 32768

red plot: CMQ approximation




www.tyndall.ie



Example: DDSM

158/168

- Different *inputs* produce different spectra

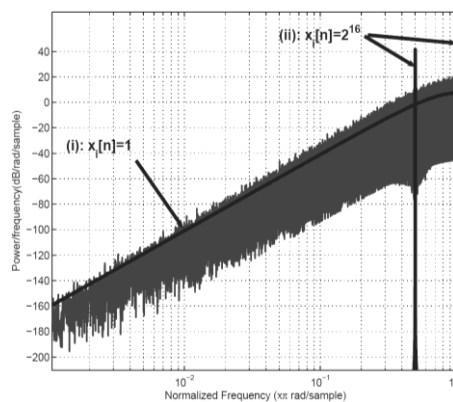

MASH 1-1-1


wordlength: 17 bits

(i) $X=1$

(ii) $X=2^{16}$



www.tyndall.ie




Example: DDSM


159/168

- The DDSM is a Finite State Machine (FSM)
- The FSM has a *finite* state space S (containing N_s states) and a *deterministic* rule G (called the *dynamic*) that governs the evolution of states
- The next state is determined *completely* by the current state and the input:

$$X[n+1] = G(X[n])$$




www.tyndall.ie



Example: DDSM

160/168

- If the input is fixed, the most complex trajectory visits each state in the state space *once* before repeating; the longest cycle has period $N = N_s - 1$
- In the worst case, the trajectory repeats with period $N = 4$



www.tyndall.ie



Stochastic approach

161/168

- Make the dynamic *stochastic*
- The next state depends on the current state s , the input x , and a *random* dither signal d

$$s[n+1] = G_S(s[n], x[n], d[n])$$

- Periodicity is destroyed
- Trajectories can be much longer than N_s




www.tyndall.ie



Stochastic approach: LSB dither

162/168

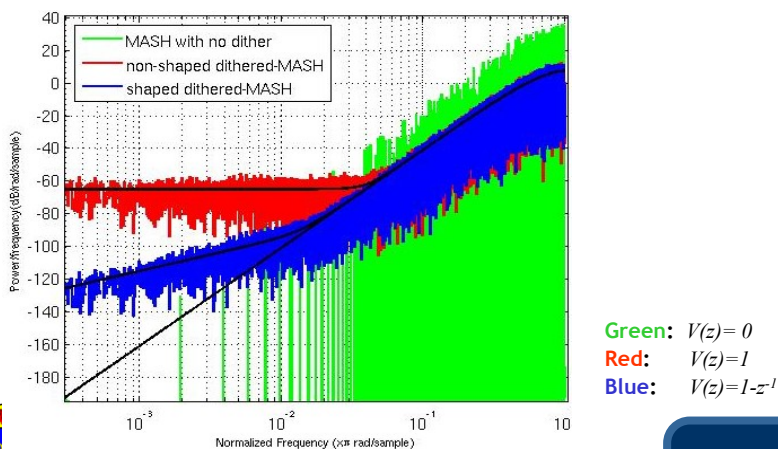- MASH 1-1-1 with LSB dither: $V(z) = (1-z^{-1})^R$




www.tyndall.ie



Deterministic approaches: ICs

163/168

- MASH 1-1-1: Choose $s_I[0]$ odd (“seeding”)

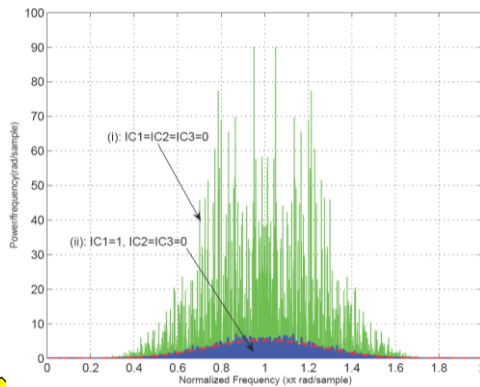

MASH 1-1-1

Input = 8 (decimal),

accumulator word length: 14 bits

cycle length for green plot: 4096

cycle length for blue plot: 32768



www.tyndall.ie




Example: DDSM

164/168

- Local: unstable equilibrium
- Global: cycles; complex basins of “attraction”
- Structural: multiple nonlinearities



www.tyndall.ie




References: DDSM

165/168


[HK07b] K. Hosseini and M.P. Kennedy. Maximum Sequence Length MASH Digital Delta-Sigma Modulators. *IEEE Trans. Circuits and Systems-Part I*, 54(12):2628-2638, Dec. 2007.

[HK08] K. Hosseini and M.P. Kennedy. Architectures for Maximum-Sequence-Length Digital Delta-Sigma Modulators. *IEEE Trans. Circuits and Systems-Part II*, 55(11):1104-1108, Nov. 2008.

[HK11] K. Hosseini and M.P. Kennedy. *Minimizing Tones in Digital Delta-Sigma Modulators*. Springer, New York, 2011.




www.tyndall.ie



Summary

166/168

- Part 2: Examples
 - SPICE DC analysis (intertwined basins of attraction)
 - Schmitt trigger (saddle-node bifurcation)
 - Colpitts oscillator (Hopf bifurcation)
 - Injection-locking (Arnold tongues)
 - DDSM (coexisting solutions)



www.tyndall.ie



Acknowledgements

167/168

- FIRB Italian National Research Program
RBAP06L4S5
- Science Foundation Ireland Grant
08/IN1/I1854


peter.kennedy@ucc.ie



Fondúireacht Eolaíochta Éireann
Science Foundation Ireland



www.tyndall.ie




Motivation

168/168

“I've wondered why it took us so long to catch on.
We saw it and yet we didn't see it.
Or rather *we were trained not to see it...*
The truth knocks on the door and you say, 'Go
away, I'm looking for the truth,' and so it goes
away...”

Robert M. Pirsig,
Zen and the Art of Motorcycle Maintenance, Corgi, 1974



www.tyndall.ie