

The Wye-Delta Center Tapped Transformer Bank

W. H. Kersting

Wayne Carr

Milsoft Utility Solutions

Introduction

- Loads to be served
 - Three-phase induction motor
 - 120/240 volt single-phase loads
- Transformer connection
 - Grounded wye-delta
 - Ungrounded wye-delta
- The question is should the neutral be grounded, grounded through an impedance or ungrounded?

General Thoughts on Grounding

- Always taught that the grounded wye-delta is preferred because when a primary phase is open the secondary will still provide three-phase voltages.
- Always taught that if the neutral is ungrounded upon the loss of a primary phase the secondary will become single-phase.

Concerns about Grounding

- Paper at the 2016 REPC demonstrated large “feedback” current for upstream ground faults when transformer is connected grounded wye-delta.
- Do both the grounded and ungrounded cases provide a dangerous backfeed voltage?
- Purpose of this paper is to investigate the magnitude of the “feedback” voltages for both connections.

Very Basic Transformer Theory

$$n_t = \frac{kVLL_{\text{Rated Primary}}}{kVLL_{\text{Rated Secondary}}}$$


$$\text{Example: } n_t = \frac{7200}{240} = 30$$

Center Tap Transformer

$$V_{t1} = V_{t2} = \frac{1}{2} \cdot VT$$

$$VT = 2 \cdot n_t \cdot V_{t1}$$

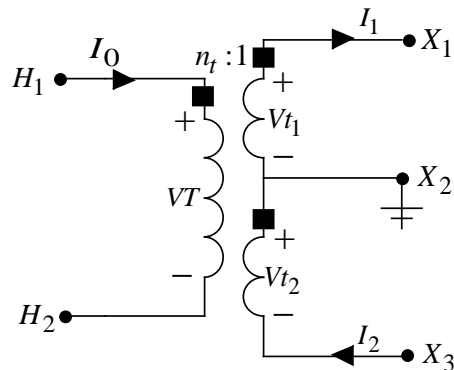
$$I_0 = \frac{1}{2 \cdot n_t} \cdot (I_1 + I_2)$$




Two Winding Transformer

$$V_t = \frac{1}{n_t} \cdot VT$$

$$I_1 = \frac{1}{n_t} \cdot I_2$$

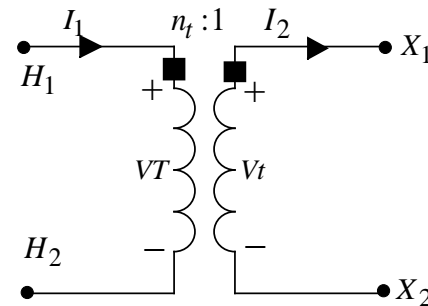

Grounded Wye-Delta Test System

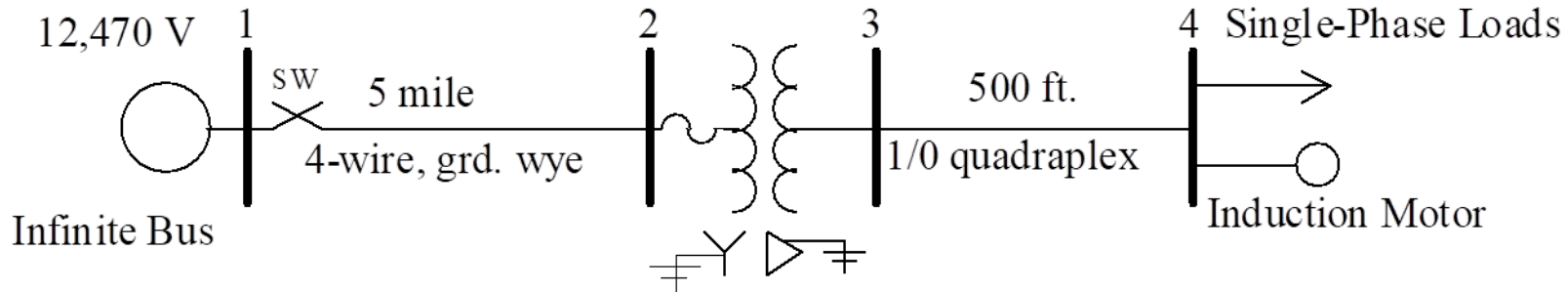

Forward Sweep:

$$[V_{2LG_{ABC}}] = [ELG_{ABC}] - [Z_{ABC}] \cdot [I_{ABC}]$$


$$[V_{3_{anbc}}] = [At]_n \cdot [V_{2LG_{ABC}}] - [Bt]_n \cdot [I_{abc}]$$

$$[V_{4_{anbc}}] = [V_{3_{anbc}}] - [Z_{S_{anbc}}] \cdot [I_{anbc}]$$

Backward Sweep:

$$[I_{ABC}] = [d_t] \cdot [I_{abc}]$$

Subtransmission Line

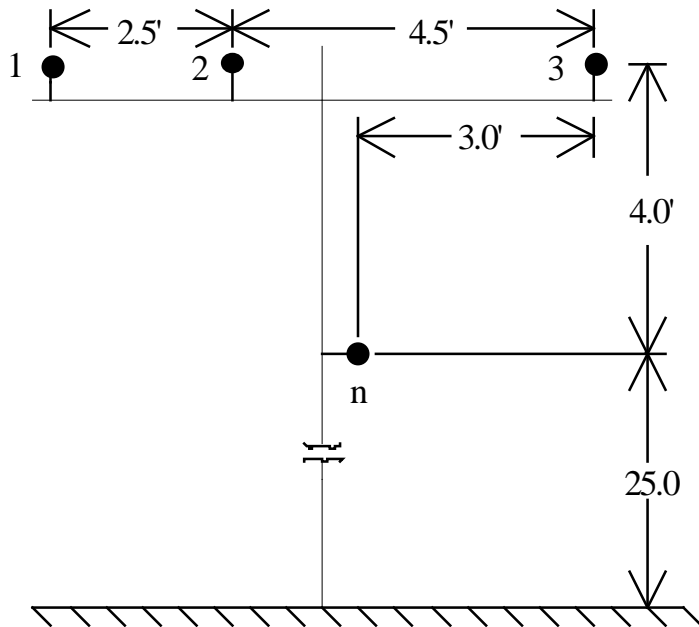


Phase Conductors: "Linnett" 336/400/ 26/7 ACSR

Neutral Conductor: 4/0 ACSR

$$Z_{.ABC} = \begin{pmatrix} 2.2878 + 5.3902i & 0.7797 + 2.5084i & 0.7674 + 1.9247i \\ 0.7797 + 2.5084i & 2.3331 + 5.2408i & 0.79 + 2.1182i \\ 0.7674 + 1.9247i & 0.79 + 2.1182i & 2.3074 + 5.3253i \end{pmatrix} \blacksquare$$

Grounded Wye-Delta Transformer Bank

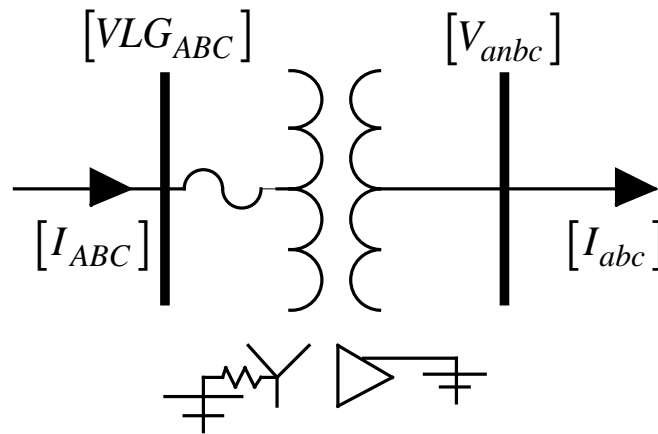

The transformer bank data are:


Lighting transformer (Phase A):

$kVA = 25$, 7200-240 volts, $Z_{t_{pu}} = 0.012 + j0.017$

Power transformers (Phases B and C)

$kVA = 10$, 7200-240 volts, $Z_{t_{pu}} = 0.016 + j0.014$

Final Grounded Wye-Delta Model

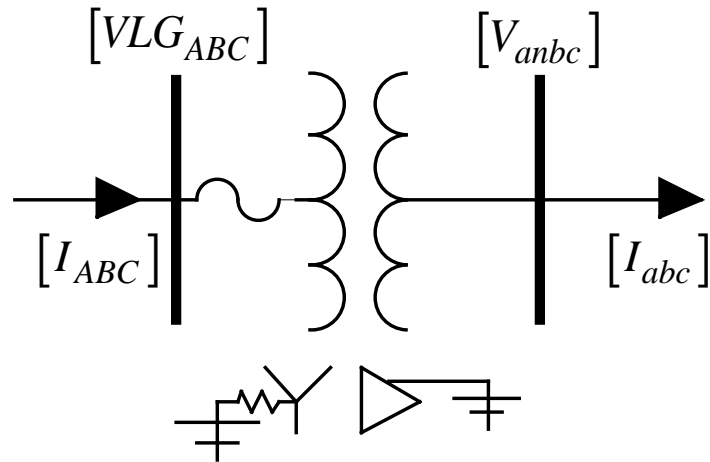

$$[V_{anbc}] = [A_t]_n \cdot [VLG_{ABC}] - [B_t]_n \cdot [I_{abc}]$$

$$[I_{ABC}] = [d_t]_n \cdot [I_{abc}]$$

where:


$$[A_t]_n = [KVL]_n \cdot [BV]$$

$$[B_t]_n = \left([KVL]_n \cdot ([BV] \cdot [Z0G] \cdot [AI] + [Z^t_{anbc}]) + [Z12]_n \right) \cdot [CI]_n$$

$$[d_t]_n = [AI] \cdot [CI]_n$$

Quadrplex Secondary

Quadrplex

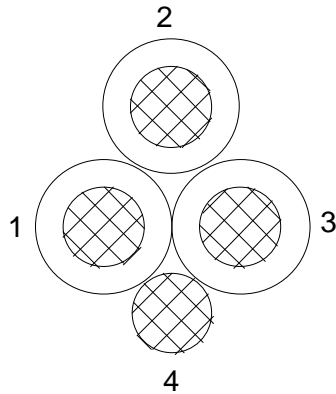


$$Z_{s_{anbc}} = \begin{pmatrix} 0.1012 + 0.1429j & 0.009 + 0.1102j & 0.009 + 0.1102j & 0.009 + 0.1163j \\ 0.009 + 0.1102j & 0.1012 + 0.1429j & 0.009 + 0.1102j & 0.009 + 0.1084j \\ 0.009 + 0.1102j & 0.009 + 0.1102j & 0.1012 + 0.1429j & 0.009 + 0.1163j \\ 0.009 + 0.1163j & 0.009 + 0.1084j & 0.009 + 0.1163j & 0.1151 + 0.1534j \end{pmatrix}$$

3 - Insulated 1/0 All Aluminum

1 - Bare 1/0 ACSR

Insulation Thickness = 80 mil

The Secondary System

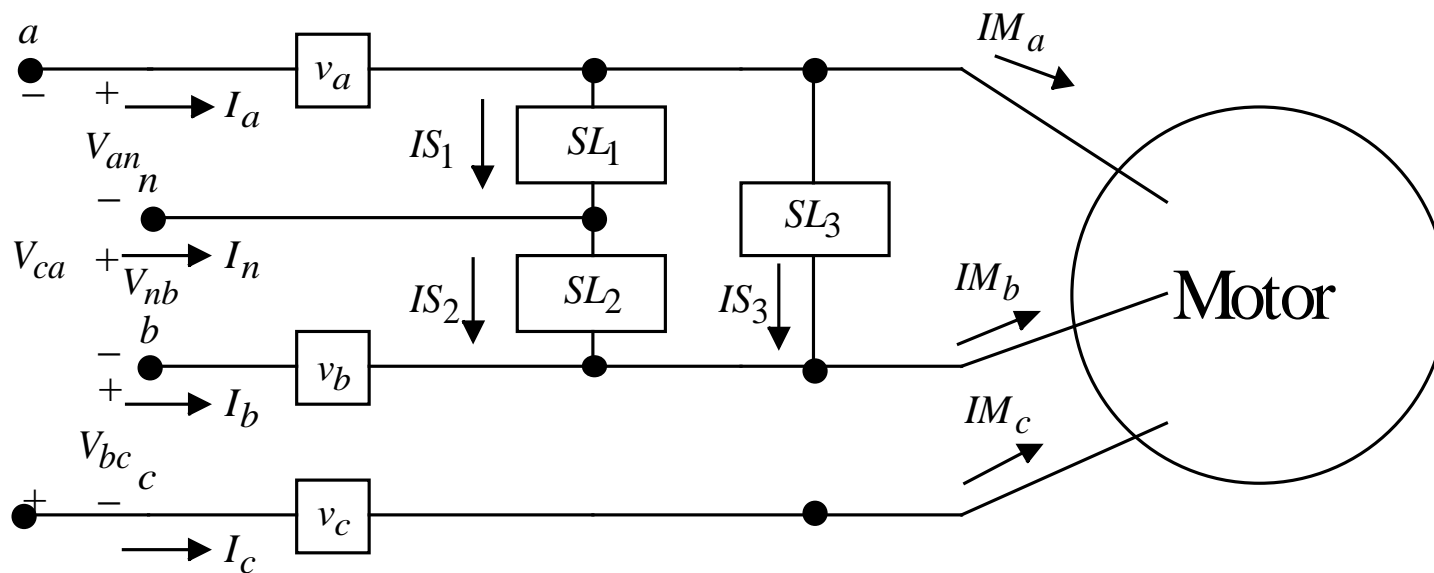

The single-phase lighting loads are:

$$S_{an} = 2.85 + j0.9367 \text{ kW+jkvar}$$

$$S_{nb} = 4.5 + j2.1794 \text{ kW+jkvar}$$

$$S_{ab} = 6.8 + j4.2143 \text{ kW+jkvar}$$

The three phase induction motor is:


25 HP, 240 volts, slip = 0.3

Stator Z: $Z_{s_{pu}} = 0.0366 + j0.08$

Rotor Z: $Z_{r_{pu}} = 0.0394 + j0.08$

Magnitizing Z: $Z_{m_{pu}} = 0 + j2.1$

Phase A Open, Motor Connected

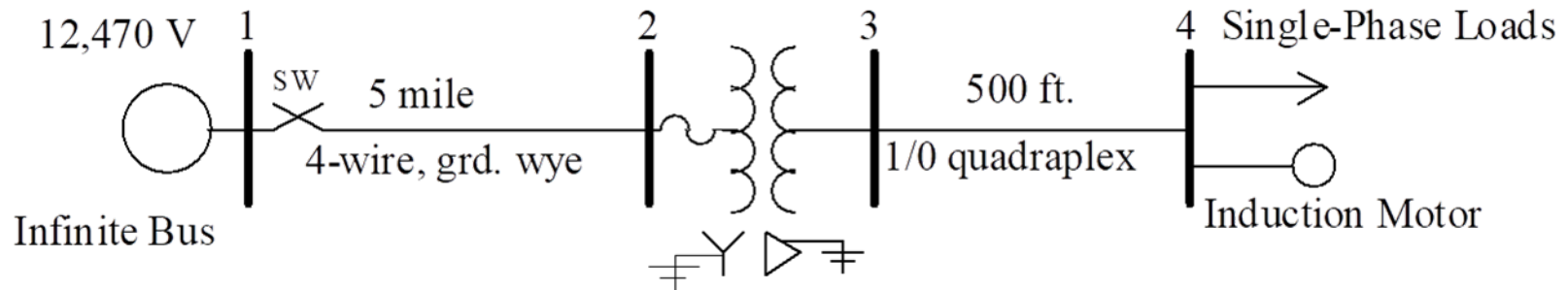

Connected Motor Voltages and Currents

$$[VM_{abc}] = \begin{bmatrix} 201.5/\underline{-0.6} \\ 219.0/\underline{-115.2} \\ 226.6/\underline{118.5} \end{bmatrix} \quad [IM_{abc}] = \begin{bmatrix} 38.8/\underline{-86.4} \\ 52.4/\underline{-158.1} \\ 73.3/\underline{51.2} \end{bmatrix}$$

$$V_{unbalance} = 6.6\%$$


$$I_{unbalance} = 33.7\%$$

Backfeed Voltages:

$$V_{1AG} = 6302.8/\underline{-1.9} \text{ volts}$$

$$V_{2AG} = 6313.7/\underline{-1.8} \text{ volts}$$

Phase A Open, Motor Off

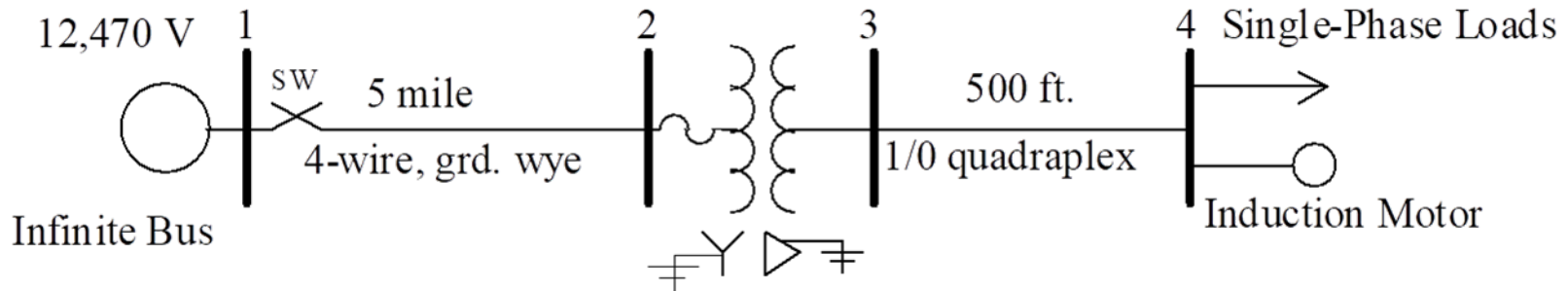

Backfeed Voltages

$$V_{1_{AG}} = 6557.0 / \underline{-1.1} \text{ volts}$$

$$V_{2_{AG}} = 6565.5 / \underline{-1.0} \text{ volts}$$

Secondary Currents

$$[I_{anbc}] = \begin{bmatrix} I_a \\ I_n \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 66.4 / \underline{-26.6} \\ 18.0 / \underline{-39.2} \\ 84.0 / \underline{150.7} \\ 0 \end{bmatrix}$$

Single-Phase Load Voltages

$$\begin{bmatrix} VL_{an} \\ VL_{nb} \\ VL_{bc} \end{bmatrix} = \begin{bmatrix} 103.4 / \underline{-0.7} \\ 108.1 / \underline{-0.8} \\ 211.5 / \underline{-0.8} \end{bmatrix}$$

Phase B and Phase C Open

Phase B Open

$$V1_{BG} = 6794.5/\underline{-120.4}$$

$$V2_{BG} = 6806.1/\underline{-120.3}$$

$$V_{unbalance} = 1.7$$

$$I_{unbalance} = 11.7\%$$

Phase C Open

$$V1_{CG} = 6874.0/\underline{119.1}$$

$$V2_{CG} = 6878.6/\underline{119.2}$$

$$V_{unbalance} = 1.2\%$$



$$I_{unbalance} = 6.9\%$$

Because the voltage unbalance is below the 3% level,
the motor will not be tripped

Summary for Grounded Wye-Delta

- No matter which phase is open, there will be a significant backfeed voltage at the open switch
- When phase A is open the voltage unbalance at the motor will be high and therefore the protective device will trip the motor off.
- When phase B or phase C is open the voltage unbalance is low so motor will continue to operate.
- In all cases the single-phase loads are served

Ungrounded Wye-Delta Circuit

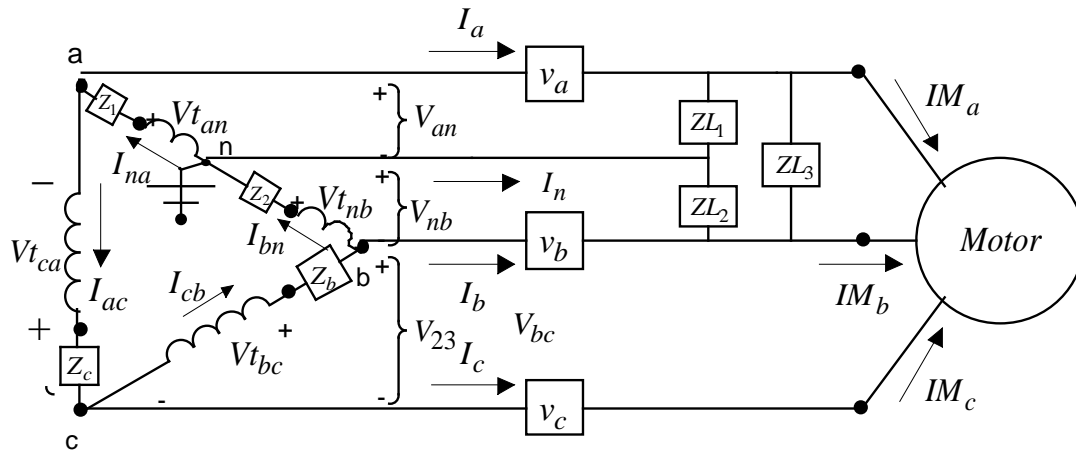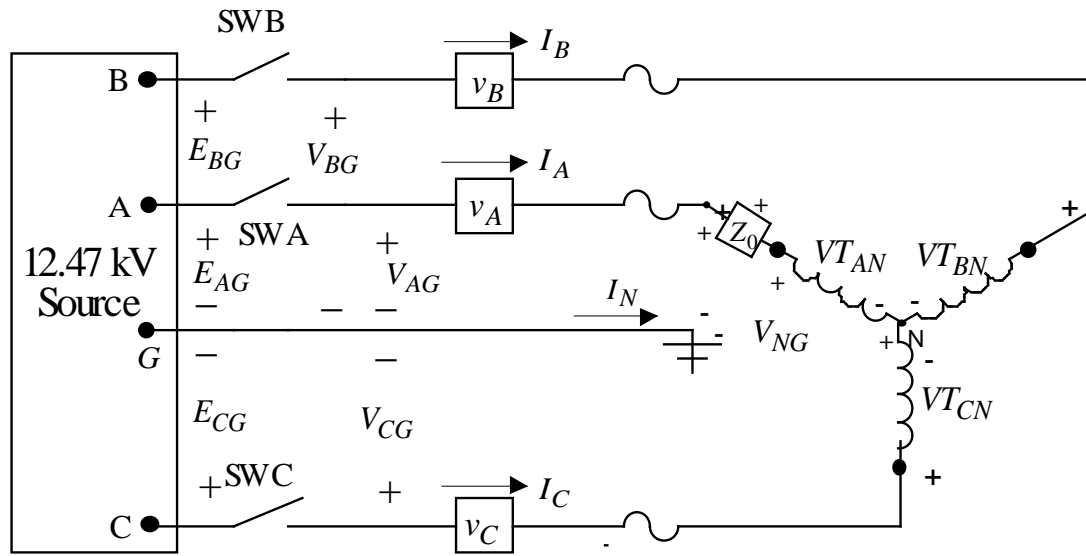

Phase A Open No-Load Operating Condition

- Motor and Single-Phase Loads are Off

$$[VM] = \begin{bmatrix} 0 \\ 207.8/\underline{-90} \\ 207.8/\underline{90} \end{bmatrix}$$

- Single-Phase voltages so motor will not start
- Without three-phase voltages the rotational magnetic field needed to start the motor is not there.

Phase A Open with Motor and Loads On


$$[VM_{abc}] = \begin{bmatrix} 117.3/\underline{-20.9} \\ 169.3/\underline{-106.0} \\ 214.0/\underline{107.1} \end{bmatrix} \quad [IM_{abc}] = \begin{bmatrix} 71.7/\underline{-168.6} \\ 78.6/\underline{-101.8} \\ 125.6/\underline{46.5} \end{bmatrix}$$

$$V_{unbalance} = 29.7 \%$$

$$I_{unbalance} = 36.5 \%$$

Because of the high voltage unbalance the protective device for the motor will open turning the motor off.

Open Phase A, Motor Off

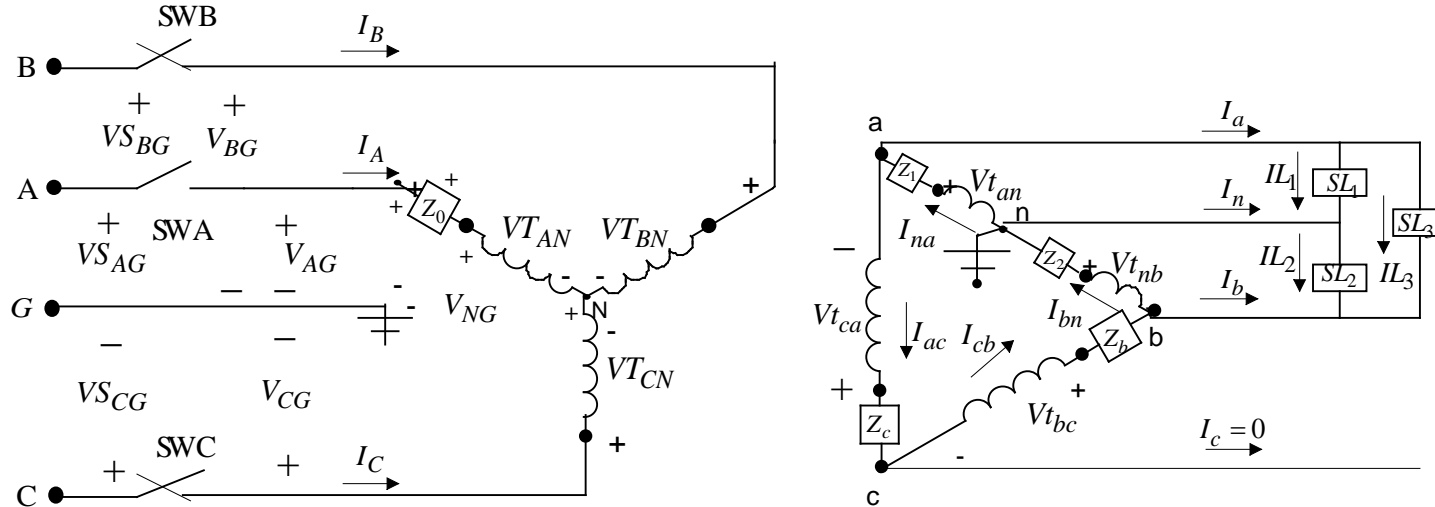

$$V_{NG} = 3600/\underline{180}$$


$$VT_{AN} = 0, \quad VT_{BN} = 6235.4/\underline{-90}, \quad VT_{CN} = 6235.4/\underline{90}$$

$$Vt_{an} = Vt_{nb} = 0, \quad Vt_{bc} = 207.8/\underline{-90}, \quad Vt_{ca} = 207.8/\underline{90}$$

$$V1_{AG} = 3600/\underline{180}, \quad V1_{BG} = 7200/\underline{-120}, \quad V1_{CG} = 7200/\underline{120}$$


All currents primary, secondary and single-phase loads = 0

Phase A Open Currents

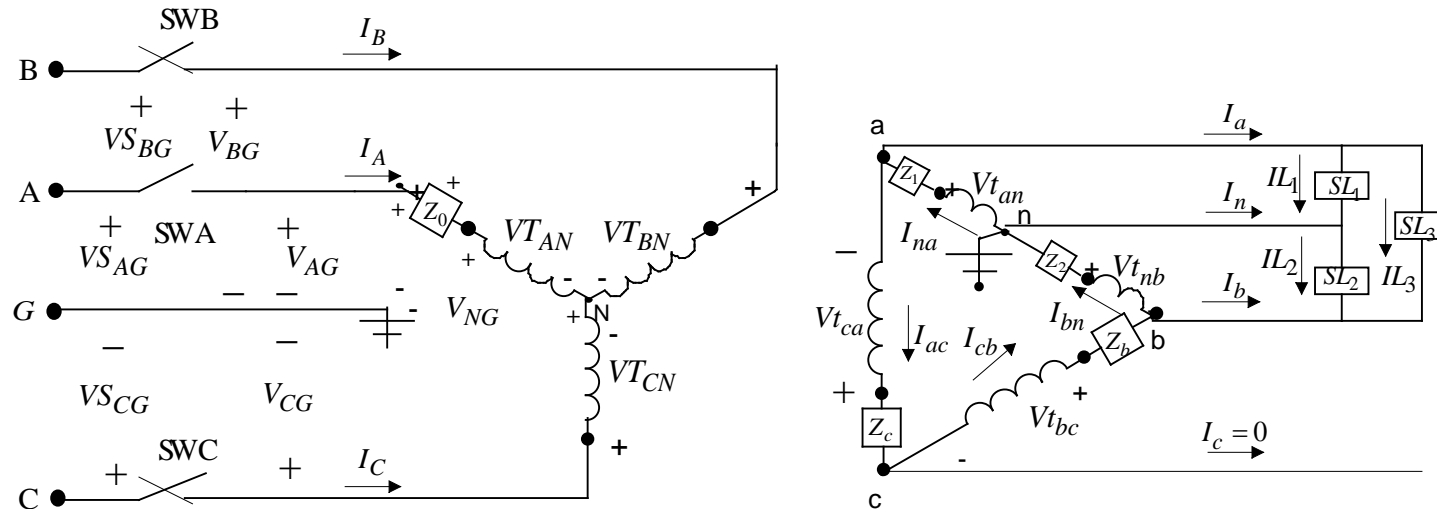


- $I_A = 0$ therefore $I_{an} + I_{bn} = 0$
- Path for I_B and I_C so $I_C = -I_B$
- Because of above $I_{ac} = -I_{cb}$
- With motor open $I_c = 0$ for all conditions
- At node c $I_c = I_{ac} - I_{cb} = 0$ this is impossible since $I_{ac} = -I_{cb}$
- Because of the above $I_{ac} = I_{cb} = 0$
- Therefore $I_B = I_C = 0$

Kirchhoff's Current Law (KCL)

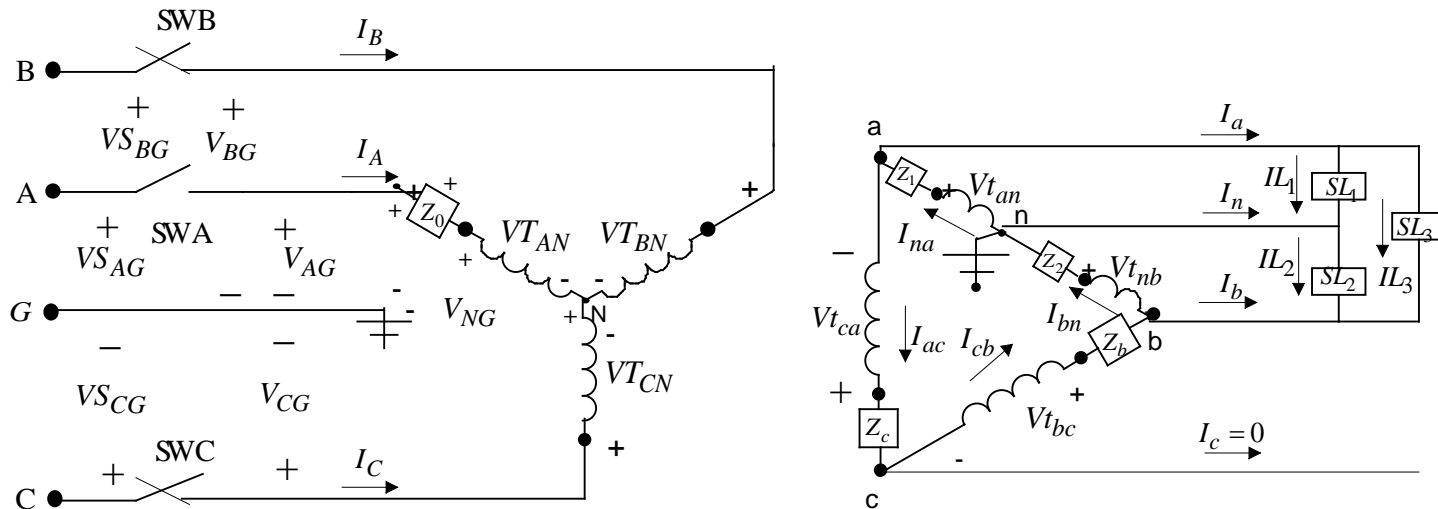

- In previous slide $I_{ac} = I_{cb} = I_{na} + I_{nb} = I_c = 0$
- Since $I_{na} + I_{bn} = 0$ then $I_{bn} = -I_{na}$
- KCL at node a: $I_a = I_{na} - I_{ac} = I_{na} - 0 = I_{na}$
- KCL at node b: $I_b = I_{cb} - I_{bn} = 0 - I_{bn} = I_{na}$
- KCL at node n: $I_n = I_{bn} - I_{na} = -I_{na} - I_{na} = -2 \cdot I_{na}$
- KCL on secondary: $I_a + I_b + I_c + I_n = 0 = I_{na} - I_{bn} + 0 - 2 \cdot I_{na}$
 $I_{na} + I_{na} - 2 \cdot I_{na} = 0$

Phase A Open Voltages

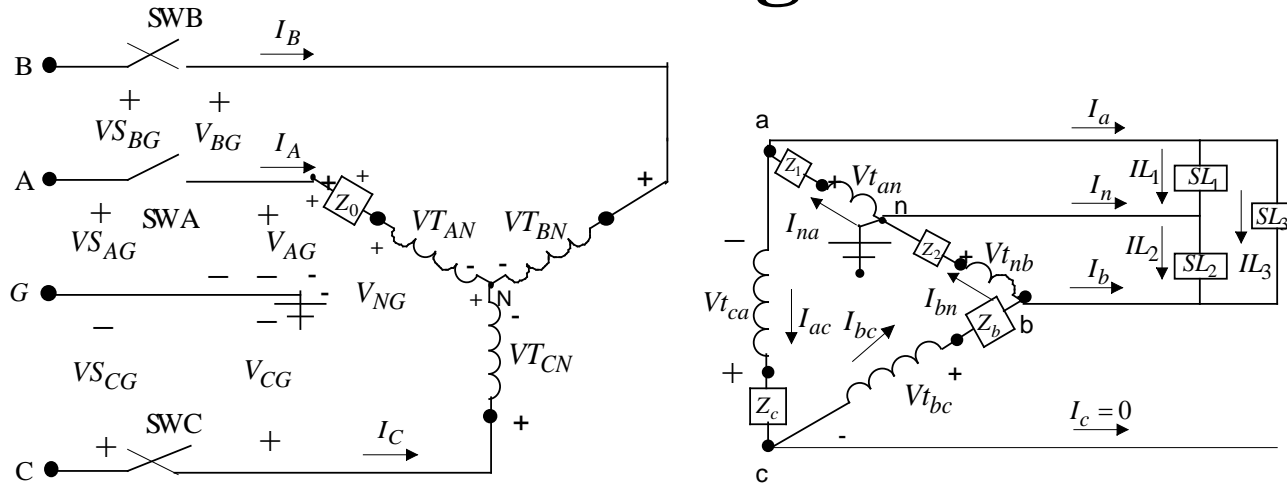

- Voltage applied to primary windings: $VT_{BC} = VT_{BN} - VT_{CN} = 12,470/\underline{-90}$
- Phase B winding voltage: $VT_{BN} = 0.5 \cdot VT_{BC} = 6235/\underline{-90}$
- Phase C winding voltage: $VT_{CN} = -0.5 \cdot VT_{BC} = 6235/\underline{90}$
- The secondary ideal voltages are: $Vt_{bc} = 207.8/\underline{-90}$ and $Vt_{ca} = 207.8/\underline{90}$
- KVL: $Vt_{an} + Vt_{nb} + Vt_{bc} + Vt_{ca} = 2 \cdot Vt_{an} + 0 = 0$
- Since: $Vt_{an} = 0$ then $VT_{AN} = 0$
- Primary neutral voltage: $V_{NG} = V_{BG} - VT_{AN} = 3600/\underline{180}$
- Phase A backfeed voltage: $V_{AG} = VT_{AN} + V_{NG} = 0 + V_{NG} = 3600/\underline{180}$

Phase B Open with Motor and Loads On


$$[VM_{abc}] = \begin{bmatrix} 192.1/\underline{-10.3} \\ 119.3/\underline{-121.4} \\ 186.0/\underline{133.0} \end{bmatrix} \quad [IM_{abc}] = \begin{bmatrix} 102.3/\underline{-84.0} \\ 36.8/\underline{54.2} \\ 78.8/\underline{114.2} \end{bmatrix}$$

$$V_{unbalance} = 28.0 \%$$

$$I_{unbalance} = 49.3 \%$$

Because of the high voltage unbalance the protective device for the motor will open turning the motor off.

Open Phase B, Motor Off

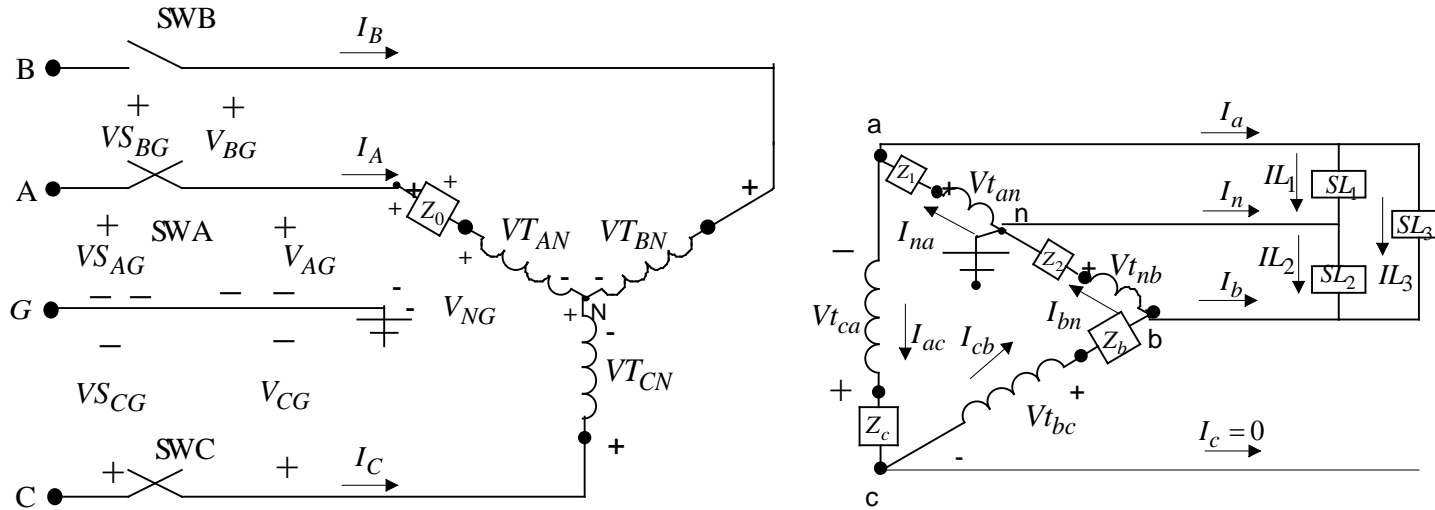

$$V_{NG} = 7200/\underline{0}$$


$$VT_{AN} = 0, \quad VT_{BN} = 12470.8/\underline{-30}, \quad VT_{CN} = 12470.8/\underline{150}$$

$$Vt_{an} = Vt_{nb} = 0, \quad Vt_{bc} = 415.7/\underline{-30}, \quad Vt_{ca} = 415 / 7/\underline{150}$$

$$V1_{AG} = 7200/\underline{0}, \quad V1_{BG} = 19049.4/\underline{-19.1}, \quad V1_{CG} = 7200/\underline{120}$$


All currents primary, secondary and single-phase loads = 0

Phase B Open Currents

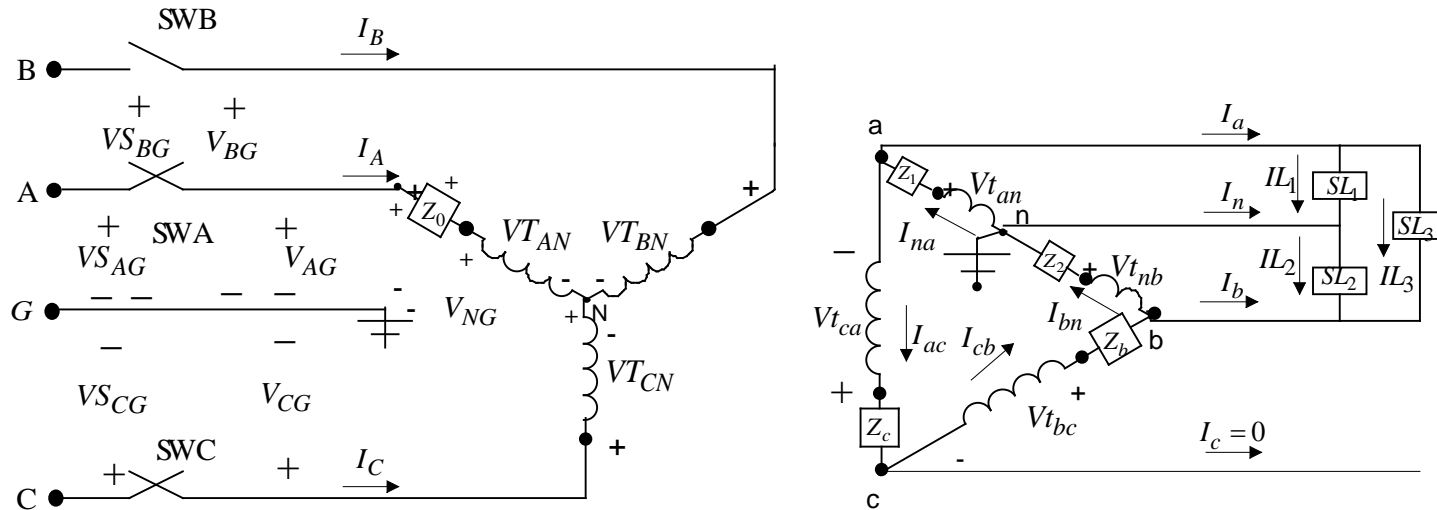


- $I_B = 0$ therefore $I_{cb} = 0$
- There is a path for I_C and I_A so $I_A = -I_C$
- With $I_{cb} = 0$ and $I_c = 0$ then KCL says $I_{ac} = 0$
- With $I_{ac} = 0$ then $I_C = 0$ and $I_A = 0$
- In short $I_A = I_B = I_C = 0$
- However: $I_{na} + I_{bn} = 0$ or $I_{bn} = -I_{na}$
- What about $V_{tan} = V_{nb} = ?$

Secondary and Load Currents

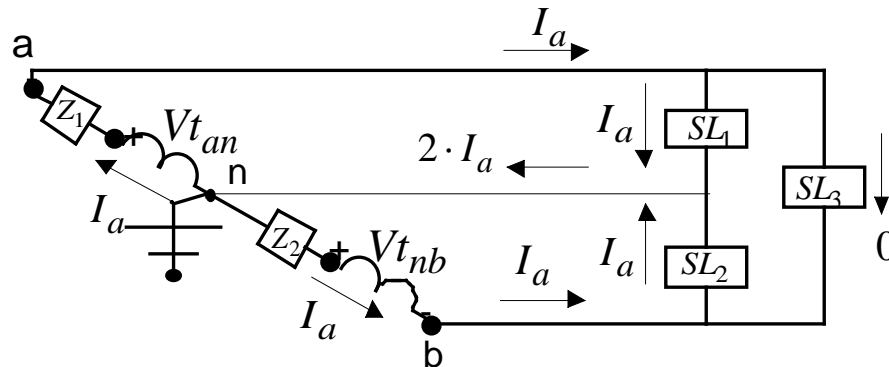



- Look at the circuit and note that $I_{bn} = -I_{na}$
- Shown in the circuit is only I_a since $I_{nb} = -I_{an} = I_a$
- This makes the same currents flow in phase a and phase b
- Now must have $2 \cdot I_a$ flowing in the neutral as shown
- Note the same current must flow thru the two 120 volt loads
- This requires the voltages $V_{L_{an}} = V_{L_{bn}}$
- This is impossible because of the polarities of $V_{t_{an}}$ and $V_{t_{nb}}$
- Therefore the only thing that works is $V_{t_{an}} = V_{t_{nb}} = V_{T_{AN}} = 0$

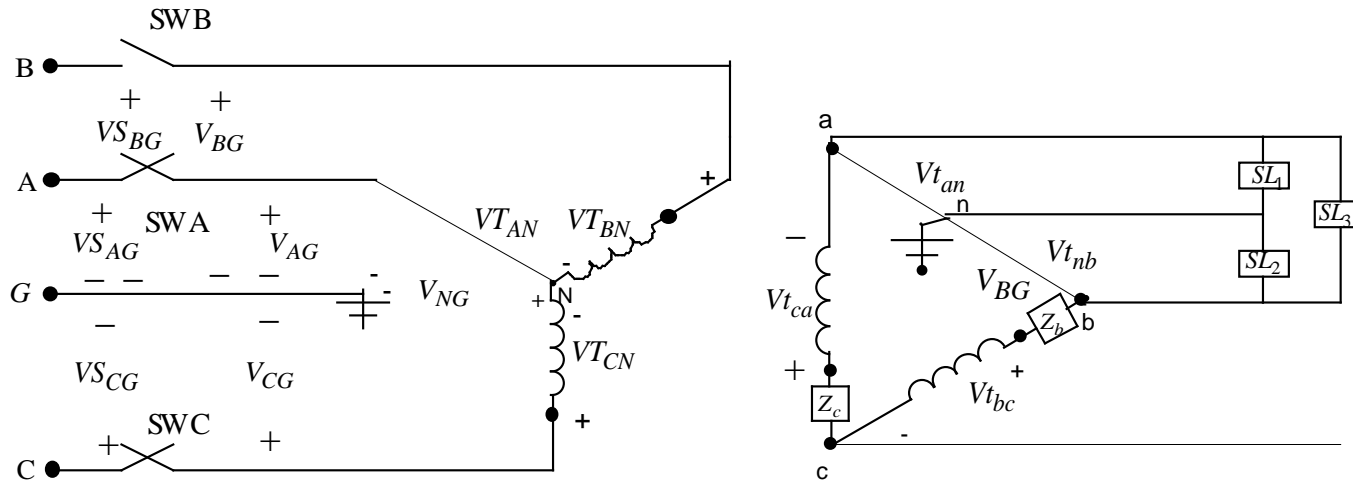Computation of Open Switch B Line-to-ground Voltage



- With the shorted voltages the only primary voltage is $VT_{CN} = VT_{CA} = 12,470/\underline{150}$
- Now $Vt_{ca} = \frac{1}{n} \cdot VT_{CA} = 415.7/\underline{150}$
- To satisfy KVL: $Vt_{bc} = -Vt_{ca} = 415.7/\underline{-30}$
- Therefore: $VT_{BN} = n_t \cdot Vt_{bc} = 12,470/\underline{-30}$
- With the neutral and phase A shorted: $V_{NG} = V_{AG} = 7200/\underline{0}$
- Now: $V_{BG} = VT_{BN} + V_{NG} = 19049.4/\underline{-19.1}$

Phase C Open with Motor and Loads On

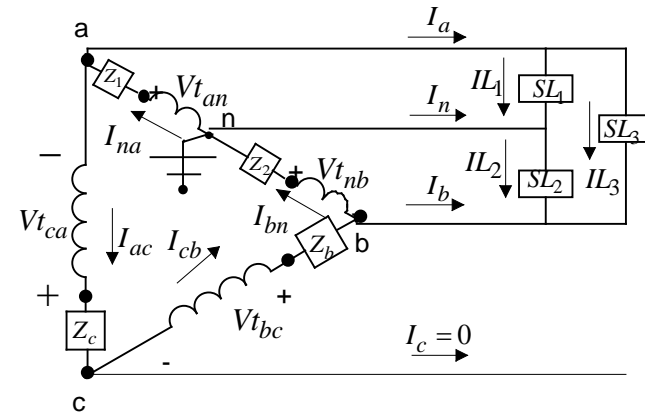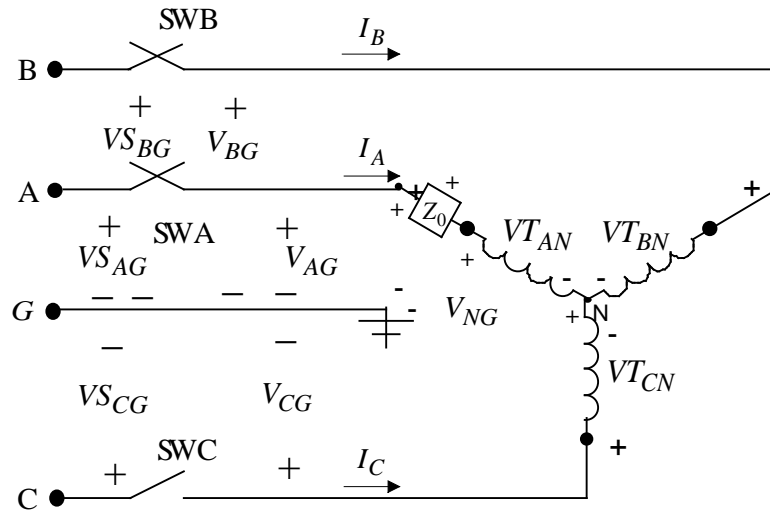

$$[VM_{abc}] = \begin{bmatrix} 165.5/\underline{2.1} \\ 229.0/\underline{-127.3} \\ 178.2/\underline{98.6} \end{bmatrix}$$


$$V_{unbalance} = 20.0 \%$$

$$[IM_{abc}] = \begin{bmatrix} 30.6/\underline{34.5} \\ 103.5/\underline{-174.7} \\ 78.2/\underline{-5.6} \end{bmatrix}$$

$$I_{unbalance} = 56.7 \%$$

Because of the high voltage unbalance the protective device for the motor will open turning the motor off.

Open Phase C, Motor Off

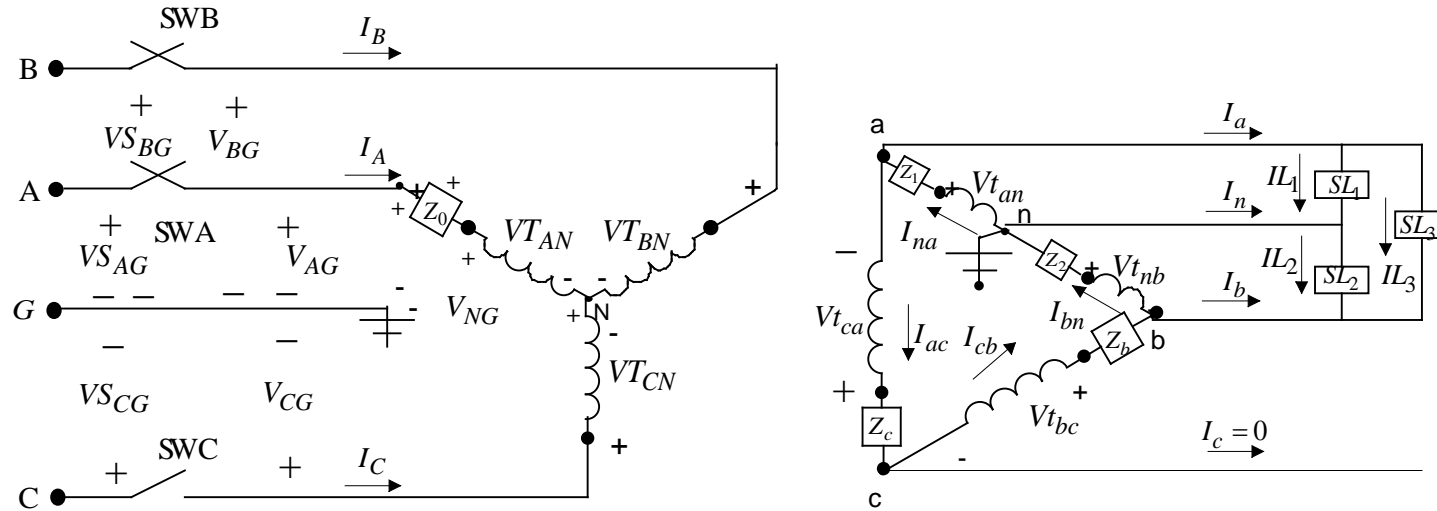

$$V_{NG} = 7200/\underline{0}$$

$$VT_{AN} = 0, \quad VT_{BN} = 12470.8/\underline{-150}, \quad VT_{CN} = 12470.8/\underline{30}$$

$$Vt_{an} = Vt_{nb} = 0, \quad Vt_{bc} = 415.7/\underline{-150}, \quad Vt_{ca} = 415 / \underline{7/30}$$

$$V1_{AG} = 7200/\underline{0}, \quad V1_{BG} = 7200/\underline{-120}, \quad V1_{CG} = 19049.4/\underline{19.1}$$

All currents primary, secondary and single-phase loads = 0

Conclusions - 1

- The original question was whether the wye should be grounded. The answer is still ???
- Grounded Wye-Delta
 - Provides three-phase service with an open phase
 - High backfeed short circuit current for upstream ground faults
 - Provides a backfeed voltage below rated LG voltage but still dangerous

Conclusions - 2

- Ungrounded Wye-Delta
 - Does not provide three-phase service with an open phase
 - Does not provide a backfeed current for upstream ground faults
 - Provides a very high backfeed voltage (2.65 times rated LG voltage) when phase B or C is open
 - Lower backfeed voltage when the center tap phase is open

Conclusions-3

- So what is the answer?
 - Good question
 - Neither connection is perfect
 - What is known is that both connections will provide a very dangerous backfeed voltage on the downstream side of the open switch
 - **Linemen must be trained to understand that just because the switch is open, it is not save to touch the line on either side of the switch**