

Voltage Source Converter (VSC) IEEE PES Winnipeg Tutorial

December 18, 2012

*Randy Wachal
Manitoba HVDC Research Centre
rww@hvdc.ca*

Acknowledgements:

NSERC Power System Simulation Chair program at
University of Manitoba ..

MHRC Staff

Dr. Farid Mosallat and Juan Carlos Garcia

Cigre DC Grid Working Groups

B4-55, 56 57 58 59 and 60 ..

ABB Siemens and Alstom Grid

VSC Tutorial

VSC Converter Theory Basics


VSC Control and Modelling

VSC system simulations


Start-up; DC Fault

DC Grid Test Case Cigre B4-57/58


Introductory Basics: LCC Single line

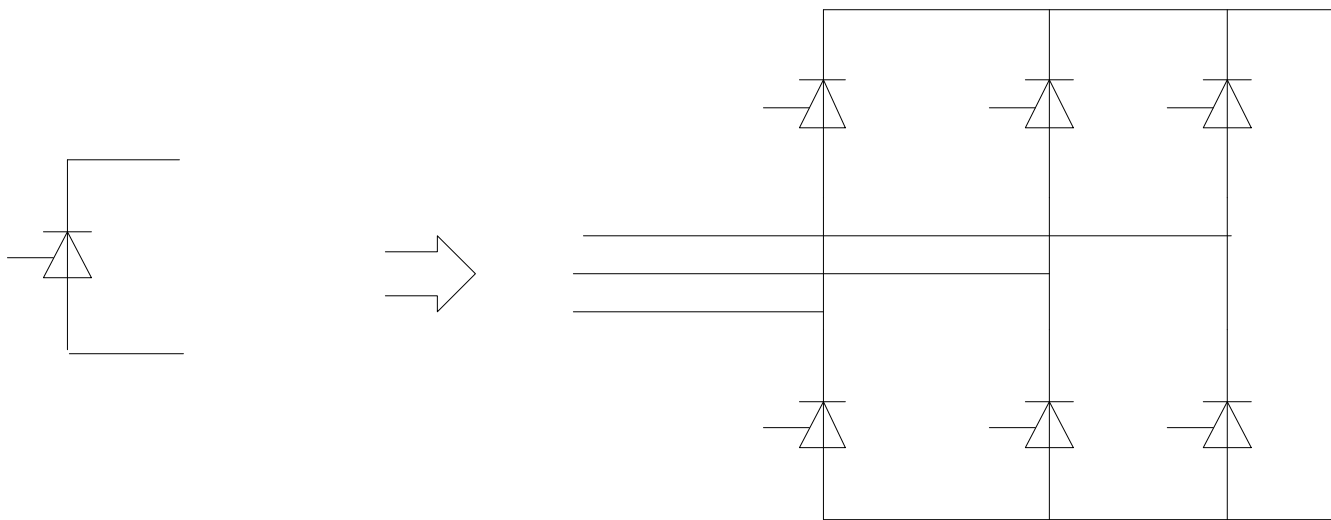


VSC: Single Line Diagram Format

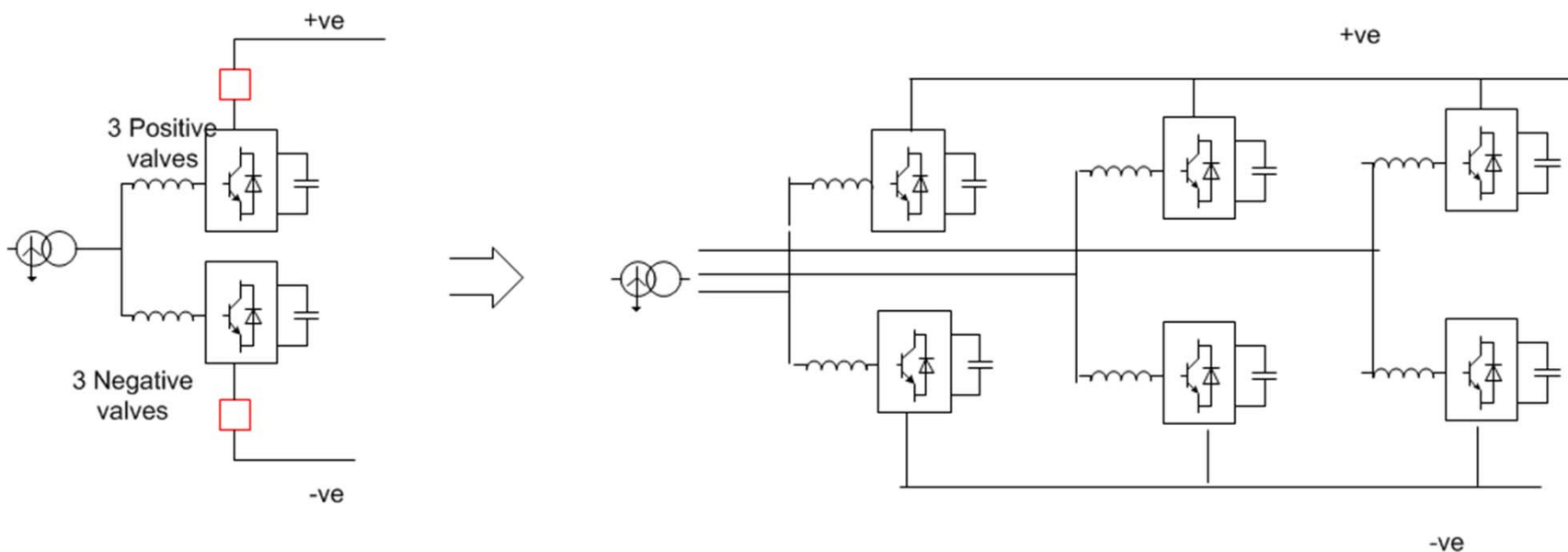


Symmetrical HVDC Monopole

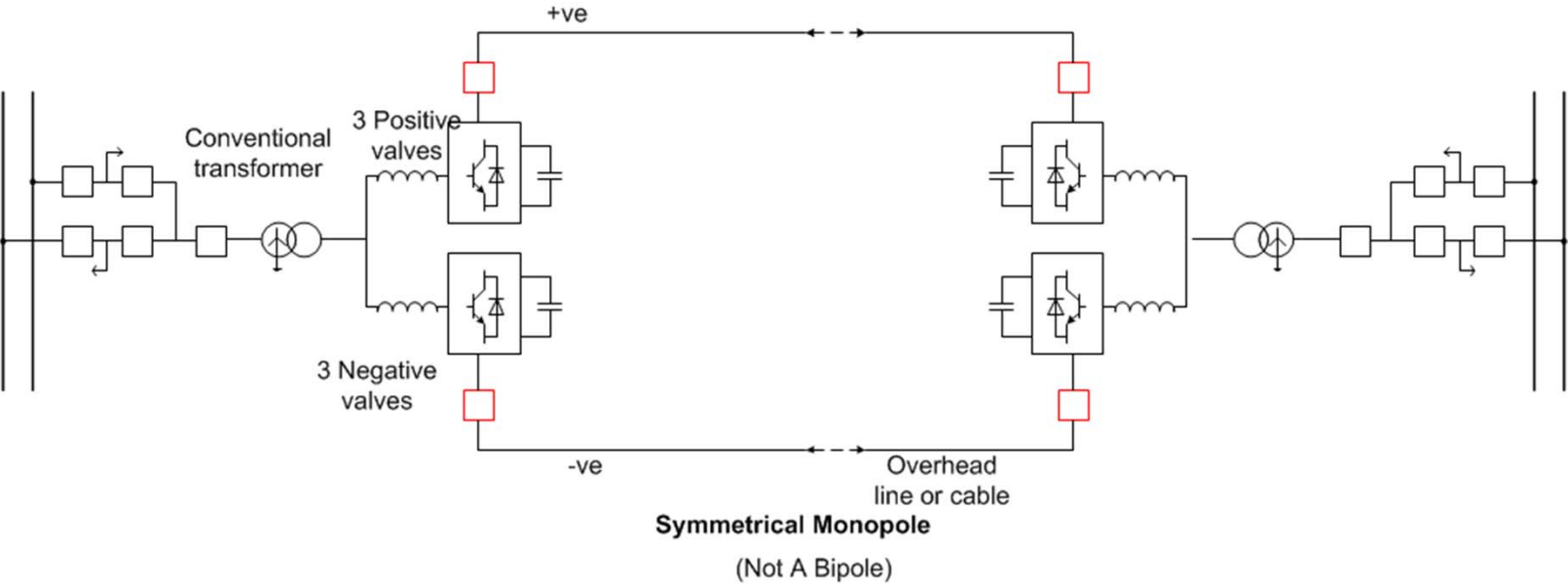

VSC: Unsymmetrical Monopole

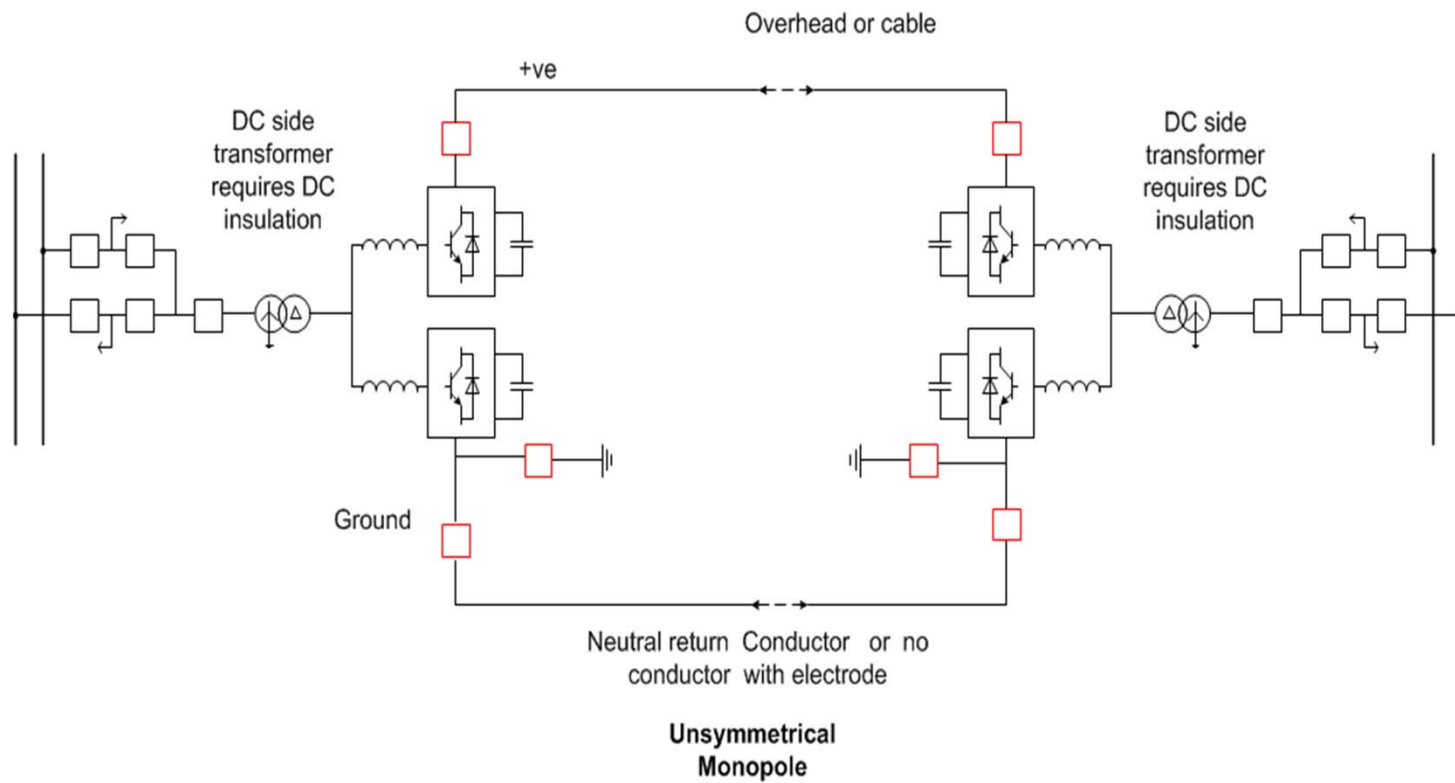

VSC: Bipole Configuration

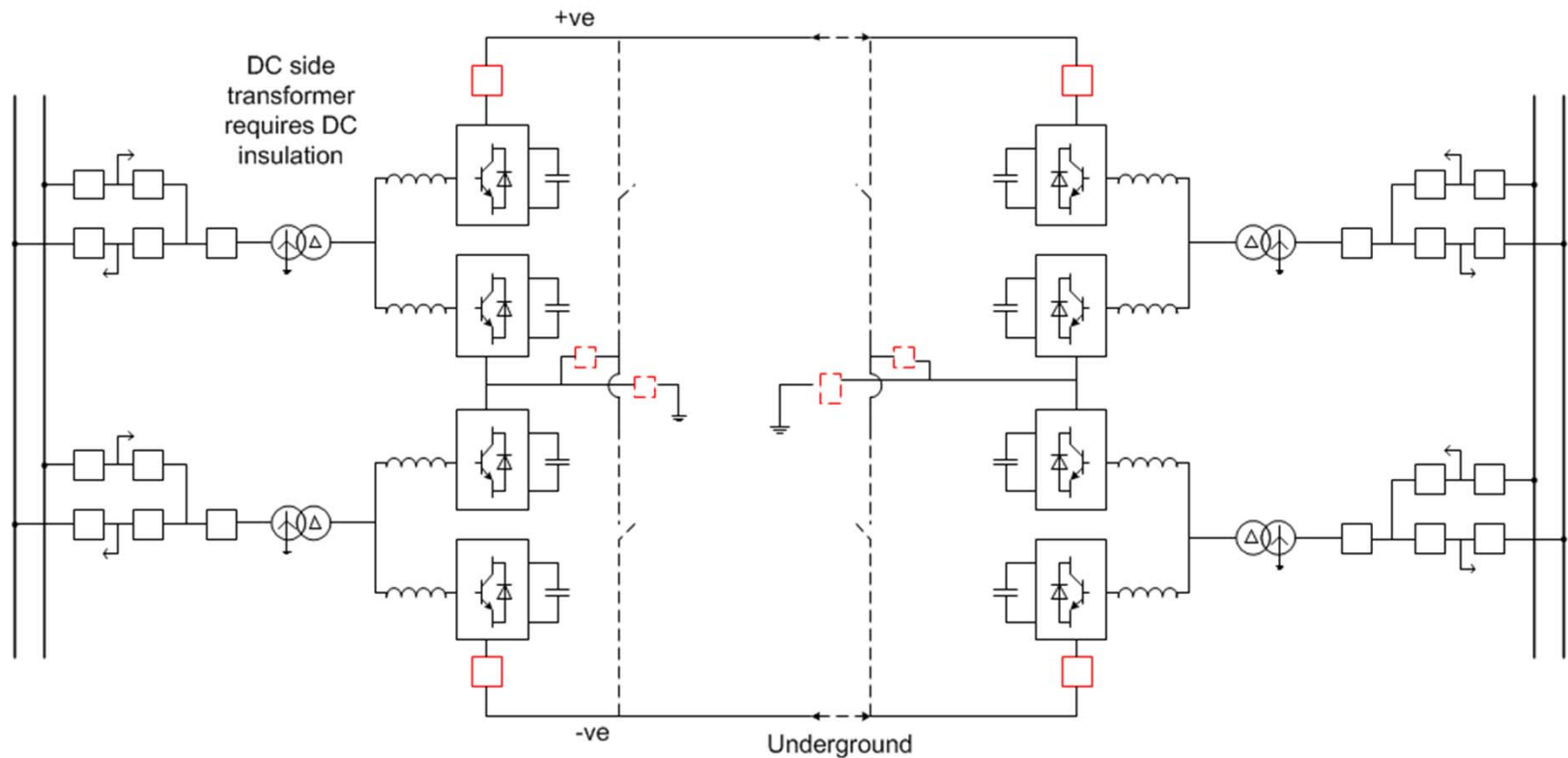

VSC Bipole

LCC - VSC Comparison

LCC HVDC

Mature Technology
"Requires" strong ac system
Lower losses 0.8% per converter
Requires 60% reactive power
AC-DC system interactions
Harmonics
Commutations failure
Special Transformers
Multi terminal operation possible but hard
Controlled DC Current to zero ($I_{dref}=0$)
Dc voltage + to - as alpha changes
rectifier to inverter

VSC HVDC

Rapid growth
Helps ac system
Control real and reactive power independently
Losses reducing 1.1- 1.2% per converter
No Commutation failure
Less Special Transformers
Flexible Dispatch
Harmonics with MMC no issue
DC Grid (multi-terminal) possible
DC voltage is a constant polarity
DC Line faults are problematic

Multi Terminal

For LCC:



Rect $\alpha < 90$ Vdc +ve

INV $\alpha > 90$ Vdc -ve

To change Conv 2 from Rect to Inv you must flip the thyristor

For VSC:

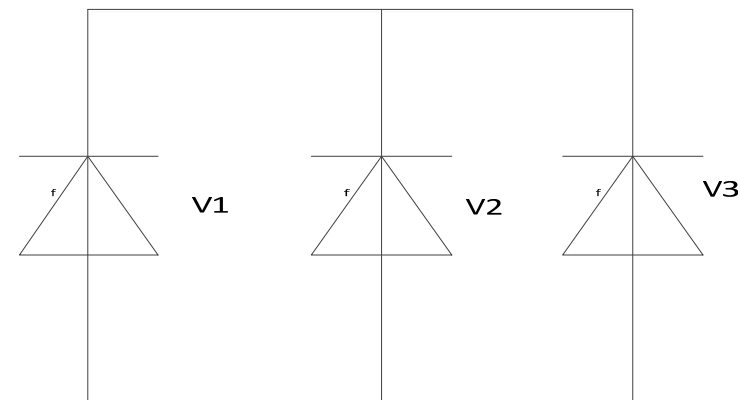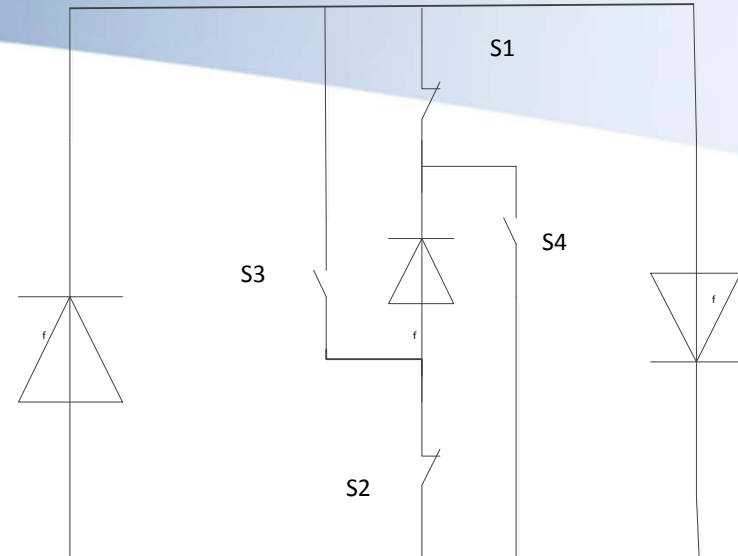Power Flow is controlled by control signals only



VSC Technology is very flexible

VSC technology can control two variables together
real power and reactive power

VSC can generate an AC Waveform....

Black start or island mode possible


Many dispatch options available

- Real Power set point in or out + or -
- Use power to control DC voltage V_{dc}
- In island mode : use power to control frequency

- Reactive Power Q set point in or out + or -
- Use Q to control V_{ac} magnitude Grid or islanded Mode...

- Other control targets are possible..

VSC Operation

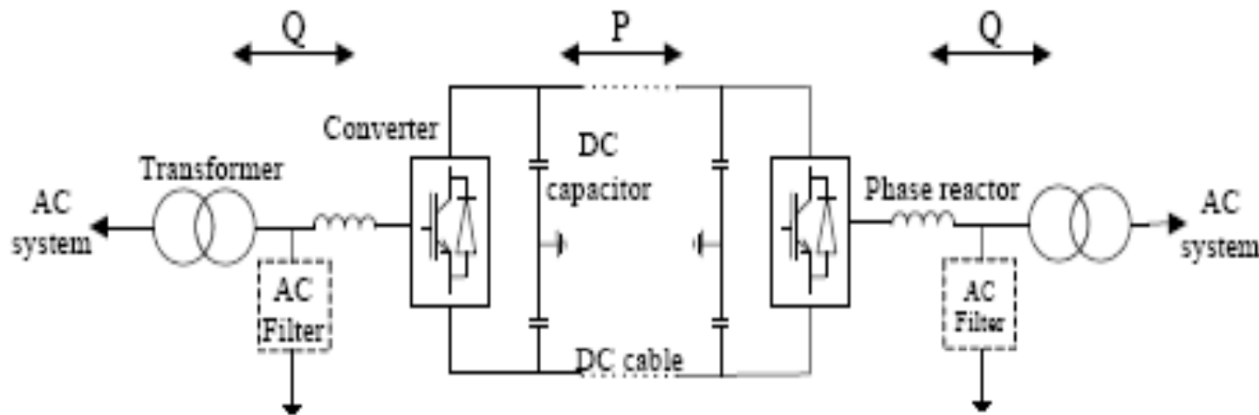


$$P = \frac{U_F \times U_C \times \sin \delta}{\omega L}$$

$$Q = \frac{U_F \times (U_F - U_C) \times \cos \delta}{\omega L}$$

We tend to think of LCC from AC side to rectifier and generate Dc voltage

For VSC ; think from the DC side.. Assume DC Capacitors are charged
 The capacitor voltages are used to piecewise build ac voltage
 We the ac voltage waveform and the ac system voltage
 now we can transfer energy to charge Dc capacitor(s)

Transfer P & Q across Reactor

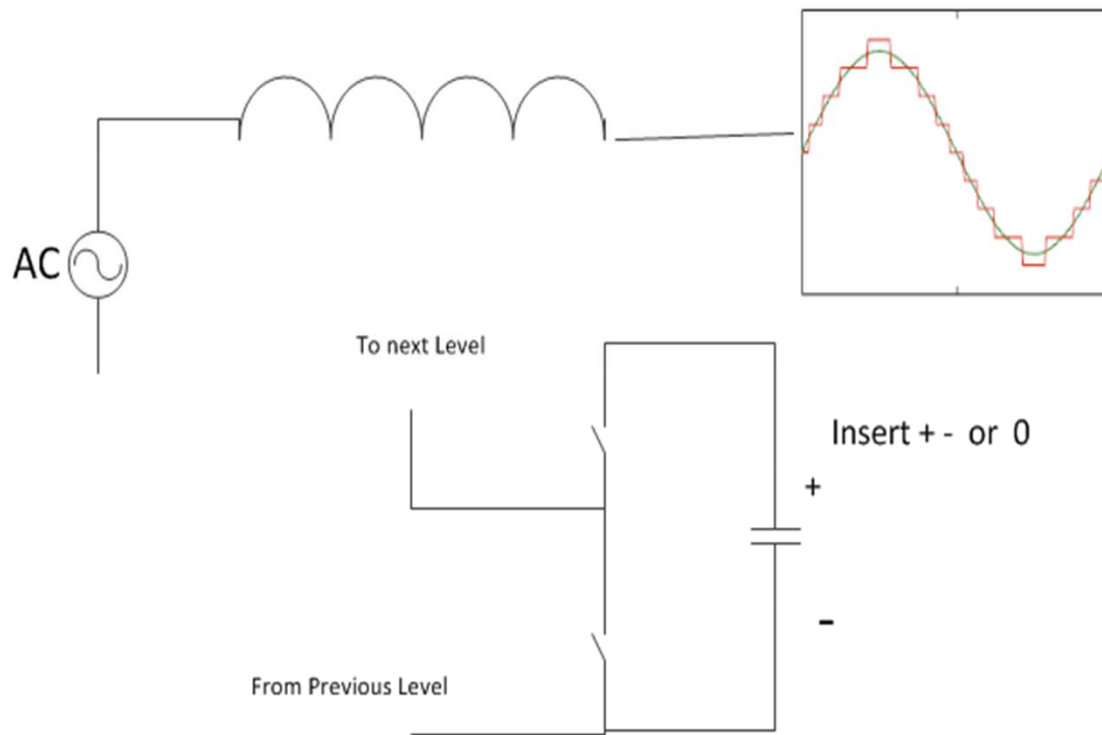

Use DC capacitor voltage (U_d) to build an ac Voltage waveform U_c

Exchange P based on δ

- $\uparrow \delta$ P into Converter $U_d \uparrow$
- $\downarrow \delta$ P from Converter $U_d \downarrow$

Exchange Q based on $|U_c|$

- $\uparrow |U_c|$ Q flows into system
- $\downarrow |U_c|$ Q flows from system

History of VSC Development: ABB, Siemens and Alstom Grid



- VSC Rapid Growth and continue to change
- Many projects but few projects have the same design
- An MMC type configuration appears to be the “winner” but many marketplace has variations
 - Not unlike LCC technology 25 years ago
- The Final VSC configuration is not decided
 - and may never occur.

HVDC Light

Historical review, 1997-2001

- **Two-level Converter, Generation 1**

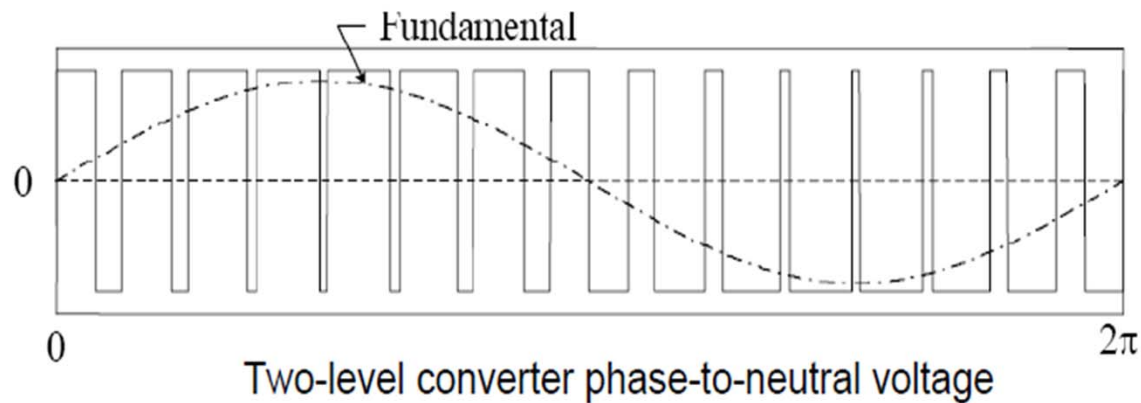
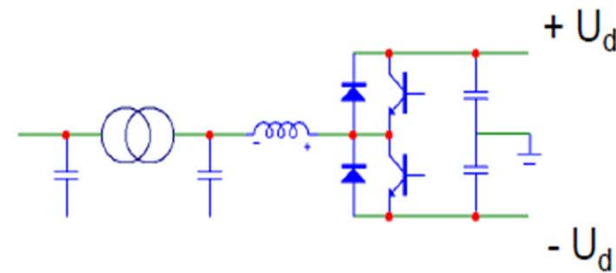
- Converter losses 3 %
- High switching frequency
- Filters required



HVDC Light Historical review, 2002-2004

▪ Three-level Converter, Generation 2

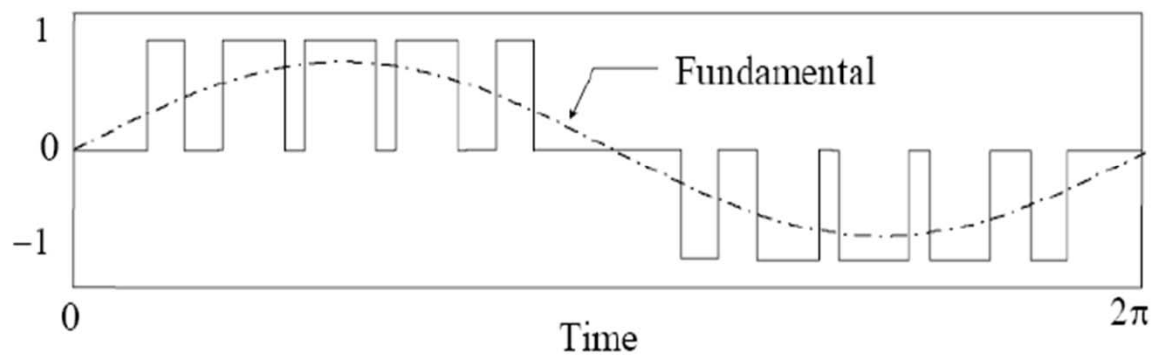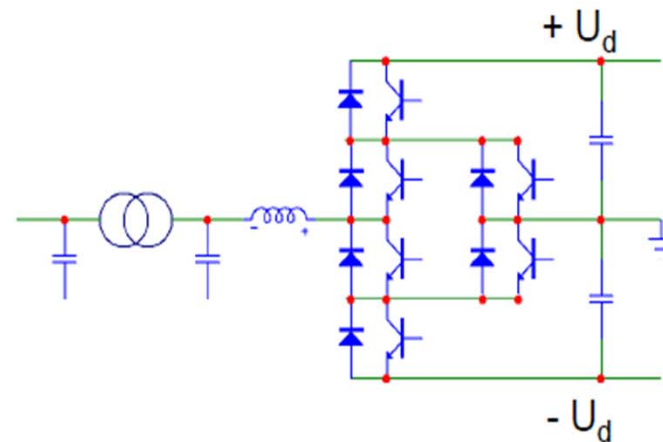- Converter losses 1.7 %
- Switching frequency reduced
- Harmonic generation improved



Three-level converter phase-to-neutral voltage

PWM Based VSC

HVDC Light Historical review, 2005-2009

- **Two-level Converter, Generation 3**
- Converter losses 1.7 %
By optimized IGBT and drive
- Lower switching frequency
- Harmonic generation maintained


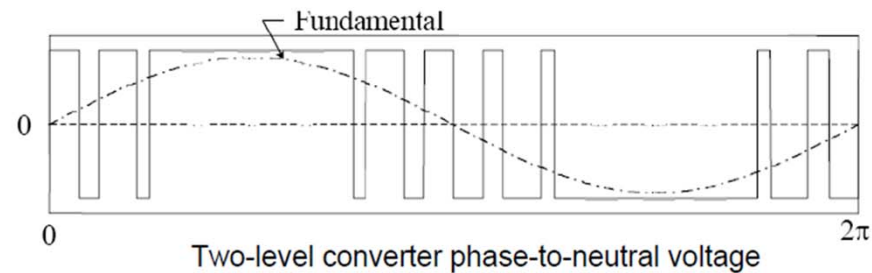
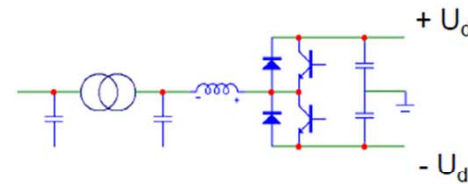
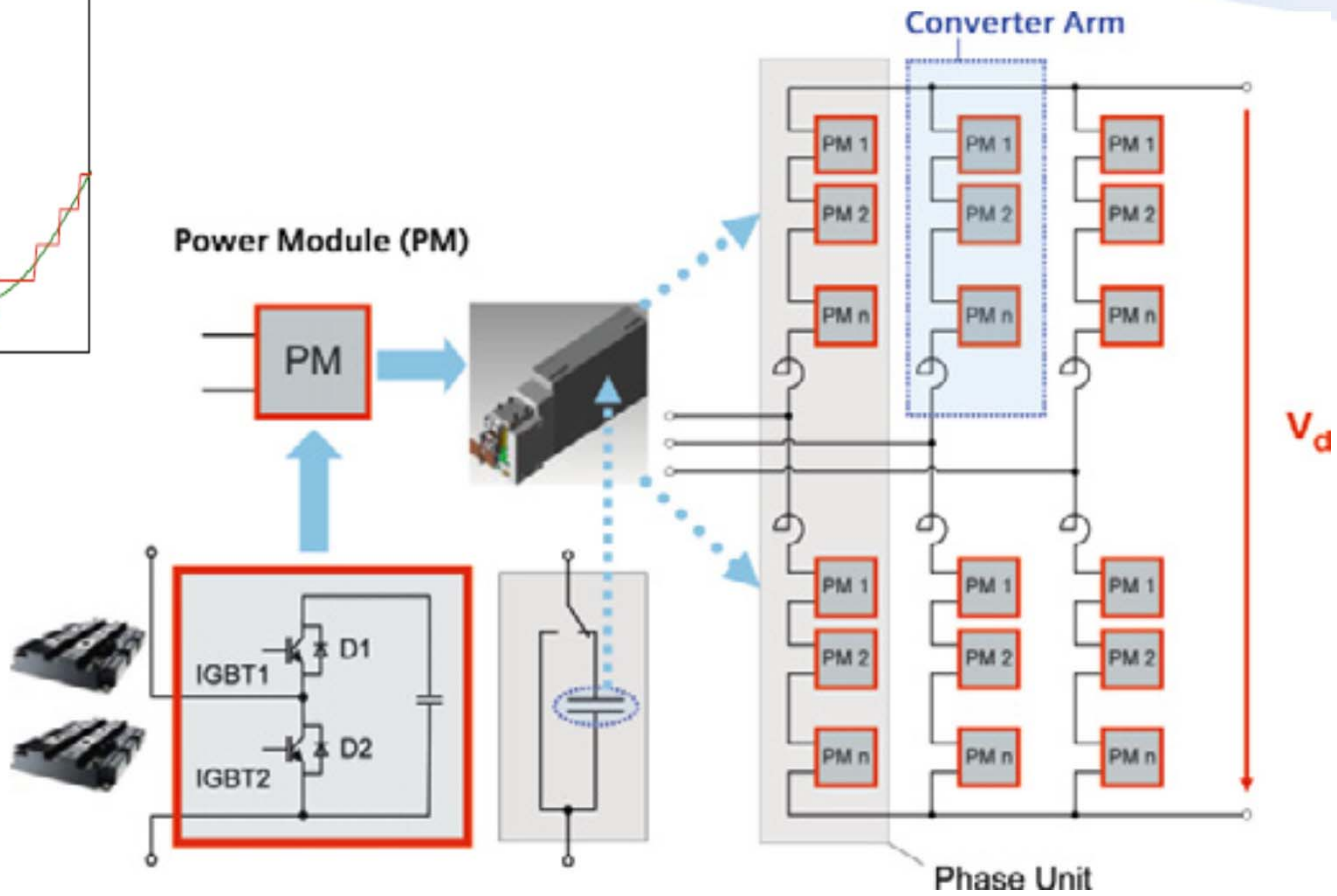


ABB slide


1/2 Bridge Multi Module Converter MMC

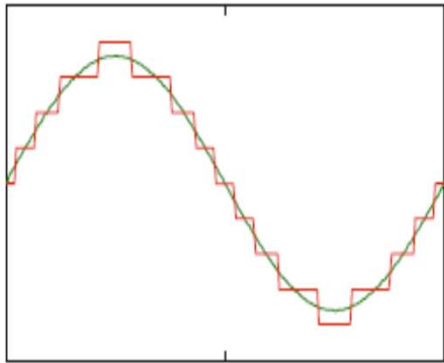


Siemens Slide

HVDC Light Generation 4

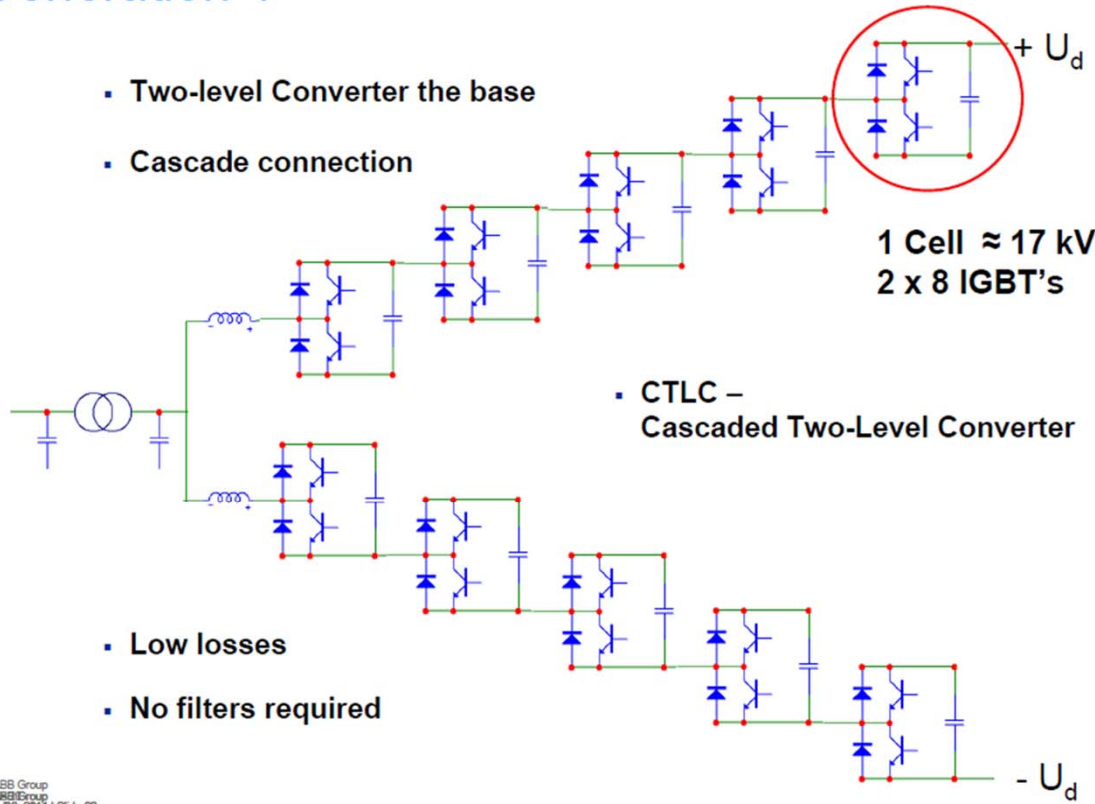- Two-level Converter the base
- Cascade connection




- Low losses
- No filters required

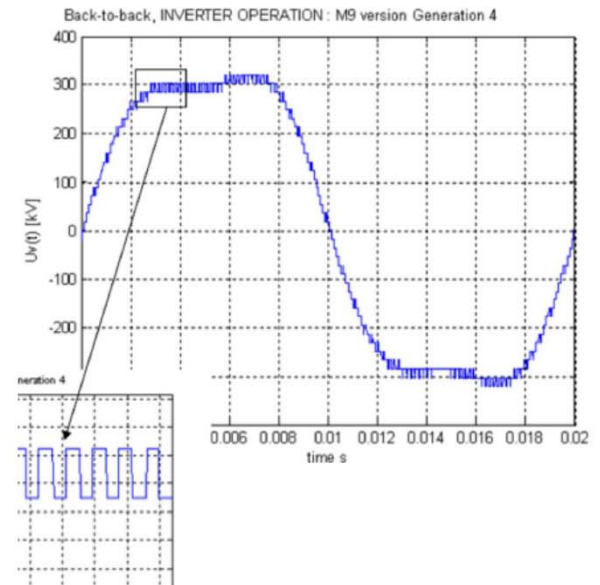


Full Bridge MMC

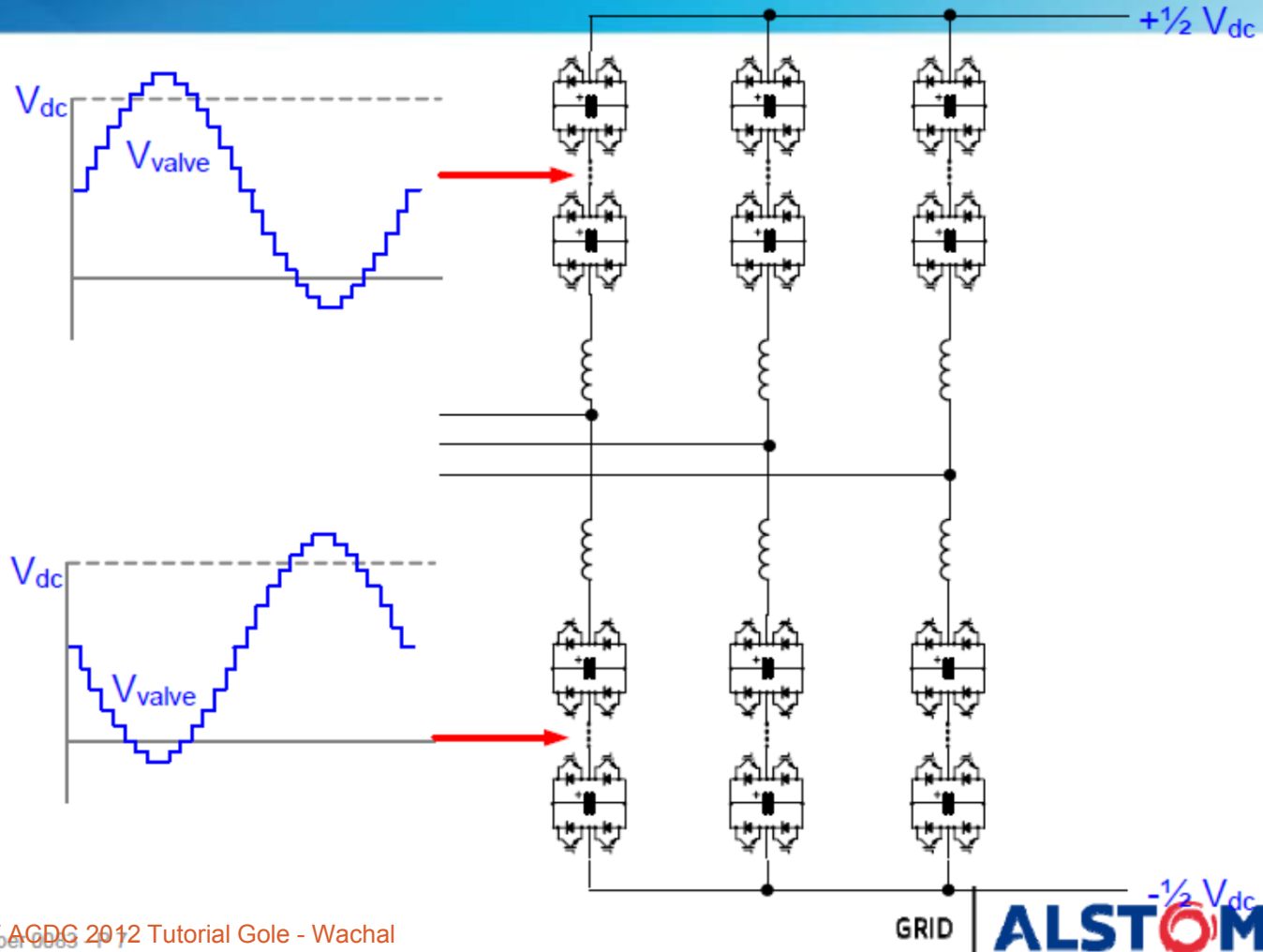Modular Multi-Level Converter (MMC) Full-bridge version



One possible Hybrid Configuration

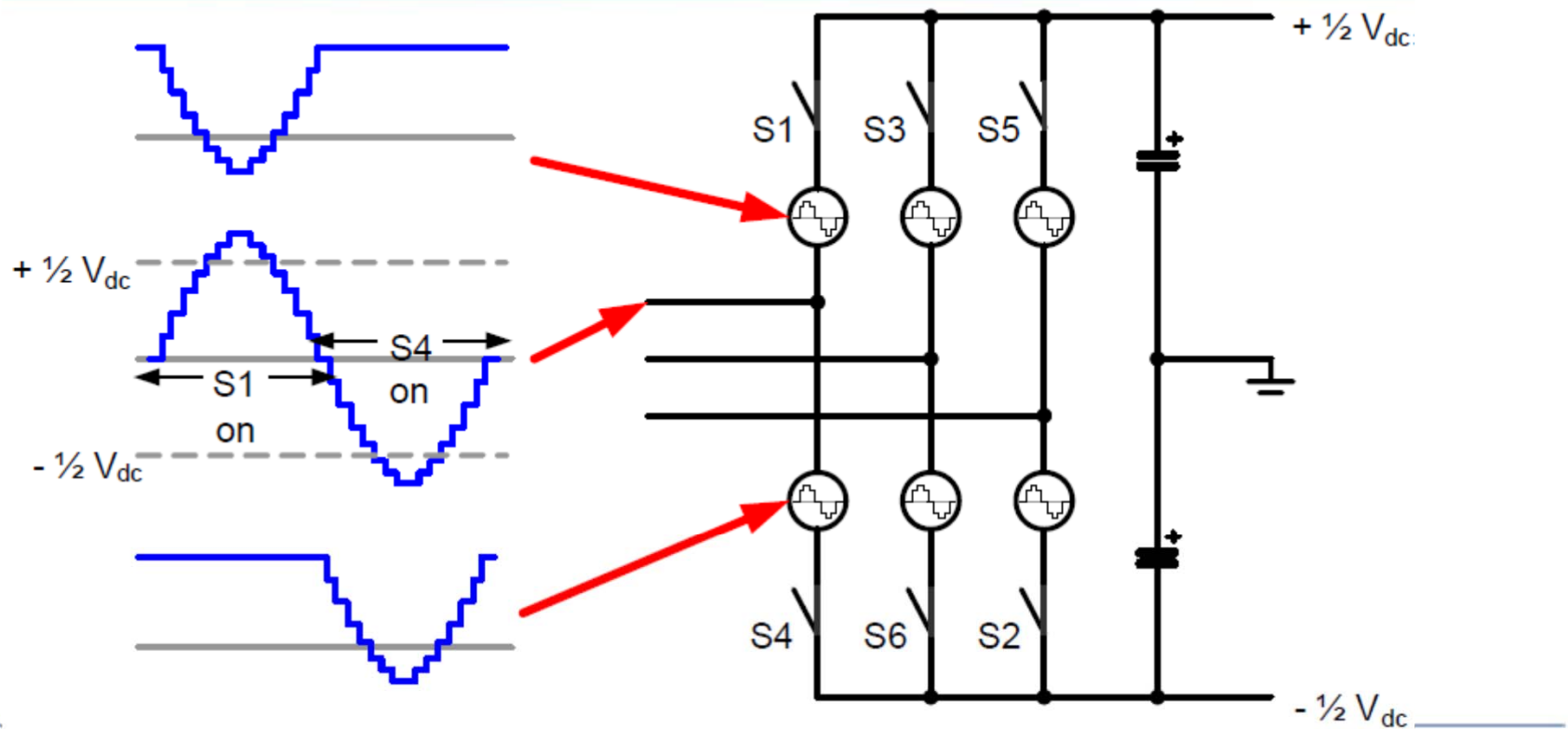Series Hybrid Circuit Wave-shaping on DC side



VSC Control and Modelling

- Control system organization
- Look at impact of diode in configuration
- High Level Control
 - D Q controller development
 - Development of Voltage reference signals based on dispatched orders

Lower level control

- Valve fire pulses (IGBT firing pulses)
- Capacitor energy balancing

Models For VSC MMC system

EMT and RMS transient (Dynamic and loadflow) type models are required

Lots of VSC configurations to consider

- PWM based (all series devices in Valve switch together)
- $\frac{1}{2}$ bridge MMC
- $\frac{1}{2}$ bridge MMC with PWM (cascaded two level converter CTLC)
- Full bridge MMC
- Hybrid mixtures of series valves, $\frac{1}{2}$ and full bridges

Traditional 'emt' solution methods not effective

Emt simulation speed is dependent on number of electrical nodes (size of simulation matrix)

MMC configurations increase electrical nodes exponentially

- LCC and PWM VSC
 - **6 nodes per 3 phase valve**
 - **entire valve arm (xx series devices) switch together**
- MMC
 - **Valve may have 400 levels (each switching independent)**
 - **$400 \times 6 = 2400$ nodes for 1 converter**


Compare 6 to 2400
simulation issue is evident ...

VSC System Control Model & Levels


- **Dispatch** What is the target of Converter ?
 - Power Set or Dc voltage (grid mode)
 - Ac voltage reference or MVar set (grid mode)
 - Frequency reference (P) and Ac Voltage (Q) (island mode)
 - Other P& Q strategy
- **High Level Controls**
 - Based on dispatch set points (Inputs)
 - Droop setting to allow autonomous control
 - d-q control will generate **Vref a, b and c** (outputs)
 - Voltage and current limits applied
- **Lower Level Controls**
 - Inputs Vref signals
 - Valve specific configurations

($\frac{1}{2}$ bridge MMC, $\frac{1}{2}$ bridge MMC with PWM, full bridge, etc.)

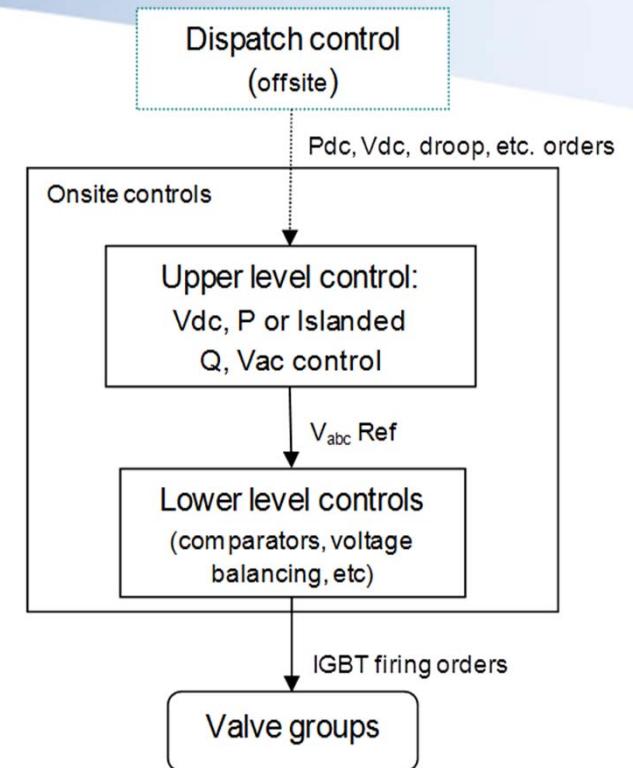 - Capacitor balancing algorithm(s)
 - Circulating current suppression algorithm(s)
 - Generates gate pulses and the ac waveforms



Control Hierarchy

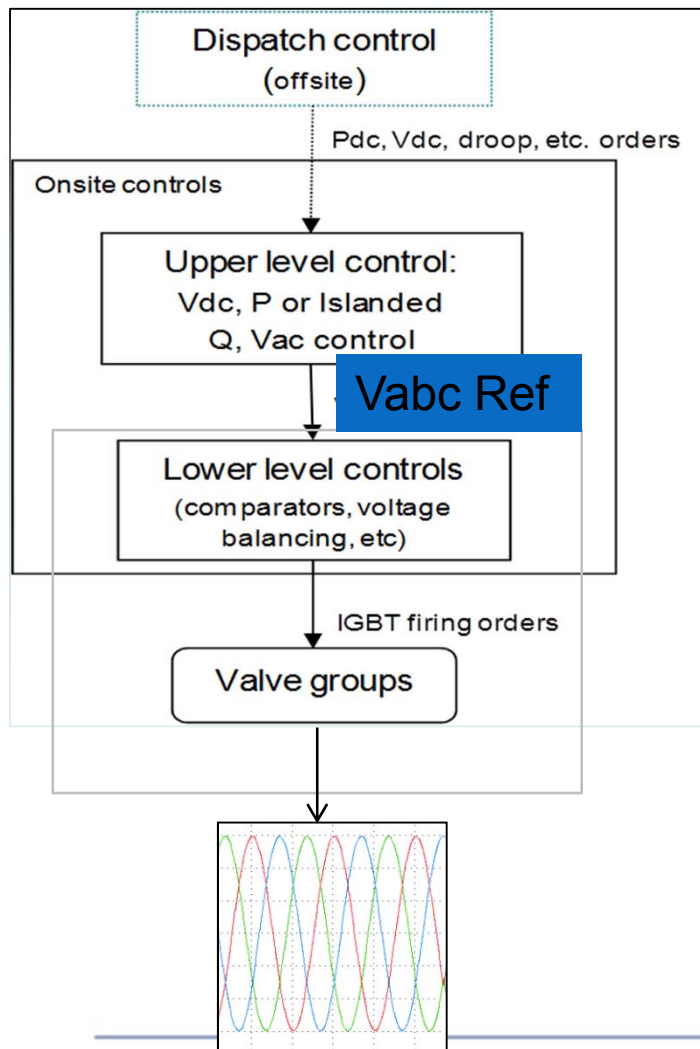

Natural separation occurs Higher Level Controls

Regardless of Dispatch Orders Higher Level controls develop

Vref A Vref B and Vref C outputs

Regardless of converter valve implementation Lower Level controls use the VREF inputs to generate the gate pulses to produce

Va Vb and Vc

Lower level controls are unique for valve topology and will have ancillary control

- Capacitor balance
- Circulating current suppression

Impact for VSC System Models


- Dispatch and Higher Levels Controls remain same regardless of Converter implementation
 - Generic or public domain models
 - Vendor specific (IP) models
- Lower Level Controls unique for different types of converter
 - Different Power electronics and control algorithm
 - Different Capacitor balance algorithm
 - Different Circulation Current suppression algorithm
 - Generic or public domain models
 - Vendor specific (IP) models
 - Different level of details for each lower level models
 - Full emt , detailed equivalent, firing pulse RMS

From a Simulation Study Point View

Choose the appropriate Lower Level Model for your study ... How ???

New Model Techniques required

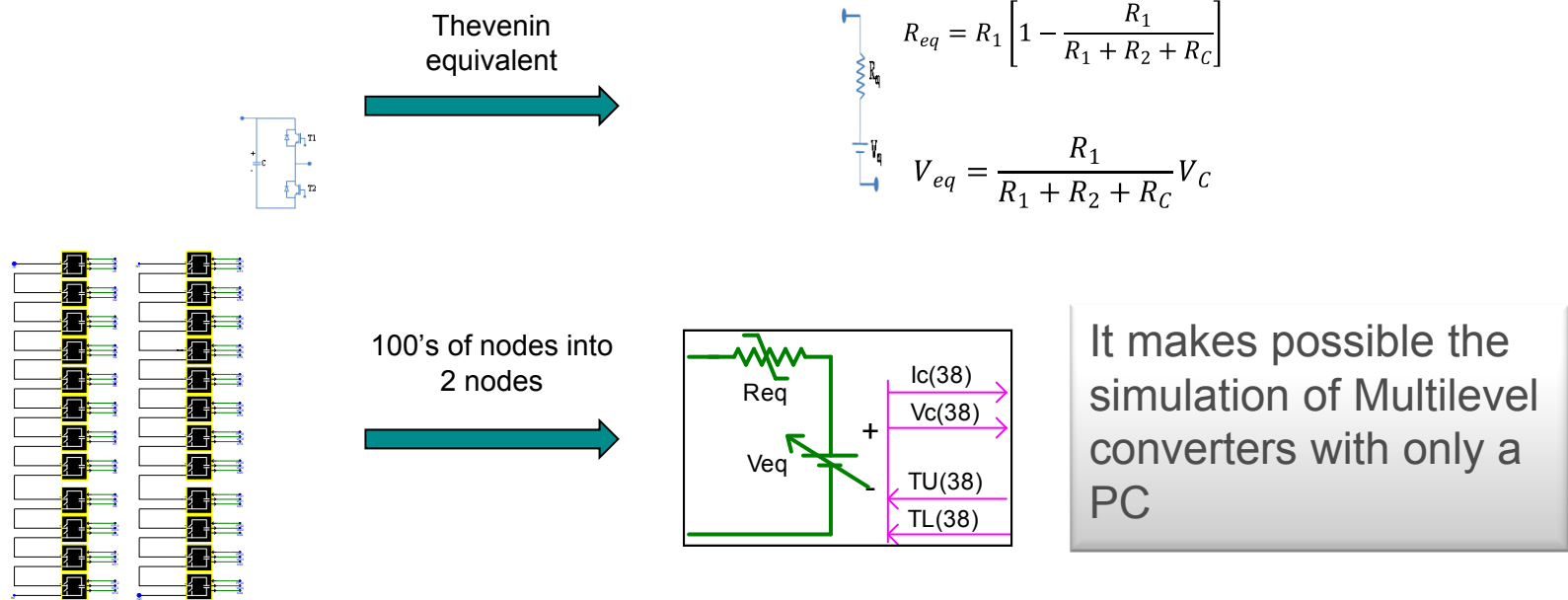Computationally efficient model developed by Simulation Chair University of Manitoba



U. N. Gnanarathna, A. M. Gole, and R. P. Jayasinghe, "Efficient Modeling of Modular Multilevel HVDC Converters (MMC) on Electromagnetic Transient Simulation Programs," IEEE Transactions on Power Delivery, vol.26, no.1, pp.316-324, Jan. 2011

Start up Concerns

Initial Energization

- Transformer
- MMC Capacitors (Precharge capacitors to $1.41 \cdot ELL$ via diodes)
- DC Line or DC Cable


Use start-up resistor to limit current.

Short resistor with by pass switch


Deblock pulses Conv 1 and then Conv 2

Ramp power to desired setpoints

Session 3: VSC system start up

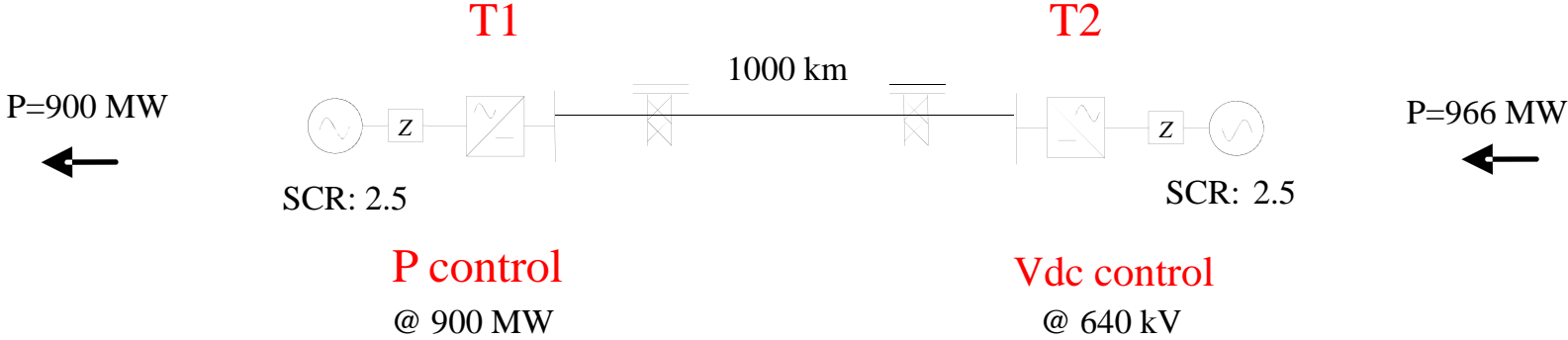

Session 3: VSC system start up

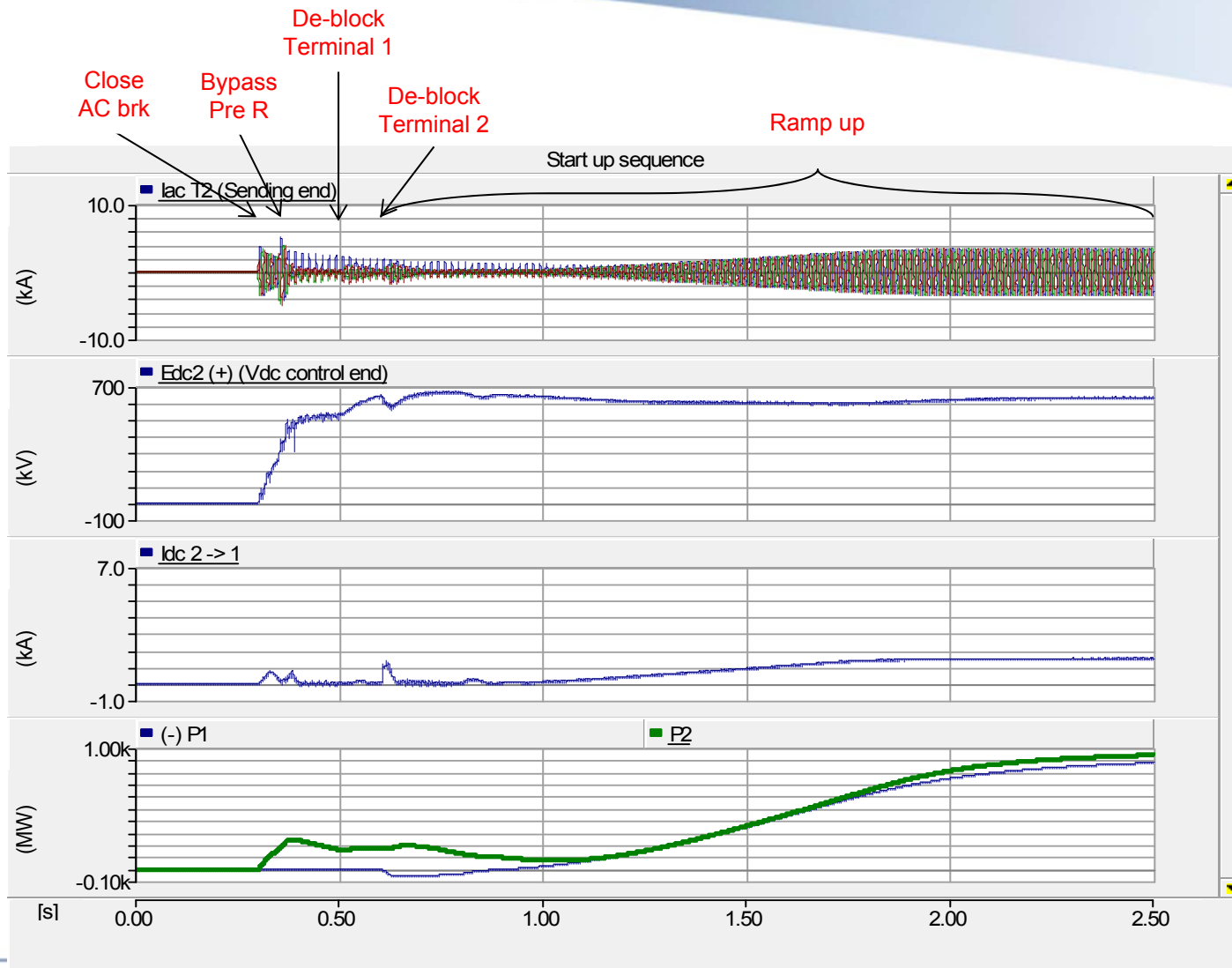

Summary Issues VSC Start-up

During start-up energization of both transformers and all capacitors therefore Larger Inrush

Inrush resistor commonly added with bypass switch


Diodes: with no firing pulse and diodes will conduct resulting in a Dc voltage

$V_{DC} = 1.41 \text{ peak of } V_{ac} \text{ L-L}$

(charge capacitors and line (or Cable))

rww1

DC Line Fault

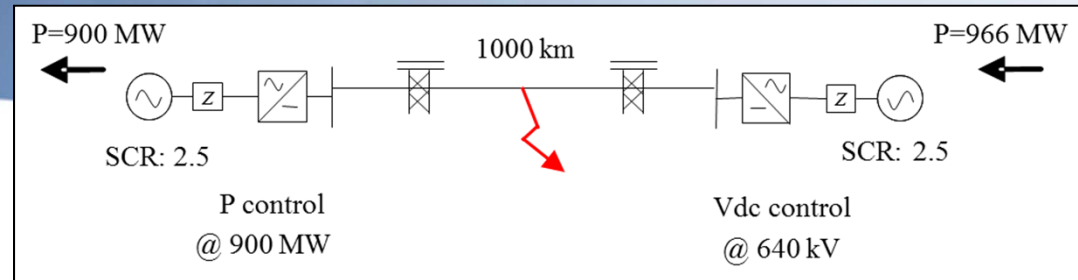

VSC scheme with overhead line (based on Caprivi)

no Dc Fast (4 msec) breaker installed

Resonant DC Breaker (50-75 msec installed)



On DC fault.. Block firing pulse.. MMC capacitors cannot discharge into line but diodes will continue to commutate and feed DC fault (as 6P LCC rectifier)

Open AC breaker .. Remove 6p rectifier diode current

DC line will discharge slowly.. Based on the R/L circuit of the Dc line will keep the post fault DC current present for seconds up to a couple of minutes .

A dc switching action is required to allow Dc fault recovery

DC Line Fault - restart

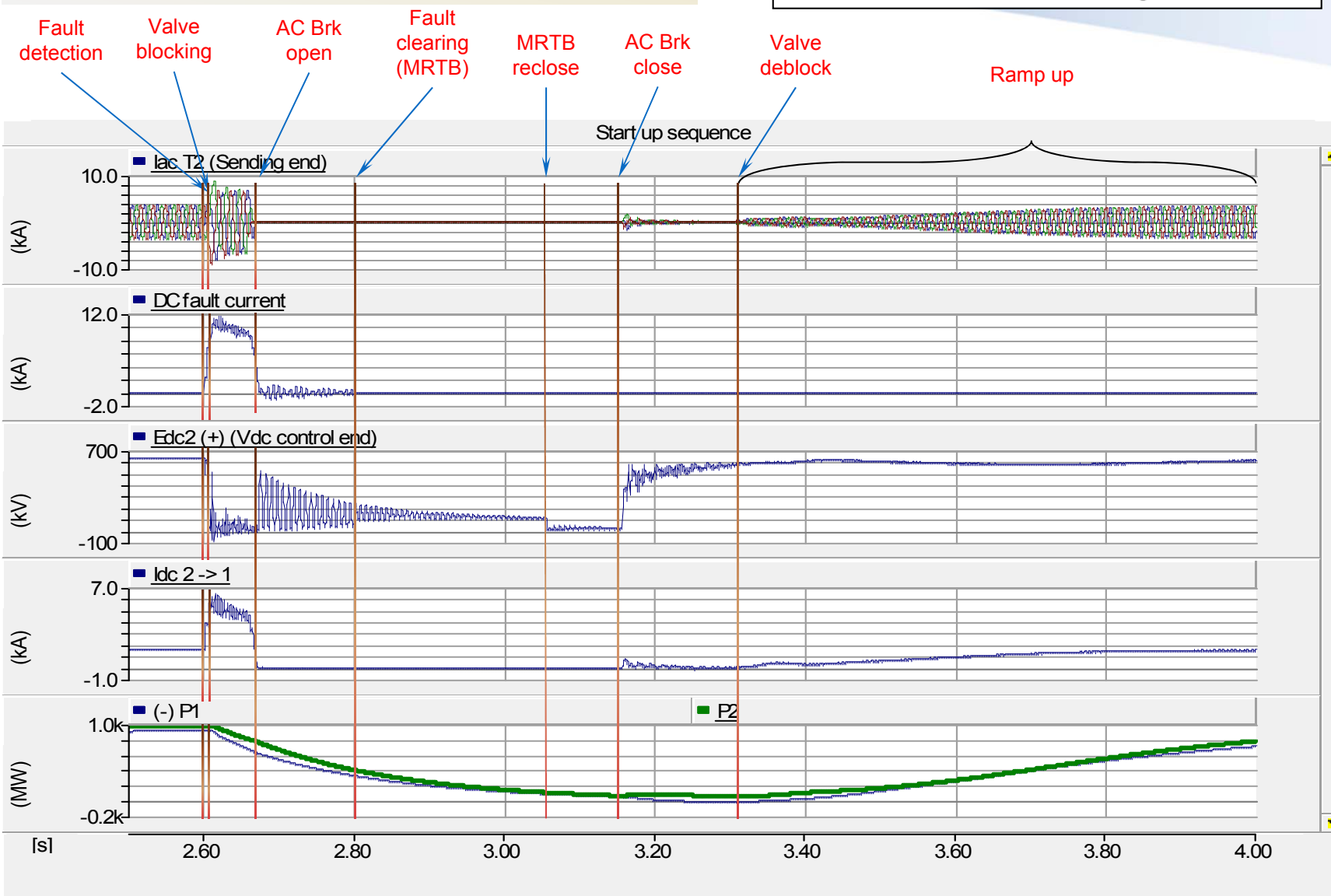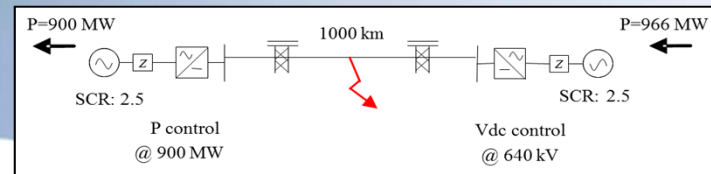


Summary for VSC Dc Line Faults


- Pulse Blocking removes discharge of capacitors quickly
- AC breaker is required to open to remove 6P diode current.
- For a weak ac system .. DC fault draws fault current from AC bus. dc fault = ac fault
- Post fault residual dc current requires resonant Dc breaker
- For recovery inrush.. MMC capacitors are already charged
- Power ramp rate is determined by ac system strength not dc controls .

Neutral Return

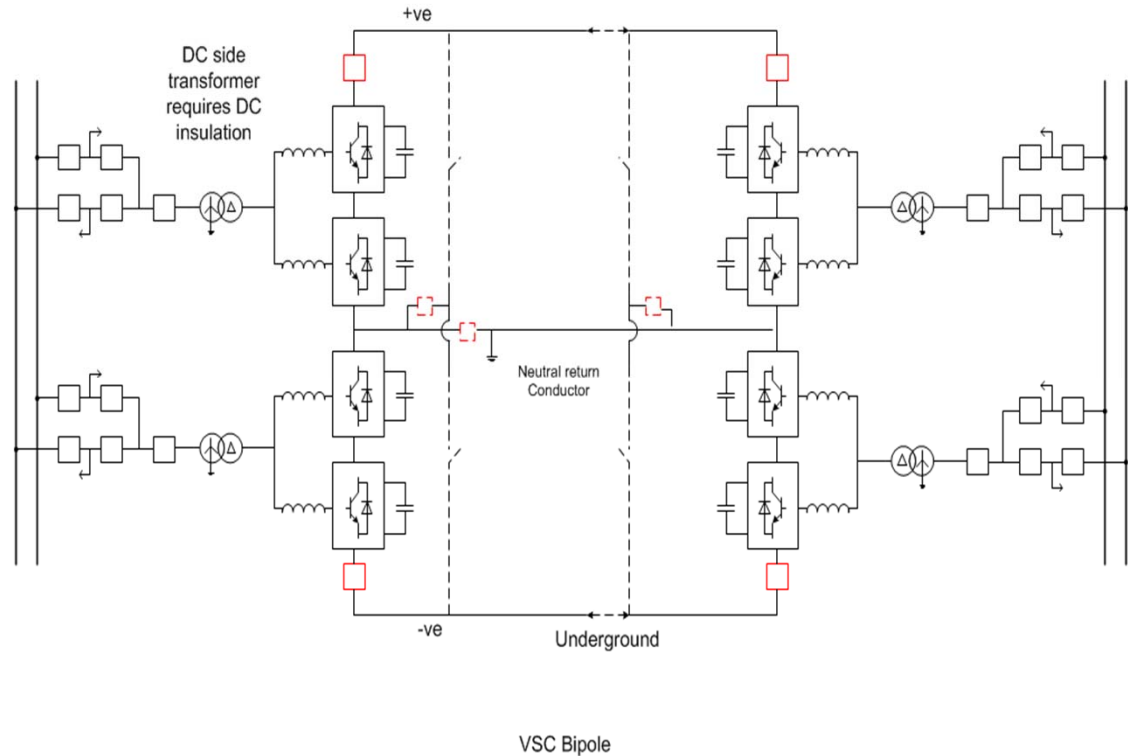- Eliminate ground currents
- Increased line losses
- DC voltage offset at remote station.. Requires more dc insulation
- Neutral current can be controlled to zero by bipole controller
- During pole outage, the pole conductor can be used to reduce losses.



DC Grid Modelling Test System (B4-58)

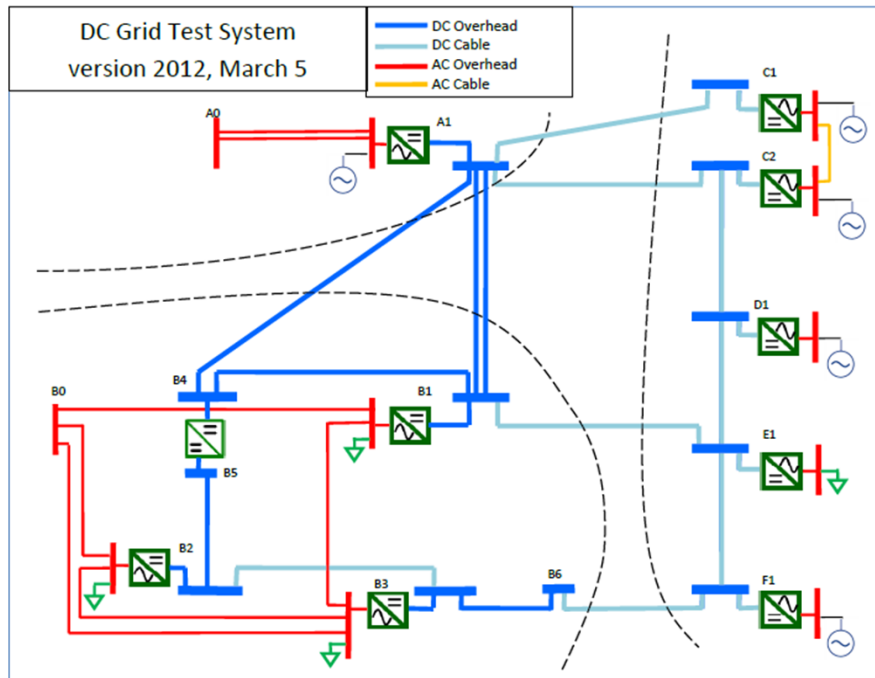

B4-57 has developed T-line and cable parameters for test case

A base PSCAD and EMPT-RV test cases are available.

Models are changing ..

Test Case alternatives

- Monopole
- Bipole with neutral return
- Bipole with ground/ sea electrodes.

Thank you...

Questions?

